

EGT1  
ENGINEERING TRIPOS PART IB

---

Wednesday 6 June 2018      2 to 4.10

---

**Paper 5**

**ELECTRICAL ENGINEERING**

*Answer not more than **four** questions.*

*Answer not more than **two** questions from any one section and not more than **one** question from each of the other two sections.*

*All questions carry the same number of marks.*

*The **approximate** percentage of marks allocated to each part of a question is indicated in the right margin.*

*Answers to questions in each section should be tied together and handed in separately*

*Write your candidate number **not** your name on the cover sheet.*

**STATIONERY REQUIREMENTS**

Single-sided script paper

**SPECIAL REQUIREMENTS TO BE SUPPLIED FOR THIS EXAM**

CUED approved calculator allowed

Engineering Data Book

**10 minutes reading time is allowed for this paper at the start of the exam.**

**You may not start to read the questions printed on the subsequent pages of this question paper until instructed to do so.**

Solutions

1.

- a) The FET input stage has a very high input impedance due to the gate capacitor of the FET. BJT collector-emitter-follower has a higher gain.

Point P is the balance point for the circuit. For differential input the voltage at P will be constant, for common mode the signal at both inputs change simultaneously and the voltage at point P will change as well.

- b) The CMRR is define at


$$CMRR = \frac{\text{Differential gain}}{\text{Common mode gain}}$$

Using the small signal model and the symmetry of the circuit at the balance point P.

For differential mode the signal at point P is constant and P appears virtually connected to ground.

The gain in this case is  $A_D \text{ gain} = -g_m R_1$ .

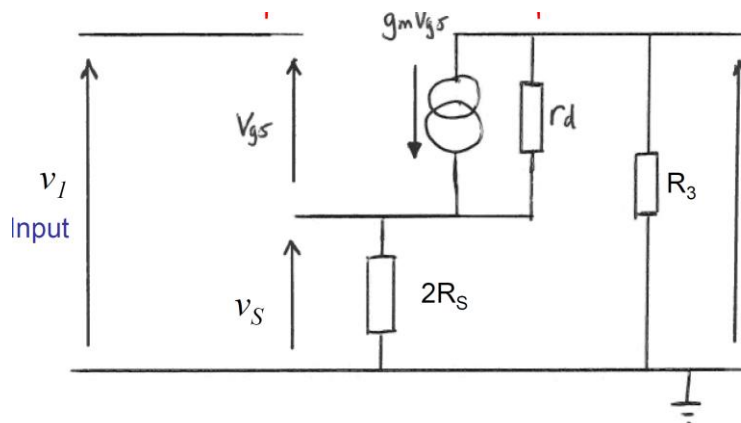For common mode signals, we exploit the symmetry of the circuit if we replace  $R_s$  with two resistors in parallel of value  $2R_s$ . The circuit can be split into two and studying only the left hand side with the  $2R_s$  resistor connected to ground. The small signal model can be sketched as below:



Version FT/3

$$V_1 = V_{gs} + V' \text{ where } V' = g_m V_{gs} 2R_s$$


$$\text{Hence } V_1 = V_{gs} (1 + 2g_m R_s)$$

$$\text{Output } (0 - V_o)/R_1 = g_m V_{gs}; \quad V_o = -g_m V_{gs} R_1;$$

So the common-mode gain will be  $A_{cm} = -g_m R_1 / (1 + 2g_m R_s)$ .

The CMRR will then be:  $CMRR = A_d \text{ gain} / A_{cm} \text{ gain} = 1 + 2g_m R_s$

c) Assume that  $Q_1 = Q_2$

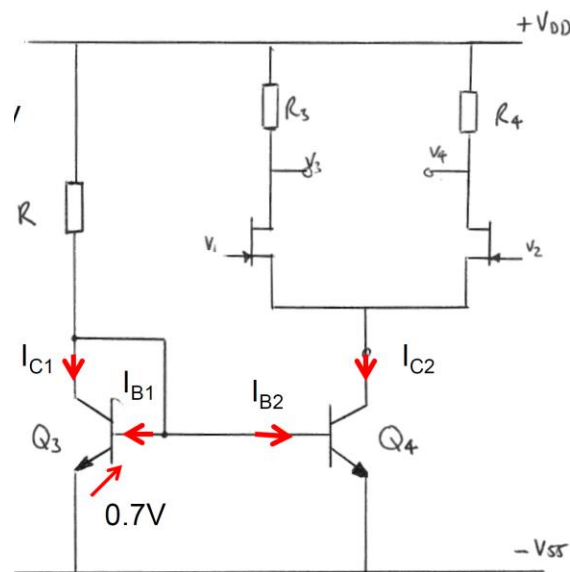

$$I_{C1} = (V_{DD} - 0.7V)/R; \text{ if } h_{FE} \text{ is very large then } I_B \ll I_C$$

$$\text{By symmetry } I = I_{C1} = (V_{DD} - 0.7V)/R$$


$$V_{be1,2} = 0.7 \text{ V}$$

$$\text{Hence } V_{ce2} = 0.7V$$

d)

$$\text{If } Q_1 = Q_2 \Rightarrow h_{fe1} = h_{fe2}, h_{ie1} = h_{ie2}, h_{ce1} = h_{ce2}$$

The small signal model is

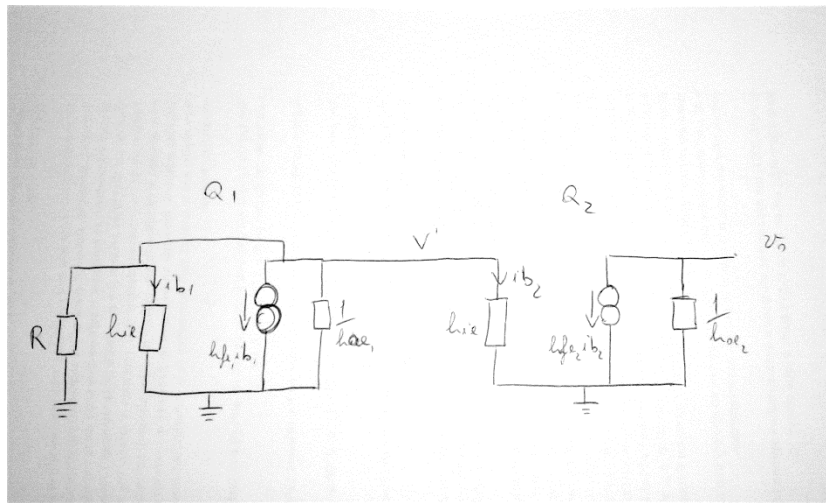

Both  $Q_1$  and  $Q_2$  have voltage  $v'$  at the base  $\Rightarrow i_{b1} = i_{b2}$

$V_{ce1} = 0.7$  constant  $\Rightarrow$  grounded. Therefore  $v'$  is grounded. Hence  $R_o = 1/h_{oe}$ .


e)

The Circuit in Figure 2 is only made of BJTs and it is compatible with integrated circuits technology, unlike the Zener diode current mirror circuit.

2.

a) The gain compensation is used to stabilise the OpAmp at higher frequency.

A general gain compensation is:

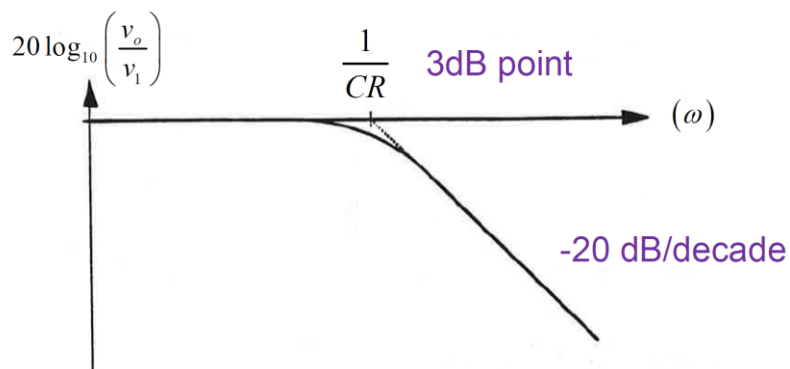

Where the function described is:  $A(\omega) = A_0 / (1 + j\omega/\omega_0)$

Because it is a first order system, the gain-bandwidth product is constant

Version FT/3

Hence we get Gain(closed loop) = gain-bandwidth (open loop)/bandwidth (closed loop)  
= 100 A<sub>0</sub>/100,000 = A<sub>0</sub>/1000

b)

In an ideal OpAmp the gain is infinite, the (V<sub>+</sub> - V<sub>-</sub>) = 0

So, we get I<sub>in</sub> = (V<sub>in</sub> - V<sub>o</sub>)/R; V<sub>in</sub> = V<sub>o</sub> Z/(R+Z) => V<sub>o</sub> = (R+Z)/Z V<sub>in</sub>

I<sub>in</sub> = V<sub>in</sub>/R - V<sub>in</sub> (R+Z)/RZ = - V<sub>in</sub>/Z => V<sub>in</sub>/I<sub>in</sub> = -Z (which is a NIC).

c)

Assuming that each NIC inverts the sign of the impedance preceding it, we can write:

The total impedance in Fig.4 is Z<sub>in</sub> = - (Y) where Y = R + (-R)(R+Z)/Z = - R<sup>2</sup>/Z => Z<sub>in</sub> = R<sup>2</sup>/Z

d)

Remembering that  $\omega = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega^2 C} = \frac{1}{(2\pi \cdot 10^{-2})^2 \cdot 10^{-4}} = 2.5 \times 10^4$  H (This inductance

is too high and impractical to manufacture).

So the inverted gyrator can be used to simulate the inductance.

The impedance of an inductor is Z=j $\omega$ L.

Using the gyrator we get: Z<sub>in</sub>= R<sup>2</sup>/j $\omega$ L => Z<sub>in</sub> =  $\frac{1}{j\omega(\frac{L}{R^2})}$

From this we get the following equivalence: C = L/R<sup>2</sup>, where R =  $\sqrt{\frac{L}{C}} = 1.59 \times 10^4 \Omega$

3.

(a) For star connection

$$I_{line} = I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{V_{line}}{\sqrt{3}Z_{ph}}$$

For delta connection

Version FT/3

$$I_{line} = \sqrt{3}I_{ph} = \sqrt{3} V_{line} / Z_{delta}$$

For equivalence  $V_{line} / I_{line}$  must be the same, so

$$Z_{delta} = 3Z_{ph}$$

(b)

For balanced star connection currents form a balanced 3 – phase set.

$$\text{So } I_A = I_B = I_C = 0$$

From Kirchoff's laws we have  $I_A + I_B + I_C + I_N = 0$  where  $I_N$  is the current through the neutral conductor. So  $I_N = 0$

(c)

$$(i) \text{ delta connected load: } Z_{star} = Z_{delta}/3 = 1/3 \text{ k}\Omega$$

So  $Z_{ph}$  of equivalent star connected load is

$$(500 + 4 \times 50 \times 2\pi j) / 3 = 293 + 61.4j \Omega$$

(ii)

$$I_{line} = \frac{V_{ph}}{|Z|} = \frac{V_l / \sqrt{3}}{|Z|} = \frac{11 \times 10^3}{\sqrt{3} |293 + 61.4j|} = 21.2 \text{ A}$$

$$P = 3I_{ph}^2 \text{Re}(Z_{ph}) = 3 \times (21.2)^2 \times 293 = 396 \text{ kW}$$

$$Q = 3I_{ph}^2 \text{Im}(Z_{ph}) = 3 \times (21.2)^2 \times 61.4 = 83.6 \text{ kVAR}$$

(iii) Reactive power unchanged.


$$\text{Real power} = 396 \text{ k} + V_{ph}^2 \left( \frac{1}{1.5\text{k}} + \frac{1}{1.0\text{k}} + \frac{1}{1.2\text{k}} \right) = 496 \text{ kW}$$

When the conductor between the star connections is not connected, the voltage at the star connection of the unbalanced load is not zero, hence the answer would change.

4.

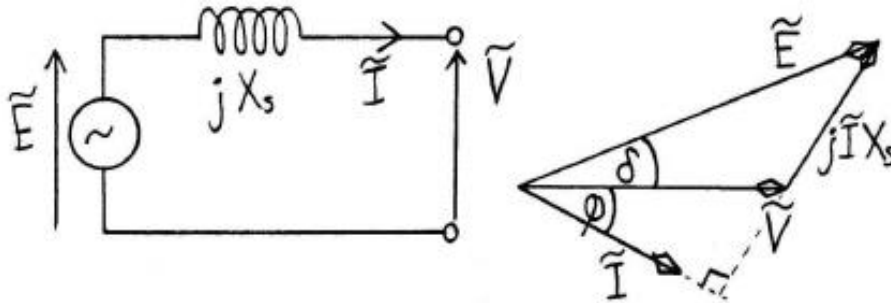(a) Bookwork.


$$\tilde{E} = \tilde{V} + j\tilde{I}X_s$$




(b)

(i) Connection to an infinite bus means that the voltage and frequency are fixed and cannot be changed by any single generator.

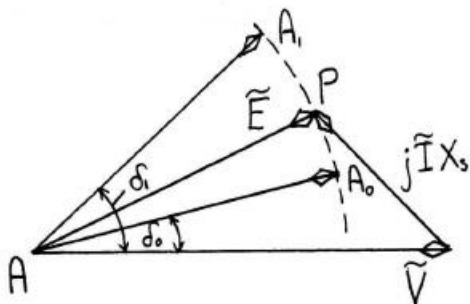(ii) Increasing torque with  $E$  constant increases  $\delta$ .



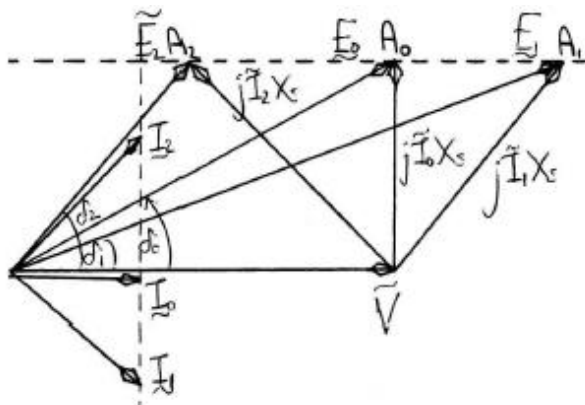(iii) Reactive power is controlled by changing  $E$ . Constant power means  $E \sin(\delta)$  is constant.



$I_1$  lags  $V$ : Generator produces reactive power.

$I_2$  leads  $V$ : Generator consumes reactive power.

Advantages: power factor correction is continuous, and can be adjusted at fast timescales. Reactive power can also be absorbed.

(c)


(i)

$$V_{ph} = \frac{V_l}{\sqrt{3}} = \frac{22k}{\sqrt{3}}$$

$$P = 3I_{ph}V_{ph}\cos(\phi). \text{ So}$$

$$I_{ph} = \frac{P}{3V_{ph}\cos(\phi)} = 11.7 \text{ kA}$$


$$\phi = \cos^{-1}(0.9) = 25.8^\circ$$

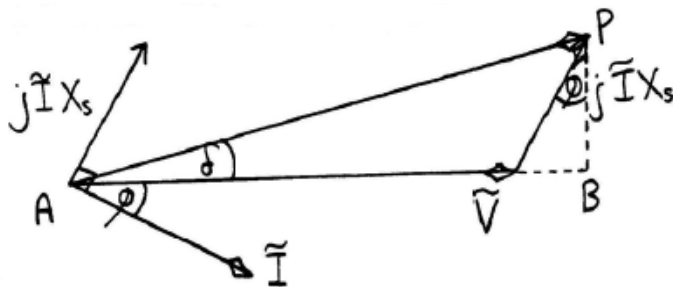

$$E^2 = (IX_s \cos(\phi))^2 + (V + IX_s \sin(\phi))^2$$

$$\text{So } E = 21.6 \text{ kV}$$

(ii)

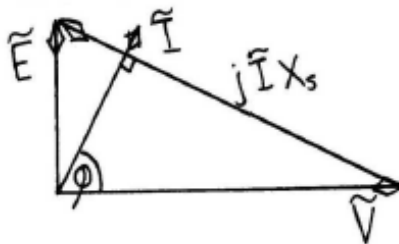

$$P_{max} \text{ occurs for } \delta = \pi/2.$$

$$I_{ph} = \frac{\sqrt{E^2 + V^2}}{X_s} = 22.8 \text{ kA}$$

$$\phi = \frac{\pi}{2} - \tan^{-1} \frac{E}{V} = 2.21$$



Version FT/3

$$Q = 3I_{ph}V_{ph} \sin \phi = 440 \text{ MVAR}$$

$$P = 3I_{ph}V_{ph} \cos \phi = 749 \text{ MW}$$

5.

(a) Increased connectivity provides:

- greater efficiency, can use the most efficient/clean generation for base load.
- greater reliability
- power stations can be located at best locations

Gas turbines: efficient, clean can be brought online faster

Coal: now used for peak load and is phased out.

(b) Types of faults:

- 3 phase symmetrical fault to earth
- line-line fault (two lines touch each other)
- line to ground fault

(c)

(i) Choose base values for VA and voltages

$$VA_b = 100 \text{ MVA}$$

$$V_b = 11 \text{ kV}, 132 \text{ kV}, 22 \text{ kV}$$

Perform changes of base for the reactances of the transformers:

$$11/132 \text{ kV transformer } X_{pu(100)} = X_{pu(150)} \times \frac{100}{150} = 0.133 \text{ pu}$$


$$132/22 \text{ kV transformer } X_{pu(100)} = X_{pu(200)} \times \frac{100}{200} = 0.05 \text{ pu}$$

Find the feeder impedance in pu

$$Z_b = \frac{V_b^2}{VA_b} = \frac{(132 \text{ k})^2}{100 \text{ M}} = 174 \Omega$$

$$Z_{pu} = \frac{Z}{Z_b} = \frac{8 + 40j}{174} = 0.0460 + 0.230j$$

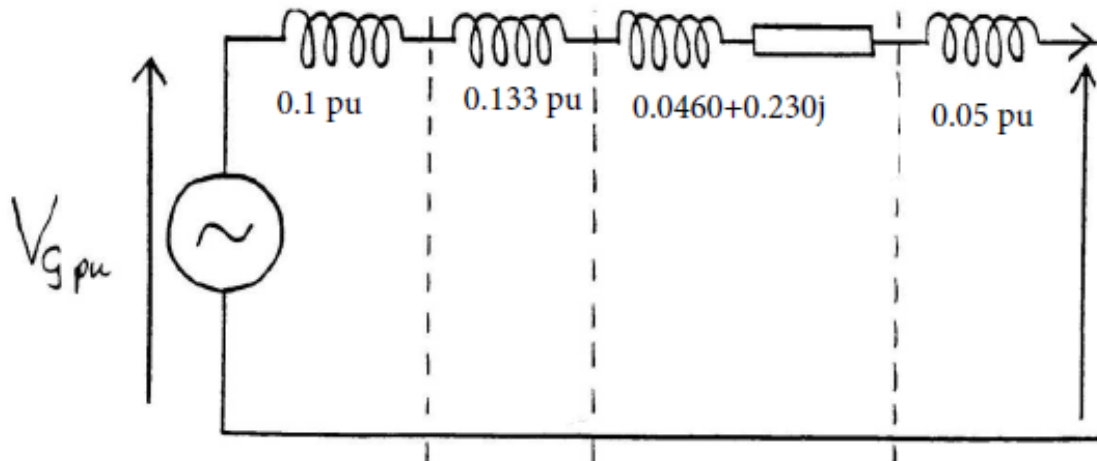The single phase line diagram in pu is therefore



$$S_{load} = \frac{P_{load}}{\cos(\phi)} = \frac{60M}{0.9}$$

$$S_{load,pu} = \frac{S_{load}}{VA_b} = \frac{60M}{0.9 \times 100M} = 0.667$$

$$S_{load,pu} = V_{pu} \times I_{pu} = I_{pu} = 0.667$$

$$P_{pu} = I_{pu}^2 R_{feeder,pu} = (0.667)^2 \times 0.0460 = 0.0204$$

$$P_{total} = P_{load} + P_{pu} \times VA_b = 60M + 0.0204 \times 100M = 62.0 MW$$

$$Q_{pu} = I_{pu}^2 X_{total,pu} = (0.667)^2 \times (0.1 + 0.133 + 0.230 + 0.05) = 0.2280$$

$$Q_{load} = P_{load} \tan(\phi) = 29.1 MVAR$$

$$Q_{total} = Q_{load} + Q_{pu} \times VA_b = 51.9 MVAR$$

(ii)

$$I_{F,pu} = \frac{1}{|0.1j + 0.133j + 0.0460 + 0.230j + 0.05j|} = 1.94$$

$$I_b = \frac{VA_b}{\sqrt{3} V_b} = \frac{100M}{\sqrt{3} 132k} = 437$$

$$I_F = I_{F,pu} \times I_b = 849 A$$

$$\text{Circuit breaker rating} = V_{pu} \times I_{F,pu} = I_{F,pu}$$

$$\text{Rating} = I_{F,pu} \times VA_b = 194 MVA$$

To decrease the fault current add additional reactance in series (increases also the need for reactive power).

6.

a)

From

$$\nabla \times E = -\dot{B} = -j\omega\mu_0 H$$

We have since  $\nabla \times E$  has only one component in the x-direction of

$$-i \cdot \frac{dE_y}{dz}$$

$$-j\omega\mu_0 H = -i \cdot -j\beta E_0 e^{j(\omega t - \beta z)}$$

Hence

$$H_x = -\frac{1}{\mu_0 c} E_0 e^{j(\omega t - \beta z)} \quad (\text{where } c \text{ is the speed of the wave})$$

And

$$H_x = -\frac{E_0}{Z_0} e^{j(\omega t - \beta z)}$$

$$\text{Mean power} = \frac{1}{2} \mathcal{R}e(E \times H^*) = \frac{E_0^2}{2Z_0}$$

b) H is perpendicular to the loop hence:

$$V = -d\phi/dt$$

$$V = -\frac{\pi a^2}{4} E_0 \frac{\omega \mu_0}{Z_0} = -\frac{\pi a^2}{4} E_0 \omega \sqrt{\epsilon_0 \mu_0} = \frac{\pi^2 a^2}{2\lambda} E_0$$

(since  $c = 1/(\mu_0 \epsilon_0)^{1/2}$  and  $v = f \cdot \lambda$  and  $\lambda = 2\pi / \omega$ )

c) voltage is inversely proportional to  $\lambda$ .  $E_0$  is proportional to the square root of the power hence we have

Version FT/3

$$\sqrt{\frac{P_{BBC}}{P_{C4}}} = \frac{\lambda_{BBC}}{\lambda_{C4}}$$

d) Iso Power density at a distance r

$$P = \frac{P_{BBC}}{2\pi r^2} \text{ (since gain is 2)}$$

Equate this to  $E_0$

$$\frac{E_0^2}{Z_0} = \frac{E_0^2}{120\pi} = \frac{P_{BBC}}{2\pi r^2}$$

Antenna is power matched to the load hence:

$$\frac{1}{2} \frac{V_0^2}{2R} = 4 \cdot 10^{-9}$$

Hence

$$V^2 = 4 * 75 * 4 \cdot 10^{-9} = 1.2 * 10^{-6}$$

Using voltage from part b we get

$$V^2 = \left(\frac{\pi^2 a^2}{2\lambda} E_0\right)^2 = \left(\frac{\pi^2 a^2}{2\lambda}\right)^2 * \frac{60P}{r^2}$$

Lambda=0.54m; a=0.15m; P=1000W

Hence

$$R = (1/(1.2 * 10^{-6})) * 3.141^2 * (0.15)^2 * (60000)^{0.5} / 1.08 = 49.6 \text{ km}$$

7.

$$V - L\delta x \frac{\partial I}{\partial t} = V + \frac{\partial V}{\partial x} \delta x$$

Version FT/3

$$I - C\delta x \frac{\partial V}{\partial t} = I + \frac{\partial I}{\partial x} \delta x$$

Hence

$$-L \frac{\partial I}{\partial t} = \frac{\partial V}{\partial x}$$

$$C \frac{\partial V}{\partial t} = \frac{\partial I}{\partial x}$$

Differentiate both with respect to x

$$-L \frac{\partial}{\partial t} \left( \frac{\partial I}{\partial x} \right) = \frac{\partial^2 V}{\partial x^2}$$

$$-C \frac{\partial}{\partial t} \left( \frac{\partial V}{\partial x} \right) = \frac{\partial^2 I}{\partial x^2}$$

Hence subbing back in for dv/dx and dI/dx

$$LC \frac{\partial^2 V}{\partial t^2} = \frac{\partial^2 V}{\partial x^2}$$

$$LC \frac{\partial^2 I}{\partial t^2} = \frac{\partial^2 I}{\partial x^2}$$

b)

$$\frac{\partial^2 V}{\partial x^2} = f_+''(x - vt) + f_-''(x + vt)$$

$$\frac{\partial^2 V}{\partial t^2} = v^2 f_+''(x - vt) + v^2 f_-''(x + vt)$$

Hence:

$$f_+''(x - vt) + f_-''(x + vt) = LCv^2 f_+''(x - vt) + v^2 f_-''(x + vt)$$

Hence

$$v = 1/\sqrt{LC}$$

Physical significance is that a transmission line supports both forward and backward travelling voltage waves which travel at a speed of  $1/\sqrt{LC}$

c)

Using the two equations given and the databook expressions for  $I_b$  and  $I_f$  in terms of  $V_0$  and  $Z_0$  together with ohms law we get

$$Z(x) = \frac{(V_F e^{-j\beta x} + V_B e^{j\beta x})}{\left(\frac{V_F}{Z_0} e^{-j\beta x} - \frac{V_B}{Z_0} e^{j\beta x}\right)}$$

Dividing through by  $V_F$  and using the voltage reflection coefficient we get:

$$Z(x) = Z_0 \frac{(e^{-j\beta x} + \rho_L e^{j\beta x})}{(e^{-j\beta x} - \rho_L e^{j\beta x})}$$

Using Eulers theorem we then get the expression given

d)

Curve is a smooth curve. Example is given below. The significance is that there will be no reflections.

