

3B1 c1B 2022

- 1(a) Radz into full sphere
Directivity = 1.5, $\rho_r = 0.90$, Radz efficiency
Range, $R = 86 \times 10^3 \text{ m}$, $P_{\text{trans.}} = 25 \text{ W}$

$$P \text{ density @ gnd} = \frac{25 \cdot 0.9 \cdot 1.5}{4\pi (86 \times 10^3)^2} = 3.63 \times 10^{-10} \text{ W/m}^2$$
$$= \frac{1}{2} E H^* = \frac{1}{2} \eta H^2 \quad \therefore H = 1.39 \times 10^{-6} \text{ A/m}$$

Assessor note; Many candidates calculated E rather than H!

(b) Antenna eqn: $G = \frac{4\pi A_e}{\lambda^2}$

Assessor note:
Remember to
include the
antenna efficiency

$$\lambda = \frac{c_0}{f} = \frac{3 \times 10^8}{920 \times 10^6} = 0.326 \text{ m}$$

$$\therefore A_e = \frac{G \lambda^2}{4\pi} = \frac{0.9 \cdot 1.5 \cdot 0.326^2}{4\pi}$$


$$= 0.0114 \text{ m}^2$$

$$P \text{ density @ space} = \frac{200 \cdot 10^{30/10}}{4\pi (86 \times 10^3)^2} = 2.15 \times 10^{-6} \text{ W/m}^2$$

$$\therefore P_{\text{recd.}} = 2.15 \times 10^{-6} \cdot 0.0114 = 2.45 \times 10^{-8} \text{ W}$$

$$= \frac{V_r^2}{75} \quad \therefore V_r = 1.36 \text{ mV}_{\text{rms}}$$
$$\equiv \underline{\underline{3.83 \text{ mV}_{\text{pp}}}}$$

- (c) Beam angle, dB

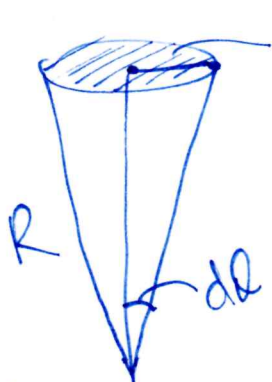

$$A = \pi (R \text{ dB})^2$$


$$G = 1000 = \frac{4\pi R^2}{A} = \frac{4\pi R^2}{\pi R^2 \text{ dB}^2}$$

$$\therefore \text{dB} = \frac{1}{\sqrt{250}} \text{ rad}$$

$$\text{off axis dist.} = \underline{\underline{R \text{ dB} = 5.4 \text{ km}}} = \underline{\underline{3.6^\circ}} \text{ full beam } 7.2^\circ$$

1(d) For $\lambda/2$ antenna, assuming cosine current dist'n
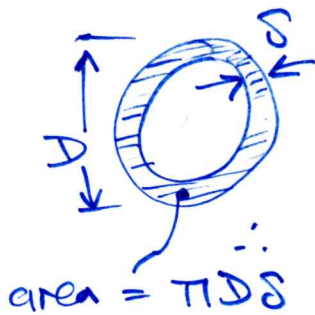
$$R_r = 30\pi^2 \left(\frac{\lambda/2}{\lambda}\right)^2 = 74 \Omega$$




$$\text{Skin depth, } \delta = \sqrt{\frac{2}{\omega \mu_0 \sigma}} = \sqrt{\frac{\rho}{\pi f \mu_0}}$$

$$\therefore \delta = \sqrt{\frac{6.92 \times 10^{-7}}{\pi \cdot 920 \times 10^6 \cdot 4\pi \times 10^{-7}}} = 1.38 \times 10^{-5} \text{ m}$$

$$R_{ohmic} \approx \frac{\frac{\lambda}{2} \cdot \rho}{\pi D \delta} = \frac{0.326 \cdot 6.92 \times 10^{-7}}{\pi D \cdot 1.38 \times 10^{-5}} = \frac{2.60 \times 10^{-3}}{D} \Omega$$

$$\text{Radn efficiency} = \frac{R_r}{R_r + R_{ohmic}} = \frac{74}{74 + R_{ohmic}} = 0.90$$
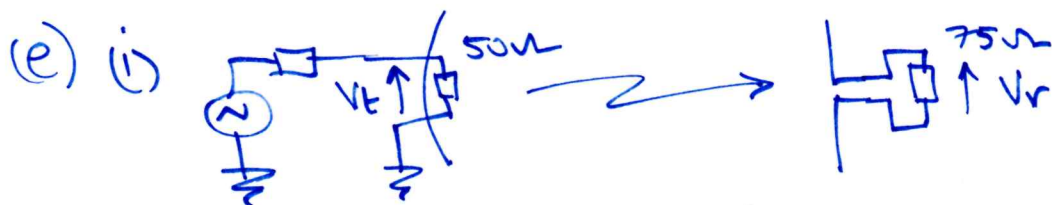
$$\therefore R_{ohmic} = 8.2 \Omega \Rightarrow \underline{D = 0.32 \text{ mm}}$$



$$P_t = \frac{V_t^2}{50} = 200 \quad \therefore V_t = 100 \text{ V}_{rms} \quad V_r = 1.36 \text{ mV}_{rms} \quad (\text{from (b)})$$

$$\therefore \text{Ratio, dB} = 20 \log_{10} \left(\frac{100}{1.36 \times 10^{-3}} \right) = \underline{97.3 \text{ dB}}$$

$$(ii) \quad P_t = 25 = \frac{V_t^2}{75} \quad \therefore V_t = 43.3 \text{ V}_{rms}$$


$$A_e \text{ grd} = \frac{G \lambda^2}{4\pi} = \frac{1000 \cdot 0.326^2}{4\pi} = 8.46 \text{ m}^2$$

$$\therefore P_{recd.} = 3.63 \times 10^{-10} \cdot 8.46 = 3.07 \times 10^{-9} \text{ W} = \frac{V_r^2}{50}$$

$$\therefore V_r = 3.92 \times 10^{-4} \text{ V}_{rms} \quad \text{and} \quad \text{Ratio, dB} = 20 \log_{10} \left(\frac{43.3}{3.92 \times 10^{-4}} \right) = \underline{100.9 \text{ dB}}$$

(not same as (i) due to 50 & 75 Ω difference)

2(a)

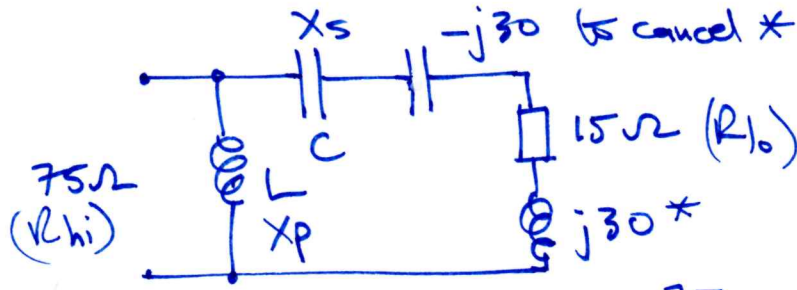

$$Q = \sqrt{\frac{R_{hi}}{R_o} - 1} = \frac{R_{hi} \leftarrow 75}{X_p} = \frac{X_s}{R_o \leftarrow 15} = 2 @ 10 \text{ MHz}$$


$$\therefore X_p = 37.5 = 2\pi f L \quad \therefore L = 59.7 \mu\text{H}$$

$X_s = 30$ but we can also include the other * capacitor into a single C with X_s

$$\therefore X'_s = 30 + 30 = 60 = \frac{1}{2\pi f C}$$

$$\therefore C = 265 \text{ pF}$$

(b)

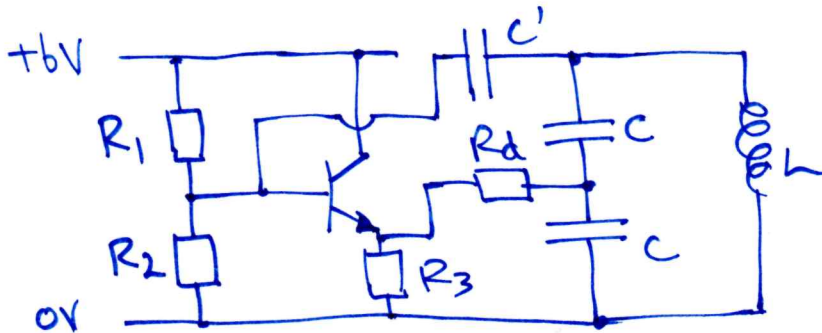

$$f = 300 \text{ MHz} = \frac{1}{2\pi\sqrt{LC}} \Rightarrow C = 50 \text{ nF}$$

$$Q = 25$$

$$\therefore 2\pi f L Q = 2.4 \text{ k}\Omega \text{ inductor loss resistance}$$

$$C' = \text{large value} = 10 \text{ nF}, \quad C = 2.81 \text{ pF}$$

$$\text{Apparent load @ C mid-point} = \frac{2.4 \text{ k}\Omega}{4} \approx 600 \Omega$$

$$\therefore \text{choose } R_3 = R_d = 390 \Omega \text{ say } (\approx \frac{2}{3} \text{ of } 600 \Omega)$$

$$V_E \approx 3 \text{ V}_{DC} \quad \therefore V_B \approx 3.6 \text{ V}$$

$$\text{If } h_{fe} \approx 200 \text{ with } I_C \approx \frac{3}{390} \text{ then } r_e = \frac{kT/q}{I_C} \approx 30 \Omega$$

and input impedance @ base $\approx h_{fe} \times [(390 \parallel 390 + 600) + 3] \approx 56 \text{ k}\Omega$

So choose R_1 & $R_2 \sim 10 \text{ s k}\Omega$ to give $V_B = 3.6 \text{ V}$

$$\therefore R_2 = 33 \text{ k}\Omega, \quad R_1 = 22 \text{ k}\Omega$$

2(c)

EGT2


ENGINEERING TRIPOS PART IIA

XXday YY April 2022, Module 3B1, Question 2


Candidate No.

CRB

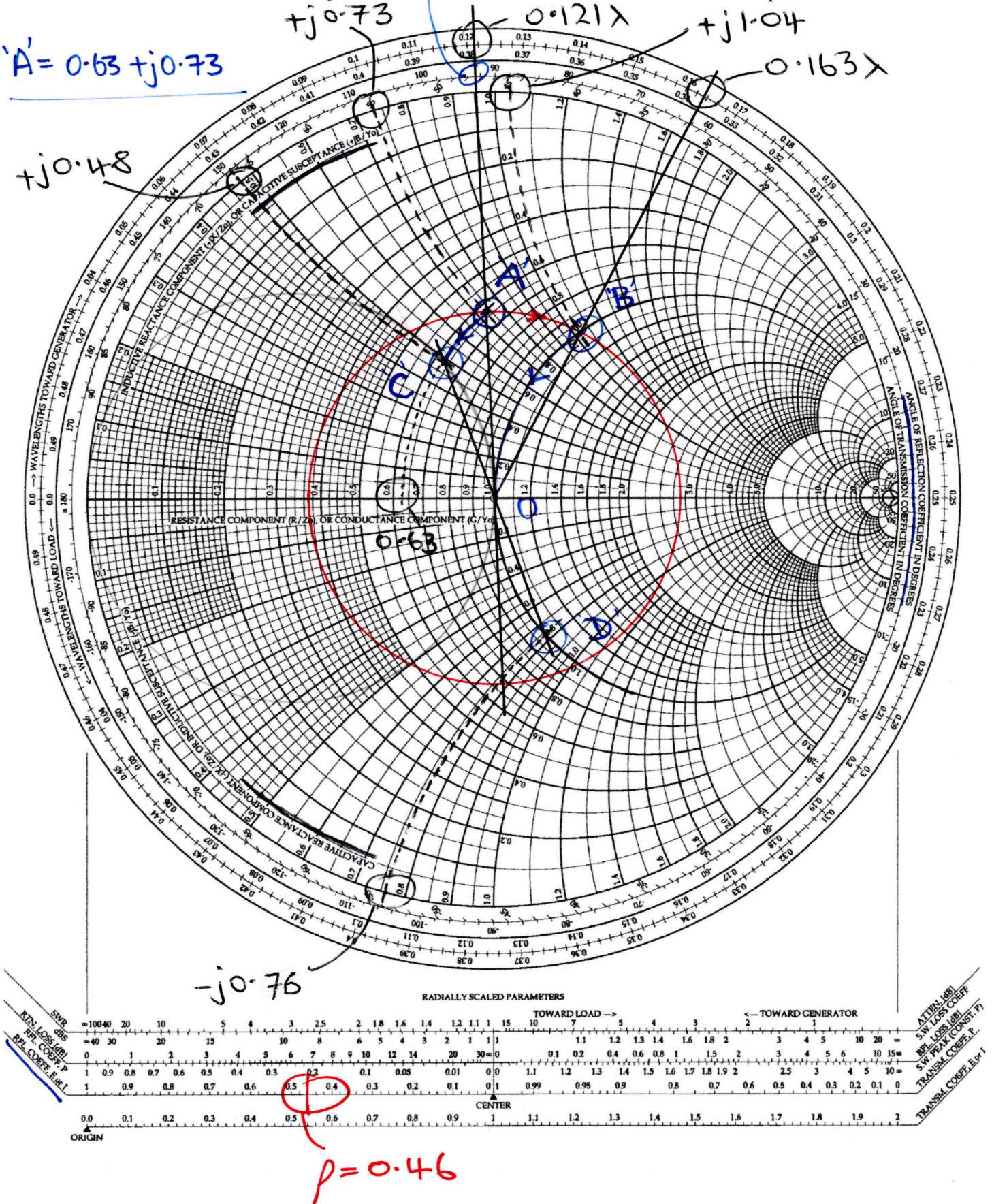Smith Chart for Question 2 - to be detached and handed in with script.



2(c)(i)

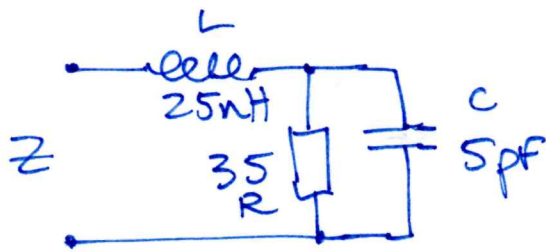

@ 300 MHz

$$Z = j2\pi fL + \frac{R}{1 + j2\pi fCR}$$

$$= j47.1 + \frac{35}{1 + j0.33}$$

$$\therefore Z = j47.1 + \frac{35(1 - j0.33)}{1.11} = \underline{31.5 + j36.7 \Omega}$$


Normalise to $50 \Omega \rightarrow$ point 'A' @ $0.63 + j0.73$ on chart

S_{11} from REF. COEFF. scale = 0.46, angle is 93°

$$\therefore \underline{S_{11} = 0.46 \angle 93^\circ}$$

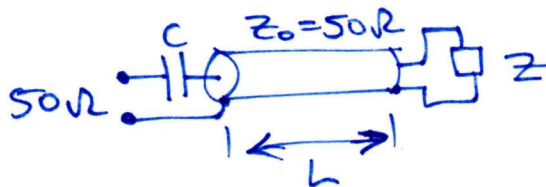(ii) $v = \frac{1}{\sqrt{LC}}$ and $Z_0 = \sqrt{\frac{L}{C}} \therefore v = f\lambda = \frac{1}{Z_0 C}$

$$\therefore v = \frac{1}{78 \times 10^{-12} \times 50} = 2.56 \times 10^8 \text{ m/s} \quad \text{and} \quad \lambda = 0.853 \text{ m @ } 300 \text{ MHz}$$



Point 'A' to 'B' = $(0.163 - 0.121)\lambda = 0.042\lambda \approx \underline{36 \text{ mm}}$

'B' \rightarrow 0 series capacitor $-j1.04 \Rightarrow -j52 \Omega = \frac{1}{j2\pi fC}$
 $\times 50$ denormalise


$$\therefore \underline{C = 10.2 \text{ pF}}$$

(iii) Matching with 2 capacitors (only possible as load is inductive):
 Series cap. 'A' \rightarrow 'C' such that $1/jC =$ 'D' point is on $|Re|=1$ circle, so that the admittance = $1 - j?$ and the $-j?$ will be cancelled with a parallel capacitor ($+j?$)

$$\therefore \text{series cap: } \frac{1}{2\pi f C_s} = 50(0.73 - 0.48) \text{ @ } 300 \text{ MHz}$$


$$\therefore \underline{C_s = 42.4 \text{ pF}}$$
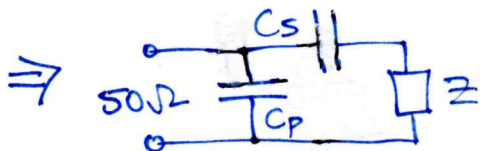
$$\text{Parallel cap: } \frac{1}{2\pi f C_p} = \frac{50}{0.76} \therefore \underline{C_p = 8.06 \text{ pF}}$$




Assessor note: Take care using the Smith Chart in this part.

3(a)

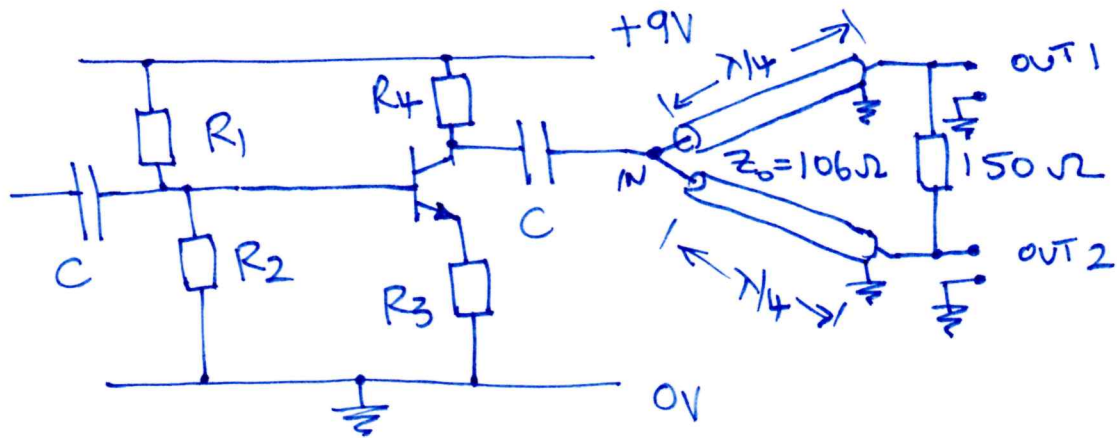

Wilkinson coupler uses a pair of $7/16$ lengths of line with $Z_0 = \sqrt{2} \times 75 \Omega$, with a $2 \times 75 \Omega$ line resistor between the output ports. This evenly splits power to IN between OUT1 and OUT2 with isolation between the 2 outputs.

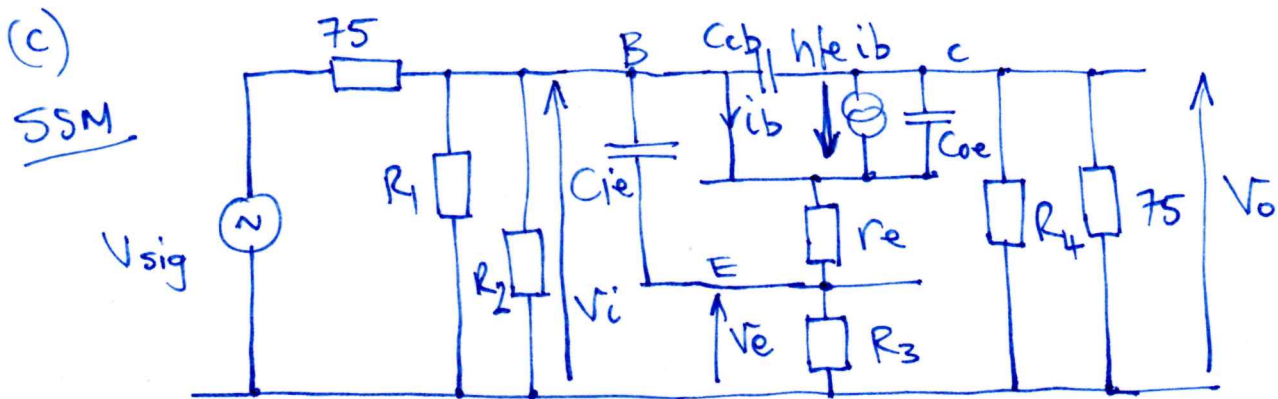- (b)
- $R_4 = 75 \Omega$ for correct output impedance
 - with 20dB net gain ($\times 10$) when loaded, open ckt. gain is $\times 20 \therefore R_3 + r_e = R_4 / 20 = 3.75 \Omega$
 - As $V_c = \frac{9}{2} V$ dc. then $I_c = \frac{4.5}{75} = 0.06 A \therefore r_e = \frac{0.025 \Omega}{0.06} \Rightarrow R_3 = 3.3 \Omega$
 - Coupling caps, C, are 'large' eg: $10 nF$
 - $R_2 \approx 1.5 \times 75 \Omega = 113 \Omega \Rightarrow 100 \Omega$ say
 - To set $V_B = V_E (0.06 \times 3.3) + 0.65V = 0.85V$, choose R_1 such that $\frac{100}{100 + R_1} \times 9 = 0.2 \Rightarrow R_1 = 880 \Omega$
 - check $R_{in} = 100 \parallel 880 \parallel 250 \times 3.75 = 82 \Omega$ vs. 75Ω o.k.



3(c) contd. $R_e = 0.42 \Omega$ from (b), $f_t = 18 \times 10^9 = \frac{1}{2\pi R_e C_{ie}}$

$\therefore C_{ie} = 21 \text{ pF}$. Also $v_e = \frac{R_3}{R_3 + r_e} \cdot v_i = 0.888 v_i$

So equivalent value of C_{ie} to $\text{gnd.} = (1 - 0.888) \cdot 21 \text{ pF}$

$\therefore C_{ie}' = 2.35 \text{ pF}$

and from Miller effect with gain of 10 (loaded) $C_{cb}' = (1+10)C_{cb}$

$\therefore C_{cb}' = 2.42 \text{ pF}$


Hence input time constant $\approx 75 \parallel 82 \Omega \times C_{ie}' + C_{cb}' (= 4.77 \text{ pF})$

$\therefore f_{-3dB} = \frac{1}{2\pi \cdot 39 \cdot 4.77 \times 10^{-12}} = 852 \text{ MHz}$
 $\therefore \text{OK @ } 520 \text{ MHz } \checkmark$

(Note: output side is higher freq. due to lower capacitance $\sim (0.24 + 0.15) \text{ pF}$ with $37.5 \Omega \Rightarrow > 10 \text{ GHz}$)

(d)

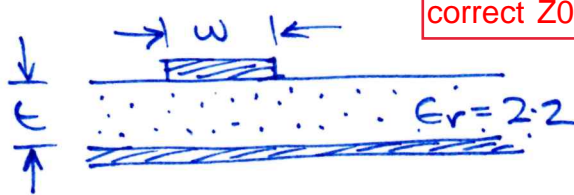Assessor note: Take care to use the correct Z_0



for $Z_0 = 106 \Omega = \sqrt{\frac{L}{C}}$
 $v = \frac{1}{\sqrt{LC}} \therefore Z_0 = \frac{1}{vC}$

With $\epsilon_r = 2.2$, $v = \frac{1}{\sqrt{\epsilon_0 \epsilon_r \mu_0}} = \frac{3 \times 10^8}{\sqrt{2.2}} = 2.02 \times 10^8 \text{ m/s}$

@ $f = 520 \times 10^6 \text{ Hz}$, $\lambda = \frac{2.02 \times 10^8}{520 \times 10^6} = 0.389 \text{ m} \therefore \frac{\lambda}{4} = 97.2 \text{ mm}$
 section lengths:

$C = \frac{A \epsilon_0 \epsilon_r}{t} \approx \frac{(w+2t) \epsilon_0 \epsilon_r}{t}$, capacitance/unit length

$\therefore Z_0 = \frac{t}{(w+2t) \epsilon_0 \epsilon_r v} = 106 = \frac{1.6 \times 10^{-3}}{(w+2.40) \times 10^{-3} \cdot 8.854 \times 10^{-12} \cdot 2.2 \cdot 2.02 \times 10^8}$


$\therefore (w+2.40) = 3.84 \Rightarrow w = 1.44 \text{ mm}$

with 150 Ω resistor between the 2 output nodes


4(a)(i) $f_{\text{dep.}} = \frac{2f v}{C_0}$, $f = 24 \times 10^9 \text{ Hz}$
 $v = 0.5 - 5 \text{ m/s}$

$\therefore f_{\text{dep.}} = 80 - 800 \text{ Hz}$

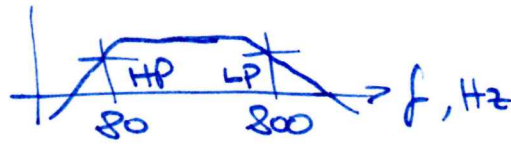choose cheby. for sharp cut-off
 high-pass & low-pass for
 bandpass filter:



$f_n = 1.231$
 $A = 1.842$

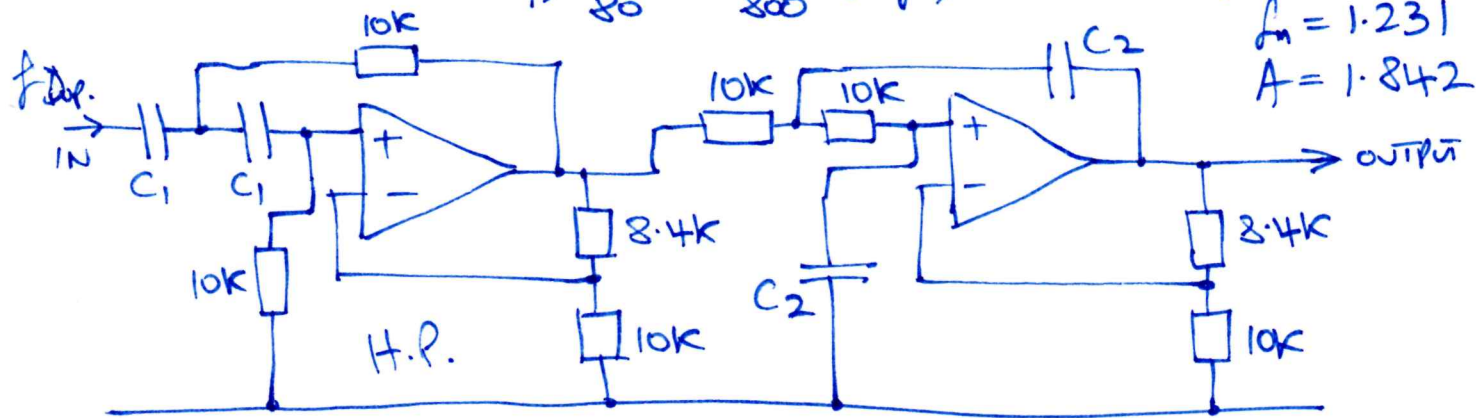


H.P. $80 = \frac{f_n}{2\pi RC_1} \leftarrow 1.231$

L.P. $800 = \frac{1}{2\pi f_n RC_2}$


$\therefore C_1 = 245 \text{ nF}$

$\therefore C_2 = 16.2 \text{ nF}$

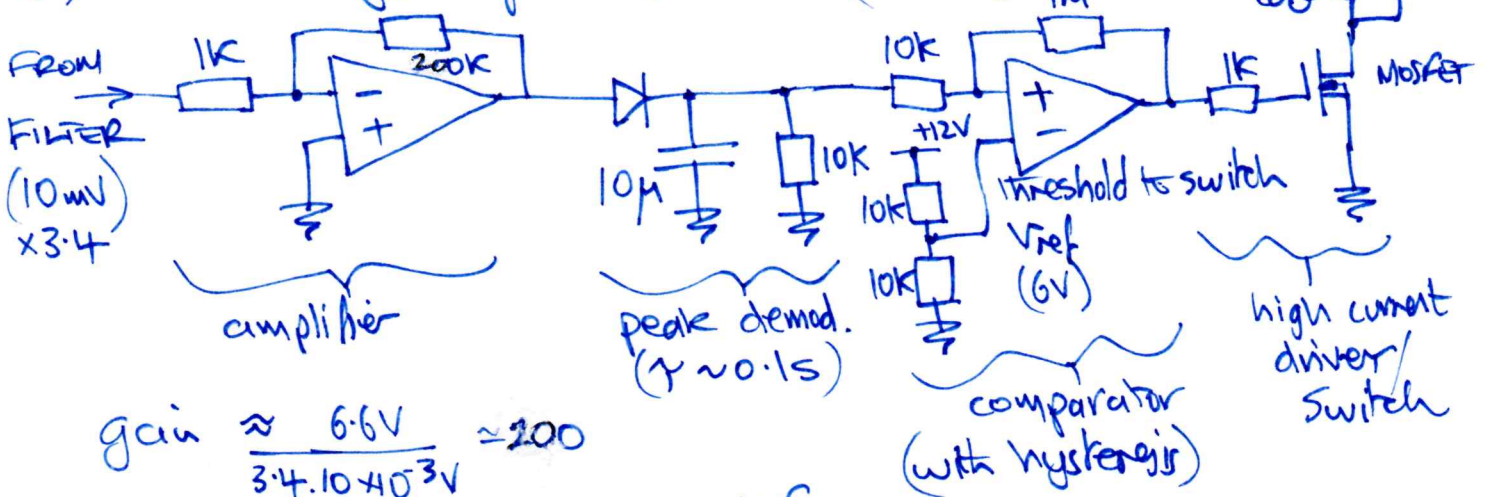(ii) mid-band gain of BP filter = $(1.842)^2 \approx 3.4$



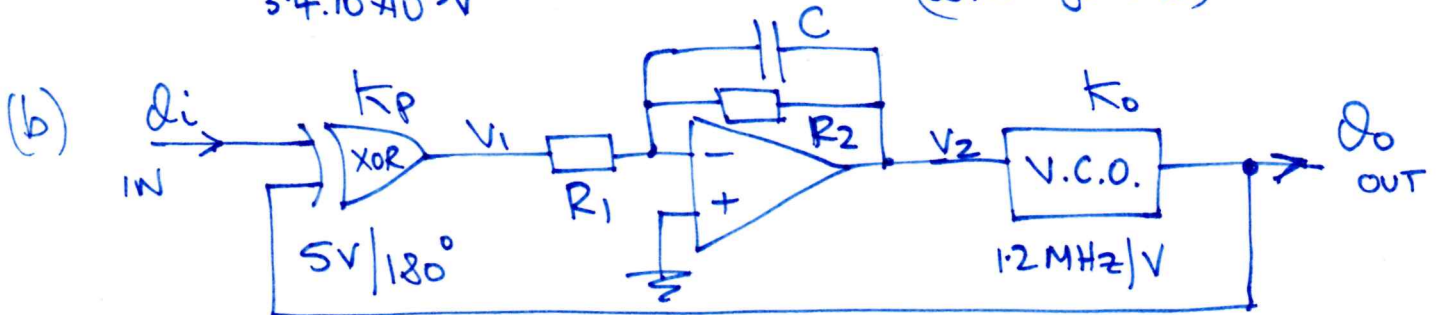gain $\approx \frac{6.6V}{3.4 \cdot 10 \cdot 10^{-3}V} \approx 200$



$C \parallel R_2 : \frac{R_2 / j\omega C}{R_2 + 1/j\omega C} = \frac{R_2}{1 + j\omega C R_2}$

$$4(b) \text{ contd. } \theta_0 \equiv e^{j(\omega t + \theta_0)} \quad \therefore \frac{d\theta_0}{dt} = j\omega\theta_0, \quad \frac{d^2\theta_0}{dt^2} = -\omega^2\theta_0$$

$$\text{Phase detector: } V_1 = K_P(\theta_0 - \theta_i) \quad \text{--- (1)}$$

$$\text{V.C.O. : } \frac{d\theta_0}{dt} = j\omega\theta_0 = K_0 V_2 \quad \text{--- (2)}$$

$$\text{Filter : } \frac{V_2}{V_1} = \frac{-R_2}{R_1(1+j\omega CR_2)} \quad \text{--- (3)}$$

Sub. for V_2 from (3) into (2):

Sub. for V_1 from (1):

$$j\omega\theta_0 = \frac{-K_0 V_1 R_2}{R_1(1+j\omega CR_2)} = \frac{-K_0 K_P(\theta_0 - \theta_i) R_2}{R_1(1+j\omega CR_2)}$$

$$\therefore j\omega\theta_0 R_1(1+j\omega CR_2) + K_0 K_P \theta_0 R_2 = K_0 K_P R_2 \theta_i$$

$$\therefore \frac{j\omega\theta_0 R_1}{K_0 K_P R_2} - \frac{\omega^2 \theta_0 R_1 R_2 C}{K_0 K_P R_2} + \theta_0 = \theta_i$$

$$\therefore \ddot{\theta}_0 \frac{R_1 C}{K_0 K_P} + \dot{\theta}_0 \frac{R_1}{K_0 K_P R_2} + \theta_0 = \theta_i$$

cf. Mechanics
Data Bk
pg 6

$$\therefore \omega_n^2 = \frac{K_0 K_P}{R_1 C} \quad \text{and} \quad \frac{2\zeta}{\omega_n} = \frac{R_1}{K_0 K_P R_2} \quad \text{Set } R_1 = 10 \text{ k}\Omega$$

$$K_0 = 12 \text{ MHz/V} = 2\pi \cdot 1.2 \times 10^6 = 7.54 \times 10^6 \text{ rad s}^{-1} \text{ V}^{-1}$$

$$K_P = 5 \text{ V}/180^\circ = 5 \text{ V}/\pi \text{ rad} = 1.59 \text{ V rad}^{-1}$$

$$\therefore \omega_n^2 = (20 \times 10^3 \cdot 2\pi)^2 = 157.9 \times 10^8 = \frac{7.54 \times 10^6 \cdot 1.59}{10^4 C}$$

$$\Rightarrow \underline{C = 76 \text{ nF}}$$

$$\text{for } 15\% \text{ overshoot, } \zeta = 0.5, \quad \omega_n = 126 \times 10^3 \text{ rad/s}$$

$$\therefore \underline{R_2 = \frac{R_1 \omega_n}{2\zeta K_0 K_P} = \frac{10^4 \cdot 126 \times 10^3}{2 \cdot 0.5 \cdot 7.54 \times 10^6 \cdot 1.59} = 105 \Omega}$$