

3B1 Crib 2023

1. (a)

Norm to $50\Omega \rightarrow 5+2j$ (B1) Plot and read off smith chart $0.71\angle 8^\circ$

n.b an analytic solution is also possible and equally valid.

(b)

Assume fringing fields extend by thickness of board.

$$C = \frac{(w + 2d)\epsilon_o\epsilon_r}{d}$$

$$Z_0 = \sqrt{\frac{L}{C}}, v = \frac{1}{\sqrt{LC}} = \frac{c_o}{\sqrt{\epsilon_r}}$$

$$Z_0 = \frac{1}{vC} = \frac{\sqrt{\epsilon_r}}{c_o} \frac{d}{(w + 2d)\epsilon_o\epsilon_r}$$

$$(w + 2d)\epsilon_o\epsilon_r c_o Z_0 = \sqrt{\epsilon_r} d$$

$$(w) = \frac{\sqrt{\epsilon_r} d}{\epsilon_o\epsilon_r c_o Z_0} - 2d$$

W=2.7mm

c)

See Smith chart. Start at B1. Rotate around centre to unit R circle (B2) clkwise towards generator.

Track length $0.5\lambda - (0.239\lambda + 0.188\lambda) = 0.449\lambda$

$\lambda = 3 \times 10^8 / (250 \times 10^6 \times \sqrt{4.2}) = 58.5\text{cm}$

so track length is 262mm.

Required reactance is $-2j \times 50$, $\rightarrow 6.4\text{pF}$

Reduce with higher ϵ_r , shunt C, or series L.

(ii) ϵ_r will change electrical length and the characteristic impedance. Z_0 is now 62.5Ω . Need to switch smith chart to this characteristic impedance.

$250+100j$ becomes $4+1.6j$ (C1)

$\lambda = 3e8 / (250e6 \times \sqrt{2.69}) = 73.2\text{cm}$, so the line is 0.358λ long.


Starting at 0.237λ this takes us to $(0.237+0.0.358)-0.5 = 0.095\lambda$ (point C2 on smith)

Capacitor needs renormalising to 62.5Ω , so is $-1.6j$

Now move around const R circle by $-1.6j$. Start at $0.3+0.63j$ so end with $0.3-1.03j$. point C3.

V reflection = $0.74\angle -86^\circ$

A popular question with a range of answers. In (a) a common mistake was reading from the wrong axis of the Smith Chart. Most could get the width in (b) a common omission was the assumption that the fringing fields expand by the board thickness. The straight forward Smith chart in the 1st part of (c) was well answered. The 2nd part, most realised that the change in ϵ_r would give a change in the electrical length, but many missed that the impedance also changes.

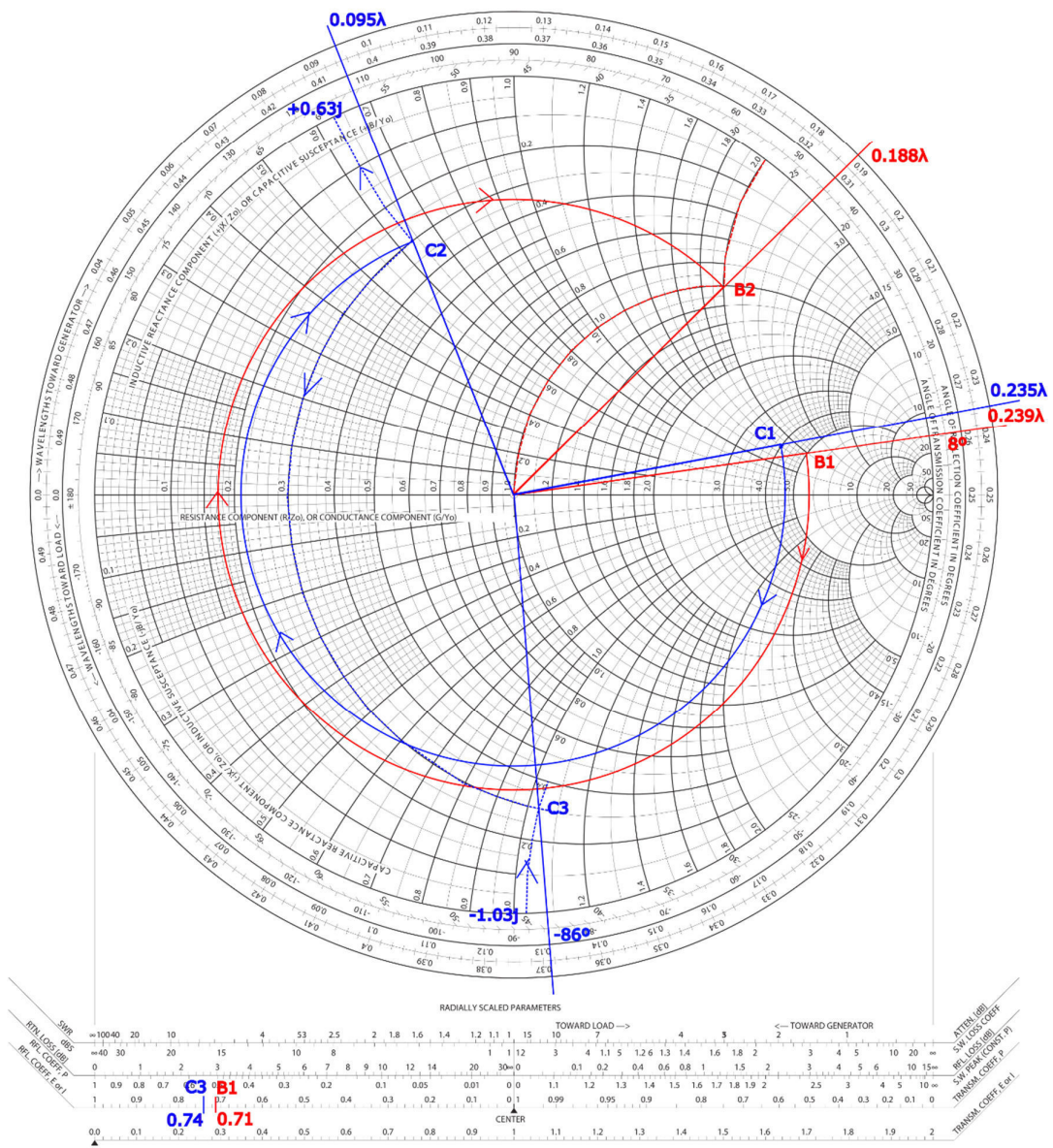

2.

a) i) efficiency = directivity / gain = -2dB = 63.1%

$$\text{efficiency} = r_{\text{rad}} / (r_{\text{rad}} + r_{\text{ohmic}})$$

$$r_{\text{rad}} + r_{\text{ohmic}} = 120$$

$$r_{\text{rad}} = 120 \times 63.1 = 75.7 \Omega$$

(ii) Use gain to account for losses.

Peak radiated power is 10dBm + 21dB = 31dBm = 1.2589W


$$S = 1.2589 / (4 \times \pi \times 10^2) = 0.001 \text{ W/m}^2$$

Dipole has gain of 2.15dB

$$A_e = 0.0156 \text{ m}^2$$

$$\text{Power} = A_e \times S = 15.6 \mu\text{W}$$

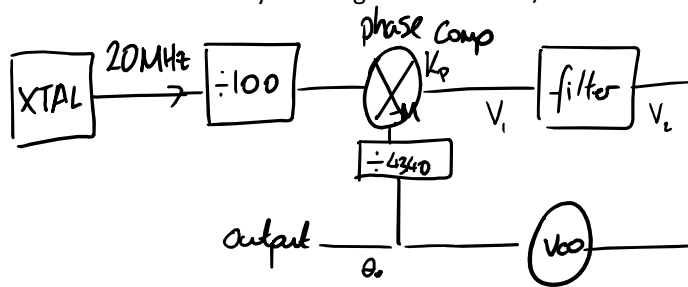b) i) Need to divide 20MHz by 100 to get 200kHz. $868 / 0.2 = 4340$ for phase comparator



Phase comparator compares $\frac{\theta_{VCO}}{M}$ and $\frac{\theta_{XTAL}}{N}$

ii) Call V_1 V_{in} and V_2 V_{out} for the filter.

$$\frac{d\theta}{dt} = j\omega\theta = K_o V_2$$

$$V_1 = K_p (\theta_{\text{ref}} - \theta_0 / M)$$

$$V_1 = -V_2 \frac{R_1 + R_1 R_2 j\omega C}{R_2}$$

$$K_p (\theta_{\text{ref}} - \theta_0 / M) = -\frac{j\omega\theta}{K_f} \left(\frac{R_1 + R_1 R_2 j\omega C}{R_2} \right)$$

$$= -\frac{j\omega R_1 \theta}{K_o R_2} + \frac{R_1 \omega^2 \theta C}{K_o}$$

Use that $-\omega\theta = \dot{\theta}$ and $\omega^2\theta = \ddot{\theta}$. Compare to Mech databook.

$$\omega_n^2 = M \frac{R_1 C}{K_o K_p}$$

$$\frac{2c}{\omega_n} = M \frac{R_1}{K_o K_p R_2}$$


$$c = \frac{\omega_n M R_1}{2 K_o K_p R_2} = \frac{M R_1}{2 K_o K_p R_2} \sqrt{\frac{M R_1 C}{K_o K_p}} = \frac{1}{2 R_2} \sqrt{\frac{M R_1}{C K_o K_p}}$$

(c)

At input side of the Wilkinson coupler, the transformed outputs appear in parallel. So need to match to 100 ohm to make a 50 ohm input. Therefore the $\lambda/4$ sections should be $\sqrt{100 \times 75} = 86.6$ ohms. A 150 ohm resistor between the outputs completes the Wilkinson.

A few very good answers along with some very poor ones. In part (a) a worrying number struggled with the conversion of gains from dB to linear in part (i). Part (ii) was mostly well answered although many double counted the antenna efficiency by using antenna gain and then multiplying by efficiency. (There is a small ambiguity as to whether a 50% matching loss occurs on both sides, both answers were accepted). In (b) most realised that a divider is needed but omitted this from the loop analysis.

3 (a)

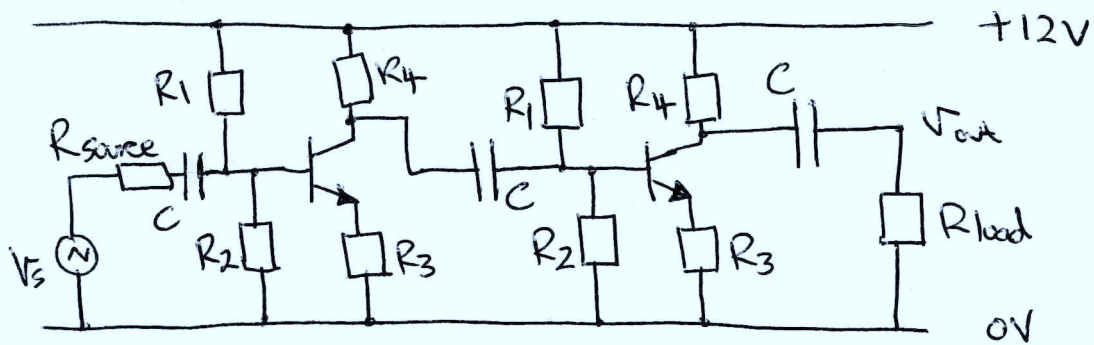

R_1, R_2 : base bias resistors - set base voltage for $V_C = \frac{V_S}{2}$ and set Z_{in} imped.
 R_3 : negative feedback to set stage gain
 R_4 : output resistance, with gain $\approx -R_4/(R_3 + r_e)$
 C : coupling capacitors to pass signal frequencies but block d.c. bias voltages between stages

(b) $R_4 = 50 \Omega$ for matched output impedance

To determine gain: $33 \text{ dB} = \times 44.7 \Rightarrow \times 6.7$ per stage
 with 2 extra coupling stages (compared to source \rightarrow load case), we have a required gain of $\times 13.3$ per stage

$$\therefore R_3 + r_e = \frac{50}{13.3} = 3.76 \Omega$$

with $R_4 = 50 \Omega$ and $V_C = 6 \text{ V d.c.}$ ($\frac{1}{2}$ supply), $I_C = 0.12 \text{ A}$

$$\therefore r_e = \frac{0.025}{I_e} = 0.21 \Omega \quad \therefore \underline{R_3 = 3.55 \Omega} \quad (\text{say } 3.3 \Omega \text{ std.})$$

Choose $R_2 = 1.5 \times 50 = 75 \Omega$ and set $V_B = 0.65 + 0.12 \times 3.3 = 1.05 \text{ V}$ $\pm 10\%$ optimal $\approx 1.1 \text{ V}$

$$\therefore \underline{R_1 = 750 \Omega}$$

C should have small impedance $< 1 \Omega$ @ 860 kHz so with

$$\underline{C = 10 \text{ nF}}, \quad |Z| \approx 0.02 \Omega \quad \text{Input imped.} = 75 \parallel 700 \parallel 750 = 62 \Omega \quad \text{O.K.}$$


(c) for -3 dB roll-off, we need value for C_{ie} and analyse

$$\text{small-signal model: } f_c = \frac{1}{2\pi C_{ie} r_e} = 22 \times 10^9 \text{ with } r_e$$

$$= 0.21 \Omega \Rightarrow \underline{C_{ie} = 34.4 \text{ pF}}$$

3 cental (c)

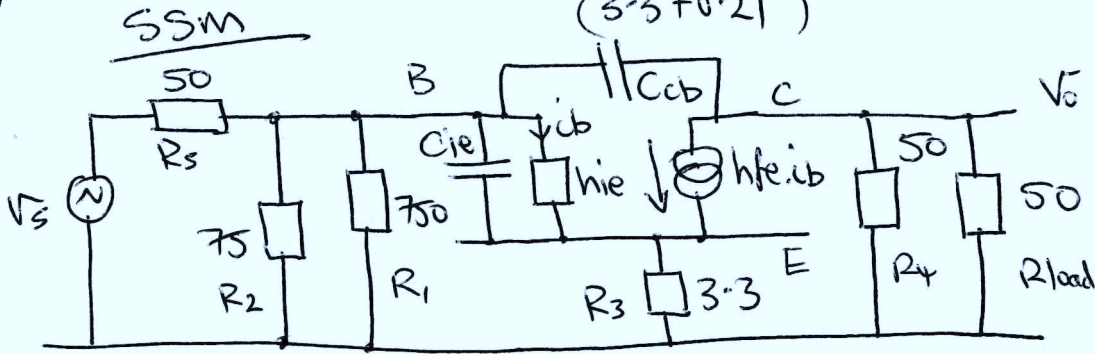Emitter gain = $\frac{3.3}{(3.3+0.21)} = 0.94$




$h_{ie} = h_{fe} \cdot r_e = 42 \Omega$. Refer input side to ground values
 for B-E equivalent components: $C_{ie} \times (1 - 0.94) \Rightarrow 2.06 \text{ pF}$
 and B-C \rightarrow \rightarrow \rightarrow $h_{ie} \times \frac{1}{(1 - 0.94)} \Rightarrow 700 \Omega$

with loaded gain = $-\frac{50/2}{(3.3+0.21)} = -7.12$

$C_{cb} \Rightarrow (1 + 7.12) \times 0.2 = 1.62 \text{ pF}$

Hence input ct becomes:

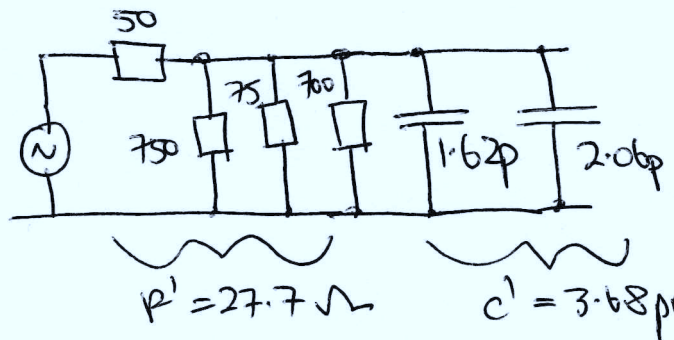


-3dB roll-off = $\frac{1}{2\pi R' C'}$
 $= 1.56 \text{ GHz}$

\therefore fine for 260 MHz operation, even with 2 stages cascaded. As 3dB is twice operating freq. then 2 stages cascaded will give $\approx -30 \text{ dB}$ operating freq. Could decrease R_3 to compensate (by $\approx 10\%$ if reqd).

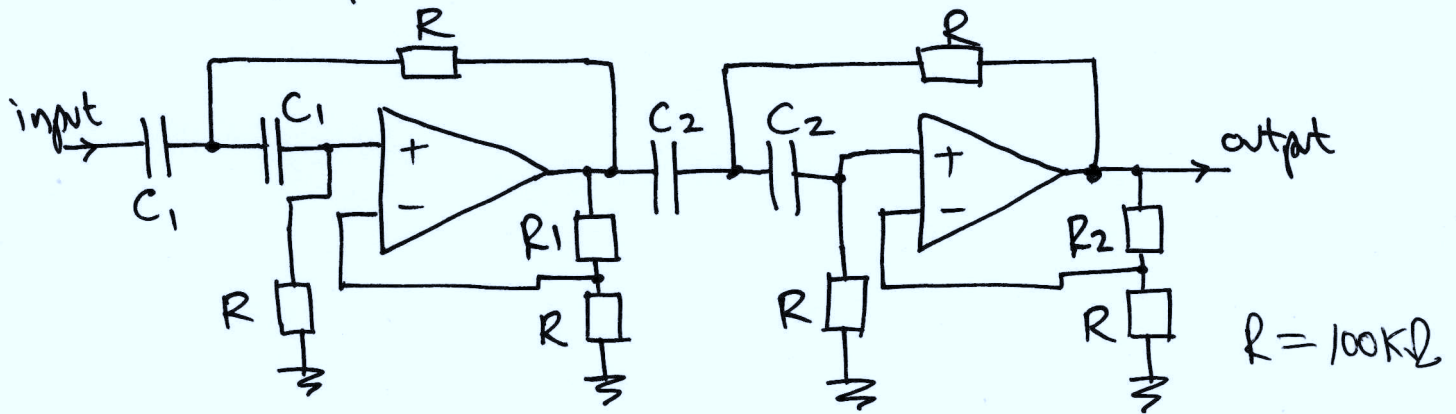(d) Use series LC between stages. $Q = 5 = \frac{\omega L}{r}$ where $r = (50 + 62)$
 in place of central coupling capacitor and $C_{res} = \frac{r}{\omega^2 L}$ but C_{res} is small and L large: 0.33 pF and 104 nH respectively. Use parallel LC with $Q = 5 = \frac{R}{\omega L}$ and $R = 50 \parallel 62 = 27.7 \Omega$ then $L = 1.03 \text{ nH}$ and $C = 33 \text{ pF}$
 coupling caps. reqd. is d.c. block. \rightarrow to stage 2 but 2 (or L will short bias to gnd.)

4(a) (i) High-pass VCVS circuit : 0.2 Hz roll-on




Use Bessel filter for pulse shape retention - important in this application. Downside is reduced sharpness in low freq. cut-off. $f_{-3dB} = \frac{f_n}{2\pi RC}$ for high-pass

$$\therefore 0.2 = \frac{1.432}{2\pi \cdot 10^5 \cdot C_1} = \frac{1.606}{2\pi \cdot 10^5 \cdot C_2}$$

$$\therefore C_1 = 11.4 \mu F, \quad C_2 = 12.8 \mu F$$


$$R_1 = (A_1 - 1)R = 8.4 k\Omega, \quad R_2 = (A_2 - 1)R = 75.9 k\Omega$$

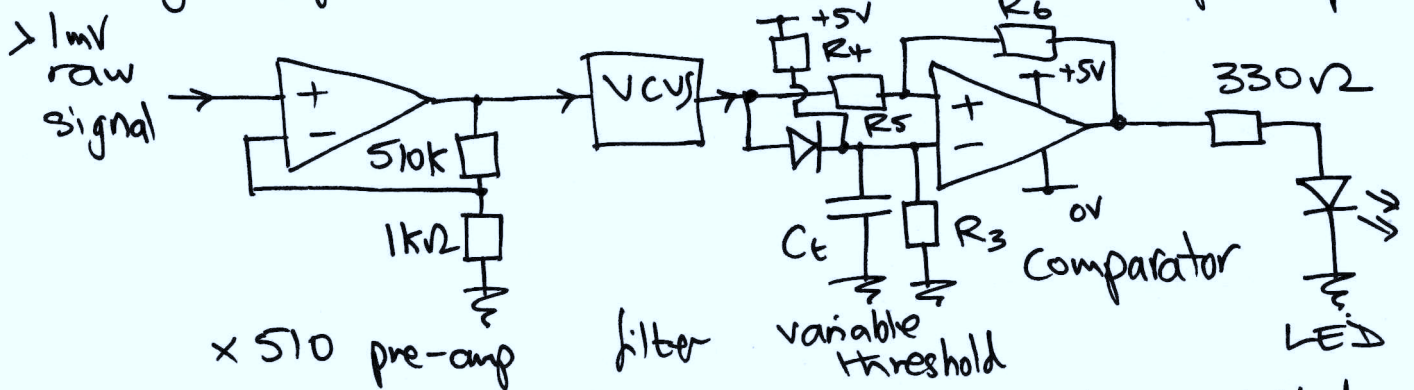(ii) Need to amplify signals by ~1000's including VCVS gain of $1.084 \times 1.759 = 1.91 \therefore \approx \times 500$ pre-amp.




filter output amplitude > 1V pulses. C_t holds threshold for say 10s $\therefore C_t = 1000 \mu F, R_3 = 10 k\Omega, R_4 = 100 k\Omega$ for 0.5V threshold. Larger pulses will increase threshold. R_5 and R_6 give switching hysteresis $\approx 0.1V$ say $\therefore R_5 = 1 k\Omega, R_6 = 47 k\Omega$

4 (b)

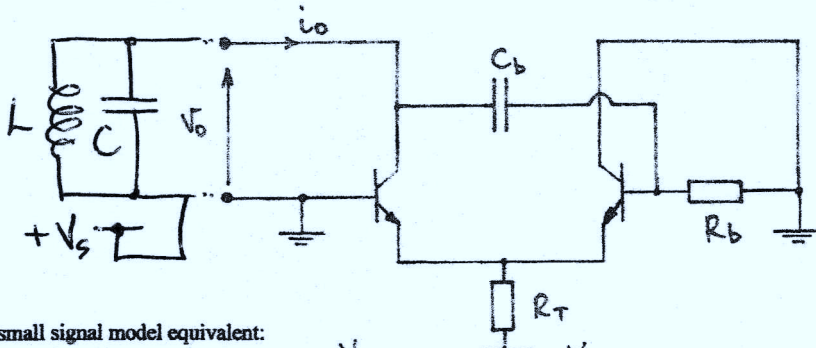

The small signal model equivalent:

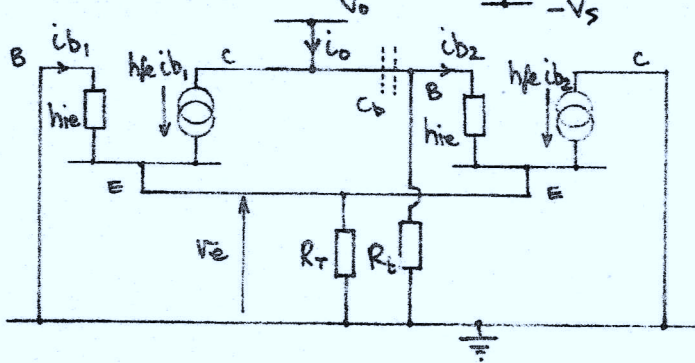

① $i_{b1} = \frac{-v_e}{h_{ie}}$, ② $i_{b2} = \frac{V_o - v_e}{h_{ie}}$, ③ $v_e \approx R_T h_{fe}(i_{b1} + i_{b2})$,
 ④ $i_o = h_{fe} i_{b1} + i_{b2} + V_o/R_b$ Subst. ① and ② into ③ :-

$$v_e = -R_T h_{fe} \frac{v_e}{h_{ie}} + R_T h_{fe} \frac{V_o - v_e}{h_{ie}} - R_T h_{fe} \frac{v_e}{h_{ie}}$$

small sf as $R_T \approx h_{ie}$

$$\therefore v_e \left(\cancel{+} \frac{2R_T h_{fe}}{h_{ie}} \right) = R_T \frac{h_{fe}}{h_{ie}} V_o \quad \therefore v_e \approx \frac{V_o}{2} \quad \text{--- (5)}$$

subst. ① and ② into ④ and subst. for v_e using ⑤

$$\therefore i_o = -\frac{h_{fe} V_o}{2h_{ie}} + \frac{V_o}{2h_{ie}} + \frac{V_o}{R_b}$$

small sf.

$$\therefore i_o = V_o \left(\frac{1}{R_b} - \frac{h_{fe}}{2h_{ie}} \right) \quad \text{and as } \frac{h_{ie}}{h_{fe}} = r_e,$$


$$Z_o = \frac{V_o}{i_o} = \left(\frac{1}{R_b} + \frac{1}{-2r_e} \right)^{-1} \Rightarrow Z_o = R_b \parallel -2r_e$$

\therefore choose $-R = -50 \Omega$ $\therefore r_e = 25 \Omega = \frac{0.025}{I_c}$

Current in $R_T \Rightarrow \frac{(3-0.65)V}{R_T \Omega} = 2 \times I_c = 2 \text{mA}$

$\therefore R_T = 1.18 \text{ k}\Omega$

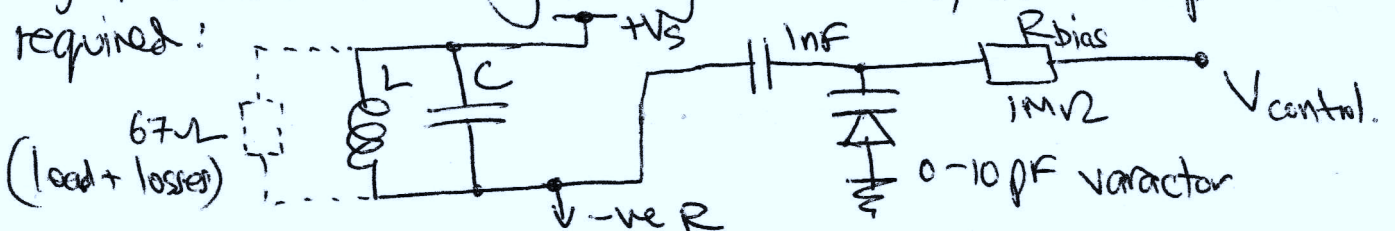To tune, add varactor across LC circuit. To reduce f_{res} by 40% means increasing C by almost 100%, hence 10 pF varactor required!



$$f_{res} = \frac{1}{2\pi\sqrt{LC}}$$

$$= 1.58 \text{ GHz}$$

with $L = 1 \text{ nH}$

$$C = 10.1 \text{ pF}$$

Parasitic \parallel loss R

$$= Q\omega L$$

$$= Q 2\pi f_{res} L$$

$$= 199 \Omega$$

Load R

$$= 100 \Omega$$

\therefore -ve resistance

$$< 100 \parallel 199 \Omega$$

$$< 67 \Omega$$

Examiner's comments

Q1 and Q2 – comments in crib text

Q3 RF amplifier

A very popular question with good attempts on the whole. The 2-stage amplifier design was well answered, although the gain was sometimes incorrect by a factor of 2 either way. The frequency response was also quite well attempted in many cases, although the unloaded gain was occasionally considered rather than the loaded value. The resonant filter section at the end attracted a number of attempts of rather variable quality.

Q4 VCVS filters and oscillator

The VCVS filter section was quite straightforward and well attempted in most cases, with a correct choice of filter type and values in many cases although a Chebyshev filter would have been a poor choice given the importance of pulse shape. The circuit design was less well answered in general, the best attempts included a variable gain section or amplitude tracking threshold. The negative impedance oscillator was generally well attempted.