

3B1 CP1B 2014

1(a)
$$\frac{P.G}{2\pi R^2} = \frac{50 \times 10^3 \cdot 1.5}{2\pi (650 \times 10^3)^2} = \underline{2.83 \times 10^{-8} \text{ W m}^{-2}}$$

assuming a transmitter antenna gain of 1.5 radiating into a hemisphere.

$$P_r \text{ density} = \frac{1}{2} E^2 / \eta = \frac{1}{2} H^2 \eta \quad \text{where } \eta = 120\pi, E = \eta H$$

$$\therefore E = 4.62 \times 10^{-3} \text{ V m}^{-1}$$

$$H = 1.23 \times 10^{-5} \text{ A m}^{-1} \quad [15\%]$$

(b)
$$R_r = 80\pi^2 \left(\frac{\Delta Z}{\lambda}\right)^2$$
 for ideal dipole, for short dipole with linear current distribution $R_r = 20\pi^2 \left(\frac{\Delta Z}{\lambda}\right)^2$

@ $77.5 \times 10^3 \text{ Hz}$ and $c = 3 \times 10^8 \text{ m/s}$
 $c = f\lambda \Rightarrow \lambda = 3871 \text{ m}$

$$\therefore R_r = 20\pi^2 \left(\frac{0.8}{3871}\right)^2 = \underline{8.43 \times 10^{-6} \Omega}$$

efficiency, $e = \frac{R_r}{R_r + R_{ohmic}}$, $R_{ohmic} = \frac{\rho l}{A}$

check skin depth, $\delta = \sqrt{\frac{2}{\omega \mu_0 \sigma}} = 1.65 \text{ mm}$ \therefore aerial wire is fully filled with current.

$$\therefore R_{ohmic} = \frac{\rho \cdot 0.8}{\pi (2 \times 10^{-3})^2 / 4} = 0.21 \Omega \quad \text{with } \rho = \frac{1}{1.2 \times 10^6} \Omega \text{m}$$

$$\therefore e = \frac{8.43 \times 10^{-6}}{(0.21 + 8.43 \times 10^{-6})} = \underline{4 \times 10^{-5} \text{ or } 0.004\%}$$

[25%]

very low, as expected from such a short antenna.

1(c) $D = G/e = 1.5$ with $e = 4 \times 10^{-5}$ from (b)

$\therefore G = 6 \times 10^{-5} = \frac{4\pi A_e}{\lambda^2}$ antenna eqn.

$\therefore A_e = 71.5 \text{ m}^2$


$\therefore V_r = EL$ into open ckt. \therefore into R_m / load = $\frac{EL}{2}$ (matched)
 $P_r = \frac{1}{2} A_e E^2 / r = \frac{E^2 L^2}{8 R_m}$ ($\frac{1}{2} \frac{V_r^2}{R_m}$)

$\therefore \frac{A_e E^2}{r} = \frac{E^2 L^2}{4 R_m}$

$\therefore R_m = \frac{r L^2}{4 A_e} = \frac{120\pi \cdot 0.8^2}{4 \times 71.5} = 0.84 \Omega$

Gain = 6×10^{-5} in dB = $10 \log_{10}(6 \times 10^{-5}) = -42.2 \text{ dB}$ [40%]

(d)

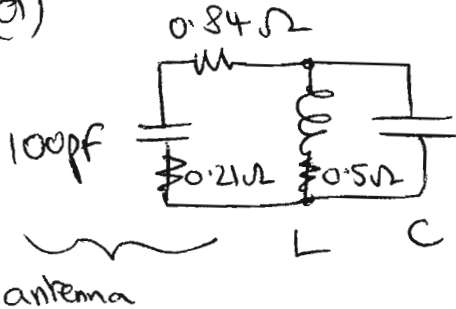

$L = 100 \mu\text{H}$

for resonance at 77.5 kHz

$f_{res} = \frac{1}{2\pi\sqrt{LC}}$ $\therefore C = 42.2 \text{ nF}$


$\therefore 42.1 \text{ nF}$ reqd.

Q-factor = $\frac{\omega L}{r} = \frac{2\pi \cdot 77.5 \times 10^3 \cdot 10^{-4}}{0.5} = 97.4$

(neglecting R_{series} with antenna)
 or incl. 0.5% difference $\rightarrow 97 = Q$.

Bandwidth = $\frac{77.5 \times 10^3}{97.4} = 796 \text{ Hz}$

[20%]

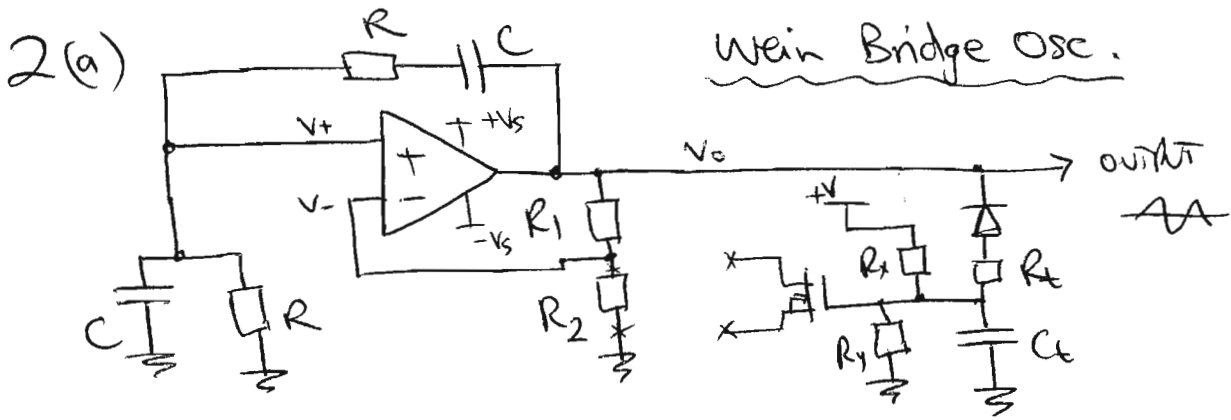

$$V_+ = \frac{V_o R}{1 + j\omega CR}$$

$$= \frac{V_o}{1 + \frac{R + \frac{1}{j\omega C}}{\frac{R}{1 + j\omega CR}}}$$

$$= \frac{V_o}{1 + (1 + \frac{1}{j\omega CR})(1 + j\omega CR)} = \frac{V_o}{3 + j\omega CR + \frac{1}{j\omega CR}}$$


Hence with $\omega = \frac{1}{CR}$ $V_+ = \frac{V_o}{3} = V_- \therefore 1 + \frac{R_1}{R_2} = 3$

for stable oscillation and $f = \frac{1}{2\pi RC}$

We can use a ntc resistor for R_1 to control gain to limit output, or use a FET/MOSFET as a variable resistance element with amplitude feedback from a diode demodulator. R_f and R_4 are bias resistors to set amplitude: initial gain > 3 for start-up. Choose R_f and C_f for long time constant to avoid sine wave distortion eg: $R_f = 100k\Omega$, $C_f = 1\mu F$. For 10kHz, $R = 10k\Omega$, $C = 1.59nF$. Supply $\pm 5V$. [35%]

(b) Bandpass filter 100Hz - 500Hz: use Bessel for minimal waveform distortion (linear phase \equiv constant time delay for all freqs. in pass-band).

HP: 100Hz
LP: 500Hz

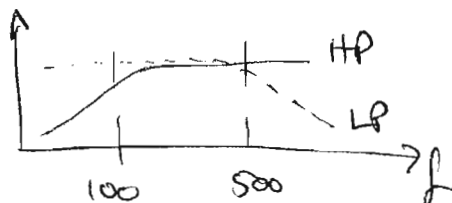

2(b)

Low Pass

High Pass

$R = 10k\Omega$

Low Pass

stage 1 $500 = \frac{1}{2\pi \cdot 10^4 \cdot C_1 \cdot 1.432} \quad \therefore C_1 = 22.2nF$ $R_n = (A-1)R$
 $R_1 = 840$

stage 2 $500 = \frac{1}{2\pi \cdot 10^4 \cdot C_2 \cdot 1.606} \quad \therefore C_2 = 19.8nF$ $R_2 = 7590$

High Pass

stage 3 $100 = \frac{1.432}{2\pi \cdot 10^4 \cdot C_3} \quad \therefore C_3 = 228nF$ $R_3 = 840\Omega$

stage 4 $100 = \frac{1.606}{2\pi \cdot 10^4 \cdot C_4} \quad \therefore C_4 = 256nF$ $R_4 = 7590\Omega$

[30%]


(c) Negative Impedance Converters (NIC) form the basis of the gyrator circuit to convert a 'C' into 'L'. Inductor synthesis is limited by opamp: slew rate, V_{limit} , freq. response, current limits

$V_- = V_i = V_+$

$i' = i$

$\therefore Z_{in} = \frac{V_i}{i} = -Z$

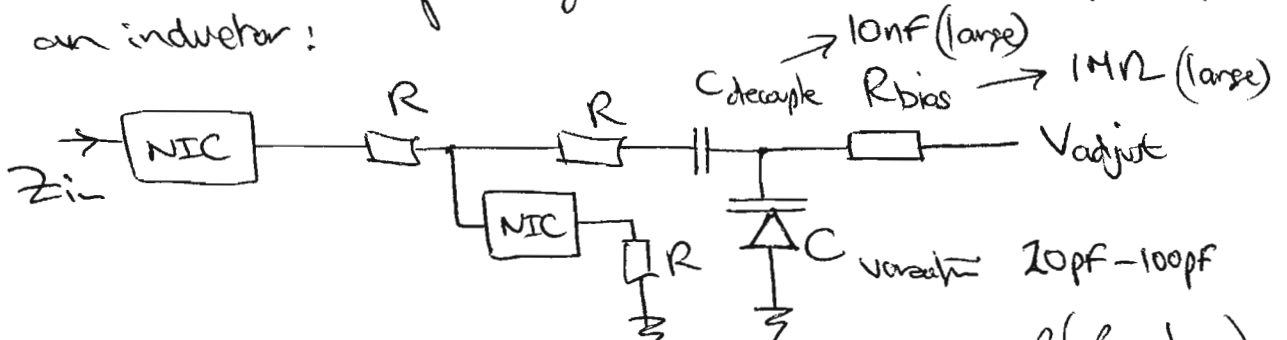Interconnect a pair of NICs and R 's and C to make an inductor:




$$Z_{in} = - \left[R + \frac{-R \parallel R + \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right] = - \left[R + \frac{-R(R + \frac{1}{j\omega C})}{-R + R + \frac{1}{j\omega C}} \right]$$

$$= - [R - R^2 j\omega C - R] = j\omega C R^2 \equiv j\omega L$$

with $L = CR^2$. To vary electronically, use varactor

3(a)

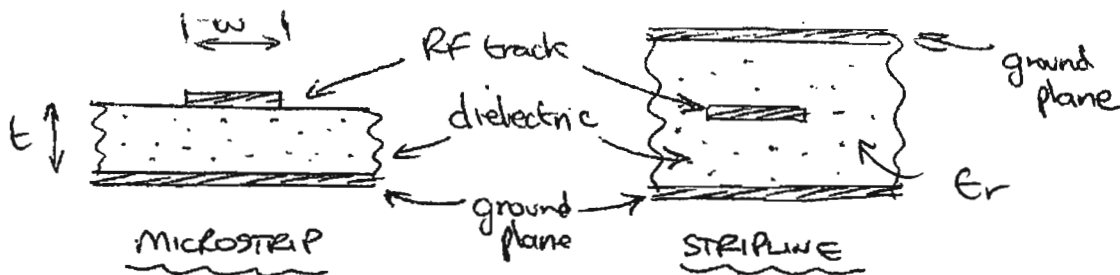

- easy to fabricate
- easy for surface mount components/connections
- higher radiation losses
- more complex fabrication
- vias required for connections
- low loss

$t = 1.6 \text{ mm}$ $\epsilon_r = 2.3$

[10%]

(b)

Antenna patch $\lambda/2$ for resonance @ 10.6 GHz

$$v = \frac{c_0}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{2.3}} = 1.978 \times 10^8 \text{ ms}^{-1} = f\lambda$$

$\therefore \lambda = 0.0187 \text{ m}$ $\therefore \lambda/2 = 9.33 \text{ mm}$
square sides

For stripline, C per unit length = $\frac{A \epsilon_0 \epsilon_r}{t} = \frac{2(w+2t) \epsilon_0 \epsilon_r}{t}$

$v = 1.978 \times 10^8 = \frac{1}{\sqrt{LC}}$ and $Z_0 = \sqrt{\frac{L}{C}} = \frac{1}{\sqrt{C}}$

$\therefore Z_0 = \frac{\sqrt{\epsilon_r} t}{\epsilon_0 2(w+2t)} = 50 \Omega$

with $t = 1.6 \times 10^{-3}$ $\Rightarrow (w+2t) 0.4028 = t$

$\therefore w = 0.77 \text{ mm}$ [30%]

(c) $0.66 \angle -39^\circ = (1.4 - 2j)$ on Smith chart $\Rightarrow (70 - 100j) \Omega$

(d) length of T-line, $l = (0.196 + 0.182)\lambda = 0.378\lambda$ [15%]

$\therefore l = 0.378 \times 18.7 \text{ mm} = 7.07 \text{ mm}$


$j1.75$ is cancel with series capacitor $\equiv -j87.5 \Omega$

$87.5 = \frac{1}{2\pi f C}$ $f = 10.6 \times 10^9 \text{ Hz}$


$\Rightarrow C = 0.172 \text{ pF}$ [25%]

3(c)

Chart for question 3; to be detached and handed in with script.

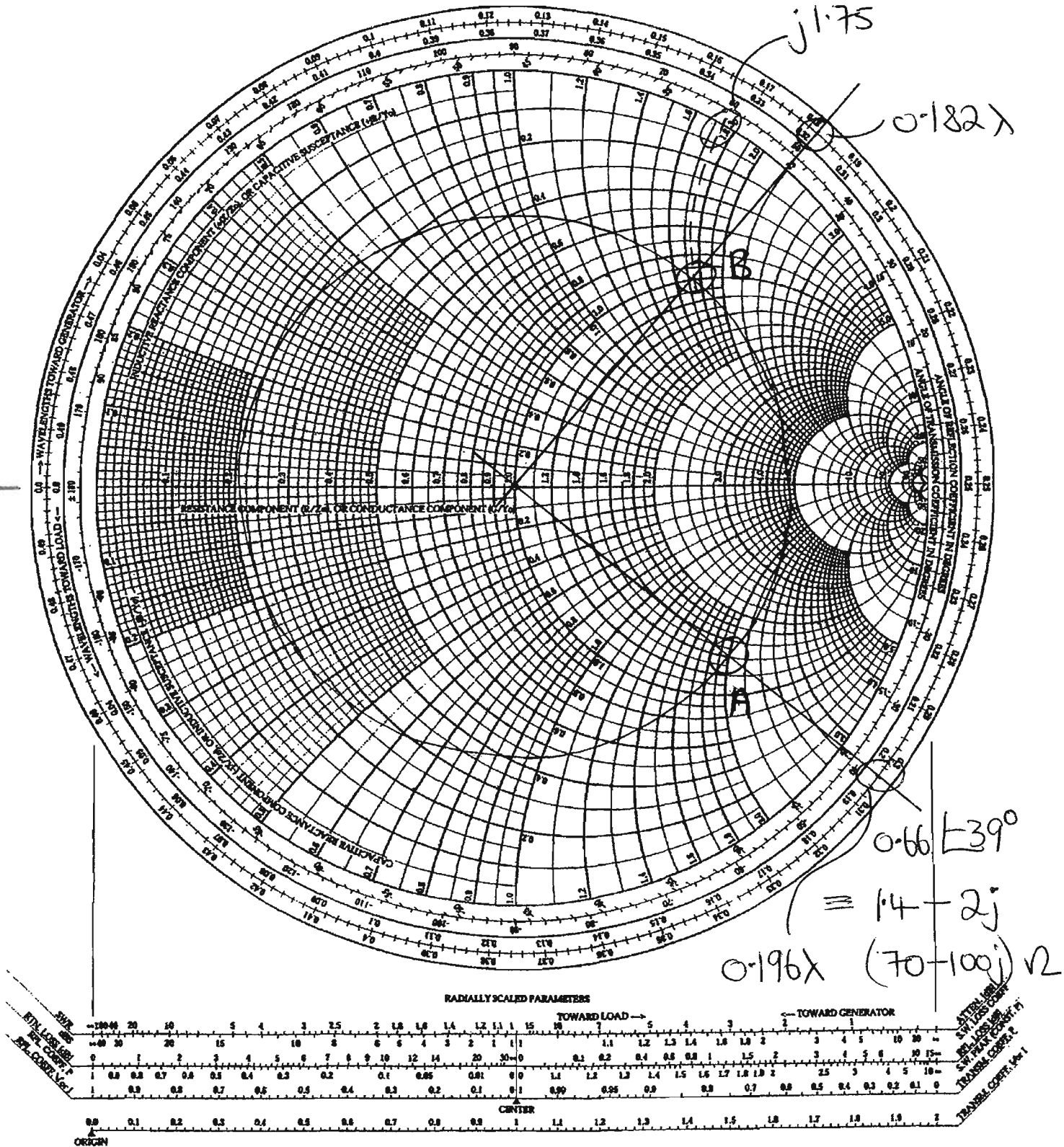

3(e)

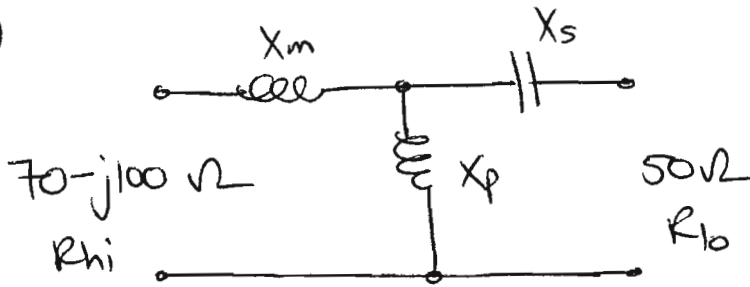


$$X_m = j100 \Omega \text{ to cancel } -j100 \Omega = 2\pi f L_m$$

$$\therefore L_m = \underline{1.50 \text{ nH}}$$

$$Q = \sqrt{\frac{R_{hi}}{R_{lo}} - 1} = 0.632 = \frac{X_s}{R_{lo}} = \frac{R_{hi}}{X_p} \quad \begin{matrix} 70 \\ 50 \end{matrix}$$


$$\therefore X_s = 31.6 = \frac{1}{\omega C_s} \quad \therefore C_s = 0.47 \text{ pF}$$
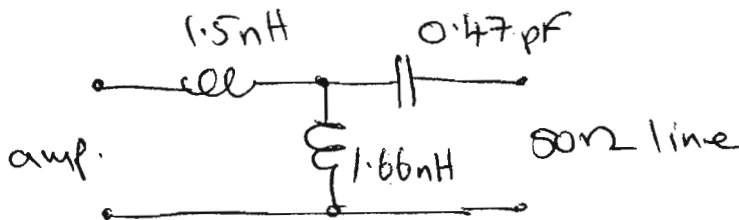
$$X_p = 110.7 = \omega L_p \quad \therefore L_p = 1.66 \text{ nH}$$



[20%]

4 a)

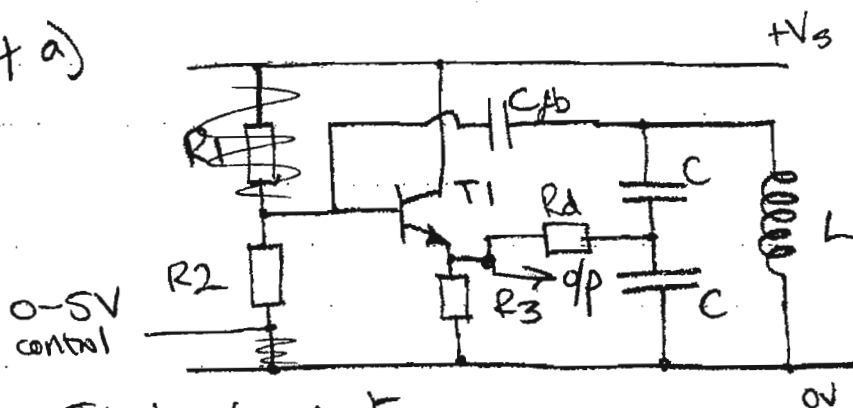

T1 : transistor

R1 + R2 : base bias resistors → can use just R2 with

R3 : emitter load resistor

L + C : resonant circuit

Cfb : feedback capacitor

Rd : diode resistor

$$f_{res} = \frac{1}{2\pi\sqrt{LC/2}}$$

0-5V control voltage see (b)

LC circuit is maintained in oscillation by transistor buffer. The capacitor's mid-point voltage is doubled at resonance and fed back to the transistor base. The buffer has a gain ≈ 1 , hence loop gain is ≈ 2 (unloaded) - so oscillation starts up. The amplitude is limited by the transistor non-linearity at voltage swings approaching the supply rails. The output can be taken from the emitter (low impedance but distorted esp. even harmonics) or the top of L (high impedance loads only - or oscillation will be damped or pulled in frequency).

(b) $27 \times 10^6 = f_{res} = \frac{1}{2\pi\sqrt{LC/2}}$ with $L = 100 \text{ nH}, C = 695 \text{ pF}$

set $R_3 = 300 \Omega$ (same as load)

$C_{fb} = 10 \text{ nF}$ (large value - appears short at @ RF)

with emitter voltage set to $V_s/2 = 4.5 \text{ V}$, then base @ 5.1 V

for $V_{BE} = 0.6 \text{ V}$. Current through $R_3 = \frac{4.5}{300} = 15 \text{ mA}$

$\therefore r_e = \frac{0.025}{0.015} = 1.67 \Omega$, as $V_{BE} R_3 \sim 75 \text{ k}\Omega$ so

choose $R_2 = 3.3 \text{ k}\Omega$ say (smaller than $V_{BE} R_3$ but $> R_{load}$)

4(b) contd.


So base current $\approx \frac{15 \text{ mA}}{250} = 60 \mu\text{A}$, so voltage drop across

$$R_2 = 60 \mu\text{A} \times 3.3 \text{ k}\Omega = 0.2 \text{ V} \quad \text{ok. } \checkmark$$

$$R_d = \frac{1}{4} \left(3300 \parallel h_{ie} \frac{R_3}{2} \parallel W L Q \right) \quad \text{with } Q = 50 \text{ say}$$

$$\approx \frac{664}{4} \Omega \quad \text{so choose } \underline{150 \Omega}$$

(c)

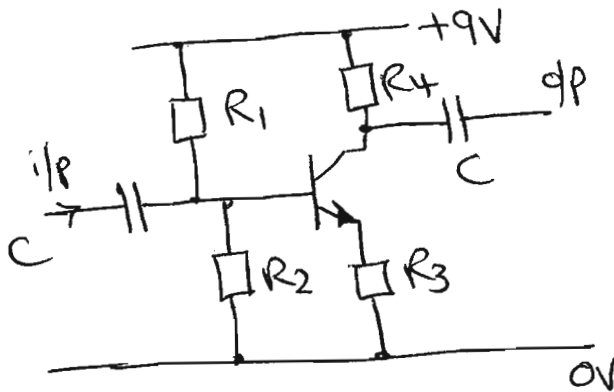

$$R_4 = 300 \Omega \quad \text{to match load}$$

$$C = 1 \text{ nF (large)}$$

$$10 \text{ dB} = \times 3.16 \quad \text{loaded gain} = 6.32 \quad \text{unloaded}$$

$$\therefore R_3 = 47 \Omega$$


$$r_e = 1.67 \Omega \quad \text{as part (b) with } I_E = 15 \text{ mA}$$

$$\therefore V_E = 0.015 \times 47 = 0.72 \text{ V} \quad \text{and } V_B = 1.42 \text{ V} \quad \text{with } V_{BE} = 0.7 \text{ V}$$

$$1.42 = \frac{R_2}{R_1 + R_2} \cdot 9 \quad \text{with } R_2 = 2.2 \text{ k}\Omega \text{ say}$$

$$\text{then } \underline{R_1 = 11 \text{ k}\Omega}$$

(d) Small sig. model of input ckt:

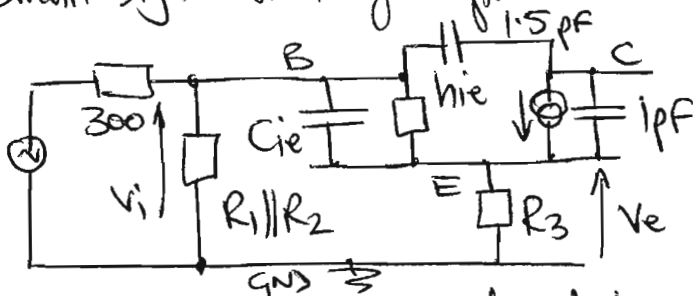


$$h_{ie} = h_{re} = 418 \Omega$$

$$\frac{V_e}{V_i} = \frac{R_3}{R_3 + r_e} = 0.966$$

$$\therefore \text{impedances B-E referred to B-GND are } \times \frac{1}{(1-0.966)} = \times 29$$

So input ckt. becomes:

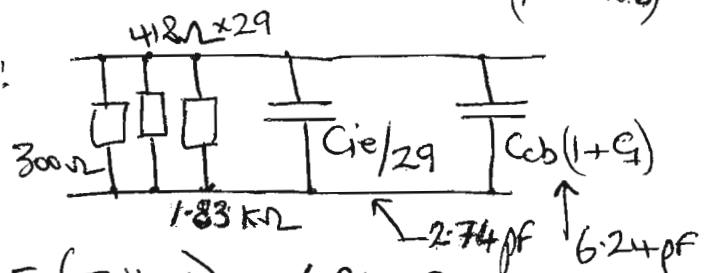

$$\text{Miller effect on } C_{cb} = 1.5 (3.16 + 1) = 6.24 \text{ pF}$$

$$f_c = \frac{1}{2\pi C_{ie} r_e} = 1.2 \times 10^9 \quad \therefore C_{ie} = 79.4 \text{ pF} \quad \text{with } r_e = 1.67 \Omega$$

$$\therefore f_{-3\text{dB}} = \frac{1}{2\pi R' C'} \quad \text{with } R' = 252 \Omega \quad C' = 8.98 \text{ pF} \quad \Rightarrow \underline{f_{-3\text{dB}} = 70.3 \text{ MHz}}$$

