

3B1 C4B 2021

1 (a)  $R = 80 \text{ km}$

$P_e = 16 \text{ kW}, G = 33 \text{ dB} = \times 1995$

$$\text{Power density} = \frac{16 \times 10^3 \cdot 1995}{4\pi R^2} = \underline{3.97 \times 10^{-4} \text{ W/m}^2}$$

$$\frac{E^2}{2\eta} = \text{Power density} \quad \therefore E = \underline{0.547 \text{ V/m}}$$

where  $\eta = 120\pi$

(b) The power delivered by an antenna to a matched load is given by  $P_r = \text{Effective aperture} \times \text{incident power density}$

Gain  $G$  is the ratio of the (peak) transmitted power density to the density from an isotropic antenna for the same power input - in the optimum direction

$$1995 = \frac{4\pi A_e}{\lambda^2} \quad \text{with } \lambda = \frac{3 \times 10^8}{2800 \times 10^6} = 0.107 \text{ m} \quad \therefore \underline{A_e = 1.822 \text{ m}^2}$$

(c)  $A_e = 0.8 \frac{\pi D^2}{4} \quad \therefore \underline{D = 1.70 \text{ m}}$

note: antenna eqn.  $G = 4\pi A_e / \lambda^2$

$$(c) (i) \quad \lambda_0 = \frac{3 \times 10^8}{2800 \times 10^6} = \frac{c_0}{f} = 0.107 \text{ m}$$


$$\therefore A_e = \frac{G \lambda_0^2}{4\pi} = \frac{1995 \times 0.107^2}{4\pi} = 1.82 \text{ m}^2$$

$$P_{\text{rec}} = \frac{4.96 \times 10^{-3} \times 1.82}{4\pi R^2 \leftarrow 80 \times 10^3} = 1.12 \times 10^{-3} \text{ W} = \frac{V_r^2}{50 \Omega \rightarrow}$$

$\therefore \underline{V_r = 2.37 \text{ } \mu\text{V}_{\text{RMS}}}$

(3.35  $\mu\text{V}$  pk)

1(c)(ii) Reduce range by 10  $\Rightarrow$  power density  $\times 10^4$   
 $\Rightarrow$  voltage  $\times 100$  (to  $23.7 \mu\text{V/m}$ )  $\Rightarrow$  40dB

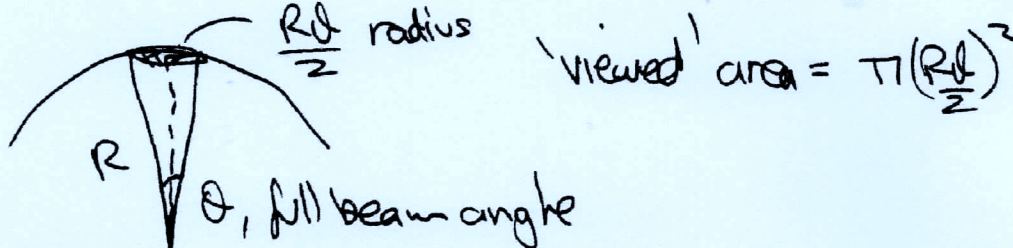(d)   $\frac{R_d}{2}$  radius 'viewed' area =  $\pi \left(\frac{R_d}{2}\right)^2$   
 $R$   $\theta$ , full beam angle


Total isotropic area =  $4\pi R^2$ ,  $G = 1995 = \frac{4\pi R^2}{\pi \left(\frac{R_d}{2}\right)^2}$

$$\Rightarrow \theta = \sqrt{\frac{16}{G}} = 0.0896 \text{ rads} = \frac{5.13^\circ}{\times \frac{180}{\pi}}$$

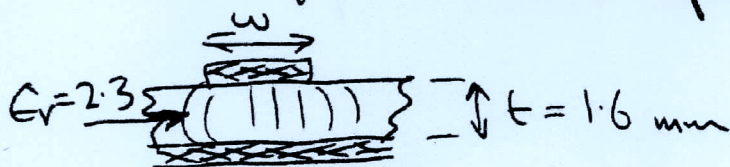(e)  $v_m = f \lambda_m = \frac{1}{\sqrt{\mu_0 \epsilon_0 \epsilon_r}} = f \frac{\lambda_0}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{2.3}} = 1.978 \times 10^8 \text{ m/s}$

$$\therefore \lambda_m = \frac{\lambda_0}{\sqrt{\epsilon_r}} = \frac{0.107}{\sqrt{2.3}} = 0.0706 \text{ m}$$

Hence half-wave resonant patch length =  $0.0353 \text{ m}$   
 (3.53 cm)




capacitance/m  
 $\downarrow$

Effective track width (incl. fringing) =  $w + 2t$   $\therefore C = (w + 2t) \times \frac{\epsilon_0 \epsilon_r}{t}$

$$Z_0 = \frac{\sqrt{L}}{\sqrt{C}} \text{ and } v_m = \frac{1}{\sqrt{L C}} \therefore Z_0 = \frac{1}{v_m C}$$

$$\therefore 50 = \frac{1.6}{1.978 \times 10^8 \cdot 8.854 \times 10^{-12} \times 2.3 (w + 2t)}$$
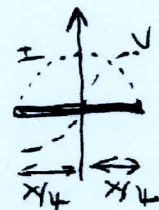
$$\therefore 0.201 (w + 3.2) = 1.6 \quad \therefore w = 4.76 \text{ mm}$$



Patch impedance is min.  $\overset{=0}{\text{at centre}}$  and max.  $\overset{=0}{\text{at edge}}$  due to V and I standing wave  $\frac{1}{2}$ : V is sine, I is cosine  $\therefore \frac{V}{I}$  is tan (approx.)



$$2(a) \quad f = 1060 \text{ MHz}, \quad Z_0 = \frac{\sqrt{L}}{\sqrt{C}} \quad \text{and} \quad v_c = \frac{1}{\sqrt{L/C}} = f \lambda_c$$

$$\therefore v_c = \frac{1}{Z_0 C} = 2.05 \times 10^8 \text{ m/s for } Z_0 = 75 \Omega,$$

$$\therefore \lambda_c = \frac{v_c}{f} = \underline{0.194 \text{ m}}$$

$$C = 65 \text{ pF/m}$$

$$L = 3.66 \times 10^{-7} \text{ H/m}$$

$$(b) \quad \text{Plot point 'A' @ } 0.68 \angle 85^\circ = 0.4 + j : \times 75 = \underline{30 + j75 \Omega}$$

Rotate to compensate for cable effects a/d w by

$$\frac{0.12}{0.194} = 0.619 \lambda \quad -0.5 \lambda \text{ whole turn} \Rightarrow 0.119 \lambda$$

$$\therefore 0.132 \lambda - 0.119 \lambda = 0.013 \lambda, \text{ point 'B'}$$

$$\text{Impedance @ B} = 0.19 + j0.08 : \times 75 = \underline{14.3 + j6 \Omega}$$

(c) For matching we need a cable length which presents an impedance at the cable end =  $1 + jX$  on  $Re=1$  circle @ point 'C' on the Smith chart.

$$\therefore \text{electrical length} = 0.185 \lambda - 0.013 \lambda = 0.172 \lambda + \frac{n\lambda}{2}$$

with  $\lambda = 0.194 \text{ m}$  (194 mm) from part (a) then

$$\text{the physical length} = (33 + 97n) \text{ mm eg: } L = 130 \text{ mm}$$

for  $n=1$

(extra 10mm from original)

$$\text{point 'C'} = 1 + 1.87j \quad \text{so series capacitor needs impedance}$$

$$= -1.87j \times 75 \Omega = -j140 \Omega$$

$$\therefore \frac{1}{2\pi f C} = 140 \quad \Rightarrow \underline{C = 1.07 \text{ pF}}$$

$$1060 \times 10^6 \text{ Hz}$$




4/9

CRIB

EGT2

ENGINEERING TRIPOS PART IIA

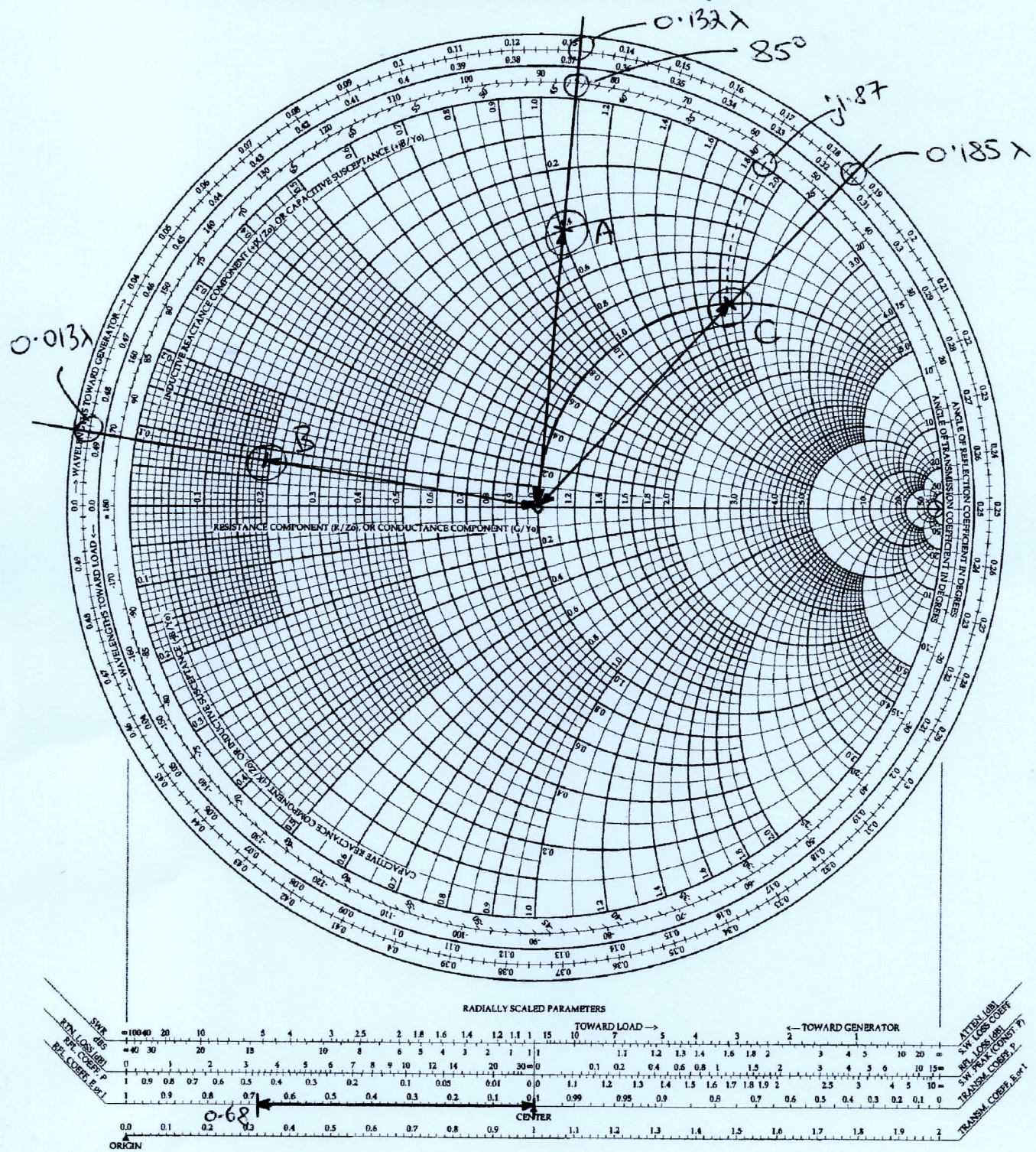
Tuesday 27 April 2021, Module 3B1, Smith Chart for reference in Question 2





2(d)

5/9

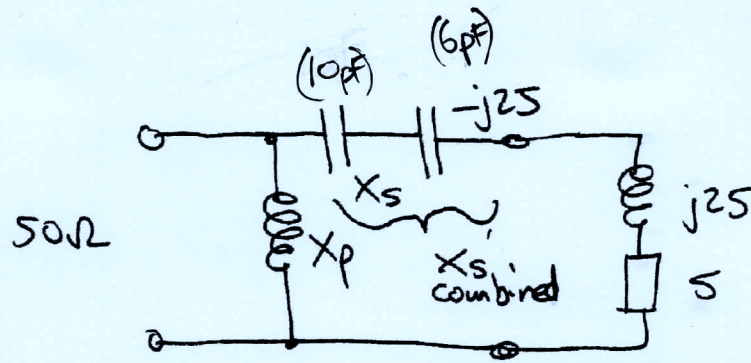

Matching eqns.

$$Q = \frac{R_{hi}}{X_p} = \frac{X_s}{R_{lo}} = \sqrt{\frac{R_{hi}}{R_{lo}} - 1}$$

Cancel  $j25$  with series cap. of  $-j25$  (will subsume this into  $X_s$  later to just have 2 components  $X_s$  and  $X_p$ ).


Then  $R_{hi} = 50 \Omega$ ,  $R_{lo} = 5 \Omega \therefore Q = 3$

$X_p = j16.7 \Omega$  and  $X_s = -j15 \Omega @ 1060 \text{ MHz}$

So for  $X_s = -j40 \Omega = \frac{1}{2\pi f C} \therefore C = 3.75 \text{ pF}$

and for  $X_p: 16.7 = 2\pi f L \therefore L = 2.51 \text{ nH}$

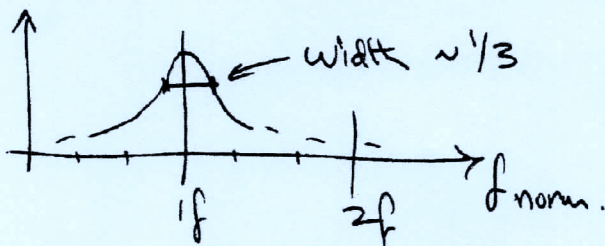The  $Q$  factor is fairly low at 3, but still quite a peak





So @  $2f$ , the response will be less and the matching not so good.

Signal amplitude likely to drop by a factor of several times.

6

3(a) Use chebyshev filter for sharp cut-off cascade high-pass (HP) and low-pass (LP) sections for band pass 23-27 MHz :

23 MHz HP  
27 MHz LP

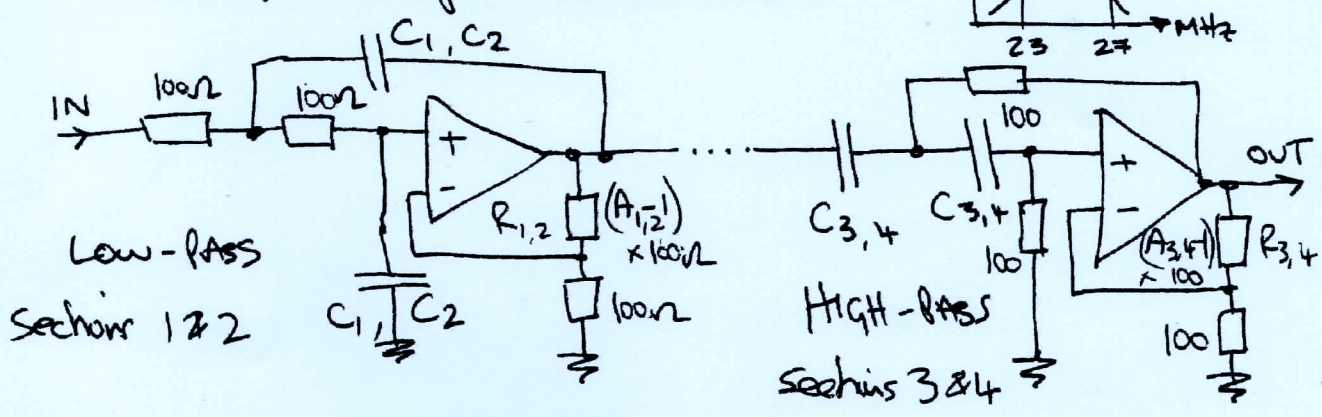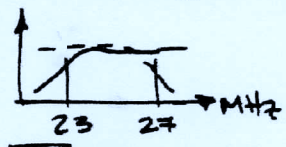

Low-pass:  $27 \times 10^6 = \frac{1}{2\pi f_n R C_{1,2}}$

High pass:  $23 \times 10^6 = \frac{f_n}{2\pi R C_{3,4}}$

$A_1 = 1.582 \therefore R_1 = 582 \Omega$

$A_3 = A_1 \therefore R_3 = 58 \Omega$

$R = 100 \Omega \quad C_1 = 99 \text{ pF}$


$C_3 = 41 \text{ pF}$

$A_2 = 2.660 \therefore R_2 = 166 \Omega$

$A_4 = A_2 \therefore R_4 = 166 \Omega$

$C_2 = 57 \text{ pF}$


$C_4 = 71 \text{ pF}$

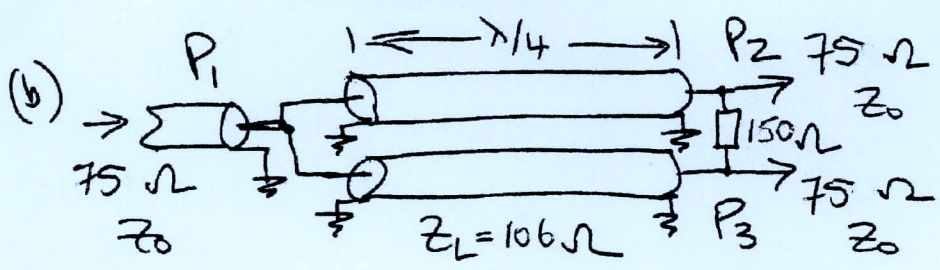


Wilkinson coupler uses a pair of  $\lambda/4$  lines with char. impedance  $Z_L = \sqrt{2} Z_0$ . The  $\lambda/4$  lengths of line transform P2 and P3 impedances of  $75 \Omega$  to  $(\frac{106}{75})^2 \cdot 75 = 150 \Omega$  each. These are in parallel at port 1 to make  $Z_0 = 75 \Omega$  match. So power input to port 1 splits equally to P2 and P3. Any power back into P2 or P3 has a phase delay of  $\lambda/2 = 180^\circ$  and cancels direct signal from  $150 \Omega$  between P2 and P3 - so they are mutually isolated (to 30dB). P1 split to P2, P3 is ideally lossless, as  $100 \Omega$  carries no current.



3(c)

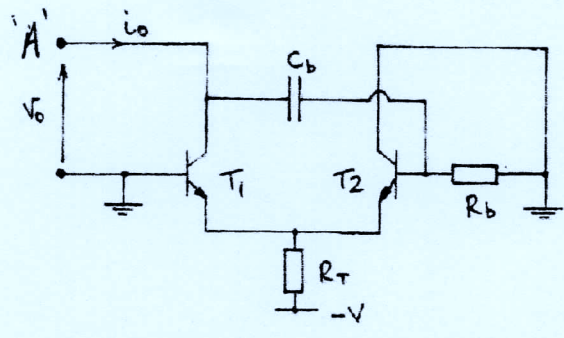

The small signal model equivalent:

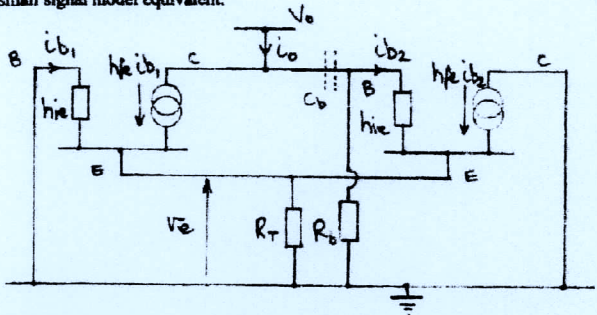


①  $i_{b1} = -\frac{v_e}{h_{ie}}$  , ②  $i_{b2} = \frac{V_o - v_e}{h_{ie}}$  , ③  $v_e \approx R_T h_{fe}(i_{b1} + i_{b2})$   
 ④  $i_o = h_{fe} i_{b1} + i_{b2} + V_o/R_B$  Subst. ① and ② into ③ :-  
 $v_e = -R_T h_{fe} \frac{v_e}{h_{ie}} + R_T h_{fe} \frac{V_o - v_e}{h_{ie}} - R_T h_{fe} \frac{v_e}{h_{ie}}$

$\therefore v_e \left( 1 + \frac{2R_T h_{fe}}{h_{ie}} \right) = R_T \frac{h_{fe}}{h_{ie}} V_o \quad \therefore v_e \approx \frac{V_o}{2}$  ⑤

subst. ① and ② into ④ and subst. for  $v_e$  using ⑤  
 $\therefore i_o = -\frac{h_{fe} V_o}{2h_{ie}} + \frac{V_o}{2h_{ie}} + \frac{V_o}{R_B}$

$\therefore i_o = V_o \left( \frac{1}{R_B} - \frac{h_{fe}}{2h_{ie}} \right)$  and as  $\frac{h_{ie}}{h_{fe}} = r_e$ ,

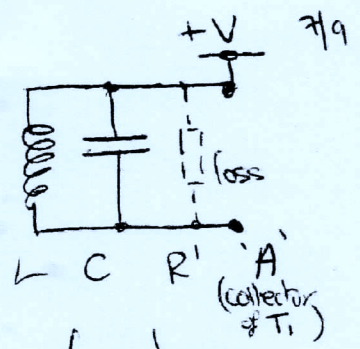$Z_o = \frac{V_o}{i_o} = \left( \frac{1}{R_B} + \frac{1}{-2r_e} \right)^{-1} \Rightarrow Z_o = R_B \parallel -2r_e$



$f = \frac{1}{2\pi\sqrt{LC}}$   
 $= 2800 \times 10^6 \text{ Hz}$   
 with  $L = 1.5 \times 10^{-9}$   
 $\Rightarrow C = 2.15 \text{ pF}$

with  $Q = 25$   
 and  $L = 1.5 \text{ nH}$

$R' = \omega L Q$   
 $= 2\pi f L Q$   
 $= 660 \Omega$   
 to compensate with  $-ve$  resistance in parallel with  $50 \Omega$  load

$R_B \parallel -2r_e \leftarrow 465 \Omega$

Aim for say  $-35 \Omega$ , so that the LC tank circuit is unbalanced and oscillations are sustained.  $r_e = \frac{R_T}{Q}$  (from Ebers-Moll)


$r_e \approx \frac{0.025}{I_C}$  : for  $r_e = 15 \Omega$ ,  $I_C = 1.66 \text{ mA}$   $\rightarrow$  say  $2 \text{ mA}$ .

Choose  $R_B$  and  $R_T = 1 \text{ k}\Omega$ , then  $I_E \approx \frac{5 - 0.65}{2 \times 1000} = 2.2 \text{ mA}$  ok. ✓

Then  $Z_o = 1 \text{ k}\Omega \parallel -2 \times 15 \Omega \approx -31 \Omega$


Take oscillation output across  $R_B$  i.e. base of  $T_2$ . o.r. should be unbalance  $V_{th}$

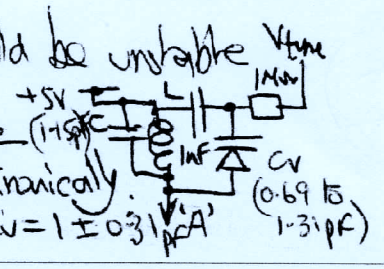Add varactor diode in parallel with LC for tuning electronically.  $\therefore$  choose eg.  $C = 1.15 \text{ pF}$  and  $C_v = 1 \pm 0.31 \text{ pF}$   
 For  $2.8 \pm 0.2 \text{ GHz}$ ,  $C_{total} = 2.15 \pm 0.31 \text{ pF}$





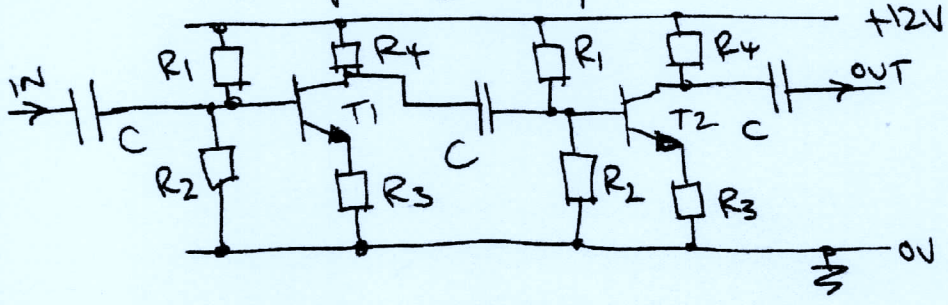4(a) 35dB power gain requires 2 transistors @ ~20dB each.



$R_1$  &  $R_2$  provide base dc bias  
 $R_3$  is  $\neg$  feedback to set gain and improve bias stability  
 $R_4$  is collector load resistor: sets output impedance  
 $C$  are dc. blocking coupling capacitors

35 dB power gain =  $\times 10^{35/20} = \times 56.2$  (linear gain)  
 also needs to compensate for 2 extra coupling losses between stages  $\therefore$  o/cct. linear gain =  $56.2 \times 2 \times 2 = \times 225$ ,  
 spread equally =  $\times 15$  ( $\times 7.5$  loaded in cct.)


$R_4 = 50 \Omega$  output imped.     $R_3 = \frac{R_4}{15} = 3.3 \Omega$  (say  $3 \Omega$ )

Choose  $R_2 = 1.5 \times 50 = 75 \Omega$ . Set base @ 1.5V dc.  
 $\therefore$   $R_1 = 510 \Omega$     ( $V_b = \frac{75}{585} \times 12 = 1.54V$  ✓ o.k.)

$I_c = \frac{6}{50} = 0.12A$      $\therefore r_e = \frac{0.025}{I_c} = 0.21 \Omega$     (0.15  $\Omega$ )

and  $\frac{V_e}{V_b} \approx \frac{3}{3.21} = 0.93$  (emitter gain),  $C = 1nF$  each

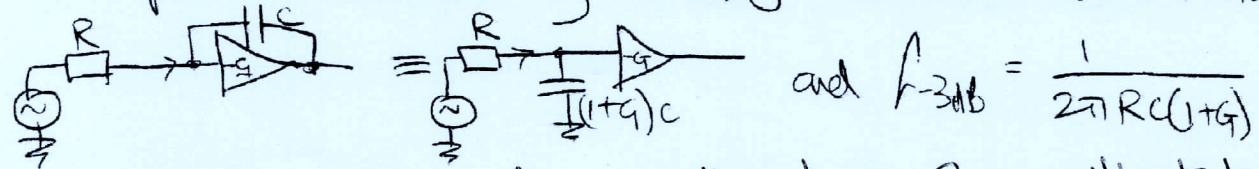(b) Miller Effect: input impedance to inverting amplifier is reduced by capacitance between output and input - value of capacitance appears larger by factor of  $(1+G)$ . This can reduce the input cct. bandwidth by increasing RC time constant, where




$R$  is source impedance from preceding stage. Can mitigate by using cascode or differential amp. cct. (see notes).



4(c) Consider input ckt. to  $T_1$  : small sig. model:

9/9

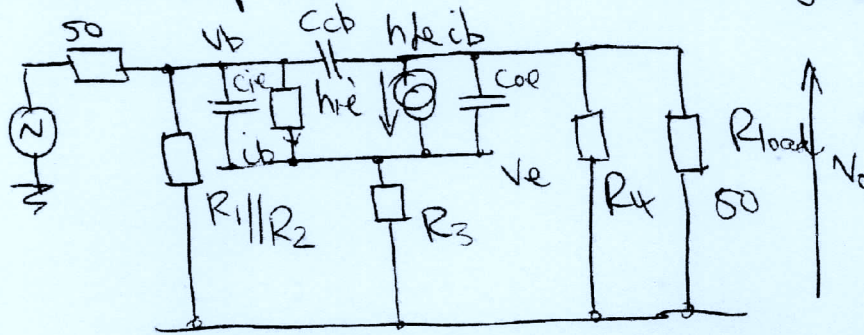

From before  $V_e = 0.93 V_b$ ,  $r_e = 0.21 \Omega$ ,  $f_t = 15 \text{ GHz}$

$$C_{ie} = \frac{1}{2\pi f_t r_e} = 50.5 \text{ pF}$$

but emitter feedback reduces effect of  $C_{ie}$  to  $(1 - 0.93) \times 50.5 = 3.54 \text{ pF}$

$$C_{cb} \text{ is multiplied by Miller Effect to: } \left(1 + \frac{50 \parallel 50}{3 + 0.21}\right) \times 0.15 = 1.32 \text{ pF}$$

(x8.78)  $\rightarrow$

So input resistances are  $50 \parallel 75 \parallel 510 \parallel \frac{h_{fe} r_e}{(1 - 0.93)} = 750 \Omega$


$$\therefore R' = 27.3 \Omega$$

$$C' = 3.54 + 1.32 = 4.86 \text{ pF}$$

$$\text{is given by } f_{-3dB} \approx \frac{1}{2\pi R' C'} = 1.20 \text{ GHz}$$

actually this will be -6dB as 2 stages, so operation @ 1.03 GHz is ok.

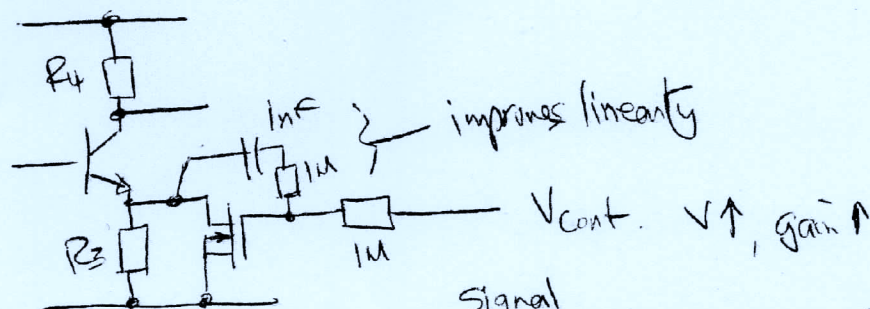(d) (i) we would need a variable gain amplifier: can shunt  $R_3$ 's with a FET to vary resistance electronically  $\Rightarrow$  increase gain for smaller signals



(ii) Range 100:1 = Power  $100^2:1 = \text{Voltage } 100:1 = 40 \text{ dB range}$   
 if 30dB compensation, we are left with 10dB variation =  $\sqrt{10}$  on  
 Signal amplitude = 3.16



## Examiner's comments

### **Q1 Antennas & microstrip**

A very popular and straightforward question, well-answered by most candidates. Most candidates knew the antenna term definitions and the antenna equation, and applied it correctly to calculate signal magnitudes although a number of attempts did not take the isotropic back scatter into account correctly. The beam angle was generally estimated correctly.

### **Q2 Smith chart and impedance matching**

A less popular question; attempted by about 40% of the cohort. Most attempts at determining the input impedance values were correct – with some latitude allowed for reading values of the screen, however, several attempts at compensating for the cable length moved around the chart in the wrong direction. The matching circuit was well attempted in many cases.

### **Q3 VCVS filters, power divider and oscillator**

This question was attempted by almost all candidates and quite well answered. The VCVS filter section was quite straightforward and well attempted in most cases, with a correct choice of filter type and values. The power divider section was less well done, although it is in the notes, many attempts did not cover the details well. The negative impedance oscillator was generally well attempted.

### **Q4 RF amplifier**

A fairly popular question with good attempts on the whole. The 2-stage amplifier design was well answered, although the gain was sometimes incorrect by a factor of 2 either way. The frequency response was also quite well attempted in many cases, although the unloaded gain was occasionally considered rather than the loaded value. The variable gain section at the end attracted a number of attempts of variable quality.