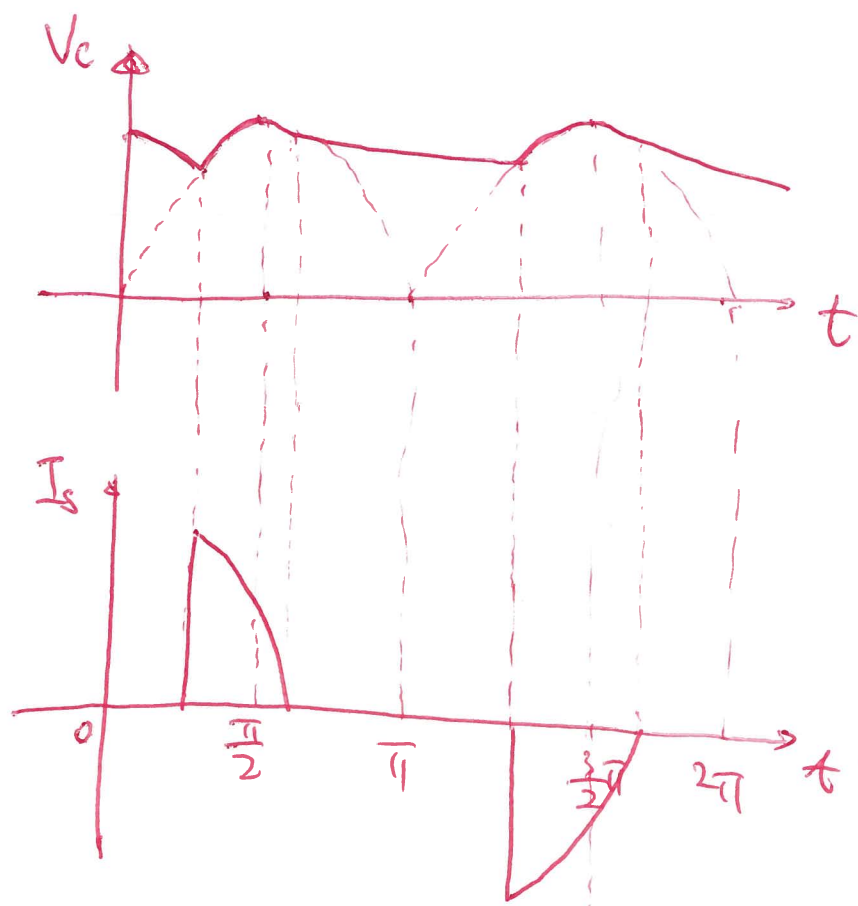


Q1 a)

Paper 3B3

Grib 2018

i)



ii) Input current is largely distorted, resulting in high harmonics. Power factor (pf) is:

$$pf = \frac{1}{\sqrt{1 + THD_i^2}} \cos \theta, \quad THD_i \text{ of current.}$$

Large THD_i , poor p.f.


iii) Assume: ① Linear discharge of capacitor.

② Very large capacitor so entire half cycle ($\frac{\pi}{2}$ to π) is for capacitor discharge.

$$\Delta V = \hat{V} - \hat{V} \left(1 - \frac{1}{2fR_L C}\right) = \frac{\hat{V}}{2fR_L C}, \quad I = \frac{\hat{V}}{R_L}, \quad \Delta V = \frac{I}{2fC}.$$

$$b) \quad i) \quad V_{oc\text{-peak}} = 415 \times \sqrt{2} = 587 \text{ V}$$

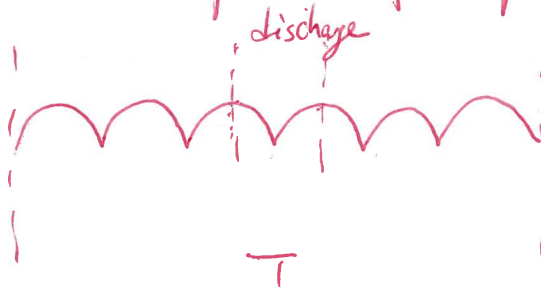Assuming discharge between two peaks of every two consecutive pulses.



$$\Delta V = I \cdot \frac{\Delta T}{C}$$

$$C = \frac{\Delta T \cdot I}{\Delta V}$$

$$\Delta V = 587 \times 0.05$$

$$\Delta T = \frac{1}{6f} = \frac{1}{6 \times 50}$$

$$I = 100$$

$$\Rightarrow C = \frac{100}{6 \times 50 \times 587 \times 0.05} = 11.36 \text{ mF}$$

ii)



The dominate harmonics is at $6 \times 50 = 300 \text{ Hz}$.

As constant load current, load impedance $Z_{load} \approx \frac{587}{100} = 5.87 \Omega$

At 300 Hz , the capacitor impedance $|Z_c| = \left| \frac{1}{j2\pi \times 300 \times 11.36 \text{ m}} \right|$

$$= 0.047 \Omega$$

$|Z_c| \ll Z_{load}$, thus, $|Z_c| \parallel Z_{load} \approx |Z_c|$.

1% voltage ripple means $\frac{|Z_c|}{|Z_c| + |Z_L|} = 0.01$

$$\frac{|Z_C|}{|Z_C| + |Z_L|} = \frac{\left| \frac{1}{j\omega C} \right|}{\left| \frac{1}{j\omega C} \right| + |j\omega L|} = \frac{1}{1 + \omega^2 LC} = 0.01.$$

$$L = \frac{99}{\omega^2 C} = \frac{99}{(50 \times 6.28)^2 \times 11.36 \times 10^{-3}} = \cancel{2.34 \text{ mH}} \\ 2.45 \text{ mH}$$

iii) The inductor keeps the current flowing. The supply current then becomes more sinusoidal with less harmonics. Less THD of current then higher power factor.

Q2. i)

a) A free-wheel diode is needed to clamp MOSFET voltage to the supply rail otherwise the voltage will keep rising causing MOSFET breakdown.

100V, 75A diode is required and the diode needs to be fast recovery diode.


ii) Conduction loss: $75 \times 75 \times 0.007 \times 0.5 = 19.7 \text{ W}$.

Switching losses (ON and OFF):

$$2 \times \frac{1}{2} \times 75 \times 1000 \times 10^3 \times 50 \times 10^{-9} \times 100 = 37.5 \text{ W}$$

Total loss: $37.5 + 19.7 = 57.2 \text{ W}$.

iii) Turn-off.

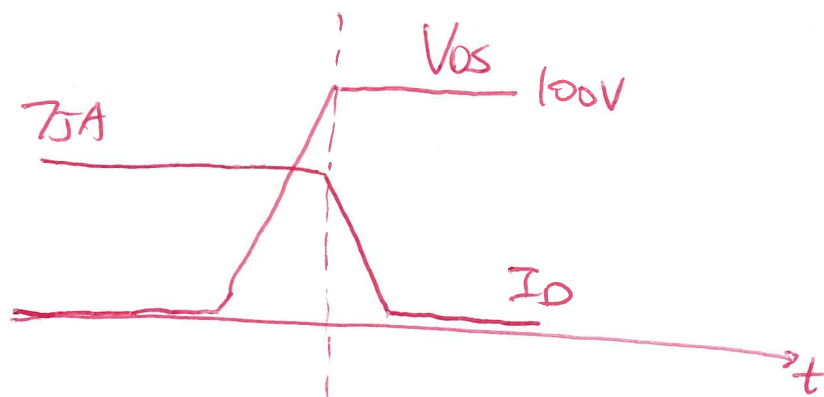


$$75 = 150 (V_{GS} - 2)^2 \longrightarrow V_{GS} = 2.71 \text{ V}$$

$$I_G = C \frac{dv}{dt} = 50 \times 10^{-12} \times \frac{100}{20 \times 10^{-9}} = 250 \text{ mA}$$

$$R_G = \frac{V_{GS}}{I_G} = \frac{2.71}{250 \times 10^{-3}} = 10.84 \Omega.$$

iv)

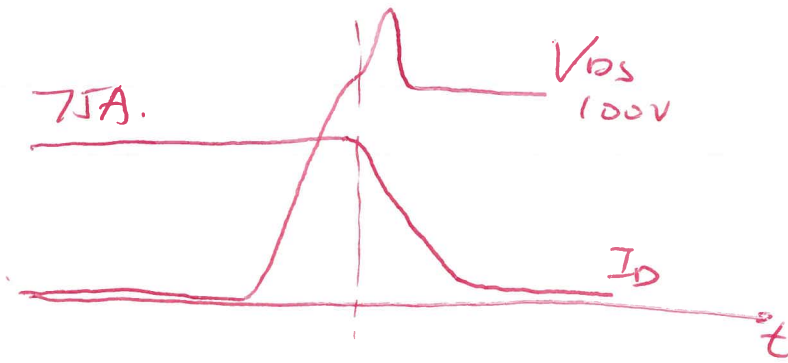

b)


Good: ① Very fast $\frac{di}{dt}$ so low losses

② Overcomes any miller capacitor induced voltages in an inverter application.


Bad:

① Very fast $\frac{di}{dt}$ will cause ringing due to stray inductances in the circuit. Some resistance can be added to damp ~~ringing~~ ringing but with additional costs.

3. (a)

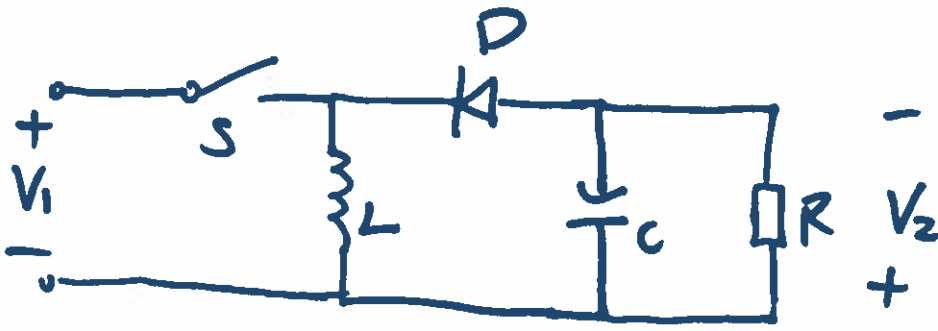


i) ON

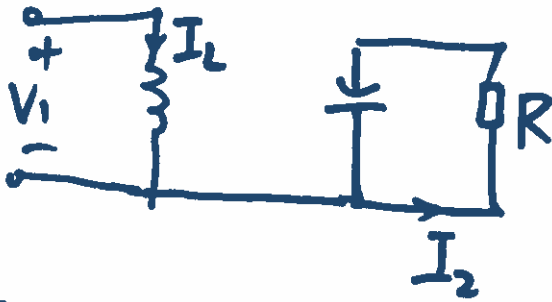


$$V_1 = L \frac{\Delta I_L}{DT} \quad \Delta I_L = \frac{DT V_1}{L}$$

OFF

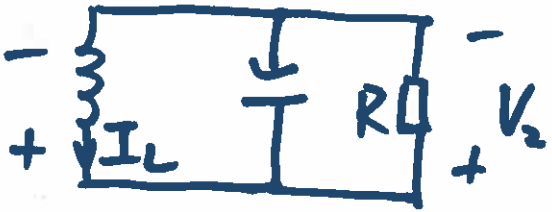


$$L \frac{\Delta I_L}{(1-D)T} = V_2$$

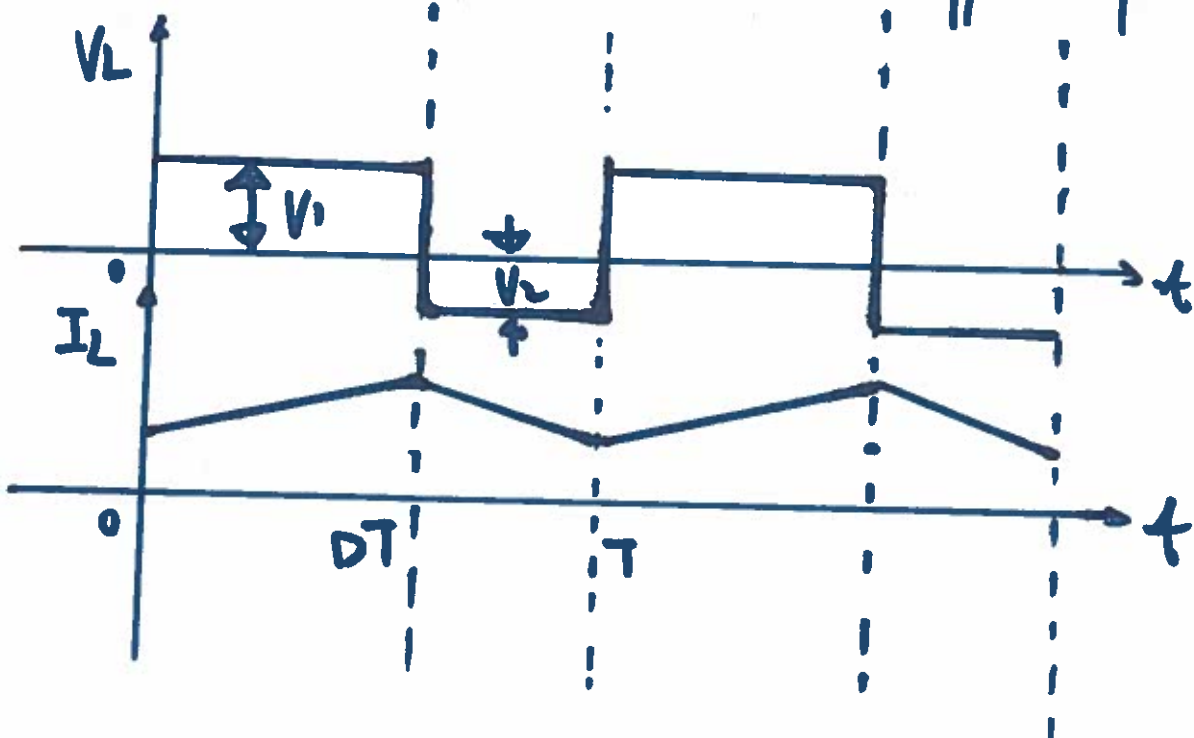$\therefore \left(\frac{D}{1-D}\right) V_1 = V_2$, V_2 has opposite polarity to V_1 .



iii) - Cannot be grounded.

- input current is discontinuous.

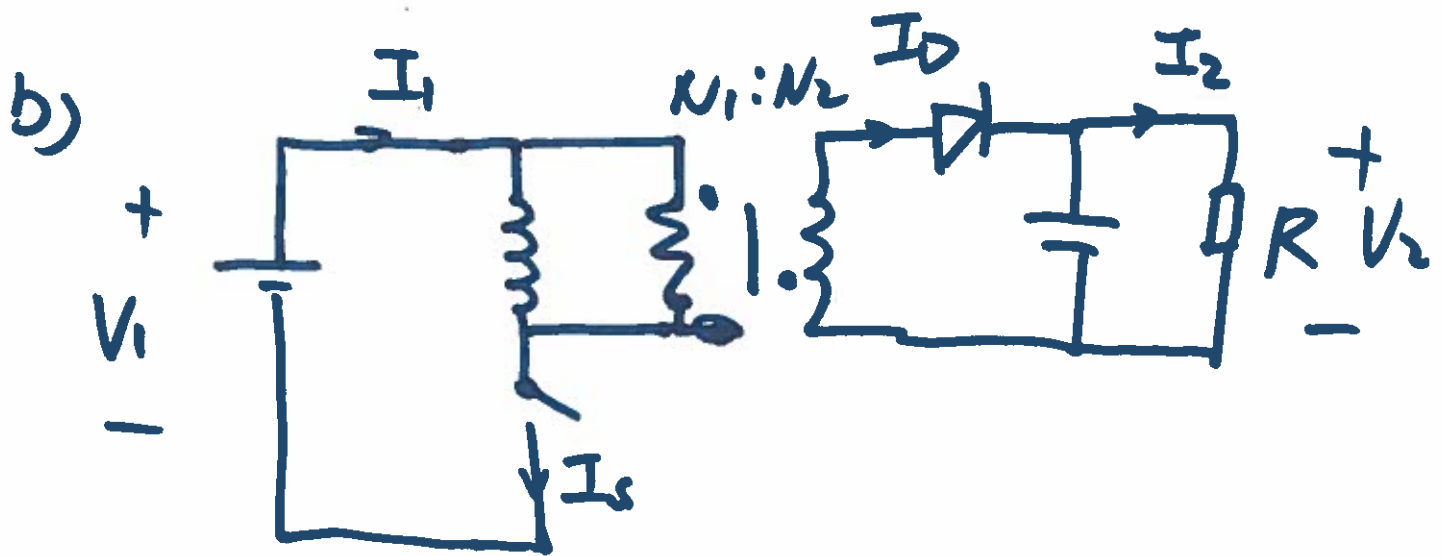


ON:
$$\Delta\phi = \int_0^{DT} \frac{V_1}{N_1} dt = DT \frac{V_1}{N_1}$$

OFF:
$$\Delta\phi = \int_{DT}^T \frac{V_2}{N_2} dt = (1-D)T \frac{V_2}{N_2}$$

$$\therefore DT \frac{V_1}{N_1} = (1-D)T \frac{V_2}{N_2}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} (1-D) \quad \text{or} \quad \frac{V_2}{V_1} = \frac{N_2}{N_1} \left(\frac{D}{1-D} \right)$$


b) (ii)

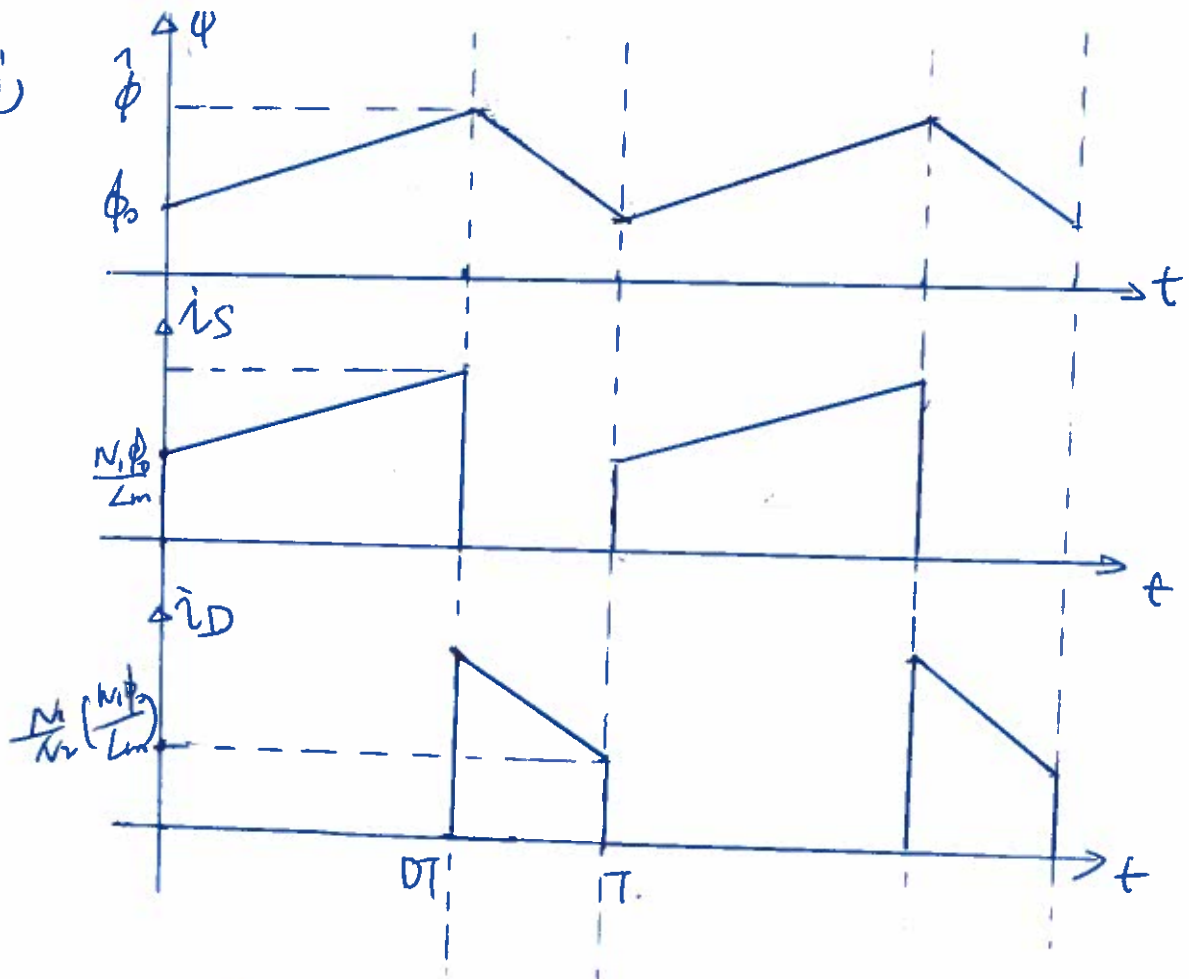

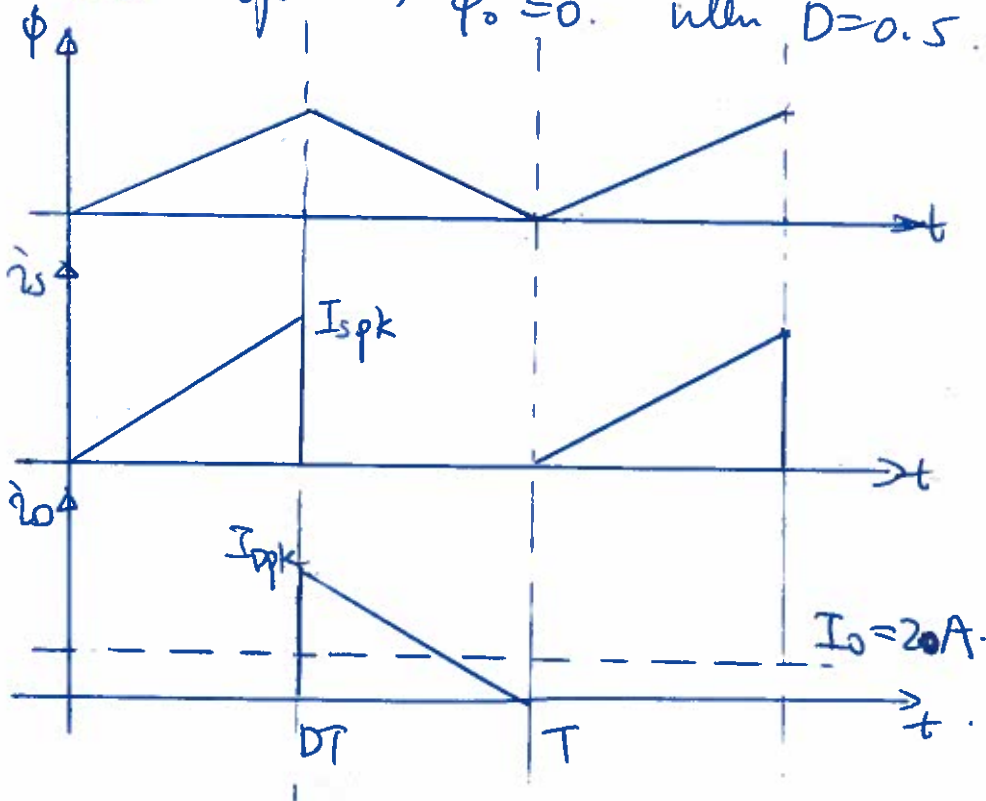iii) The initial flux should be as small as possible to avoid saturation of the transformer core.

$$iv) \frac{V_2}{V_1} = \frac{N_2}{N_1} \frac{P}{1-D} \Rightarrow N_2 = 20$$

At desired operation, $\phi_0 = 0$ when $D = 0.5$.



The output average current I_o

$$I_o = \frac{V_o}{R} = \frac{50}{25} = 2A.$$

At the secondary side, the diode current must be:

$$I_o \cdot T = \frac{1}{2} I_{Dpk} \cdot DT, \quad (I_{Dpk} \text{ is the diode peak current})$$

$$\Rightarrow I_{Dpk} = 4 \cdot I_o = 8A.$$

$$\frac{I_{Spk}}{I_{Dpk}} = \frac{N_2}{N_1}, \quad I_{Spk} = \frac{20}{60} \times 8 = \frac{8}{3} A. \quad (I_{Spk} \text{ is the switch peak current})$$


$$\Delta\phi = I_{Spk} \cdot \left(\frac{L_m}{N_1} \right) = \int_0^{DT} \frac{V_i}{N_1} dt.$$

$$I_{Spk} L_m = D \cdot \frac{1}{f} V_i$$

$$f = \frac{D \cdot V_i}{I_{Spk} \cdot L_m} = \frac{0.5 \times 150}{0.001 \times \frac{8}{3}} = 28.125 \text{ kHz}.$$

Q4.

a) i)

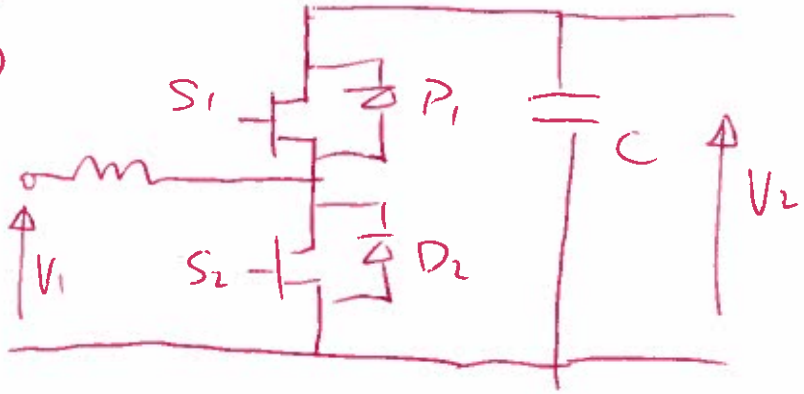


S_1 is inhibited permanently. Switch S_2 only.

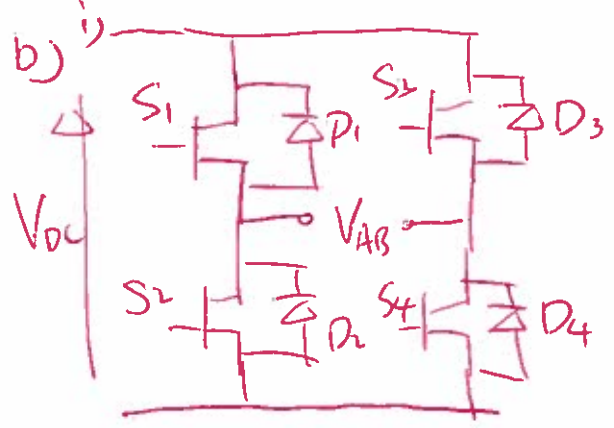ii) $V_2 = \left(\frac{1}{1-D}\right)V_1$

$$I_{OBS} = \frac{1}{2} \Delta I_o = (1-D) \Delta I_L = \frac{V_1 \cdot T}{2L} (D-D^2)$$


$$I_{OBS} = \frac{V_2 T}{2L} (1-D)^2 \cdot D$$




bipolar: S_1, S_4 switch together
 S_3, S_2 switch together
 S_1, S_2 switch complementary.

Unipolar. S_1, S_4 not switch together

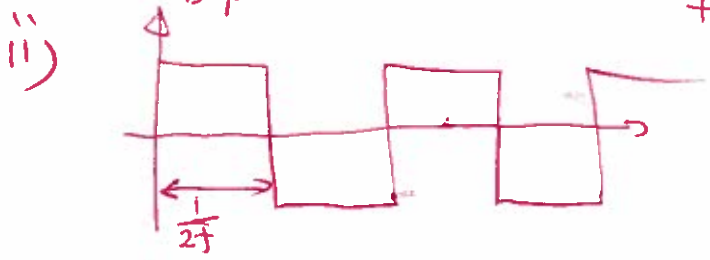Unipolar doubles the ripple frequency when the voltage is used, reducing the size of the filter.



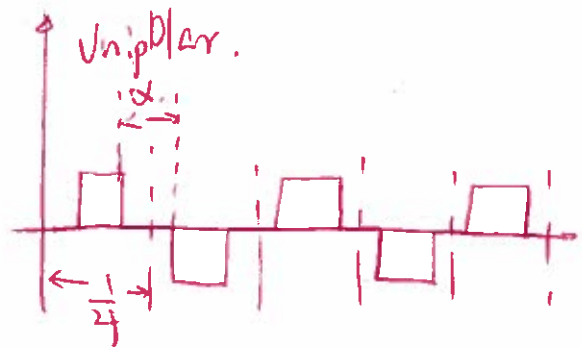
$$V_{AB} = \frac{4}{\pi} V_{oc} \sin \omega t, \quad (\omega = 2\pi f)$$





$$V_{AB} = \frac{4}{\pi} V_{oc} \sin \omega t \cdot \cos \frac{\alpha}{2}, \quad (\omega = 2\pi f)$$

(Using Fourier transforms from Detabols)

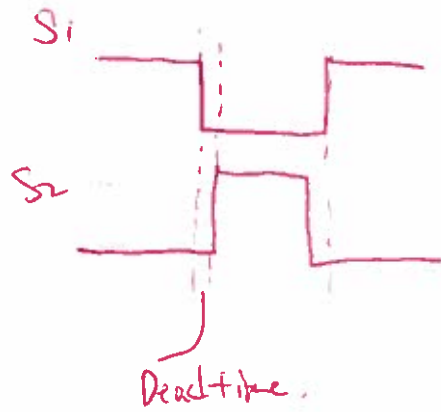ii) S_1 and S_2 have a short of time both switched off,
(Deadtime)



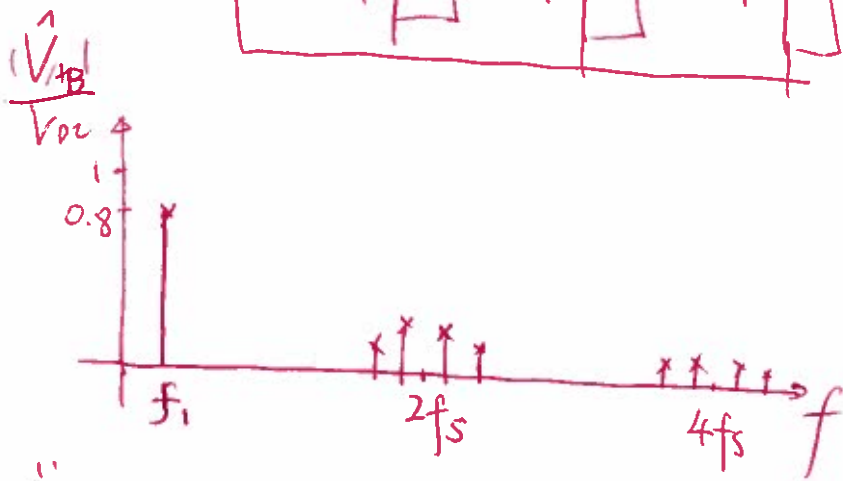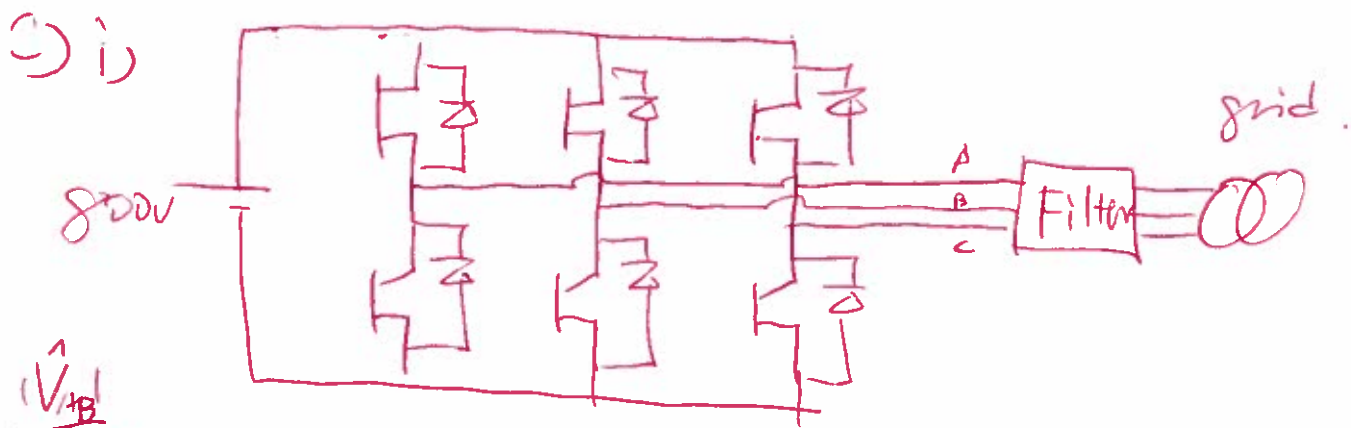The deadtime ensures ~~no~~ both of ~~be~~ devices never switched on together even some delay of devices.



ii) $\hat{V}_{AB} = 0.866 \cdot V_{DC} = ~~490V~~ = 693V$
 Sin Pwm: $V_{AB} = \frac{693}{\sqrt{2}} = 490V$ (rms)

SU Pwm: $\hat{V}_{AB} = V_{DC} = 800V$
 $V_{AB} = \frac{800}{\sqrt{2}} = 566V$ (rms)

iii) Increasing f_s , Draw back: switching losses increase lower efficiency.