

EGT3  
ENGINEERING TRIPOS PART IIA

---

Tuesday 24 April 2018 2 to 3.40

---

**Module 3B3**

**SWITCH-MODE ELECTRONICS**

*Answer not more than **three** questions.*

*All questions carry the same number of marks.*

*The **approximate** percentage of marks allocated to each part of a question is indicated in the right margin.*

*Write your candidate number **not** your name on the cover sheet.*

**STATIONERY REQUIREMENTS**

Single-sided script paper

**SPECIAL REQUIREMENTS TO BE SUPPLIED FOR THIS EXAM**

CUED approved calculator allowed

Engineering Data Book

**10 minutes reading time is allowed for this paper at the start of the exam.**

**You may not start to read the questions printed on the subsequent pages of this question paper until instructed to do so.**

- 1 (a) A single phase rectifier is shown in Fig 1.
- (i) Sketch the smoothing capacitor voltage waveform and the input current waveform for a constant current load. [10%]
  - (ii) Explain why this rectifier has a poor power factor at the input. [15%]
  - (iii) Find the simplified expression for the ripple voltage in terms of the supply frequency, stating your assumptions. [15%]

 


Fig. 1: Single phase rectifier

- (b) A three phase rectifier is shown in Fig 2. The load current is smooth with a DC value of 100 A.
- (i) Estimate the smoothing capacitance required to reduce the output ripple voltage to 5% of the peak rectified voltage for an AC line voltage of 415 V. [20%]
  - (ii) The ripple voltage at the output is to be reduced to 1% of the peak rectified voltage by adding a smoothing inductor. Sketch the circuit with the smoothing inductor and find the inductance. [25%]
  - (iii) Comment on the expected input current waveform and power factor when adding a smoothing inductor. [15%]

 


Fig. 2: Three phase rectifier

2 A Metal-Oxide-Semiconductor Field Effect Transistor (MOSFET) is used to switch an inductive load as shown in Fig 3. The gate-drain capacitance of the MOSFET can be considered constant at 50 pF and the conduction resistance  $R_{DSon}$  is 7 m $\Omega$ . The MOSFET drain current  $I_D$  obeys  $I_D = 150(V_{GS} - 2)^2$  where  $V_{GS}$  is the gate to source voltage. The application requires a switching frequency of 100 kHz when  $V_{dc} = 100V$ . The drain current  $I_D$  is 75 A and the duty cycle is 50%. The total switching time is 50 ns.

 


Fig. 3: MOSFET in a circuit

- (a) (i) Explain why a diode is necessary for this circuit to work and state the minimum current and voltage ratings and type of diode to be used. [20%]
- (ii) Estimate the total power losses, assuming an ideal diode and the MOSFET turn-on loss is assumed to be the same as the turn-off loss. [20%]
- (iii) Sketch the MOSFET drain to source voltage  $V_{DS}$  and drain current  $I_D$  for a turn-off event and find a value of gate resistance which gives a 20 ns rise time of  $V_{DS}$  if the gate driver applies 0 V at turn-off. Assume an ideal diode is used. [20%]
- (iv) Sketch the waveform for the MOSFET  $V_{DS}$  and  $I_D$  at a turn-off event with a non-ideal diode. [20%]
- (b) A gate voltage clamp circuit is proposed, which applies a dead short between the gate and source as soon as the end of the voltage rise is detected. List two reasons why this is a good idea particularly for use in inverter circuits and give one drawback. [20%]

3 (a) Draw a non-isolated step-up-step-down DC/DC converter with using one MOSFET, one diode and one capacitor. The load is a resistor. Indicate the input voltage  $V_1$ , output voltage  $V_2$ , input current  $I_1$ , output current  $I_2$  and the inductor current  $I_L$  on the drawing. [10%]

(i) Derive the expression of the output voltage  $V_2$  as a function of the duty ratio  $D$  and input voltage  $V_1$ , assuming ideal devices and continuous inductor current. [10%]

(ii) At the steady state, sketch both the inductor voltage  $V_L$  and the inductor current  $I_L$  against time. [10%]

(iii) Explain the disadvantage of this converter from the perspective of earthing and input power measurement. [10%]

(b) A fly-back converter is shown in Fig 4. The flyback converter is fed by an ideal battery and the load is a resistor.

 


Fig. 4: Flyback converter

(i) Derive the expression of the output voltage  $V_2$  as the function of duty ratio  $D$  and input voltage  $V_1$ , assuming ideal devices and continuous flux of the transformer. [15%]

(ii) Sketch the flux of the transformer  $\phi$  against time, the current at the MOSFET  $I_s$  against time and the current at the diode  $I_d$  against time. [15%]

(iii) Explain why the flux of the transformer at the boundary continuity, i.e. just continuous, is preferable for the flyback converter. [10%]

(iv) The input voltage is 150 V and output voltage is 50 V. The duty ratio of the MOSFET is 50%. The load is 25  $\Omega$ . The transformer has 60 turns at the primary side,  $N_1 = 60$ , and the magnetising inductance,  $L_m$ , is 1 mH. If the output voltage is 50 V, determine the turns of the secondary side of the transformer,  $N_2$ , and the preferable switching frequency of the MOSFET. Ignore all losses of the converter. [20%]

4 A half-bridge power module is shown in Fig 5.

(a) Using one half-bridge with one inductor and one capacitor as a boost converter to feed a resistive load,

(i) Draw the circuit and explain the operation of switches. Derive the expression of the output voltage  $V_2$  as the function of duty ratio  $D$  and input voltage  $V_1$ , assuming ideal devices and continuous inductor current. [20%]

(ii) Derive the expression of the load current to achieve boundary inductor current continuity when the output voltage  $V_2$  is fixed. [10%]

(b) Using two half-bridges to build a DC to AC inverter,

(i) Draw the circuit (without AC filter). Explain the switching principle of bipolar switching and unipolar switching and state the advantage of unipolar switching over bipolar switching. [10%]

(ii) Using square wave modulation, sketch the output AC voltage against time and derive the expression of fundamental AC voltage amplitude for bipolar switching and unipolar switching, respectively. [20%]

(iii) The switching of a non-ideal device can be delayed, which can cause device failure when both upper and lower devices in a half-bridge are used. Explain the consequence of this failure caused by switching delay and the method of using gate signal to avoid such failure. State one drawback of this method. [10%]

(c) Using three half-bridges to build a DC to AC inverter feeding a three phase grid from an ideal 800 V battery,

(i) Draw the circuit. Sketch the line voltage harmonic spectrum when sine Pulse Width Modulation (PWM) is used. The switching frequency is  $f_s$  and fundamental frequency is  $f_1$ . [10%]

(ii) Determine the maximum Root Mean Square (RMS) value of the line voltage if using sine PWM and using space vector PWM, respectively. [10%]

(iii) Explain one method of reducing the size of the AC filter connecting the output of the inverter and the grid. State the main drawback of this method. [10%]

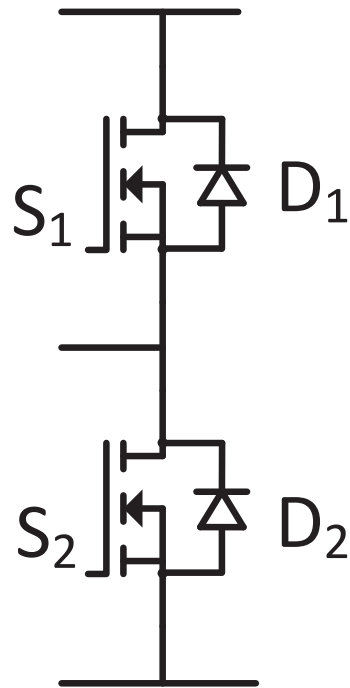


Fig. 5: Half-bridge module

**END OF PAPER**