Q1. Ptotal = 134 W P base = 2,5 W

Q2 I_1 =2.6 A I_2 =1.3 A, Sharing 66.67% vs 33.33%, V_{CE1} = 3 V and V_{CE2} = =3V