

SECTION A

Question 1)

If an amplifier with gain A is subject to positive feedback from its output to its input via a network B , explain what conditions would result in an oscillatory output.

[4]

For oscillations to occur the loop gain should be unity and the loop phase should be 0 or 2π , i.e. $AB=1$

The circuit in Fig. 1 is an oscillator based on four ideal operational amplifiers (OP1, OP2, OP3 and OP4), where a D.C. voltage $V_{ref} = 2.5$ V is provided to OP1 to provide a D.C. offset for the signal to allow for operation with a single-ended 5V power supply.

If V_X and V_Y denote the voltages at the points X and Y marked on the circuit in Fig. 1, by considering the signal passing through OP1, show that

$$V_Y = -\frac{R_2}{R_1}(V_X - V_{ref}) + V_{ref}$$

[3]

Current at inverting input is

$$\frac{V_X - V_{ref}}{R_1} = \frac{V_{ref} - V_Y}{R_2}$$

Hence

$$V_Y = -\frac{R_2}{R_1}(V_X - V_{ref}) + V_{ref}$$

As required

By considering the signal passing clockwise around the circuit from Y to X, passing through OP2, OP3 and OP4, show that

$$V_X = \left(\frac{1}{1 + j\omega RC}\right)^4 V_Y$$

[4]

Simple potential divider at the input of the OP2 gives

$$\frac{V_+}{V_Y} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

So output of OP2 is $V_- = V_+ = \frac{V_Y}{1 + j\omega RC}$.

This voltage is then divided at the input to OP3, so that the output of OP3 is $\frac{V_Y}{(1 + j\omega RC)^2}$.

Hence the input to OP4 is $\frac{V_Y}{(1 + j\omega RC)^3}$. This is also the output of OP4 which is then divided by the RC circuit to give

$$V_X = \frac{V_Y}{(1 + j\omega RC)^4}$$

as required

Derive an expression for the oscillation frequency for the circuit in Fig. 1 and the required value for R_2/R_1 for stable oscillations at this frequency.

[7]

For an A.C. signal the effect of V_{ref} may be neglected since it only corresponds to a D.C. offset, therefore the loop gain is

$$AB = -\frac{R_2}{R_1(1 + j\omega RC)^4}$$

We require $|AB| = 1$ and $\angle AB = 0$

The phase shift for the loop is

$$\pi - 4 \tan^{-1}(\omega RC)$$

Which should be total of zero phase

So $\tan^{-1}(\omega RC) = \pi/4$ and hence $\omega_r = 1/RC$

Therefore for a round trip unity gain gives

$$\left| \frac{1}{1 + j} \right|^4 \frac{R_2}{R_1} = 1$$

Therefore $\frac{R_2}{R_1} = 4$

Due to finite resistor values the amplifier gain is 4% higher than the ideal, calculate the corresponding percentage change in the oscillation frequency. You may assume that this small deviation has a minimal impact on the loop phase.

[7]

$$[1 + (\omega RC)^2]^2 = 4 \times 1.04$$

So

$$1 + (\omega RC)^2 = 2 \times 1.02$$

So

$$(\omega RC)^2 = 1.04$$

Therefore

$$\omega RC = 1.02$$

So the oscillation frequency will increase by 2%.

Question 2)

In the amplifier circuit shown in Fig. 2, the transistor is biased at an operating point such that $I_B = 10 \mu\text{A}$, $I_C = 2 \text{ mA}$, $V_{BE} = 0.7 \text{ V}$, and $V_{CE} = 5 \text{ V}$. At this operating point $h_{fe} = 250$, $h_{ie} = 5 \text{ k}\Omega$ and the other transistor parameters h_{re} and h_{oe} may be neglected.

(a) Assuming the transistor is biased to maximise the output signal before clipping occurs, i.e. $V_C = V_{CC}/2$, determine appropriate values for the R_C and R_E stating any assumptions made.

[4]

Set $V_C = V_{CC}/2 = 10 \text{ V}$ therefore

$$R_C = \frac{10}{2 \times 10^{-3}} = 5 \text{ k}\Omega$$

If $V_{CE} = 5 \text{ V}$ and $V_C = 10 \text{ V}$ then $V_E = 5 \text{ V}$. Assume that $I_E \approx I_C$ therefore

$$R_E = \frac{5}{2 \times 10^{-3}} = 2.5 \text{ k}\Omega$$

(b) If the current flowing through R_2 is designed to be $10I_B$, determine appropriate values for R_1 and R_2 .

[4]

$V_E = 5 \text{ V}$ therefore $V_B = 5.7 \text{ V}$. The voltage across R_2 is therefore $20 - 5.7 = 14.3 \text{ V}$. Current through $R_2 = 10 \times I_B = 100 \mu\text{A}$ therefore


$$R_2 = \frac{14.3}{100 \times 10^{-6}} = 143 \text{ k}\Omega$$

the current flowing through R_1 will be $9 \times I_B = 90 \mu\text{A}$ and the voltage across R_1 will be 5.7 V therefore

$$R_1 = \frac{5.7}{90 \times 10^{-6}} = 63.3 \text{ k}\Omega$$

Draw a small-signal equivalent circuit for the amplifier valid for mid-band frequencies (where the reactance of the capacitors C_i , C_o and C_E may be assumed to be zero).

[4]

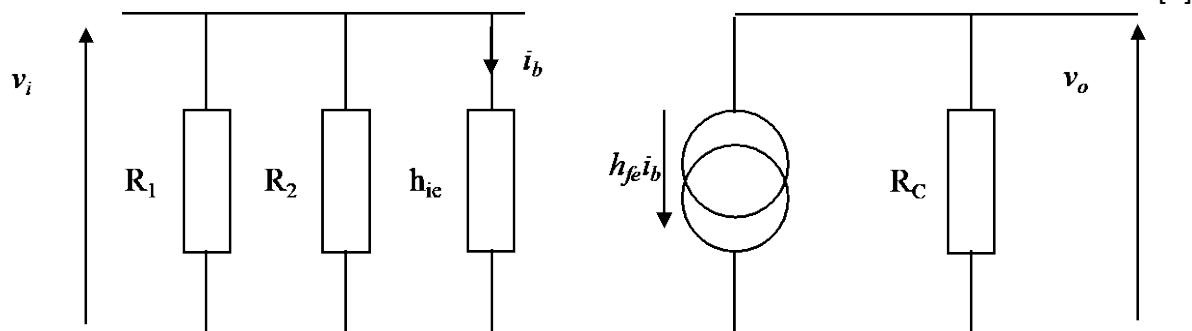

Using the small-signal circuit, calculate

- (i) The small-signal voltage gain
- (ii) The small-signal input resistance
- (iii) The small-signal output resistance

[6]

i)

$$i_b = \frac{v_i}{h_{ie}}$$

$$v_o = -h_{fe}i_bR_C = -\frac{h_{fe}v_iR_C}{h_{ie}}$$

Therefore small signal gain is

$$\frac{v_o}{v_i} = -\frac{h_{fe}R_C}{h_{ie}} = \frac{-250 \times 5 \times 10^3}{5 \times 10^3} = -250$$

ii) Small signal input resistance is

$$R_1 || R_2 || h_{ie} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{h_{ie}} \right)^{-1} = \left(\frac{1}{63.3 \times 10^3} + \frac{1}{143 \times 10^3} + \frac{1}{5 \times 10^3} \right)^{-1} = 4.5 \text{ k}\Omega$$

iii) Small-signal output resistance is


$v_i = 0$, therefore $i_b = 0$ therefore current source becomes an open circuit such that

$$r_o = R_C = 5 \text{ k}\Omega$$

If the capacitor C_E is now omitted from the circuit such that the impedance between the emitter and the ground is R_E , draw the small-signal equivalent circuit for this modified circuit and calculate

- (i) The small-signal voltage gain
- (ii) The small-signal input resistance
- (iii) The small-signal output resistance

[7]

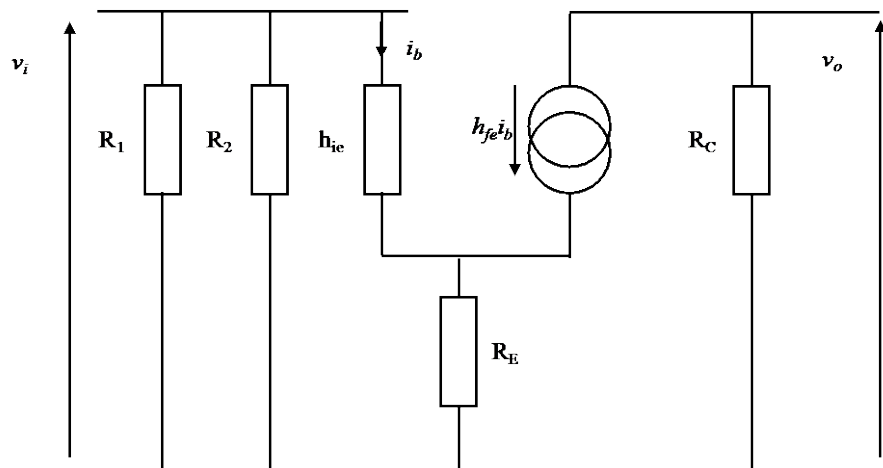

- (i) The small-signal voltage gain

$$v_o = -h_{fe}i_bR_C$$

$$v_i = i_b h_{ie} + (1 + h_{fe})i_b R_E$$

$$\frac{v_o}{v_i} = -\frac{h_{fe}R_C}{h_{ie} + (1 + h_{fe})R_E} = -\frac{250 \times 5 \times 10^3}{5 \times 10^3 + 251 \times 2.5 \times 10^3} = -1.97$$

- ii) The small-signal input resistance

$$\text{Input current } i_i = \frac{v_i}{R_1} + \frac{v_i}{R_2} + i_b$$

$$v_i = h_{ie}i_b + (1 + h_{fe})i_b R_E$$

Therefore

$$i_i = \frac{v_i}{R_1} + \frac{v_i}{R_2} + \frac{v_i}{h_{ie} + (1 + h_{fe})R_E}$$

Therefore input impedance

$$\begin{aligned} r_i = \frac{v_i}{i_i} &= \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{h_{ie} + (1 + h_{fe})R_E} \right)^{-1} \\ &= \left(\frac{1}{63.3 \times 10^3} + \frac{1}{143 \times 10^3} + \frac{1}{5 \times 10^3 + 251 \times 2.5 \times 10^3} \right)^{-1} \\ &= 41 \text{ k}\Omega \end{aligned}$$

- iii) The small-signal output resistance $v_i = i_b h_{ie} + (1 + h_{fe})i_b R_E$
Set $v_i = 0$ therefore $i_b = 0$, hence current source becomes open circuit as before and thus

$$r_o = R_C = 5 \text{ k}\Omega$$

As before

Question 3)

(a) (i)

Start with Load D:

R and X parallel, so simply

$$P = 3 \text{ V}^2/R = 3 \times (415 \text{ V})^2/12 \Omega = 43 \text{ kW}$$

$$Q = 3 \text{ V}^2/X = 3 \times (415 \text{ V})^2/8 \text{ V/A} = 65 \text{ kVar}$$

$$S = \text{sqrt}(P^2 + Q^2) = 78 \text{ kVA}$$

Continue with Load Y:

R and X in series and different in each arm!

Calculate current of the first two arms

$$I_{Y1,2} = 240 \text{ V}/\text{sqrt}((20 \Omega)^2 + (10 \text{ V/A})^2) = 10.7 \text{ A}$$

Calculate current of the third arm

$$I_{Y3} = 240 \text{ V}/\text{sqrt}((10 \Omega)^2 + (5 \text{ V/A})^2) = 21.5 \text{ A}$$

Power is now the sum (with the respective resistance):

$$P = 2 \times (I_{Y1,2}^2 20 \Omega) + 1 \times (I_{Y3}^2 10 \Omega) = 4608 \text{ W} + 4608 \text{ W} = 9.2 \text{ kW}$$

Reactive power would be

$$Q = -2 \times (I_{Y1,2}^2 10 \text{ V/A}) - 1 \times (I_{Y3}^2 5 \text{ V/A}) = 2304 \text{ Var} + 2304 \text{ Var} = 4.6 \text{ kVar}$$

$$S = 10.3 \text{ kVA}$$

(ii)

Calculate the needed compensation in star configuration.

For compensation, the three arms would need to become equal. Increasing with a parallel load is not possible, so can only bring the arms with larger resistance and reactance down:

Add 20Ω in series with 10 V/A to the first two arms in star configuration, open circuit to the third.

(iii)

Simply three times 10Ω active and 5 V/A reactive in series.

(b)(i)

Line current of Load D

$$I_{d,act} = 415 \text{ V}/12 \Omega = 34.6 \text{ A}$$

$$I_{d,react} = 415 \text{ V}/8 \text{ V/A} = 51.9 \text{ A}$$

Power (which would also lead to line current of Load R):

$$P_r = 3 \times I_{Y3}^2 10 \Omega = 13.8 \text{ kVA}$$

$$Q_r = 3 \times I_{Y3}^2 5 \text{ V/A} = 6.9 \text{ kVar}$$

$$\Rightarrow I_{r,act} = P_r/(3 \times 240 \text{ V}) = 19.2 \text{ A}$$

$$\Rightarrow I_{r,react} = Q_r/(3 \times 240 \text{ V}) = 9.6 \text{ A}$$

(check total current magnitude: 21.5 A as in (a))

Full line current through power:

$$P_{total} = 43 \text{ kW} + P_r = 56.8 \text{ kW}$$

$$Q_{total} = 65 \text{ kVar} - Q_r = 58 \text{ kVar}$$

$$\Rightarrow I_{total,act} = P_{total}/(3 \times 240 \text{ V}) = 78.9 \text{ A}$$

$$\Rightarrow I_{total,react} = Q_{total}/(3 \times 240 \text{ V}) = 80.5 \text{ A}$$

$$I_{total} = 112.7 \text{ A}$$

(ii)

$$\tan \phi = 80.5 \text{ A}/78.9 \text{ A} = 1.02 \Rightarrow \phi = 45.58^\circ$$

$$\cos \phi = 0.7$$

(c)(i)

Unity power factor needs $-58 \text{ kVar} = 3 \text{ V}^2/X_c$ with three capacitors

$$\Rightarrow X_c = -3 (240 \text{ V})^2/58000 \text{ Var} = -3.0 \text{ V/A} = -1/(j\omega C)$$

$$\Rightarrow C = 1.06 \text{ mF}$$

(ii)

$$\cos \phi = 0.95 \Rightarrow \tan \phi = 0.329$$

$$\Rightarrow Q_{target} = P \tan \phi = 56.8 \text{ kW} \times 0.329 = 18.7 \text{ kVar}$$

$$\Rightarrow Q_{comp} = 58 \text{ kVar} - 18.7 \text{ kVar} = 39 \text{ kVar}$$

$$\Rightarrow X_c = -3 (240 \text{ V})^2/39 \text{ kVar} = -4.4 \text{ V/A}$$

$$\Rightarrow C = 0.72 \text{ mF}$$

(d)

Unity case: $S = P \Rightarrow I_L = 56.8 \text{ kW}/(3 \times 240 \text{ V}) = 78.9 \text{ A}$ from previously 112.7 A

\Rightarrow 70% of previous current or -30%

$\cos \phi = 0.95$:

$$I_{L,react} = Q_{target}/(3 \times 240 \text{ V}) = 26 \text{ A}$$


$$\Rightarrow I_L = \text{sqrt}((26 \text{ A})^2 + (78.9 \text{ A})^2) = 83.1 \text{ A}$$

\Rightarrow 74% of previous current or -26%

SECTION B

Question 4)

(a)

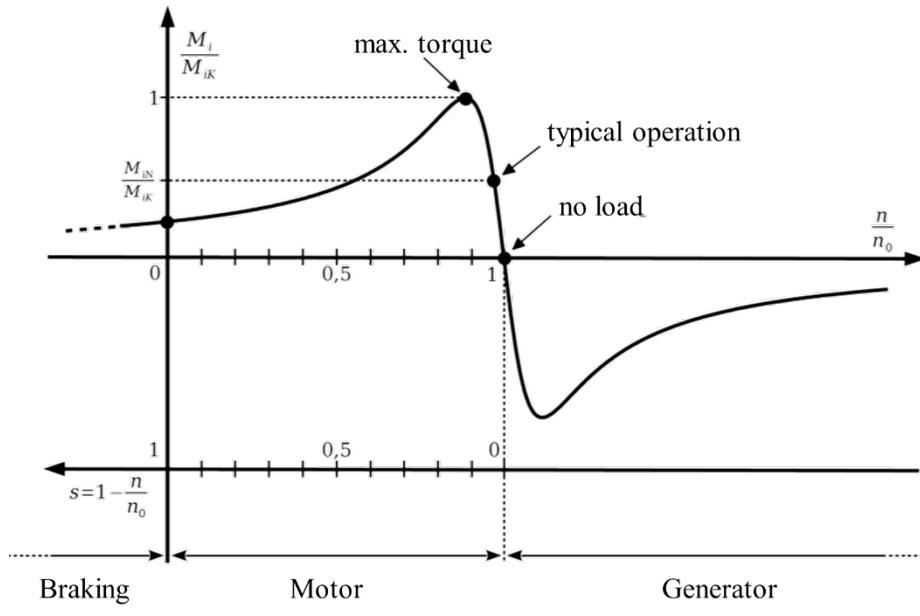

Slip in braking mode < 0

At synchronous speed (no load, no friction) $s = 0$

At speed 0, $s = 1$


When braking, torque points in opposite direction compared to speed \Rightarrow neg. mechanical power

(b)(i)

Blocked rotor: $s = 1$

Other point must be synchronous at exactly 3000 rpm $\Rightarrow s = 0$

(ii)

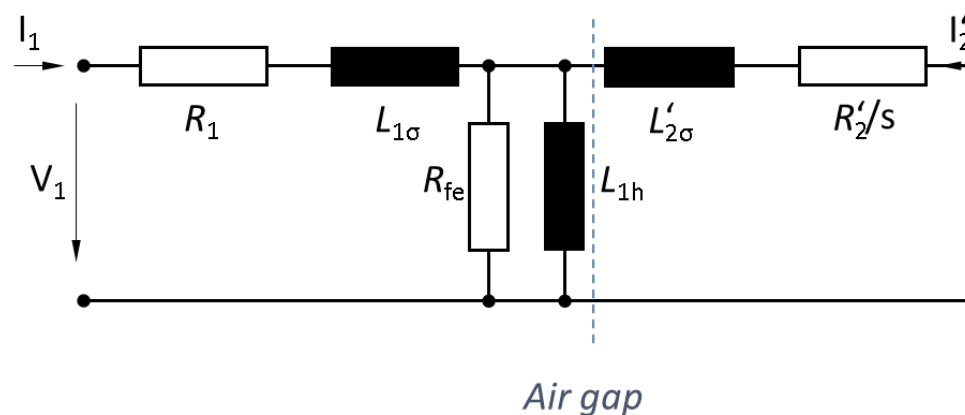

R_1 : copper resistance in stator

L_1 : stator stray inductance/reactance

R_{fe} or R_i : equivalent iron-loss resistance

L_{1m} : magn. reactance

L'_2 : rotor stray inductance/reactance (referred to stator)

R' : rotor resistance (can be split into loss and the equivalent part converted into mechanical power, both referred to the stator)

(iii)

No-load test at 3000 rpm, R'_2/s infinitely large

R_i and X_1 large compared to X_1 and $R_1 \Rightarrow$ entire voltage drop on them

$$\Rightarrow 3 V^2/R_i = 1200 \text{ W} \Rightarrow R_i = 430.6 \Omega$$

$$\Rightarrow I_{R_i} = 1/\sqrt{3} 415 \text{ V}/R_i = 0.556 \text{ A}; I_{X_h} = \sqrt{(8 \text{ A})^2 - I_{R_i}^2} = 7.98 \text{ A} = 1/\sqrt{3} 415 \text{ V}/X_h$$

$$\Rightarrow X_h = 30 \text{ V/A}$$

Locked rotor with $s = 1$, neglect R_i and X_i

$$X_1 = X'_2$$

$$3 (I/\sqrt{3})^2 (R_1 + R'_2) = 667 \text{ W} \Rightarrow R_1 + R'_2 = 2.61 \Omega$$

$$(16 \text{ A}/\sqrt{3})^2 (4 X_1^2 + (R_1 + R'_2)^2) = (30 \text{ V})^2$$

$$\Rightarrow X_1^2 = \frac{1}{4} ((30 \text{ V})^2 / (16 \text{ A}/\sqrt{3})^2 - (R_1 + R'_2)^2) = 0.934 \text{ V}^2/\text{A}^2$$

$$\Rightarrow X_1 = X'_2 = 0.966 \text{ V/A}$$

From sole stator measurement

$$(R_1 16 \text{ A}/\sqrt{3})^2 + (X_1 16 \text{ A}/\sqrt{3})^2 = (22.6 \text{ V})^2$$

$$\Rightarrow R_1^2 = (22.6 \text{ V})^2 - (X_1 16 \text{ A}/\sqrt{3})^2 \quad 3/(16 \text{ A})^2 = 3/(16 \text{ A})^2 (22.6 \text{ V})^2 - (X_1)^2 = 4.99 \Omega^2$$

$$\Rightarrow R_1 = 2.2 \Omega$$

$$\Rightarrow R'_2 = 2.61 \Omega - 2.2 \Omega = 0.41 \Omega$$

(c)(i)

Rotor resistance $R'_2/s = R'_2 (1 + 1/s - 1)$

loss resistance: R'_2

component modelling the power transfer to the mechanical domain: $R'_2 (1/s - 1)$

(ii)

$$s = 1 - 2700 \text{ rpm}/3000 \text{ rpm} = 0.1$$

(iii)

Total current path: $R_1 \rightarrow X_1 \rightarrow X'_2 \rightarrow R'_2 \rightarrow R'_2 (1/s - 1)$

$$\text{Current: } I = \sqrt{3} 415 \text{ V}/\sqrt{(R_1 + R'_2/s)^2 + 4 X_1^2} = \sqrt{3} 415 \text{ V}/\sqrt{(2.2 \Omega + 0.41 \Omega/0.1)^2 + 4 \times 0.934 \text{ V}^2/\text{A}^2} = \sqrt{3} 415 \text{ V}/6.59 \text{ V/A} = 109 \text{ A}$$

$$P_r = 3 \times R'_2 (I/\sqrt{3})^2 = 4878 \text{ W}$$

$$P_s = 3 \times R_1 (I/\sqrt{3})^2 = 26175 \text{ W}$$

Question 5)

a)

$$V = 1/\sqrt{LC} = 1/(400 \times 10^{-9} \times 100 \times 10^{-12})^{0.5} = 1.58 \times 10^8 \text{ m/s}$$

$$Z = (L/C)^{0.5} = 63.25 \Omega$$

Assuming $\mu_r = 1$

$$V = \frac{1}{\sqrt{\epsilon_0 \epsilon_r \mu_0 \mu_r}} = \frac{c}{\sqrt{\epsilon_r}}$$

With $c = 3 \times 10^8 \text{ m/s}$

Therefore

$$\epsilon_r = c^2/v^2 = 3.61$$

b)

wavelength $\lambda = V/f = 1.58 \times 10^8 / 250 \times 10^6 = 0.632 \text{ m}$

for open circuit, length = $\lambda/4 = 0.158 \text{ m}$

for short circuit, length = $\lambda/4 = 0.316 \text{ m}$

c)

$$\rho_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{150 - 63.25}{150 + 63.25} = 0.41$$

$$\text{VSWR} = \frac{1 + |\rho_L|}{1 - |\rho_L|} = 2.39$$

d)

$$V_{\text{GEN}}=150 \text{ V rms}$$

$$V_L=V_{\text{GEN}}(1+\rho_L)=211.5\text{V}$$

$$\text{Power}=V_L^2/R=298.2\text{W}$$

Question 6)

a)

$$\text{Peak power intensity} = \frac{\text{Gain} \cdot \text{Power}}{4\pi r^2} = \frac{2500 \cdot 30}{4\pi(3 \cdot 10^7)^2} = 6.63 \text{ pW m}^{-2}$$

b)

i) Power received = $A_{\text{eff}} \times \text{peak power intensity} = 19.9 \text{ pW}$

ii) Perfect matching: all power received goes to the power electronics (neglecting re-emission).

$$\text{Therefore } 19.9\text{pW}=0.5 VI= 0.5 I^2Z_0$$

$$\text{Then } I = \sqrt{\frac{19.9 \cdot 10^{-12}}{0.5 \cdot 50}} = 892.2\text{nA and } I_{\text{rms}}=630.9\text{nA}$$

c)

The signal is broadcast isotropically. Hence the power per unit area, P , at a distance r from the source is:

$$P=10000/(4\pi r^2) \text{ W/m}^2$$

The receiver area is 0.03m^2 , hence the power received at the antenna, P_{rec} , is:

$$P_{\text{rec}}=P \times 0.03 \text{ W} = 300/(4\pi r^2) \text{ W}$$

At the maximum distance, r_{max} , $P_{\text{rec}}=10^{-9}\text{W}$

$$\text{Hence } r_{\text{max}}=[300/(4\pi \times 10^{-9})]^{0.5}=154.51 \text{ km}$$

d)

If the receiver is placed at 85% r_{max} , then the power received is $(1/0.85)^2$ times the minimum required level

If the receiver is inclined at an angle θ to the optimum angle for picking up the signal, then the effective area is reduced by a factor $\cos(\theta)$

Hence, the antenna can be misoriented by and still pick up the minimum required signal, with

$$\text{Cos}(\theta_{\text{max}})=(0.85)^2$$

$$\text{Hence } \theta_{\text{max}}=43.74^\circ$$