

1(a) Radiation resistance, R_r : power radiated $P_r = \frac{1}{2} I^2 R_r$
 Gain, G : $\frac{\text{max. power density radiated}}{\text{power density from isotropic antenna}} = G$

Radiation efficiency, $e = \frac{P_r}{P_{in}}$ where $P_{in} = \frac{1}{2} I^2 (R_r + R_{ohmic})$

Effective Aperture, A_e : power delivered into a matched load by antenna = $A_e \times \text{power density}$

$$G = 4\pi A_e / \lambda^2$$

(b) Power density @ Earth = $\frac{P_r \cdot G_{gain}}{4\pi (\text{Range})^2}$

$$= \frac{75 \cdot 1.5}{4\pi (145 \times 10^9)^2}$$

$$= 4.26 \times 10^{-22} \text{ W/m}^2$$


(c) (i) $P_{rec} = \frac{\pi (35)^2}{4} \cdot 4.26 \times 10^{-22} = 4.10 \times 10^{-19} \text{ W}$

$= \frac{V^2}{R}$ with $R = 150 \Omega$

$\therefore V = (150 \times 4.10 \times 10^{-19})^{1/2} = 7.84 \text{ nV rms}$
22.2 nV pk-pk

(ii) $G = 4\pi A_e / \lambda^2$ where $A_e = 962 \text{ m}^2$
 $\lambda = \frac{c}{f} = \frac{3 \times 10^8}{11 \times 10^9} = 0.0273 \text{ m}$

$\therefore G = 16.2 \times 10^6$

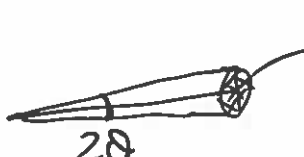
Estimate beam angle:  $A_a = \pi (R\theta)^2$
 $A_t = 4\pi R^2$

$$G = \frac{4\pi R^2}{\pi R^2 \theta^2} = \frac{4}{\theta^2} = 16.2 \times 10^6 \quad \therefore \theta = 4.97 \times 10^{-4} \text{ rad.}$$

$$= 0.0285^\circ$$

or full beam angle 0.057°

1(d) Lander antenna length = $\frac{\lambda}{4} = 6.83 \text{ mm}$
 skin depth = $\sqrt{\frac{2\rho}{\omega\mu}} = \left(\frac{2 \cdot 6.9 \times 10^{-7}}{2\pi \cdot 11 \times 10^9 \cdot 4\pi \times 10^{-7}} \right)^{1/2}$



$$A = 2\pi r \delta$$

$$\text{Antenna resistance} = \frac{\rho L}{A} = \frac{6.9 \times 10^{-7} \cdot 6.83 \times 10^{-3}}{2\pi \cdot 0.25 \times 10^{-3} \cdot 3.96 \times 10^{-6}} = 0.76 \Omega$$

$$R_r = 30\pi^2 \left(\frac{\Delta z}{\lambda} \right)^2 \text{ for cosine dist. (74}\Omega\text{)}$$

$$\text{OR } 20\pi^2 \left(\frac{\Delta z}{\lambda} \right)^2 \text{ for linear dist. (50}\Omega\text{)}$$

\therefore Take for cosine distribution for current $e \approx 99\%$


(e) For lander antenna $A_e = \frac{G \lambda^2}{4\pi} = \frac{1.5 \cdot 0.0273^2}{4\pi}$
 $A_e = 8.90 \times 10^{-5} \text{ m}^2$

Power density = $\frac{P_r \cdot G}{4\pi R^2} = \frac{1000 \cdot 16.2 \times 10^6}{4\pi (145 \times 10^9)^2} = 6.13 \times 10^{-14} \text{ W/m}^2$
 @ lander

$$\therefore P_{rec} = 8.9 \times 10^{-5} \cdot 6.13 \times 10^{-14} = \frac{V_s^2}{75}$$

$$\therefore \underline{V_s = 20.2 \text{ nV}_{rms} \quad (57.2 \text{ nV}_{pk-pk})}$$


2(a)(i)

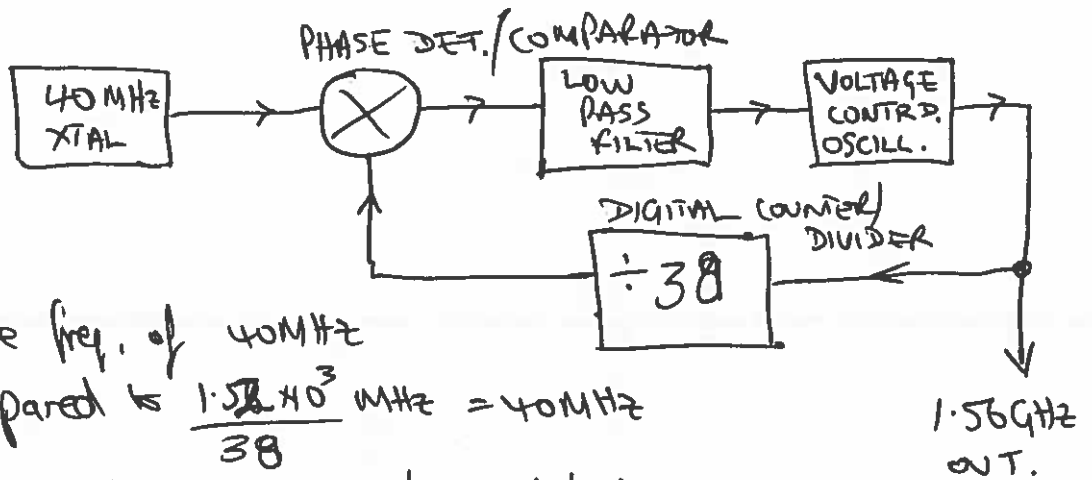

Reference freq. of 40 MHz is compared to $\frac{1.56 \times 10^3}{38} \text{ MHz} = 40 \text{ MHz}$

VCO scaled output is phase detector. The low-pass filter smooths the PD output to provide input to VCO. Before phase lock, the beat freq. puts side-bands on the VCO. ~~sp~~ - one is at same freq. as reference and mixer in PD to provide DC offset to push the VCO to the correct frequency. Once locked the divided VCO freq. matches the reference.

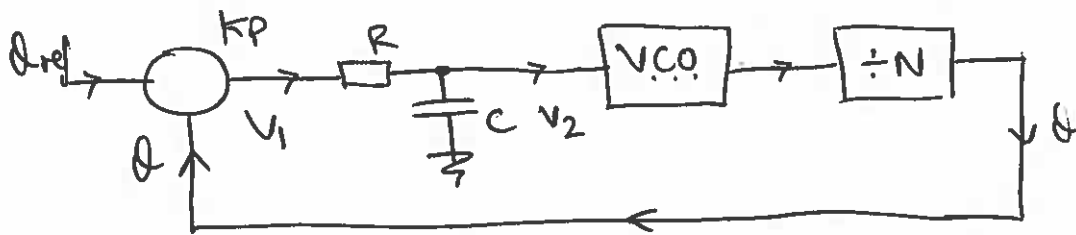(ii) (Note: if using XOR gate, best is $\div 19$ then $\div 2$ to get 50:50 square wave for phase comparison)



$$\textcircled{1} \quad V_1 = K_p (\omega_{ref} - \theta)$$

$$K_p = 3.3 \text{ V for } 180^\circ = \pi \text{ rad.}$$

$$\therefore K_p = 1.05 \text{ V/rad.}$$

$$\text{with } \theta = e^{j(\omega t + \theta)}, \quad \frac{d\theta}{dt} = \dot{\theta} = j\omega\theta, \quad \frac{d^2\theta}{dt^2} = \ddot{\theta} = -\omega^2\theta$$

$$V_2 = \frac{V_1}{1 + j\omega CR} \quad \therefore V_1 = V_2 + j\omega CR V_2 \quad \textcircled{2}$$

① & ②:

$$\therefore K_p (\omega_{ref} - \theta) = \frac{V_2}{K_p} + j\omega CR \frac{V_2}{K_p} \quad \text{with } \frac{K_0 V_2}{N} = \frac{d\theta}{dt} = j\omega\theta$$

$$\therefore \omega_{ref} = \frac{j\omega N \theta}{K_p K_0} + \frac{j\omega CR}{K_p} \frac{j\omega N \theta}{K_0} + \theta$$

(d) 2(ii) contd. $\delta \omega = \delta \frac{N}{K_p K_o} + \delta + \delta \frac{CRN}{K_p K_o}$

See page 6 Mechanics Data Book:

$\frac{CRN}{K_o K_p} = \frac{1}{\omega_n^2}$, $\frac{N}{K_o K_p} = \frac{2c}{\omega_n}$ with $c=1$ for critical damping

$K_p = 1.05 \text{ V/rad}$, $N = 3 \text{ \AA}$, $K_o = 2\pi \times 10^9 \text{ rad/s/V}$

$\therefore \omega_n = \frac{2K_o K_p}{N} = 347 \times 10^6 \text{ rad/s}$

$\therefore CR = 1.44 \times 10^{-9} \text{ s}$ $\therefore R = 100 \Omega$, $C = 14.4 \text{ pF}$

2(b)(i)



$C/\text{unit length} \stackrel{\text{ringing approx.}}{\approx} \frac{2(w+2t)\epsilon_r}{t}$
for $C \approx \frac{A\epsilon}{t}$

velocity of propagation, $v = \frac{1}{\sqrt{\mu_o \epsilon_o \epsilon_r}} = \frac{1}{\sqrt{\mu \epsilon}}$


characteristic imp., $Z = \frac{\sqrt{\mu}}{\sqrt{\epsilon}} = \frac{1}{\sqrt{C}} = \frac{\sqrt{\mu_o \epsilon_o \epsilon_r} t}{2(w+2t)\epsilon_r}$

$\therefore 50 = \frac{\sqrt{4\pi \times 10^{-7}} \cdot 10^{-3} \cdot 0.6}{2(w+1.2 \times 10^{-3}) \sqrt{8.854 \times 10^{-12}} \cdot 2.5}$

$\therefore \frac{w}{10^3} + 1.2 = \frac{71.48}{50} \Rightarrow \underline{w = 0.23 \text{ mm}}$

(ii) Impedance mismatch will cause voltage reflection of magnitude $\frac{Z_1 - Z_2}{Z_1 + Z_2} = 0.2$ (= 4% power reflection) but more of a problem is the reflected wave, which can cause 'ringing' = edge spikes on transitions, disturbing the signals.

3(a)

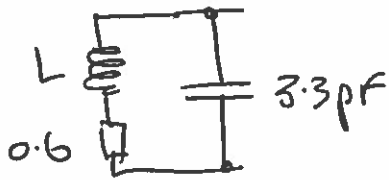


$$f = 868 \times 10^6 = \frac{1}{2\pi\sqrt{LC}}$$

$$\therefore L = 10.2 \text{ nH}$$

$$Q = \frac{\omega L}{R} = \frac{55.6}{0.6} = 92.7 = \frac{868}{\text{B.W.}} \therefore \text{B.W.} = 9.37 \text{ MHz}$$

(b)(i) From Smith chart, normalised imp. = $0.5 - j1.4 = 'A'$

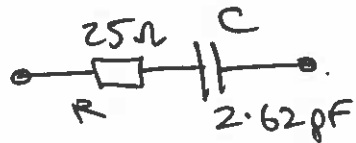\therefore de-normalise from $50 \Omega \Rightarrow Z = 25 - j70 \Omega$



$$\frac{1}{2\pi f C} = 70 \text{ with } f = 868 \times 10^6 \text{ Hz}$$

$$\therefore C = 2.62 \text{ pF}$$

(ii) From impedance point 'A' $0.5 - j1.4$, move 180°

to admittance point 'B' $0.22 + j0.64$

Move 'B' \rightarrow 'D' with parallel inductor: inductive susceptance of $-j0.22$ such that 180° around from 'D' is the impedance point 'C' $1 - j1.9$.

Then cancel $-j1.9$ with series inductor of $+j1.9$ is far to match point 'O' @ centre.


$$\text{Inductive suscept. } -j0.22/50 = j4.4 \times 10^{-3}$$

$$\Rightarrow \text{impedance} = \frac{1}{j4.4 \times 10^{-3}} = j227 \Omega = j2\pi f L$$


$$\therefore @ 868 \times 10^6 \text{ Hz, } L = 41.7 \text{ nH in parallel}$$

$$\text{Then series impedance} = j1.9 \times 50 = j95 = j2\pi f L$$

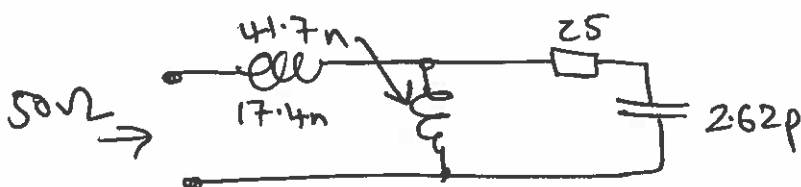
$$\therefore L = 17.4 \text{ nH in series}$$



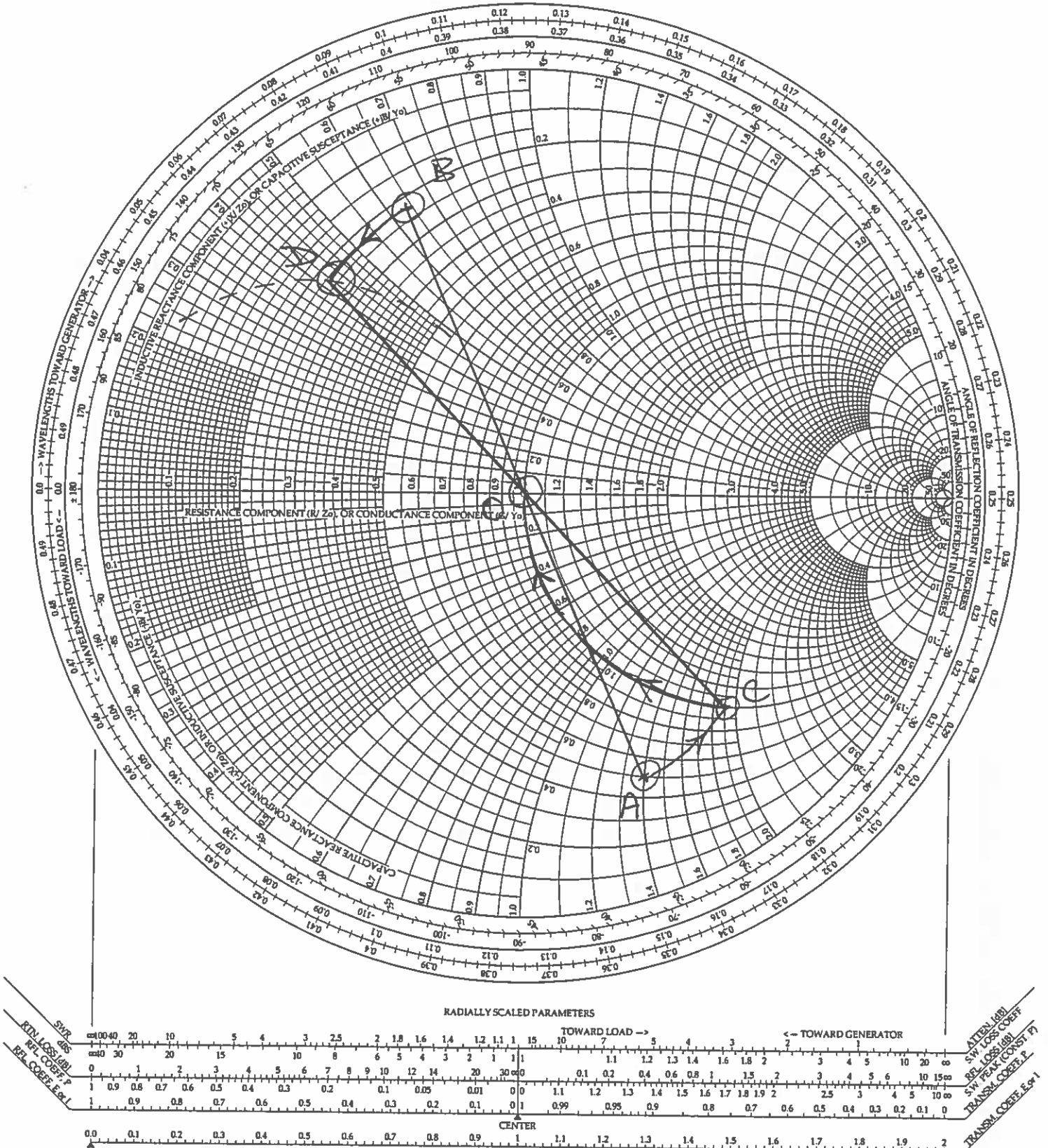Smith Chart to be detached and handed in with script if required




3(c) I.F. filter

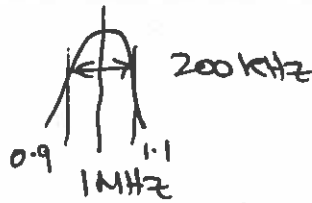

∴ low pass to 1.1 MHz
high pass from 0.9 MHz

Use Chebyshev for steep band edges


Low pass VCVS cct:

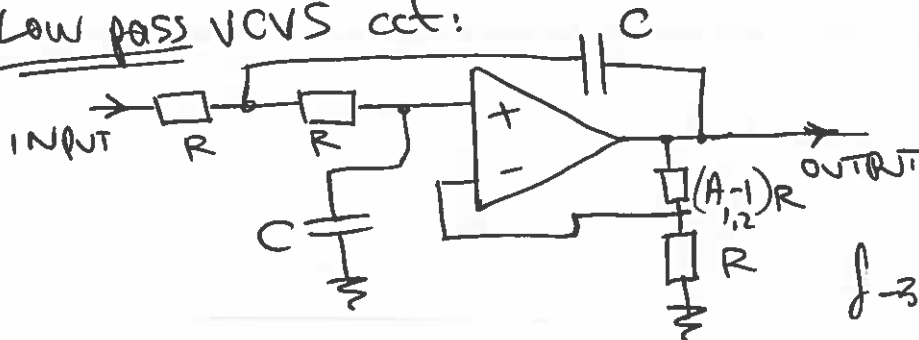

1, 2 stages
x 2 cascaded

$$f_{-3dB} = \frac{1}{2\pi f_n RC}$$

High pass VCVS cct.

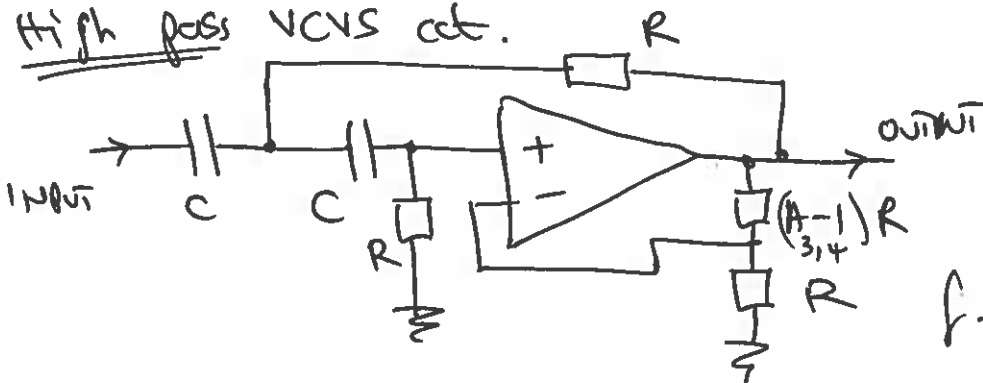

3, 4 stages
x 2 casc.

$$f_{-3dB} = \frac{f_n}{2\pi RC}$$

Low pass stages 1 & 2

$$1.1 \times 10^6 = \frac{1}{2\pi \cdot 0.597 \cdot 10^3 \cdot C_1} = \frac{1}{2\pi \cdot 1.031 \cdot 10^3 \cdot C_2}$$

$$C_1 = 242 \text{ pF}, C_2 = 140 \text{ pF}, R_1 = 582 \Omega, R_2 = 1.66 \text{ k}\Omega$$

High pass stages 3 & 4

$$0.9 \times 10^6 = \frac{0.597}{2\pi \cdot 10^3 \cdot C_3} = \frac{1.031}{2\pi \cdot 10^3 \cdot C_4}$$


$$C_3 = 106 \text{ pF}, C_4 = 182 \text{ pF}, R_3 = 582 \Omega, R_4 = 1.66 \text{ k}\Omega$$



time constant
~ 10ms

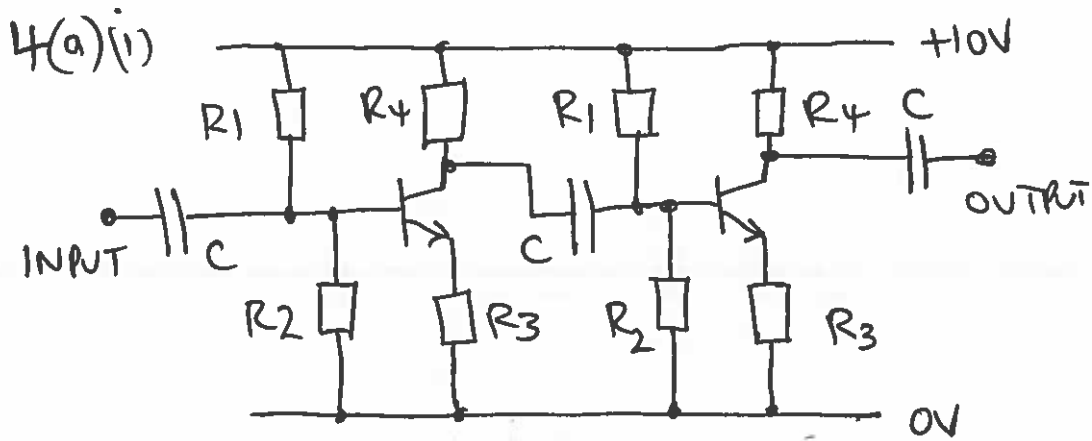optional R_i & C
to help
linearity of FET





R_1, R_2 : base bias resistors, set base-emitter voltage at $\approx 0.6V$ and V_c at $\approx 1/2$ supply

R_3 : emitter feedback resistor, sets gain and -ve feedback for bias to set V_c at $\approx 1/2$ supply

R_4 : output resistor C : coupling (dc blocking) caps.

(ii) $R_4 = 50\Omega$ for matched impedance

then $I_c = 0.1A$ for V_c @ $+5V$ d.c. ($1/2$ supply)

$$\therefore r_e = \frac{0.025}{0.1} = 0.25\Omega$$

For 30 dB extra gain when loaded $30 = 20 \log_{10} \left(\frac{V_o}{V_i} \right)$

$\therefore \frac{V_o}{V_i} = 31.6$ with 2 extra couplings to compensate

\therefore open circ. gain total = $31.6 \times 2 \times 2 = 127$

\therefore each stage gain (linear) = $\sqrt{127} = 11.27$ say (a bit of spare)

$$\therefore 12 = 50 / R_3 + r_e \quad \therefore R_3 = 3.9\Omega$$

Choose R_2 at 68Ω say, then $R_1 = 560\Omega$ to give $V_B \approx 1.1V$ and $R_{in} = 68 // 560 // 250 \times 42 \approx 57\Omega$ ok.


Choose C for low impedance \therefore say $10nF$ (0.02Ω)

(iii) $A = 12 \times 10^9 = \frac{1}{2\pi C_i e r_e} \leftarrow 0.25 \quad \therefore C_i e = 53 pF$


$$\frac{V_e}{V_i} = \frac{R_3}{R_3 + r_e} = 0.94 \quad \therefore \text{impedances} \rightarrow \text{ground are } \times \frac{1}{(1-0.94)} = \times 16.6$$

base-emitter


4(a)(iii) contd. small sig. model.

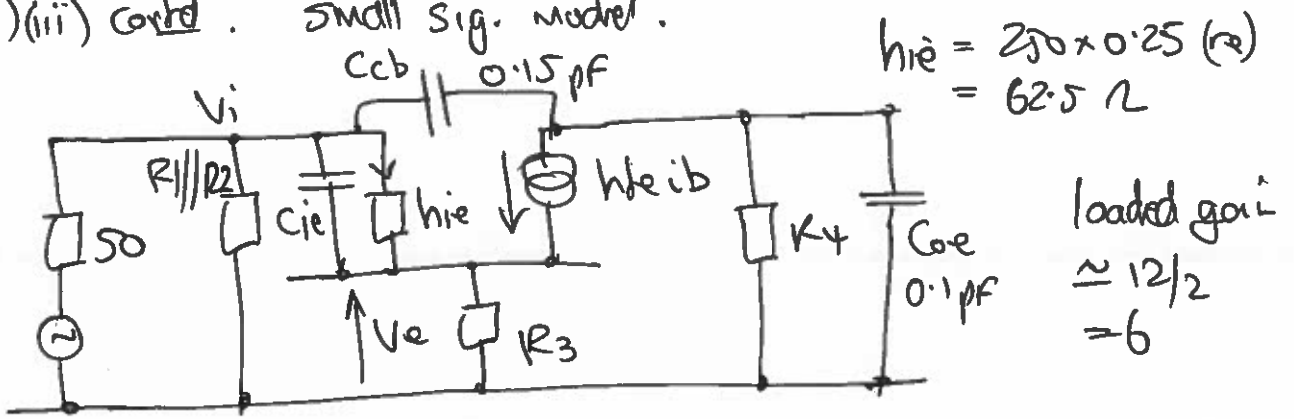

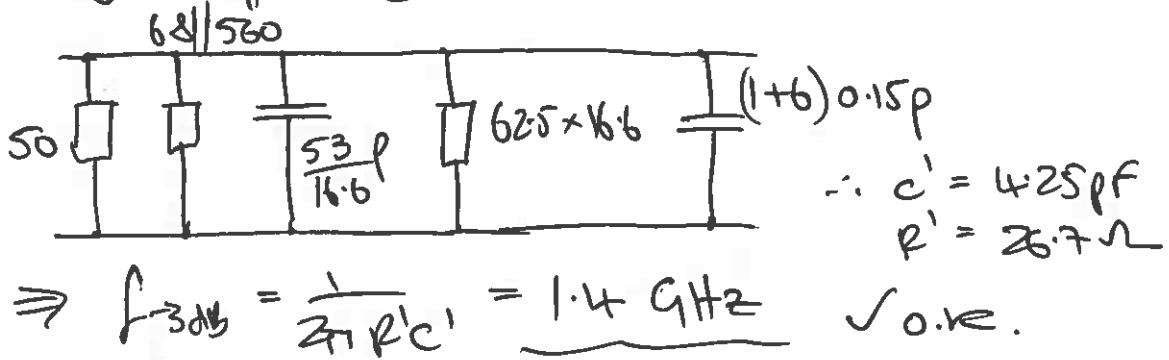Looking @ input only with values referred to gnd :-



4(b) Basic Colpitts ckt.

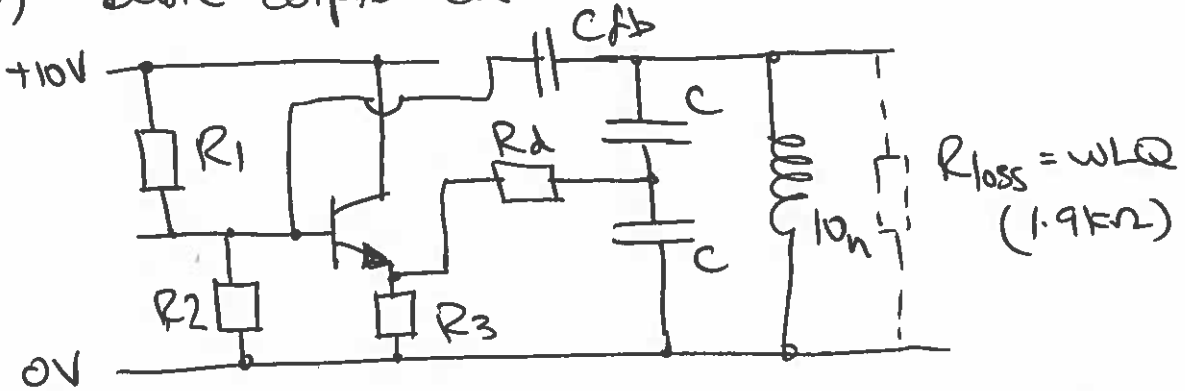

R_1 and R_2 set base @ $\sim 5.6V$ and are \sim few $k\Omega$ each (to match loss resistor). $\therefore R_1 = 2k7, R_2 = 3k3$

$$f = \frac{1}{2\pi \sqrt{L C/2}} = 868 \text{ MHz} \therefore C = 6.72 \text{ pF} \quad (\text{for } C_{be} \text{ compensation})$$

Resistance referred to C-C midpoint $\cong \frac{2k7 // 3k3 // 1k9}{4} \approx 200 \Omega$

\therefore Choose $R_d < 200 \therefore$ say 150Ω with $R_3 = 220 \Omega$
 $\therefore r_e \approx 11 \Omega, C_{be} = 12 \text{ pF}$

check $h_{fe} \times R_3 \gg$ few $k\Omega = 250 \times 220 = 55k\Omega \checkmark$
 Cfb for small impedance $\Rightarrow 1 \text{ nF}$ and C_{ce} refernd = $\frac{12 \text{ pF}}{221} \approx 0.05 \text{ pF} \checkmark$

Examiner's comments

Q1 Antennas

A popular and straightforward question, well-answered by most candidates. Most candidates knew the antenna term definitions and the antenna equation, and applied it correctly to calculate signal magnitudes. The beam angle was also estimated correctly in many cases.

Q2 Phase Locked Loop & waveguide

A less popular question; only attempted by about a third of the cohort. The basic PLL architecture and description was handled quite well although the detail of including a 'divide by 38' function to achieve the correct frequency was often omitted in the analysis. The stripline impedance calculation was generally well done.

Q3 Impedance matching & filters

This question was attempted by all candidates and quite well answered. There were several correct solutions available in the Smith Chart matching section, and the attempts seen covered all of them – although in some cases they started with the analytical matching equation and then illustrated the solution on the chart. The VCVS filter section was quite straightforward and well attempted in most cases.

Q4 RF amplifier & oscillator

A fairly popular question with good attempts on the whole. The 2-stage amplifier design was well answered, although the gain was often incorrect by a factor of 2 either way. The frequency response was also quite well attempted in many cases, although the unloaded gain was often considered rather than the loaded value. The oscillator design was also quite straightforward.