

1 a) i) Half wave rectifier. Two diodes to split the higher off voltage requirement, to the same as for a bridge. (Reduces EMI).

10%

~~100%~~

ii) Full bridge, lower ^{off state} ~~on state~~ voltage diodes. Symmetrical ac waveform. 2 pulses per cycle so smaller smoothing capacitor

15
~~20%~~


iii) $i = C \frac{dV}{dt}$ so surge current when diodes come on is reduced. L_{in} (R_{F2} in 1(a)) and C_{in1} , C_{in2} also form a filter for the pulses of current drawn by the SMPS. So the high freq. current is kept out of C_{in1}

10
~~15%~~

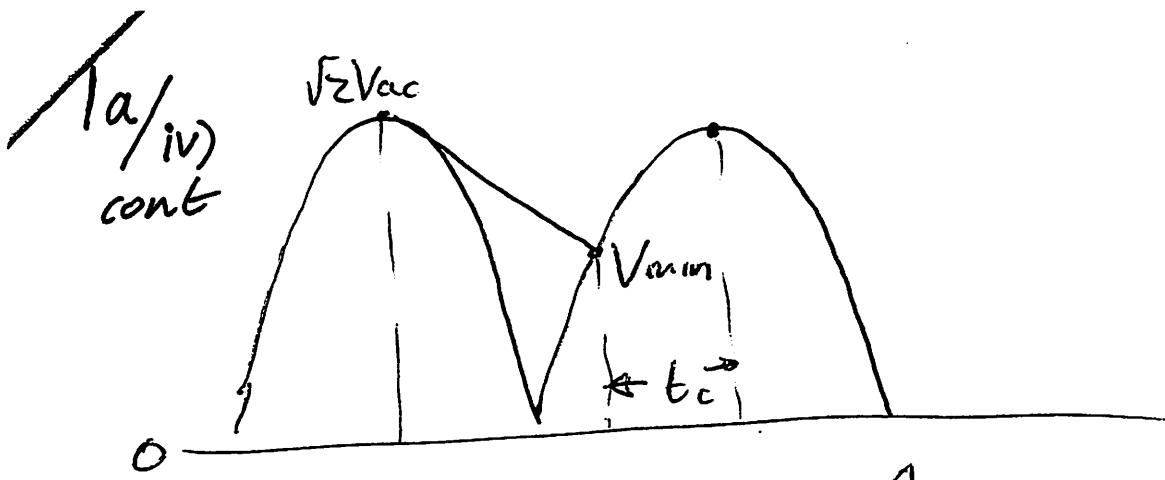iv) V_{ac} is rms. Stored energy is $\frac{1}{2} C V^2$

$$\frac{1}{2} C_{in} V_{ac}^2 \cdot \sqrt{2}^2 = C_{in} V_{ac}^2$$

P_o is the overall output, so this circuit needs P_{in} ! $P_{in} = \frac{P_o}{\eta}$. $\frac{1}{2f}$ is the period of $\frac{1}{2}$ a cycle.



assume discharge from \hat{V}

V_{min} when it starts to charge again.
 t_c diodes are on, so power from ac mains.
 $(\frac{1}{2f} - t_c)$ is the discharge time.

Energy supplied by $C_{in} = C_{in} V_{ac}^2 - \frac{C_{in} V_{min}^2}{2}$

20
~~25%~~

= Energy used $\frac{P_o}{\eta} (\frac{1}{2f} - t_c)$

ignore diode losses.

b) i) It operates as a step-up converter such that the current in L_1 is sinusoidal. Depending on the polarity of V_{ac} , D_3 or D_4 conduct and S_2 & D_1 alternate. So its or S_1 & D_2 .


15%

$D_4 D_1, D_4 S_1, D_4 D_1, \dots$

ii) D_4 is slow - rectifier type (or even MOSFET)

10%

D_1 must be fast

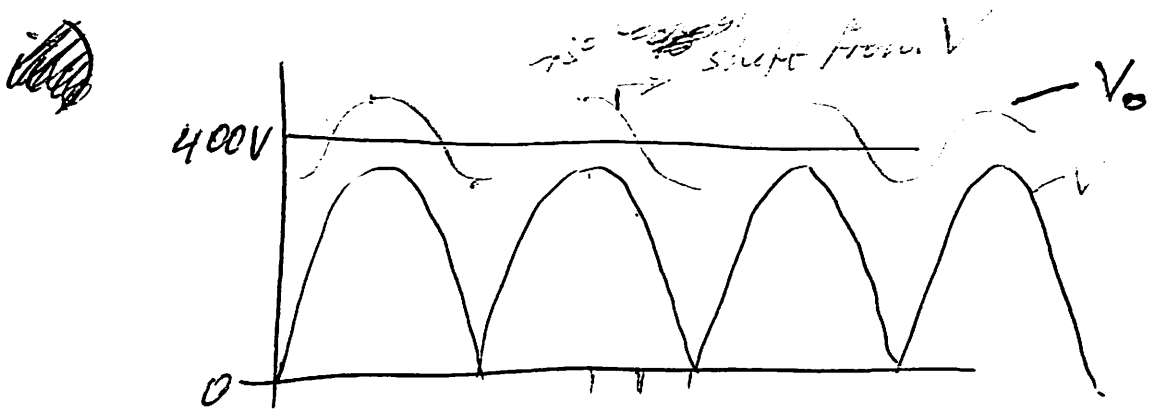

Higher harmonics are attenuated so 2nd dominates.

iii) F.S.

20%

$$6.25A \rightarrow \frac{2}{\pi} - \frac{4}{3\pi} \cos 2\omega t - \frac{4}{15\pi} \cos 4\omega t \dots$$


R small

$$I_2 = 6.25 \times \frac{2}{3} = 4.17A \text{ peak. } V_{o2} = 40V$$

$$V_{o2} = I_2 \cdot \frac{1}{2\pi f C} \Rightarrow C = \frac{4.17}{2 \times 100\pi \times 40} = 0.166 \mu F$$

$0.22 \mu F \Rightarrow 30V$

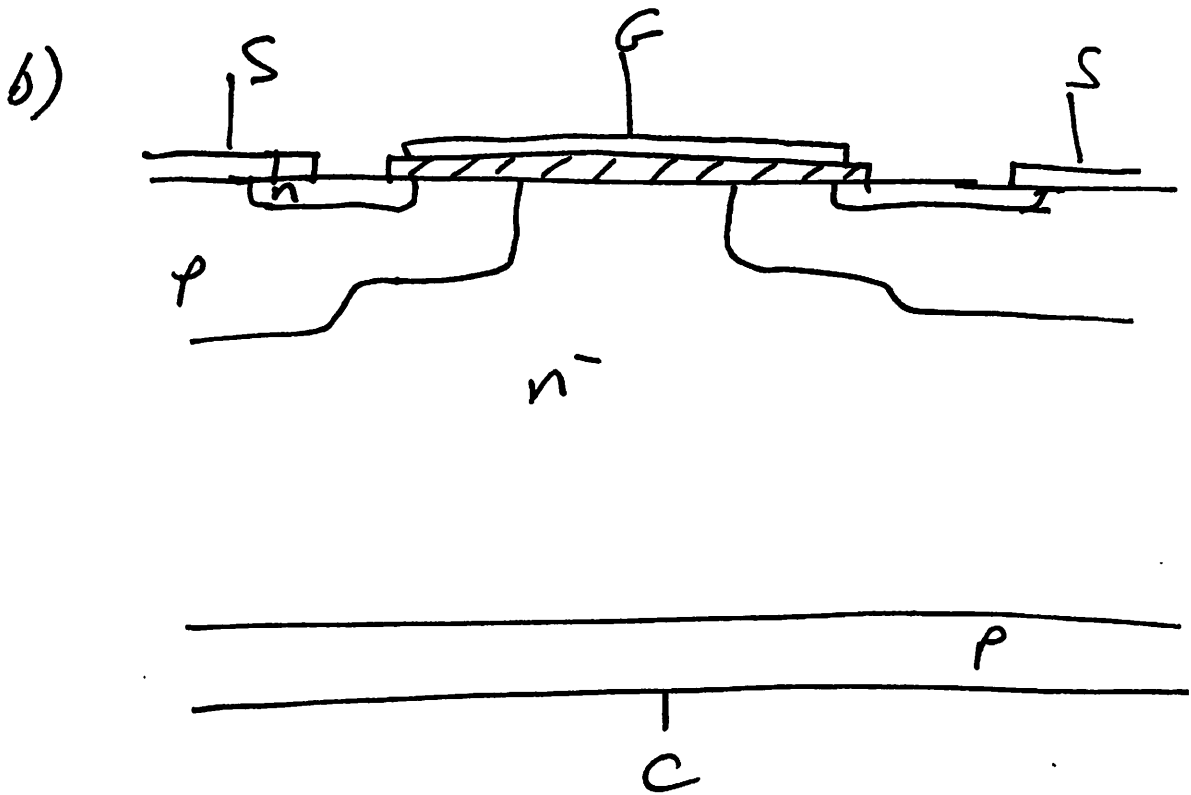
2/a) Base current replaces majority carriers lost by recombination in the base & extended base and lost across the b-e junction.



The bipolar is pnp so electrons are needed. These are provided by the MOS Channel formed in the p at the top

2/c) i


15%

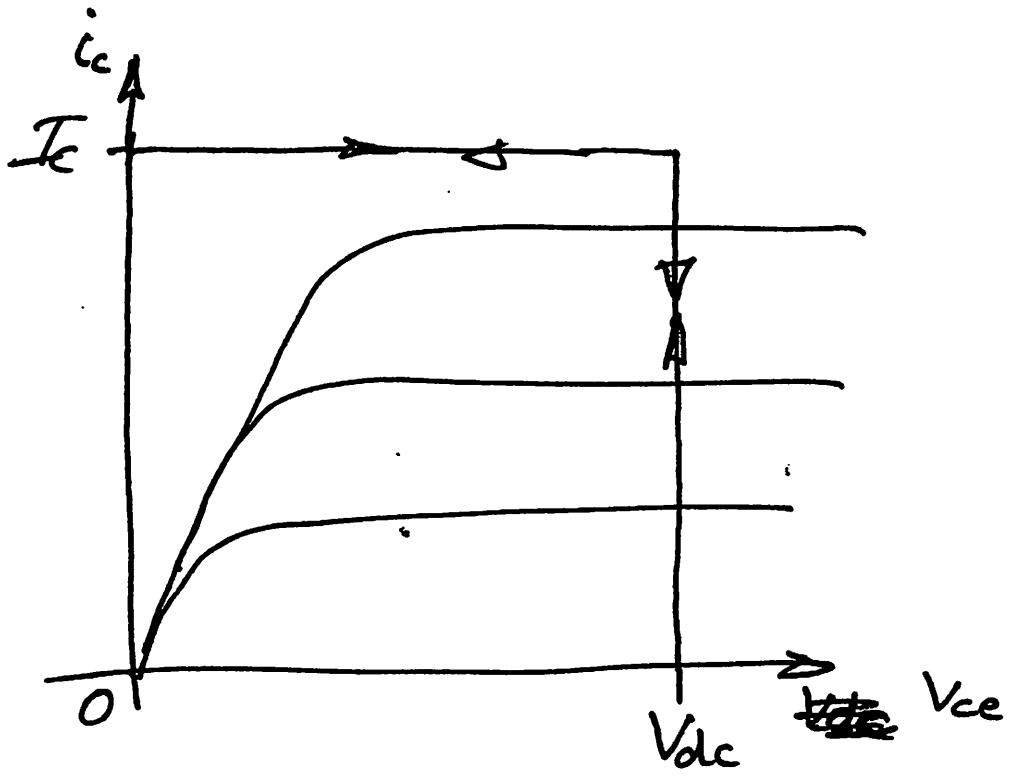

$$2/c) \text{ i) } f = 40 \text{ kHz} \quad D = 50\% \quad 25 \mu\text{s}.$$

$$\text{On-state } 1.5 \times 2 \times 0.5 = 1.5 \text{ W}.$$
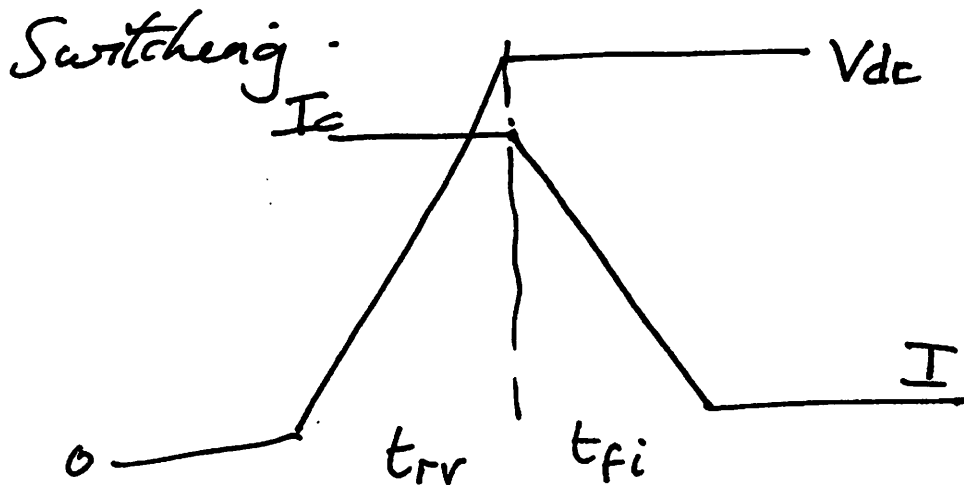
$$\text{Base losses } 0.3 \times 1 \times 0.5 = 0.15 \text{ W}.$$



$$\begin{aligned} \text{Energy} &= I_c \cdot V_{dc} \cdot \frac{t_{rr}}{2} + V_{dc} \cdot I_c \cdot \frac{t_{fi}}{2} \\ &= \frac{I_c V_{dc}}{2} (t_{rr} + t_{fi}) \end{aligned}$$


$$\Rightarrow 300 \times 1.5 \times \left[\frac{1.5 \mu}{2} + \frac{3.5 \mu}{2} \right] \times 40 \text{ k} = 45 \text{ W}.$$

30%


Its a lot! Switching is slow.

$$\text{Total } 46.65 \text{ W}$$

c iii) Inductive load

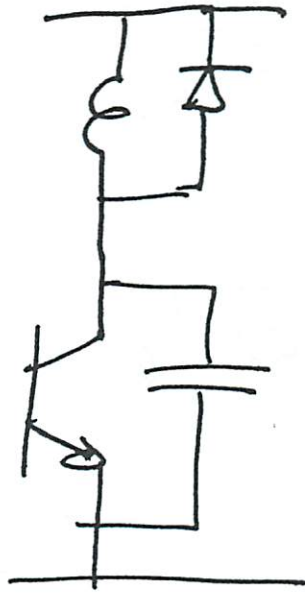

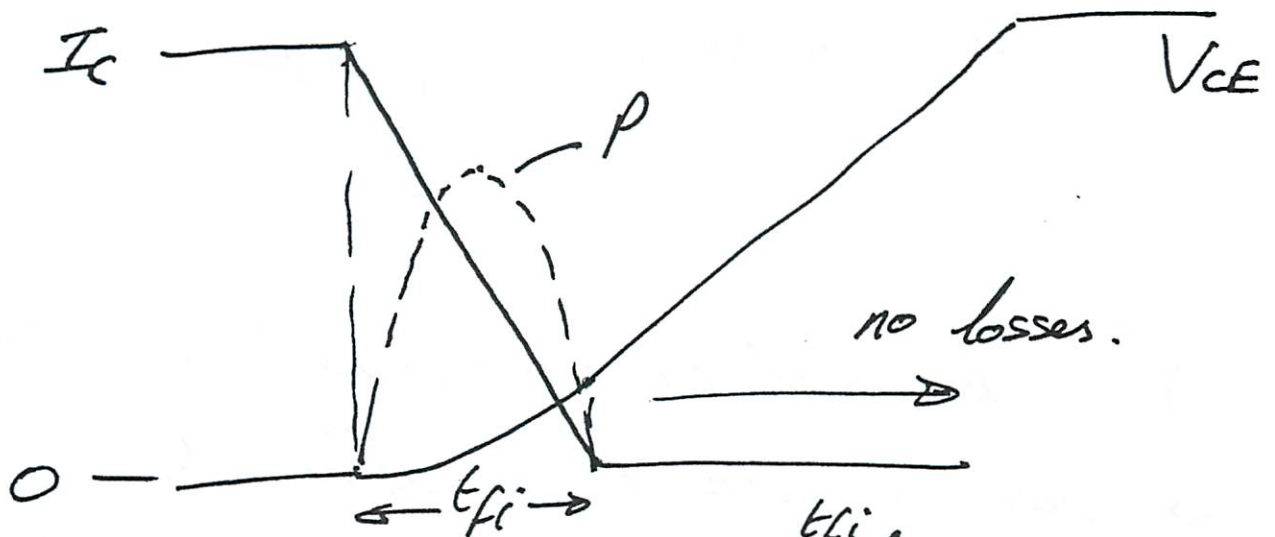As soon as V_{CE} rises the current in the BJT falls. — rate the same.



$$V_{CE} = \frac{1}{C} \int i_c dt = \frac{1}{C} \int_0^{t_{fi}} \frac{I_c}{t_{fi}} dt$$

$$= \frac{1}{C} \frac{I_c}{2} \frac{t^2}{t_{fi}} \Big|_0^{t_{fi}} = \frac{1}{C} \frac{I_c t_{fi}}{2}$$

$$V_{CE} = \frac{1}{0.02 \mu} \times \frac{1.5}{2} \times 2 \mu = 75V$$

15%

$$P = \frac{1.5}{2} \times \frac{75}{2} \times 2 \mu \times 40k = 0.45 W$$

2ciii cont. / It's a quadratic.

$$\text{Energy} = \int_0^{t_{fi}} \frac{I_c}{C} \frac{t^2}{2t_{fi}} \times I_c \left(1 - \frac{t}{t_{fi}}\right) dt$$
$$= \frac{I_c^2}{2Ct_{fi}} \left(\frac{t^3}{3} - \frac{t^4}{4t_{fi}} \right) \Big|_0^{t_{fi}} = \frac{I_c^2}{2Ct_{fi}} t_{fi}^3 \left(\frac{1}{3} - \frac{1}{4} \right)$$

$$= \frac{I_c^2}{24C} t_{fi}^2$$


$$= \frac{1.5^2}{24 \times 0.2 \mu} \cdot (2 \mu)^2$$

$$\text{Power} = \text{Energy} \times f = \frac{9}{24 \times 0.2 \mu} \times 40 \mu \text{ m}$$
$$= \underline{75 \text{ mW. !}}$$

iv) Must be used in a resonant converter
as turn on needs to be after the
15/0 capacitor has discharged, or the transistor
will blow up!

3 a) Step-down.

ii)

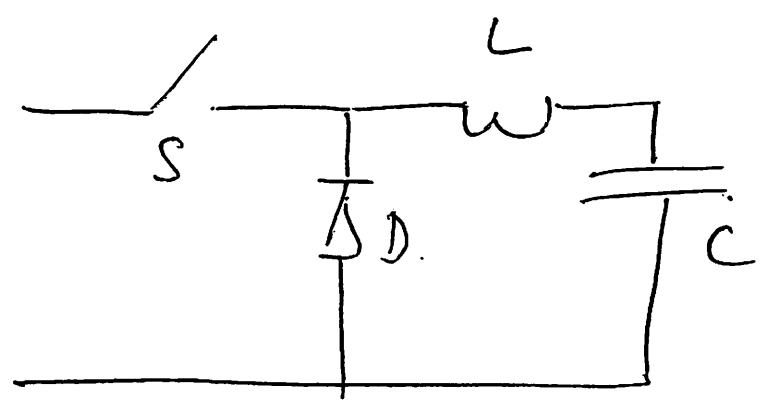


	DCM	CCM
Waveform		
	current reaches zero	current never zero.
L	small.	bigger
D	cheap	fast recovery expensive.
S	high \hat{I}	lower \hat{I}
C	larger C	smaller C
η	low switching losses.	higher sw losses.

35%
10%

ii.) Step down is more efficient as some energy is delivered directly to the load. Also no transformer is needed.

10%

3a iii) Link Switch - TN current

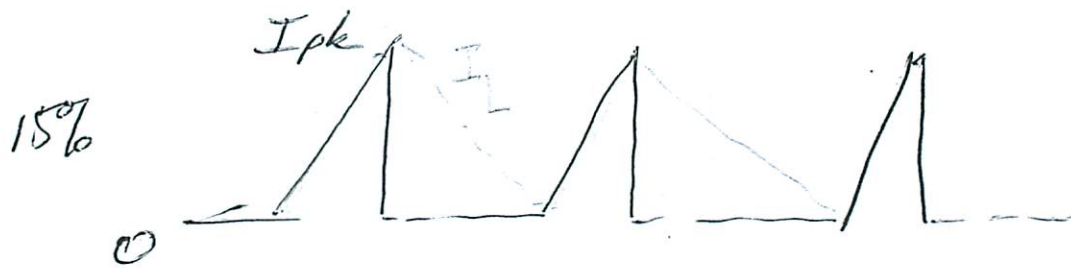

iv). RMS of a triangle.

Current rise - $\frac{I}{DT} t$; current fall $I \left[1 - \frac{t'}{(1-D)T} \right]$

squared. & mean

$$\frac{1}{T} \int_0^{DT} \frac{I^2 t^2}{(DT)^2} dt + \frac{1}{T} \int_0^{(1-D)T} \frac{I^2 \left[1 - \frac{t'}{(1-D)T} \right]^2 dt'}$$

$$\Rightarrow \frac{I^2}{T} \frac{DT}{3} + \frac{I^2}{T} \frac{(1-D)T}{3} = \frac{I^2}{3}$$

$$RMS = \frac{I}{\sqrt{3}}$$

The average is $\frac{I}{2}$ so the RMS is worse

25% for heating. As the inductor gets smaller I goes up, but an off time starts to appear so the RMS does not run away too fast. But I stresses the switch device, but L has less resistance! DCM more efficient

~~39~~ v)


Duty cycle $D = \frac{V_o}{V_{in}} = \frac{15}{325}$.

15% This is a very small D and small errors would lead to massive voltage movement in V_o . Much better just to skip cycles and keep D fixed.

4 a) "Two level" as output is either '0' or '1' or '0' or ' V_{dc} '. No middle state even if the voltages are $-V_{dc}$ and V_{dc} . So it is a good description.

Sine reference + triangular carrier.

20%

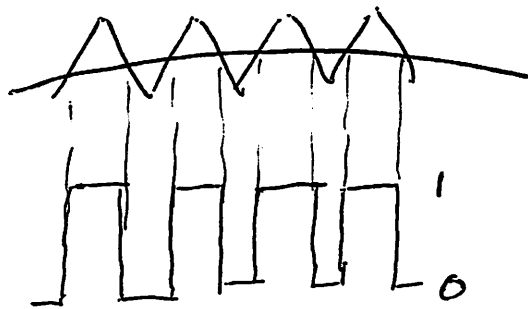


'1' \rightarrow T_1 on T_2 off
 '0' \rightarrow T_1 off T_2 on.

20%

b) i) No third, ninth, fifteenth as there are three legs and the third harmonics are in phase in a 3 phase system.

10%

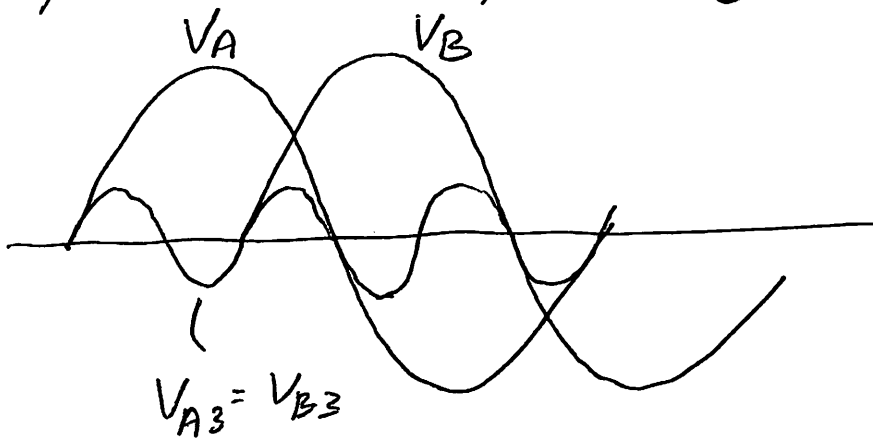

Since any output is across any two legs eg. $V_A - V_B = V_{AB}$ then the third harmonics have no contribution to V_{AB} as they cancel.

15%

~~b) ii)~~ In the Fourier series of a square wave the 3rd harmonic is at a magnitude of $\frac{1}{3}$. With just fundamental and $\frac{1}{3}$ of third the sum will exceed the peak level of the fundamental so overmodulation will occur. (Gibbs phenomenon)

$$\frac{d}{d\theta} \left(\sin\theta + \frac{1}{3} \sin 3\theta \right) = 0 = \cos\theta + \frac{3}{3} \cos 3\theta = 0$$

$$\theta \approx 30^\circ \quad 0.866 + \frac{3 \cdot 0}{3} = 0 \quad \times \quad 60^\circ \quad 0.5 - \frac{3 \cdot 1}{3} = 0$$

20% also ~~the~~ $\sin\theta + \frac{1}{3} \sin 3\theta = 1$ max value.
20%

check
With $\frac{1}{3}$ th. New peak is $1 - \frac{1}{3} = 0.833$.
at 90°

iii) at 30° . $0.5 + \frac{1}{3} = 0.666$.

at 60° $0.866 + 0 = 0.866$. ← max.


15% at 50° $0.766 + 0.0833 = 0.849$

at 70° $0.939 - 0.0833 = 0.855$

H.c) There are two zero states 000, 111

To optimize switching losses move from one state to the next with as few changes as possible. \rightarrow careful use of V_0 & V_z

Also switch between adjacent vectors eg.

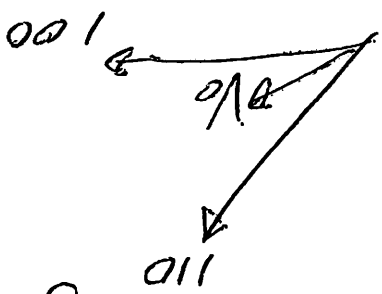


as there is only one change 100 to 110

Then the order matters

1000
000-100 \rightarrow 110 \rightarrow 111 \rightarrow 110-100-000

This is direct inverse. This reduces ripple.

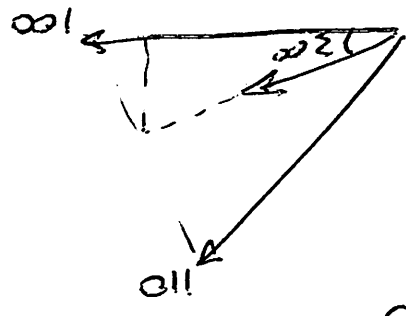(ii) At 30° magnitude of $\frac{1}{2}$ relative to the maximum



duty ratio is $\frac{1}{4}$ in 110, $\frac{1}{4}$ in 100, $\frac{1}{4}$ in 111

$\Rightarrow D_A = \frac{3}{4}, D_B = \frac{1}{2}, D_C = \frac{1}{4}$
 $\frac{1}{4}$ in 000

~~ii)~~ To stay there we could add a $\frac{1}{4}$ to each.

$\Rightarrow D_A = 1, D_B = \frac{3}{4}, D_C = \frac{1}{2}$


So now we have the same conditions for optimal BUT no switching in A!

Drawback is calculating how much to add!


Adding $\frac{1}{4}$ to each is making III bigger by a $\frac{1}{4}$

30% so gets rid of $\frac{1}{4}$ of 000 unnecessary.

In wave forms is easy to show!

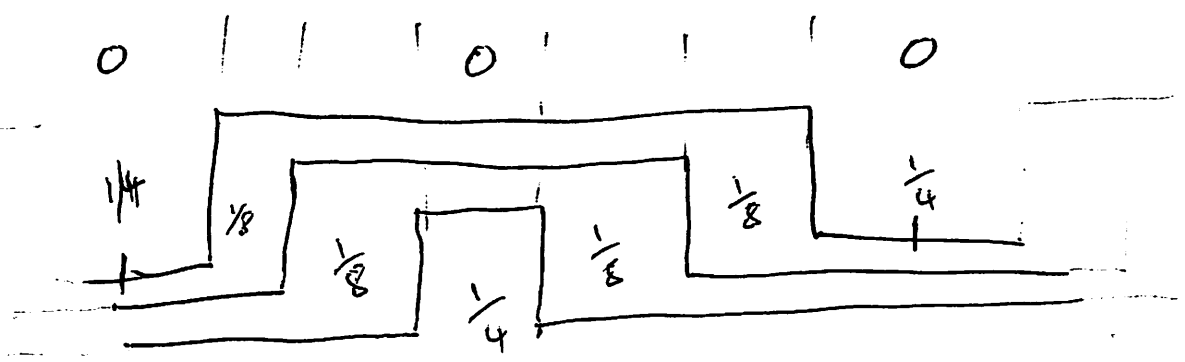

\Rightarrow

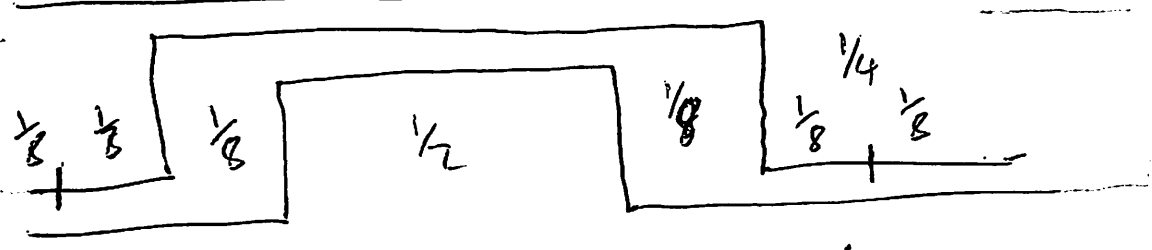

~~iii)~~

Higher ripple, also bootstrap may not work, asymptotical