

Solutions to 4B21


2018

Sanyiv Sambandan.

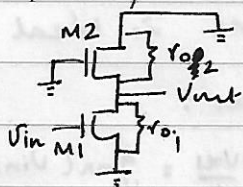- 1) (a) The primary advantage of CMOS is the high gain that is possible in a common source amplifier. (and subsequent amplifier families)

The reason for the high gain is that the output impedance of a CMOS common source is very high (Theoretically ∞ if we ignore channel length modulation).


As an example consider a non-CMOS and CMOS common source amplifier. for analysis.



$$g_{m1} V_{in} + \frac{V_{out}}{r_{o1}} = -g_{m2} V_{out} - \frac{V_{out}}{r_{o2}}$$

This is the problem.
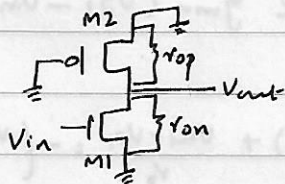
$$\frac{V_{out}}{V_{in}} = -g_{m1} (\underbrace{g_{m2}^{-1}}_{\text{low}} \parallel \underbrace{r_{o1} \parallel r_{o2}}_{\text{high}}) \Rightarrow \text{Gain is low.}$$



$$g_{m1} V_{in} + \frac{V_{out}}{r_{o1}} = -\frac{V_{out}}{r_{o2}}$$

no current due to V_{out} in the PMOS.

$$\Rightarrow \frac{V_{out}}{V_{in}} = -g_{m1} (\underbrace{r_{o1} \parallel r_{o2}}_{\text{High}}) \Rightarrow \text{Gain is high.}$$

Marking method (see highlight below)

WHILE MARKING:-

I am looking for two statements: (i) High gain (ii) High output impedance being the reason for the high gain.

(b) (i) Current through the MOSFETs = $\frac{\mu C_{ox}}{2} \frac{W}{L} (V_{ov})^2$
Gate overdrive voltage.

for the NMOS M1 & M2, the current = 0.1 mA, $V_{ov} = 0.2V$

$$\Rightarrow \frac{\mu_n C_{ox}}{2} \frac{W}{L} (0.2)^2 = 0.1 e^{-3}$$

$$\mu_n = 1000 \text{ cm}^2/Vs, C_{ox} = 400 e^{-9} \text{ F/cm}^2 \Rightarrow \left(\frac{W}{L}\right)_{M1} = \left(\frac{W}{L}\right)_{M2} = 12.5$$

for the PMOS M3 & M4, current = 0.1 mA, $V_{ov} = 0.2V$

$$\Rightarrow \frac{\mu_p C_{ox}}{2} \frac{W}{L} (0.2)^2 = 0.1 e^{-3} =$$

$$\mu_p = 250 \text{ cm}^2/Vs, C_{ox} = 400 e^{-9} \text{ F/cm}^2 \Rightarrow \left(\frac{W}{L}\right)_{M3} = \left(\frac{W}{L}\right)_{M4} = 50.$$

for the nmos MS, $i_{\text{ms}} = 0.2 \text{ mA}$ as it sinks the current from both branches $\Rightarrow (W/L)_{\text{MS}} = 25$.

(ii) We need to solve ^{for} the gain in the a.c circuit.

$$\text{Differential Gain} = \frac{v_{\text{out}}}{(v_{\text{in}+}) - (v_{\text{in}-})}$$


We will find output v_{o1} due to v_{in1} (i.e. v_{in+}) alone

v_{o2} due to v_{in2} (i.e. v_{in-}) alone

Then by superposition: $v_{\text{out}} = v_{o1} + v_{o2}$

We then calculate: $\frac{v_{\text{out}}}{v_{in1} - v_{in2}} = A_d = \text{Differential Gain}$.

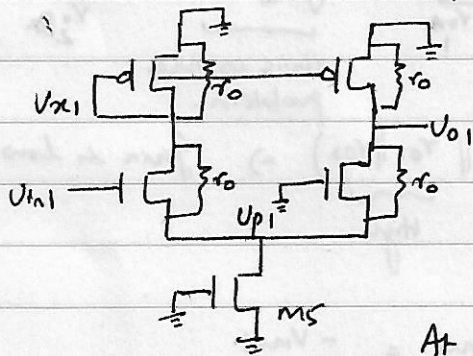Consider v_{in1} alone and ground v_{in2} . (MS is ideal.)



At node v_{x1} :

$$-g_{mp} v_{x1} - \frac{v_{x1}}{r_o} = g_{mn}(v_{in1} - v_{p1}) + \frac{v_{x1} - v_{p1}}{r_o}$$

Since $(g_{mn}r_o, g_{mp}r_o) \gg 1$

$$v_{x1} g_{mp} \approx g_{mn}(v_{p1} - v_{in1}) \rightarrow (1)$$

At node v_{p1} :

$$g_{mn}(v_{in1} - v_{p1}) + \frac{v_{x1} - v_{p1}}{r_o} = -\left(\frac{v_{o1} - v_{p1}}{r_o} - g_{mn}v_{p1}\right)$$

$$\Rightarrow g_{mn} v_{in1} - \frac{v_{x1}}{r_o} = -\frac{v_{o1}}{r_o} + v_{p1} \left(2g_{mn} + \frac{2}{r_o}\right)$$

Using (1) & the fact $(g_{mn}r_o, g_{mp}r_o) \gg 1$.

$$v_{p1} \approx \frac{v_{in1}}{2} + \frac{v_{o1}}{2g_{mn}r_o} \rightarrow (2)$$

At node v_{o1} :

$$-\frac{v_{o1}}{r_o} - g_{mp} v_{x1} = \frac{v_{o1} - v_{p1}}{r_o} - g_{mn} v_{p1}$$

$$\text{Using (1)} \Rightarrow -\frac{v_{o1}}{r_o} - g_{mn} v_{p1} + g_{mn} v_{in1} = \frac{v_{o1}}{r_o} - \frac{v_{p1}}{r_o} - g_{mn} v_{p1}$$

$$\text{Using (2)} \Rightarrow \left(g_{mn} + \frac{1}{2r_o}\right) v_{in1} = \left(\frac{-1}{2g_{mn}r_o} + 2\right) \frac{v_{o1}}{r_o} \Rightarrow v_{o1} = \frac{g_{mn}r_o}{2} v_{in1} \rightarrow (3)$$

Consider v_{in2} alone and ground v_{in1} (MS is ideal)

At node v_{x2} :


$$-\frac{v_{x2}}{r_o} - g_{mp} v_{x2} = \frac{v_{x2} - v_{p2}}{r_o} - g_{mn} v_{p2} \Rightarrow v_{x2} g_{mp} = g_{mn} v_{p2} \rightarrow (4)$$

At node V_{p2} :

$$-\left(\frac{V_{x2} - V_{p2}}{r_o} - g_{mn} V_{p2} \right) = \frac{V_{o2} - V_{p2}}{r_o} + g_{mn} (V_{in2} - V_{p2})$$

Using (4)
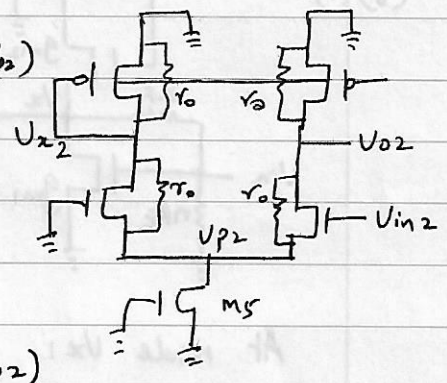
$$\Rightarrow 2g_{mn} V_{p2} = \frac{V_{o2}}{r_o} + g_{mn} V_{in2} \rightarrow (5)$$



At node V_{x2} :

$$-\frac{V_{o2}}{r_o} - g_{mp} V_{x2} = \frac{V_{o2} - V_{p2}}{r_o} + g_{mn} (V_{in2} - V_{p2})$$

using (4) $\Rightarrow V_{o2} = -\frac{g_{mn} r_o}{2} V_{in2} \rightarrow (6)$

From (3) & (6)

$$V_{o1} = +\frac{g_{mn} r_o}{2} V_{in1}$$

$$V_{o2} = -\frac{g_{mn} r_o}{2} V_{in2}$$

$$\Rightarrow V_{out} = \frac{g_{mn} r_o}{2} (V_{in1} - V_{in2})$$

Superposition of V_{o1} & V_{o2} .

$$\Rightarrow A_d = \frac{V_{out}}{V_{in1} - V_{in2}} = \frac{g_{mn} r_o}{2}$$

$$g_{mn} = \mu_n C_{ox} \frac{W}{L} \underbrace{(V_{gs} - V_t)}_{V_{ov}} = 1000 \times 400e-9 \times (12.5) \times 0.2 = 1e-3 \text{ A/V}$$


$$r_o = 100e3$$

$$A_d = \frac{g_m r_o}{2} = 50$$

Marking: this derivation is the key point that is being tested.

MARKING: Looking for (i) $C_{gd}(1-A)$
(ii) $A = -g_m R_{out}$
(iii) Miller Effect

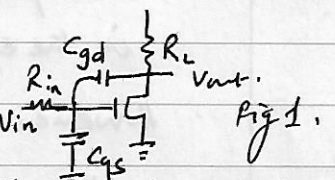
2) (a) The problem with a large overlap capacitance is that it provides a feedback pathway between the output and input. This results in the signal source seeing an effective capacitance that is larger than anticipated. The equivalent circuit becomes that shown in Fig 2.



Seeing an effective capacitance that is larger than anticipated. The equivalent circuit becomes that shown in Fig 2.

This is called the "Miller Effect".

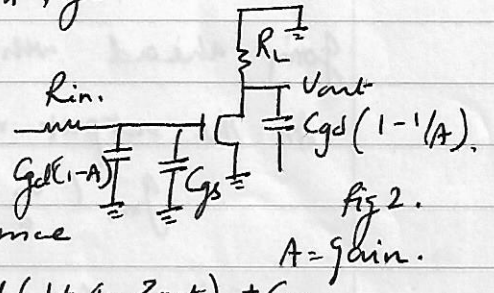
For a common source amplifier the gain is $-g_m Z_{out}$, with Z_{out} the output impedance. The effective capacitance



capacitance becomes $C_{gd}(1-A) + C_{gs} = C_{gd}(1 + g_m Z_{out}) + C_{gs}$.

In the example of Fig 1, $Z_{out} \approx R_L || r_o$. This larger effective input capacitance makes the input pole $R_{in} / (C_{gd}(1 + g_m Z_{out}) + C_{gs})$ more

(b) (1)

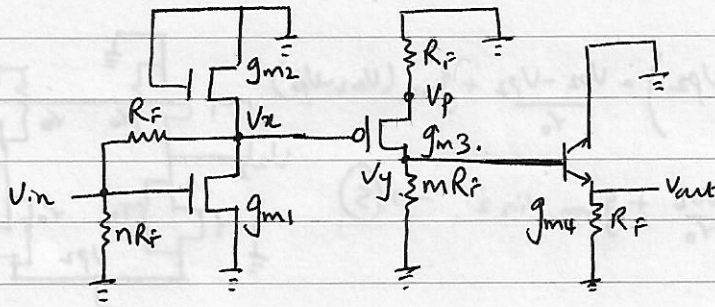

Marking:

The derivation is being marked.
Small careless errors: -1 point or sometimes forgiven.

Serious conceptual errors: -2 to -3 points.

At node V_x :

$$-g_{m2} V_x = \frac{V_x - V_{in}}{R_f} + g_{m1} V_{in} \Rightarrow -\left(g_{m2} + \frac{1}{R_f}\right) V_x = V_{in} \left(g_{m1} - \frac{1}{R_f}\right)$$

$$\Rightarrow V_x = -V_{in} \left(\frac{g_{m1} R_f - 1}{g_{m2} R_f + 1} \right)$$

At node V_p :

$$-\frac{V_p}{R_f} = -g_{m3} (V_x - V_p) \Rightarrow -V_p \left(\frac{g_{m3} R_f + 1}{R_f} \right) = -g_{m3} V_x$$

$$\Rightarrow V_p = \frac{g_{m3} R_f}{1 + g_{m3} R_f} V_x$$

At node V_y :

$$\frac{V_y}{mR_f} = -\frac{V_p}{R_f} = -\frac{g_{m3}}{1 + g_{m3} R_f} V_x \Rightarrow V_y = -\frac{g_{m3} m R_f}{1 + g_{m3} R_f} V_x$$

Note:- Here there is an assumption that the input impedance of the BJT is exceedingly high & is ignored. (This was stated as an assumption the students could use in the context of the time constraints in the exam).

However more accurately:

$$-\frac{V_p}{R_f} = \frac{V_y}{mR_f} + V_y \frac{-V_{out}}{R_f}$$


Going ahead with the assumption that $V_y \frac{-V_{out}}{R_f} \ll \frac{V_y}{mR_f}$, $V_y = -\frac{g_{m3} m R_f}{1 + g_{m3} R_f} V_x$

At the output node:

$$g_{m4} (V_y - V_{out}) = \frac{V_{out}}{R_f} \Rightarrow V_{out} \left(\frac{g_{m4} R_f + 1}{R_f} \right) = g_{m4} V_y$$

$$\therefore \frac{V_{out}}{V_{in}} = \left(\frac{g_{m4} R_f}{1 + g_{m4} R_f} \right) \left(\frac{g_{m3} m R_f}{1 + g_{m3} R_f} \right) \left(\frac{-1 + g_{m1} R_f}{1 + g_{m2} R_f} \right) = \text{Small signal gain.}$$

(ii)

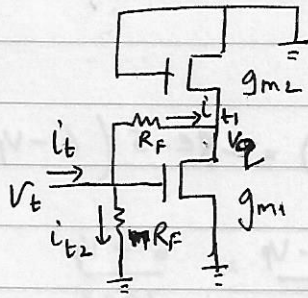

To measure the input impedance, we apply a test voltage V_t .

$$Z_{in} = \frac{V_t}{i_t}$$

$$i_t = i_{t1} + i_{t2}$$

$$i_{t1} = \frac{V_t - V_g}{R_F}, \quad i_{t2} = \frac{V_t}{nR_F}$$

$$g_{m1} V_t = -g_{m2} V_g - \frac{V_g - V_t}{R_F}$$

$$\Rightarrow -V_t (g_{m1} R_F - 1) = V_g (g_{m2} R_F + 1)$$


$$i_{t1} = \frac{V_t - V_g}{R_F} = \frac{V_t}{R_F} \left[1 + \frac{g_{m1} R_F - 1}{g_{m2} R_F + 1} \right] = \frac{V_t}{R_F} \left[\frac{g_{m2} R_F + g_{m1} R_F}{1 + g_{m2} R_F} \right]$$

$$i_{t2} = \frac{V_t}{nR_F}$$

$$i_t = \frac{V_t}{R_F} \left[\frac{1}{n} + \frac{g_{m2} R_F + g_{m1} R_F}{1 + g_{m2} R_F} \right]$$

$$\frac{V_t}{i_t} = \frac{R_F}{\left[\frac{1}{n} + \frac{g_{m2} R_F + g_{m1} R_F}{1 + g_{m2} R_F} \right]} = Z_{in}$$

3.) (a)

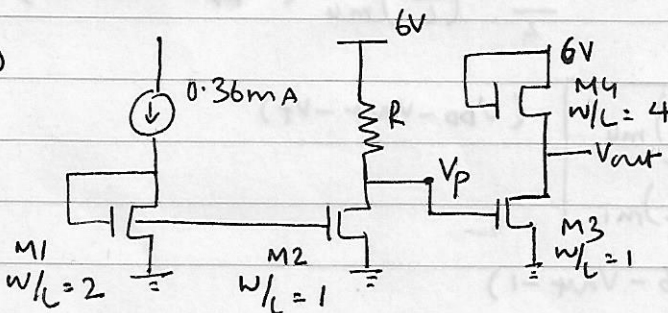

(i) for $m_1 - m_2$ to be a good current mirror, current in $m_2 = 0.18 \text{ mA}$.
& M_2 must be in saturation.

$$\text{Gate voltage of } m_2 = \text{Gate voltage of } m_1 = \sqrt{\frac{2 \times (0.36 \times 10^{-3})}{\mu C_{ox} (W/L)_{m_1}}} + V_T$$

$$\mu = 1000 \text{ cm}^2/\text{Vs}, \quad C_{ox} = 40 \text{ fF}/\text{cm}^2, \quad (W/L)_{m_1} = 2, \quad V_T = 1$$

$$\therefore \text{Gate voltage of } m_2 = 4 \text{ V}$$

for m_2 to be in saturation $V_p \geq 4 - V_T = 3 \text{ V}$

$$\& \frac{6 - V_p}{R} = 0.18 \text{ mA} \Rightarrow R \leq 16.67 \text{ k}\Omega$$

(ii) $R = 20k\Omega \Rightarrow m_2$ is not in saturation.

\therefore Current through $m_2 =$

$$\mu_{\text{COX}} \left(\frac{W}{L}\right)_{m_2} \left((V_{GS, m_2} - V_T) V_p - \frac{V_p^2}{2} \right) = 2.8e-5 (6 - V_p) V_p.$$

$$\text{Current through the resistor } R = \frac{V_{DD} - V_p}{R} = \frac{6 - V_p}{20e3}.$$

The two currents are equal

$$\therefore (2.8e-5) (6 - V_p) V_p = \frac{(6 - V_p)}{20e3}$$

$$\Rightarrow V_p = \frac{100}{20 \times 2} = 2.5V.$$

Cross-check $V_p = 2.5V$ is indeed $\leq (V_{GS, m_2} - V_T)$

(iii) When $R = 10k\Omega$, m_2 is in saturation.

\therefore Current through $m_2 = 0.18mA$

$$V_p = 6 - (0.18e-3)(10k\Omega) = 4.2V$$

Considering the output stage, both m_3 & m_4 are in saturation.

NOTE: m_4 clearly is, but we assume $V_{out} > V_p - V_T$ & m_3 is in saturation.

We will verify this assumption later.


Since current through $m_3 =$ current through m_4 .

$$\frac{\mu_{\text{COX}}}{2} \left(\frac{W}{L}\right)_{m_3} (V_p - V_T)^2 = \frac{\mu_{\text{COX}}}{2} \left(\frac{W}{L}\right)_{m_4} (V_{DD} - V_{out} - V_T)^2$$

$$\Rightarrow V_p - V_T = \sqrt{\frac{\left(\frac{W}{L}\right)_{m_4}}{\left(\frac{W}{L}\right)_{m_3}}} (V_{DD} - V_{out} - V_T)$$


$$\Rightarrow 4.2 - 1 = 2 (6 - V_{out} - 1)$$
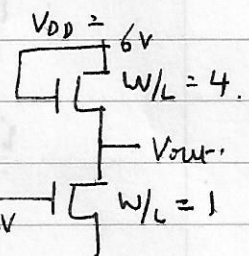
$$\Rightarrow 3.2 = 10 - 2V_{out} \Rightarrow V_{out} = 3.4V.$$




(a) The corner frequency is the fre.

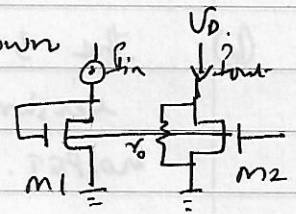3)(b) Consider the conventional 2 MOSFET current mirror shown. When both MOSFETs are in saturation, the current in M_2 in the absence of channel length modulation would be I_{in} .



However, channel length modulation corrupts this current & the real current is $I_{in} + V_D/r_o = I_{out}$. A fluctuation in V_D creates transients. A cascode current mirror mitigates this problem.

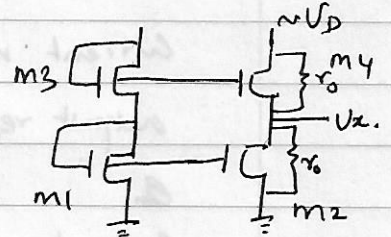The current now is corrupted by V_x/r_o . If there is a small signal fluctuation in V_D , what is V_x/r_o ?



$$-g_{m4} V_x + \frac{(V_D - V_x)}{r_o} = \frac{V_x}{r_o}$$

$$\Rightarrow V_x \left(\frac{2}{r_o} + g_{m4} \right) = \frac{V_D}{r_o} \Rightarrow V_x = \frac{V_D}{2 + g_{m4} r_o}$$

$g_{m4} r_o \gg 1 \Rightarrow V_x$ varies very little and $\frac{V_x}{r_o} \rightarrow 0$.

$\therefore M_4$ protects the output current from variation in V_D . M_3 is used to bias M_4 in saturation.

MARKING: I am looking for (i) the argument on why V_x is practically insensitive to V_D due to the presence of M_4 . (ii) The role of M_3


4)(a) The corner frequency is the frequency at which the thermal noise voltage equals the flicker noise voltage.

The flicker noise is dominant at low frequencies and $\propto \frac{\alpha}{\omega W L f}$. The thermal noise is constant at all frequencies and

at $f = f_c$.

$$4kT \left(\frac{2}{3} \right) \frac{1}{g_m} = \frac{\alpha}{\omega W L f_c}$$
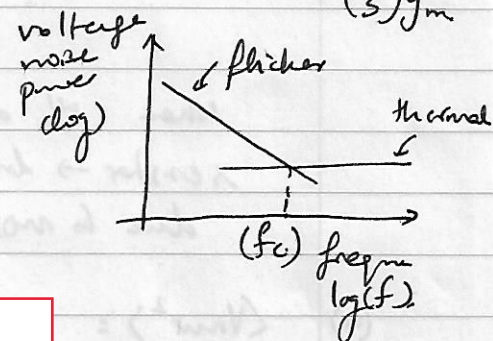
$$\Rightarrow f_c = \frac{3g_m \alpha}{8kT \omega W L}$$



While marking: I am looking for the definition, the figure and the equation.


While marking: I am seeing if the students considered all 3 noise sources: thermal in RL, thermal in MOSFET, flicker in MOSFET. And then if the students scaled each one separately with the scaling of gm

8/8

(b) The 3 noise components are (i) thermal noise in the resistor (ii) thermal noise in the MOSFET (iii) Flicker noise in the MOSFET.


We consider them one at a time and apply superposition.

Gain = $-g_m R_L = A$
 $Z_{out} = R_L$

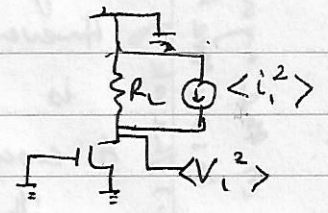


Current noise due to $R_L = \langle i_1^2 \rangle = \frac{4kT}{R_L}$
 output referred noise ^{voltage} due to $R_L = \langle V_1^2 \rangle = \langle i_1^2 \rangle Z_{out}^2 = 4kT R_L$

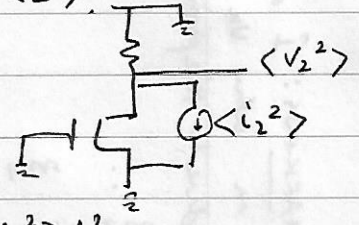Current noise due to MOSFET = $\langle i_2^2 \rangle = 4kT \left(\frac{2}{3}\right) g_m$
 output ref. voltage noise due to MOSFET = $\langle V_2^2 \rangle = \langle i_2^2 \rangle Z_{out}^2 = 4kT \left(\frac{2}{3}\right) g_m R_L^2$



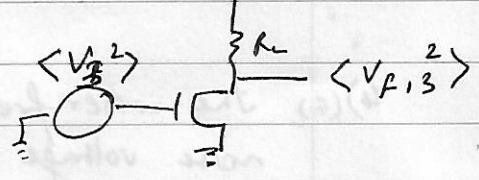Flicker noise due to MOSFET = $\langle V_3^2 \rangle$
 output noise voltage due to flicker = $\langle V_{F,3}^2 \rangle = \langle V_3^2 \rangle A^2 = \frac{\alpha}{C_{ox} W L f} \cdot g_m^2 R_L^2$



Total output referred voltage noise
 $\langle V_{out}^2 \rangle = 4kT R_L + 4kT \left(\frac{2}{3}\right) g_m R_L^2 + \frac{\alpha}{C_{ox} W L f} g_m^2 R_L^2$

Total input ref voltage noise
 $\langle V_{in}^2 \rangle = \frac{\langle V_{out}^2 \rangle}{A^2} = \frac{4kT R_L}{g_m^2 R_L^2} + \frac{4kT \left(\frac{2}{3}\right)}{g_m} + \frac{\alpha}{C_{ox} W L f}$

When w/L doubles, g_m doubles and thermal noise due to resistor \rightarrow drops $1/4$, noise due to MOSFET drops $1/2$, flicker noise due to MOSFET is invariant.

(c) $\langle V_{out}^2 \rangle = \langle V_{in}^2 \rangle |H(f)|^2$
 Across inf bandwidth, $\langle V_{out}^2 \rangle_{f \rightarrow \infty} = \int_0^{\infty} \langle V_{in}^2 \rangle |H(f)|^2 df$
 $\langle V_{out}^2 \rangle_f = \int_0^{\infty} 4kT R \cdot \frac{1}{1 + 4\pi^2 R^2 C^2 f^2} df$
 $= \frac{4kT R}{2\pi R C} \tan^{-1}(2\pi R C f) \Big|_0^{\infty} = \frac{2kT}{\pi C} \cdot \frac{\pi}{2} = \frac{kT}{C}$
 $|H(f)|^2 = \frac{1}{1 + 4\pi^2 R^2 C^2 f^2}$

\therefore When capacitance doubles, the noise reduces by $1/2$.