

EGT1
ENGINEERING TRIPOS PART IB

Wednesday 5 June 2019 2 to 4.10

Paper 5

ELECTRICAL ENGINEERING

*Answer not more than **four** questions.*

*Answer not more than **two** questions from any one section and not more than **one** question from each of the other two sections.*

All questions carry the same number of marks.

*The **approximate** percentage of marks allocated to each part of a question is indicated in the right margin.*

Answers to questions in each section should be tied together and handed in separately.

*Write your candidate number **not** your name on the cover sheet.*

STATIONERY REQUIREMENTS

Single-sided script paper

SPECIAL REQUIREMENTS TO BE SUPPLIED FOR THIS EXAM

CUED approved calculator allowed

Engineering Data Book

10 minutes reading time is allowed for this paper at the start of the exam.

You may not start to read the questions printed on the subsequent pages of this question paper until instructed to do so.

SECTION A

Answer not more than **two** questions from this section

1 (a) Define Thevenin and Norton's theorem and explain how they can be used to simplify the analysis of circuits. [3]

(b) The circuit shown in Fig. 1 is a single stage amplifier based on a single bipolar junction transistor. The amplifier is biased using the component values $R_1 = 47k\Omega$, $R_2 = 10k\Omega$, $R_3 = 5k\Omega$, $R_4 = 1k\Omega$ and $V_{cc} = 10\text{ V}$.

(i) Explain the role of each of the components in the circuit when setting up a suitable operating point. [3]

(ii) Using circuit analysis, calculate the percentage variation in V_{CE} when the DC current gain, h_{FE} varies from 50 to 300. [7]

(c) Sketch the small signal model for the amplifier in Fig. 1 when working at mid-band frequencies. [4]

(d) Derive an expression for the mid-band gain (v_{out}/v_{in}) of the amplifier, using the small signal parameters h_{ie} , h_{fe} and neglecting the effects of h_{re} and h_{oe} . [4]

(e) Discuss the effects of R_4 in the analysis of this circuit. How might the limitations it introduces be avoided? [4]

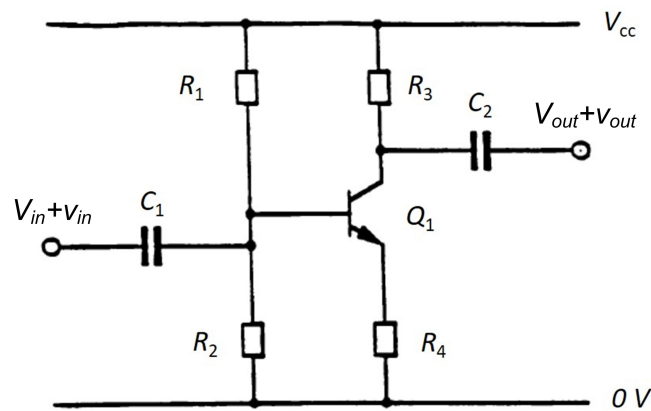


Fig. 1

2 (a) If an amplifier with a gain of A is subject to feedback from its output to its input via a network B , explain what conditions would result in an oscillatory output. [5]

(b) The circuit shown in Fig. 2 is an oscillator based around an ideal amplifier.

(i) Derive an expression for the oscillation frequency of the circuit. [8]

(ii) Explain how R_1 and R_2 can be used to control the output level of the oscillator. [5]

(c) The circuit in Fig. 2 is used to drive a low impedance ultrasonic transducer, via a power amplifier such that in Fig. 3. What class is this power amplifier and what are its limitations in amplifying a sinusoidal signal? [7]

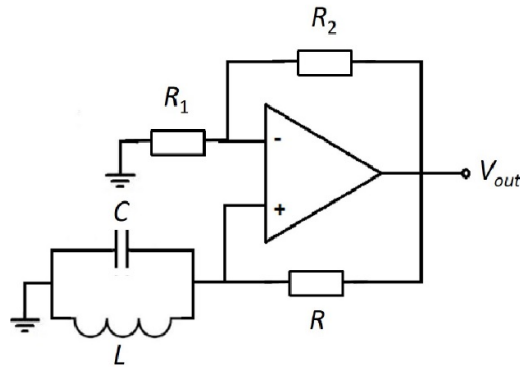


Fig. 2

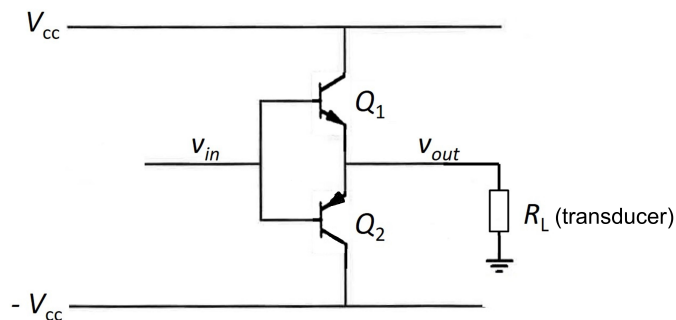


Fig. 3

SECTION B

Answer not more than two questions from this section

3 A three-phase 415 V, 50 Hz supply is connected to a balanced star-connected load and a balanced delta-connected load. The impedance of each leg of the delta-connected load is $300 + j150 \Omega$ and each phase of the star-connected load consists of a 400Ω resistor in parallel with a $10 \mu\text{F}$ capacitor.

- (a) Draw the most simplified structure of the equivalent one-phase circuit. [4]

- (b) Calculate
 - (i) the line current; [4]
 - (ii) the input power; [4]
 - (iii) the input VARs. [4]

- (c) We wish to alter the power factor of the system to 0.95 lagging.
 - (i) Explain whether delta-connected capacitors or inductors must be used. [2]
 - (ii) Derive the required value of the capacitors/inductors. [5]
 - (iii) Explain whether each of the following parameters change after correcting the power factor: [2]
 - A. The total dissipated power;
 - B. The supply current.

- 4 (a) Explain why three-phase power generation is superior to any other number of phases. [4]
- (b) A synchronous generator is connected to an infinite bus.
- (i) What is an infinite bus? Give an example where an infinite bus assumption may not hold. [3]
- (ii) What conditions must be satisfied for a synchronous AC generator to produce steady torque? Explain why these conditions must be met. [4]
- (c) A synchronous star-connected generator with 4 poles and a synchronous reactance of $X_s = 0.2 \Omega$, is connected to a 50 Hz infinite bus with a line voltage of 11 kV.
- (i) Find the speed of rotation and the torque of the prime mover if the prime mover power is set to 400 MW. [2]
- (ii) If the prime mover power is kept at 400 MW and the power factor at the terminals of the machine is 0.9 lagging, find the excitation voltage. [6]
- (iii) If the prime mover power reduces to 250 MW, while the excitation voltage that you obtained in (ii) remains unchanged, calculate the new power factor. [6]

- 5 (a) Explain why the induction motor is sometimes known as an asynchronous motor. [3]
- (b) Consider an induction motor.
- (i) Draw its equivalent circuit model. [2]
 - (ii) What is the locked rotor test? How is the equivalent circuit approximated for this test? [3]
 - (iii) What is the no-load test? How is the equivalent circuit approximated for this test? [3]
- (c) A four-pole star-connected, three-phase induction motor is operated at 1350 rpm, when driven by a line voltage of 600 V at 50 Hz. The equivalent circuit of this induction motor has the following circuit parameters: $R_1 = R'_2 = 2 \Omega$, $R_0 = 2500 \Omega$, $X_m = 500 \Omega$, $X_1 = X'_2 = 6 \Omega$.
- (i) Calculate the value of slip. [3]
 - (ii) Stating any approximations, calculate the peak torque. [5]
 - (iii) Find the speed at which the maximum torque occurs. [3]
 - (iv) How can we maximize the starting torque of this motor? Calculate the required changes in the circuit elements of the equivalent circuit model. [3]

SECTION C

Answer not more than *two* questions from this section

6 The terminals of an AC voltage source are connected to two parallel microstrip conductors in a printed circuit board (PCB), which have specific inductance L and specific capacitance C . The voltage source amplitude is V and $x = 0$ is at the nodes of the two wires connecting to the source.

(a) Show that the telegraphers equations for the voltage V and current I in the parallel wires may be expressed as functions of distance x along the wires at any given instant of time t . Hence comment on the form of the time-varying V and I on the microstrips. [3]

(b) Derive the general solutions for the voltage and current in the two parallel wires as functions of x and t . [4]

(c) Using the solutions to (a) and (b) above obtain an expression for the impedance presented by the two parallel wires to the voltage source. [3]

(d) Two parallel microstrips on the PCB have values of $L = 4.0 \times 10^{-7} \text{ H m}^{-1}$ and $C = 2.5 \times 10^{-10} \text{ F m}^{-1}$ and are used to connect a voltage source of 10 MHz to a load on the board. Estimate the maximum length l of the parallel metal tracks which allows the following assumption to be made: the voltage at the source may be considered to be equal to that at the load connected, as the voltage difference between the source voltage and the voltage $V(x, t)$ at the load is no more than 1%. [5]

(e) A two parallel wire transmission line of length 5 m having the same L and C values as for the two parallel microstrips on the PCB in (d) is used to connect a load $Z_L = 50 + j10 \Omega$ to an ideal (i.e. internal impedance of 0Ω) voltage source $\hat{V}_s = 5 + j0 \text{ V}$ operating at a frequency of 10 MHz.

(i) What is the reflection coefficient at the load? [2]

(ii) Derive an expression for the steady state voltage as a function of distance x over the transmission line (Hint: Consider the conditions imposed by the ideal voltage source on the sum of the forward and reflected waves at $x = 0$). [5]

(iii) Hence, calculate the steady state voltage at the load. [3]

7 (a) Using Maxwell's equations, show that the time varying electric field \underline{E} and the associated magnetic field \underline{H} in free space give rise to electromagnetic wave propagation. [3]

(b) Based on the results from (a), how can one conclude that visible light in free space is a form of electromagnetic wave? [3]

(c) Considering \underline{E} and \underline{H} fields to be plane waves in the $x - y$ plane

(i) calculate the characteristic impedance of free space. [4]

(ii) In which direction is the electromagnetic power transmitted? Justify your answer. [3]

(d) A $\frac{3}{4}\lambda$ dipole antenna is used to transmit a radio signal with a carrier frequency of 100 MHz. In polar coordinates, the antenna is oriented vertically at $\theta = 0$, perpendicular to the r, ϕ plane with coordinates $(\frac{3}{4}\lambda \underline{e}_r, 0\underline{e}_\theta, 0\underline{e}_\phi)$. In the far field, which is a distance many wavelengths away from the antenna, the electric field \underline{E} at a distance r is given as

$$\underline{E} = [E_0 \sin\theta \sin(\omega t - 2\pi r/\lambda)] \underline{e}_\theta / r \quad (1)$$

where E_0 is the rms magnitude of the electric field at the transmitting antenna and λ is the wavelength.

(i) What is the corresponding magnetic field (make clear its orientation)? [3]

(ii) Derive an expression for the power density in the electromagnetic field at a distance r from the antenna and comment on the direction of the power transmission. [4]

(iii) A receiving antenna on a radio is located a distance 100λ away in parallel with and on the same plane as the transmitting antenna at coordinates $(100\lambda \underline{e}_r, \pi/2 \underline{e}_\theta, \phi \underline{e}_\phi)$. The receiving antenna has a signal capture area extending over $\delta\theta = 0.1$ rad and $\delta\phi = 0.1$ rad. What is the average power of the signal received by the radio antenna when the strength of the transmitting electric field $E_0 = 40 \text{ V m}^{-1}$. [5]

END OF PAPER