

EGT2  
ENGINEERING TRIPOS PART IIA

---

Monday 29 April 2019      2 to 3.40

---

**Module 3B1**

**RADIO FREQUENCY ELECTRONICS**

*Answer not more than **three** questions.*

*All questions carry the same number of marks.*

*The **approximate** percentage of marks allocated to each part of a question is indicated in the right margin.*

*Write your candidate number **not** your name on the cover sheet.*

**STATIONERY REQUIREMENTS**

Single-sided script paper

**SPECIAL REQUIREMENTS TO BE SUPPLIED FOR THIS EXAM**

CUED approved calculator allowed

Supplementary page: one copy of Smith Chart (Question 3)

Engineering Data Book

**10 minutes reading time is allowed for this paper at the start of the exam.**

**You may not start to read the questions printed on the subsequent pages of this question paper until instructed to do so.**

1 A Mars lander utilises a Radio Frequency (RF) telemetry link to Earth operating at 11 GHz. The Earth base station uses a 35 m diameter dish to transmit and receive signals to/from the Mars lander, which is equipped with a quarter-wave antenna. The distance between Mars and the Earth was  $145 \times 10^6$  km when the lander touched down.

(a) Explain the terms *Radiation Resistance*, *Gain*, *Radiation Efficiency* and *Effective Aperture* as applied to antennas. [20%]

(b) If the lander transmits a radio signal with a radiated power of 75 W, what is the power density of this signal received on Earth? [10%]

(c) (i) Given that the *Effective Aperture* of a dish antenna is approximately equal to the area of a circle with the same diameter as the dish, calculate the voltage amplitude of the received signal when the dish antenna drives a matched load of  $150 \Omega$ . [20%]

(ii) Calculate the gain of the dish antenna and estimate its beam angle. [20%]

(d) Estimate the radiation efficiency of the lander antenna if it is fabricated from non-magnetic stainless steel wire with a diameter of 0.5 mm, taking the electrical resistivity of stainless steel to be  $6.9 \times 10^{-7} \Omega\text{m}$ . [15%]

(e) If the dish is also used to transmit control signals from Earth to Mars with a radiated power of 1 kW, calculate the voltage amplitude of the signal delivered into a  $75 \Omega$  matched load on the lander. [15%]

State all assumptions and approximations made.

- 2 (a) (i) Draw a schematic block diagram for a Phase Locked Loop (PLL) to produce a 1.52 GHz local oscillator signal in a GPS receiver, referenced to a 40 MHz quartz crystal oscillator, and briefly describe the function of each block. [15%]
- (ii) If the phase comparator comprises a 3.3 V logic XOR gate with an output of  $1.05 \text{ V rad}^{-1}$ , the loop filter is a simple RC network and the VCO has an output of  $1 \text{ GHz V}^{-1}$ , derive an expression for the transfer function of the loop and hence determine values for R and C, if the loop transient response is to be critically damped. [50%]
- (b) (i) If the RF system is to be constructed in stripline using a substrate with a total dielectric thickness of 1.2 mm and relative permittivity,  $\epsilon_r = 2.5$ , what width should the tracks be to realise a characteristic impedance of  $50 \Omega$ ? [25%]
- (ii) If the input impedance to an amplifier has been mistakenly specified as  $75 \Omega$ , instead of  $50 \Omega$ , what effect will this have on the RF signal magnitude and integrity? [10%]

State all assumptions and approximations made.

- 3 (a) A radio control system for an industrial process operates at 868 MHz and contains a resonant coil inductor with parallel capacitor as a combined antenna and front-end filter. If the capacitor has a value of 3.3 pF and the coil has a resistance of  $0.6 \Omega$ , calculate the value of the inductor and the bandwidth of the resonant circuit. [20%]
- (b) (i) The input impedance to a low noise amplifier is given by  $S_{11} = 0.73 \angle -67^\circ$  when operating at a frequency of 868 MHz in a  $50 \Omega$  system. Plot this point on the Smith Chart provided at the back of this paper, and determine the equivalent series passive component values which would represent this impedance point. [15%]
- (ii) Design an impedance matching circuit, comprising a pair of passive components, to match this amplifier input impedance to  $50 \Omega$  at the operating frequency. Plot the matching scheme on the Smith Chart and hence briefly describe how the matching is achieved. [25%]
- (c) The radio receiver in an industrial controller operates with a Superheterodyne architecture and is to use an Intermediate Frequency (IF) of 1 MHz, realised with a VCVS band-pass filter circuit predominantly employing  $1 \text{ k}\Omega$  resistors. The filter circuit is to have a bandwidth of 200 kHz with a sharp cut-off each side. Design a suitable IF filter using 4 operational amplifiers, giving the values of all passive components used. Table 1 gives the design parameters for 4-pole VCVS filters. [25%]
- (d) The IF amplifier in a radio system is required to have variable gain, with a response time of around 10 ms, in order to normalise the IF signal amplitude before demodulation. Draw the circuit for a variable gain amplifier with a gain range of  $\times 1$  to  $\times 100$ , for operation with 1 MHz signals, such that the output signal is maintained at an amplitude of approximately 1 V. [15%]

Table 1 4-pole VCVS design table

Bessel		Butterworth		Chebyshev (0.5 dB)	
$f_n$	A	$f_n$	A	$f_n$	A
1.432	1.084	1.000	1.152	0.597	1.582
1.606	1.759	1.000	2.235	1.031	2.660

4 (a) A 2-stage RF amplifier for a radio telemetry system operating at 868 MHz comprises a pair of bipolar transistors configured to give 30 dB of power gain when connected into a  $50 \Omega$  system. The amplifier operates from a 10 V supply and you may assume that the transistors have the following properties:  $h_{fe} = 250$ ,  $f_t = 12$  GHz,  $c_{cb} = 0.15$  pF,  $c_{oe} = 0.10$  pF.

(i) Draw the circuit diagram for such an amplifier and briefly describe the function of each component. [20%]

(ii) Give suitable passive component values to realise the required gain with input and output impedances matched to approximately  $50 \Omega$ . [25%]

(iii) Calculate the  $-3$  dB high frequency cut-off for the amplifier circuit in operation. [25%]


(b) Design a Colpitts oscillator circuit to produce a sinusoidal output signal at 868 MHz using a transistor of the same type as given in part (a). Assume that the circuit operates from a 10 V supply, utilises an inductor of value 10 nH with a Q-factor of 35, and that its output feeds into a high impedance buffer. Draw the circuit diagram and give the values of all other components used. [30%]

State all assumptions and approximations made.

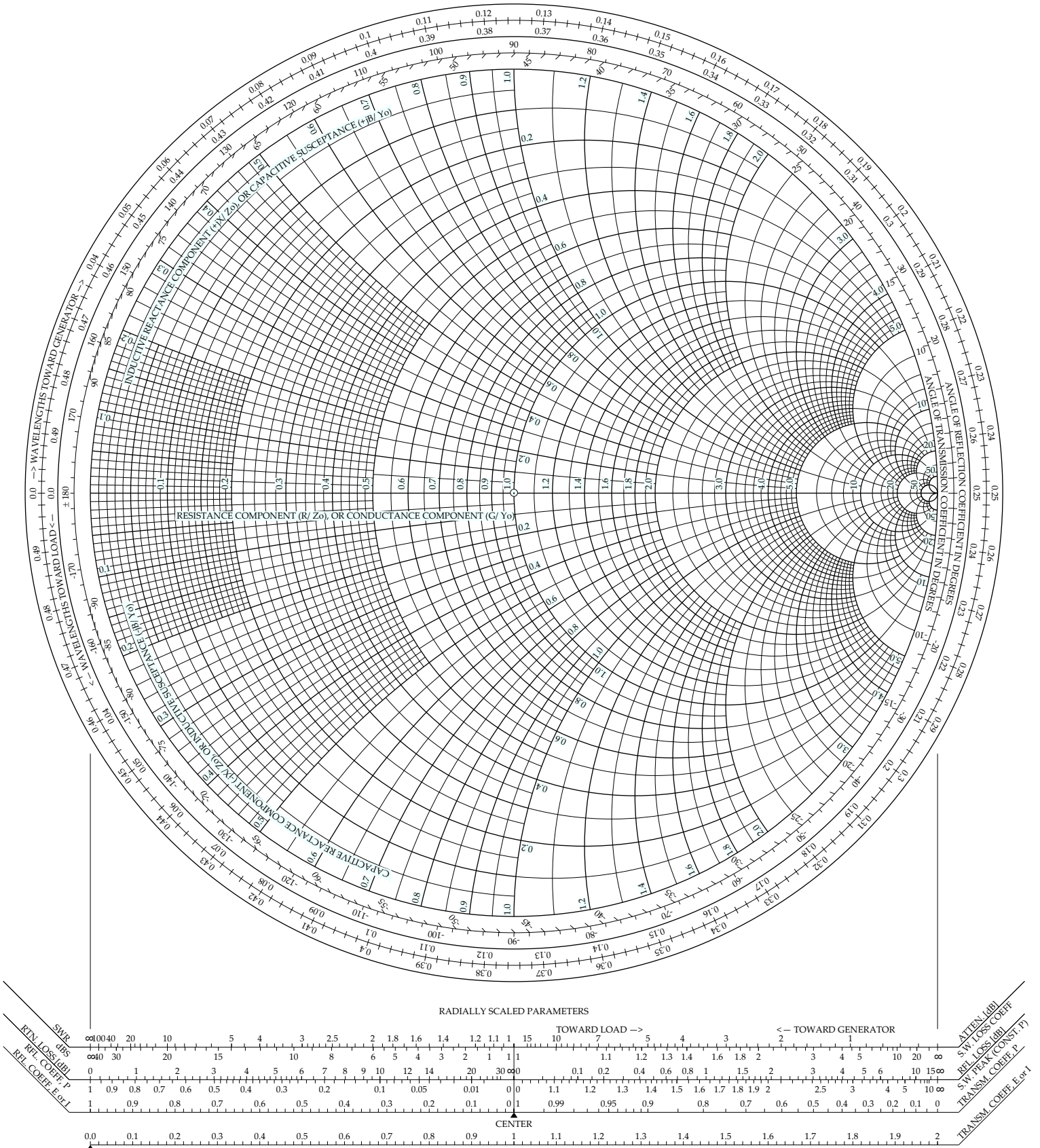**END OF PAPER**

THIS PAGE IS BLANK

Smith Chart to be detached and handed in with script if required



3B1 2019 – Numerical answers

1(b)  $4.26 \times 10^{-23} \text{ W m}^{-2}$

1(c)(i) 22.2 nV pk-pk

1(c)(ii)  $G = 16.2 \times 10^6$ , full beam angle = 0.057°

1(d) 99%

1(e) 20.2 nV rms

2(a)(ii)  $CR = 1.44 \text{ ns}$ ,  $R = 100 \Omega$ ,  $C = 14.4 \text{ pF}$

2(b)(i)  $w = 0.23 \text{ mm}$

3(a)  $L = 10.2 \text{ nH}$ ,  $BW = 9.37 \text{ MHz}$

3(b)(i)  $Z = 25 - j70 \Omega$ ,  $C = 2.62 \text{ pF}$

3(b)(ii) 41.7 nH parallel + 17.4 nH series or 8.8 nH parallel + 2 pF series

3(c) Chebyshev  $C1 = 242 \text{ pF}$ ,  $C2 = 140 \text{ pF}$ ,  $R1 = 582 \Omega$ ,  $R2 = 1.66 \text{ k}\Omega$  (low pass)

$C3 = 106 \text{ pF}$ ,  $C4 = 182 \text{ pF}$ ,  $R3 = 582 \Omega$ ,  $R4 = 1.66 \text{ k}\Omega$  (high pass)

4(a)(ii)  $R1 = 560 \Omega$ ,  $R2 = 68 \Omega$ ,  $R3 = 3.9 \Omega$ ,  $R4 = 50 \Omega$ ,  $C = 10 \text{ nF}$

4(a)(iii)  $f_{-3\text{dB}} = 1.4 \text{ GHz}$

4(b)  $R1 = 2.7 \text{ k}\Omega$ ,  $R2 = 3.3 \text{ k}\Omega$ ,  $R3 = 220 \Omega$ ,  $Rd = 150 \Omega$ ,  $C_{fb} = 1 \text{ nF}$ ,  $C = 6.72 \text{ pF}$