

Engineering Tripos, Part IA, 2023
Paper 3 Electrical and Information Engineering

Solutions

Section A: Prof T. Hasan


Section B: Prof O. Akan

Section C: Dr Q. Cheng

SECTION A


1. (short)

① Short

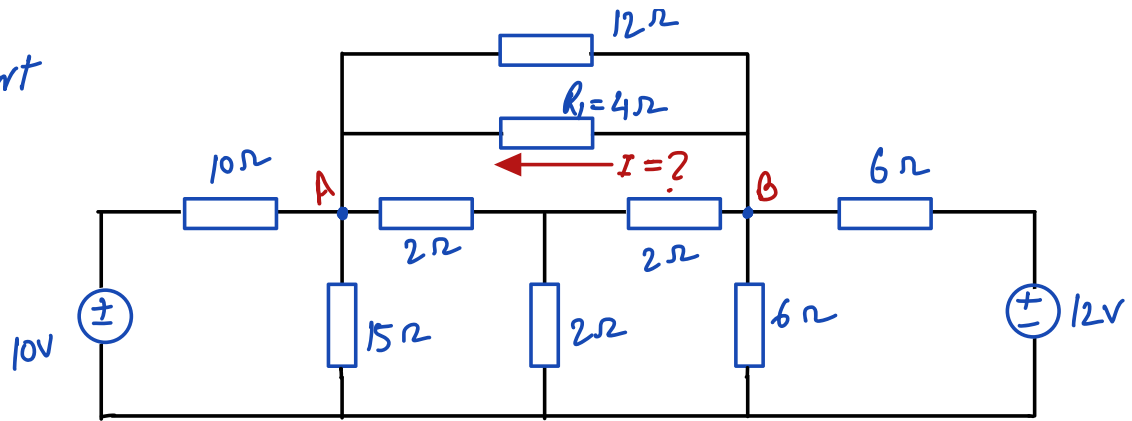


Converting the central 2Ω combination:

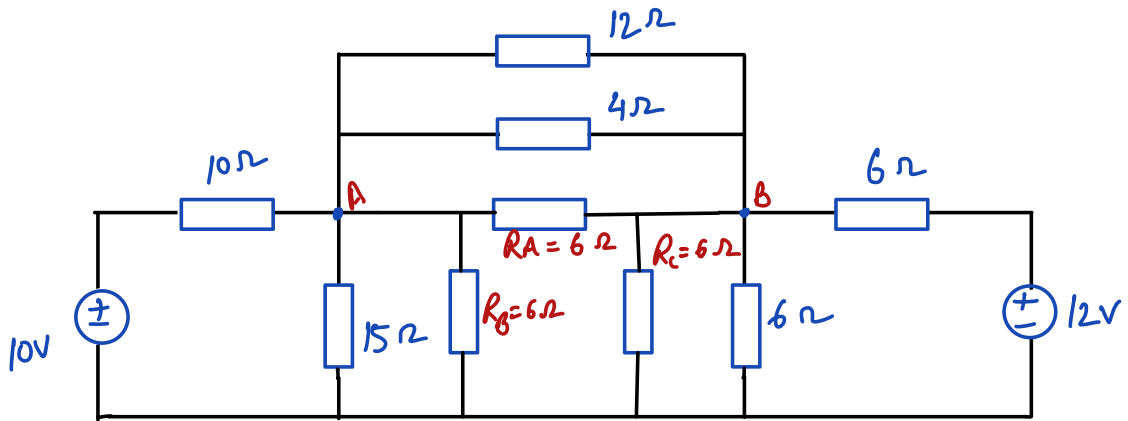
$$R_A = R_B = R_C = \frac{2 \times 2 + 2 \times 2 + 2 \times 2}{2} = 6\Omega$$



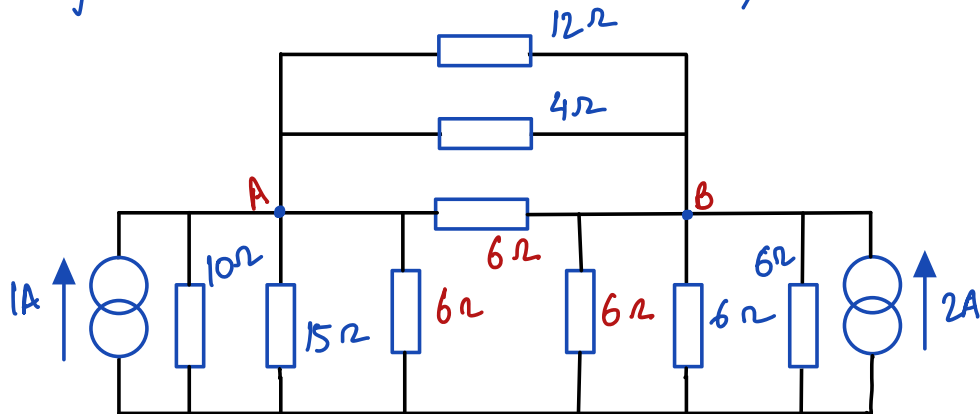Converting the sources to Norton equivalents?




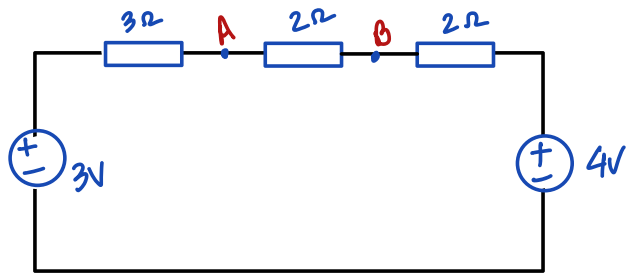Combining the resistors in parallel & current to voltage source equivalents:



$$V_{BA} = \frac{(4-3) \times 2}{3+2+2} = \frac{2}{7} \quad \text{Current in } 4\Omega \text{ is } = \frac{2}{7 \times 4} = \frac{1}{14} \text{ Amp.}$$

② Short

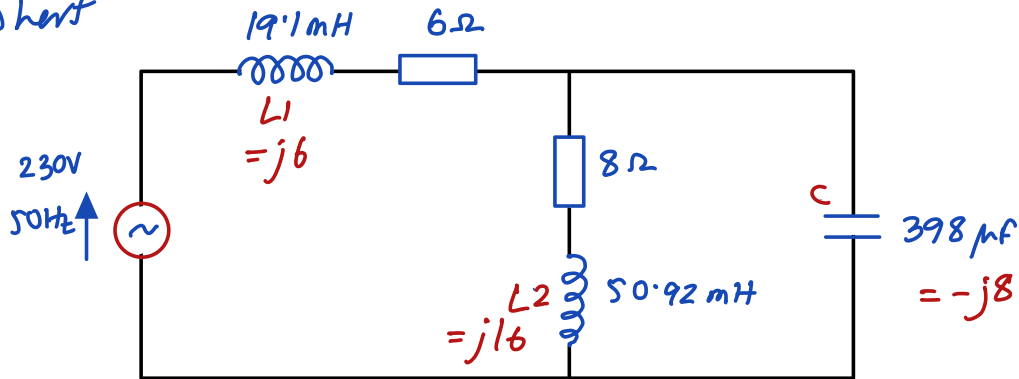

Reactances:

$$\text{For } L_1 \Rightarrow j\omega L_1 = j \times 2\pi \times 50 \times 19.1 \times 10^{-3} = j6 \Omega$$

$$\text{For } L_2 \Rightarrow j\omega L_2 = j \times 2\pi \times 50 \times 50.92 \times 10^{-3} = j16 \Omega$$

$$\text{For } C \Rightarrow \frac{1}{j\omega C} = -j8 \Omega$$

$$\text{Total complex impedance} = 6 + j6 + [(8 + j16) \parallel (-j8)]$$

$$= 6 + j6 + 4 - j12$$

$$= 10 - j6 \Omega$$


$$= 11.66 \angle -30.96^\circ$$

This can be done
in calculator in a
single step

$$\text{Therefore current magnitude is } \frac{230}{11.66} = 19.72 \text{ Amp}$$

$$\text{Phase} = 30.96^\circ$$

③ Short

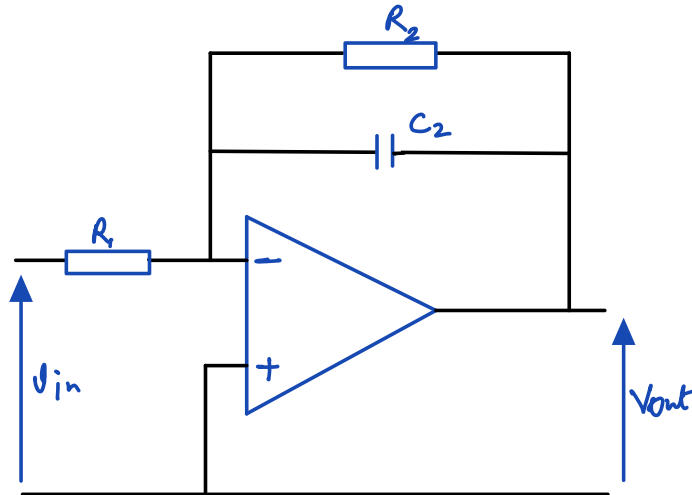

Gain expression:

$$V_{in}/R_1 = -\frac{V_{out}}{(R_2 \parallel C_2)} \quad (\text{equating current at the virtual ground})$$

$$V_{in}/R_1 = -\frac{V_{out}(1 + j\omega C_2 R_2)}{R_2}$$

$$\text{Gain } V_{out}/V_{in} = \frac{-R_2}{R_1(1 + j\omega C_2 R_2)}$$


At low frequencies, the feedback is dominated by R_2 .

$$V_{out}/V_{in} \text{ at low frequencies, } V_{out}/V_{in} = -\frac{R_2}{R_1} = -10.$$


$$-3\text{dB point, } 1 = \omega C_2 R_2 = 2\pi f C_2 R_2$$

$$f = \frac{1}{2\pi C_2 R_2} = \frac{1}{2\pi \times 20 \times 10^{-12} \times 10 \times 10^3} = 0.795 \text{ MHz}$$
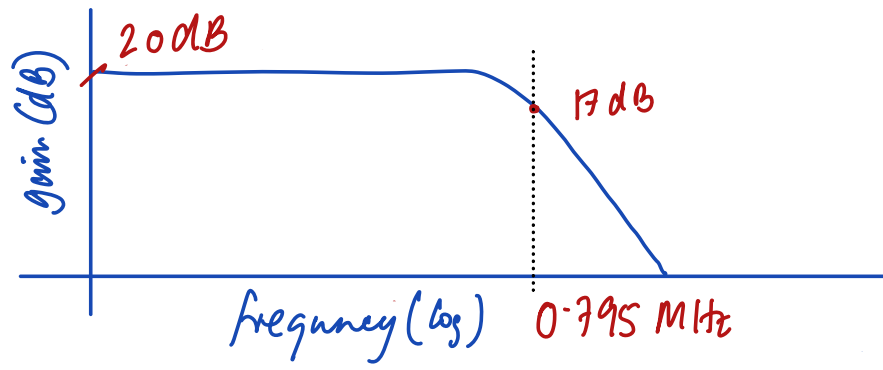
$$\text{Gain at } -3\text{dB} = -\frac{10}{1.41 \angle 45^\circ} = -7.09 \angle -45^\circ$$



④ (long)

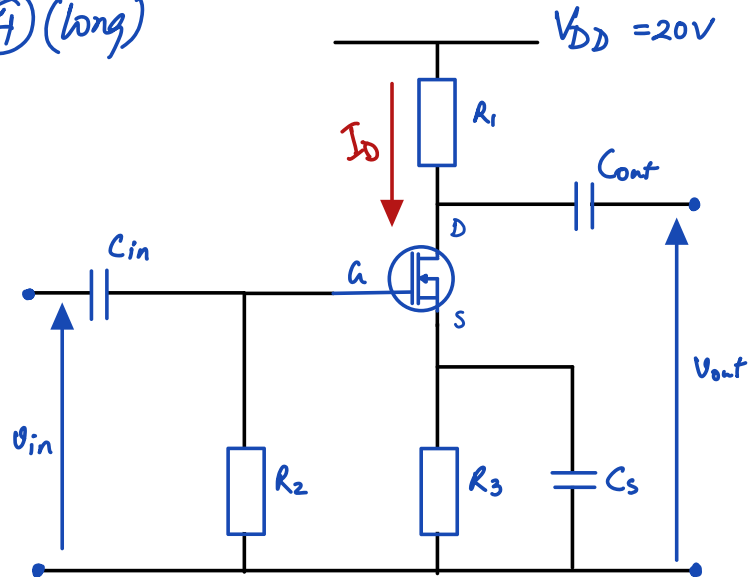

① There is no gate current into the FET. C_{in} is also open to d.c. R_2 therefore puts the gate to 0V. The $I_D R_3$ drop across sets $V_{GS} = -I_D R_3$. This biases the FET. The choice of R_1 , R_3 , I_D dictates the operating point.

② R_1 & R_3 to achieve the operating point:

$$V_{GS} = -3V \quad V_{DS} = 8V \quad I_D = 3mA$$

with $g_m = 6mA/V$ & $r_d = 10k\Omega$, $V_{DD} = 20V$.

$$R_3 \times I_D = -V_{GS} = 3.$$


$$R_3 = \frac{3}{3mA} = 1k$$

$$\text{Also, } V_{DD} = I_D R_1 + V_{DS} + V_S$$

$$20 = 3 \times 10^{-3} \times R_1 + 8 + 3$$

$$R_1 = \frac{9}{3 \times 10^{-3}} = 3k\Omega.$$

© Small signal model

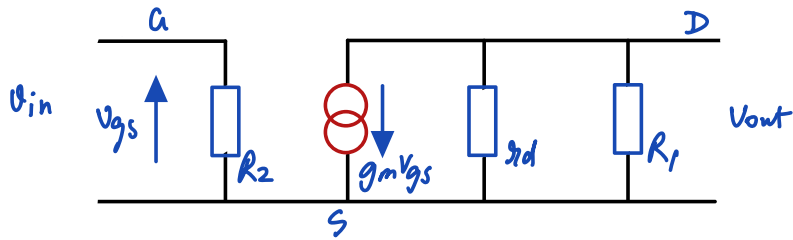


$$V_{gs} = U_{in} \quad V_{out} = -g_m V_{gs} (R_L || R_D)$$

$$gain = \frac{V_{out}}{U_{in}} = -\frac{g_m V_{gs} (R_L || R_D)}{V_{gs}} = -g_m (R_L || R_D)$$


$$o/p \text{ impedance} = (R_L || R_D)$$

$$i/p \text{ impedance} = R_2$$

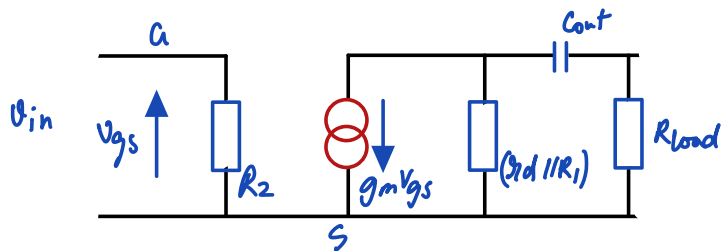① The low -3dB cut off is 20Hz for a 5k Ω resistor.



The o/p section can be redrawn as :

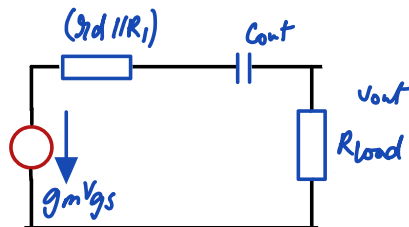

$$V_{out} = \frac{-g_m V_{gs} R_{load}}{R_{load} + (R_L || R_D) + \frac{1}{j\omega C_{out}}}$$

The real & imaginary part in the denominator are same.

$$\text{Therefore, } |G_{out}| = \frac{1}{R_{load} + (R_1 || R_2)}$$

$$C_{out} = \frac{1}{2\pi \times 20 \times [5K + (3K || 10K)]}$$

$$C_{out} = 1.089 \mu F$$

(e) To maximize the signal power, $R_{load} = \text{Output impedance}$.

C_{out} remains unchanged.

$$1.089 \times 10^{-6} = \frac{1}{2\pi \times f_{new} \times 2 \times (3K || 10K)}$$

$$f_{new} = 31.67 \text{ Hz.}$$

⑤ (long)

We know $P = VI \cos \phi$. Given, power of machine $P_m = 200 \text{ kW}$

$$200 \times 10^3 = 1 \times 10^3 \times I \times 0.85$$

$$I = \frac{200}{0.85} = 235.29 \text{ Amp.}$$

$$\begin{aligned} \text{Feeder power loss, } P_f &= I^2 R = (235.29)^2 \times 0.8 \\ &= 44.290 \text{ kW} \end{aligned}$$

$$\begin{aligned} Q_f &= I^2 X_f = (235.29)^2 \times 1.6 \\ &= 88.581 \text{ KVAR} \end{aligned}$$

$$\begin{aligned} \text{Q of machine } Q_m &= P_m \tan \phi \\ &= 200 \tan [\cos^{-1}(0.85)] \text{ KVAR} \\ &= 123.94 \text{ KVAR.} \end{aligned}$$

$$\text{For the source, } P_s = 200 + 44.29 = 244.29 \text{ kW.}$$

$$Q_s = 88.58 + 123.94 = 212.52 \text{ KVAR}$$

$$\begin{aligned} \text{Apparent power } S_s &= \sqrt{P_s^2 + Q_s^2} \\ &= 323.8 \text{ kVA} \end{aligned}$$

$$\text{Source voltage } V_s = \frac{323.8}{235.29} = 1.376 \text{ kV.}$$

⑥ Machine terminal voltage = 1 kV.

For power factor correction, capacitor must generate the same reactive power consumed by the machine, Q_m .

This is 123.94 kVAR.

$$\text{Power } \frac{V^2}{X_L} = 123.94 \times 10^3 = (1000)^2 \times 2\pi \times 50 \times C$$

$$C = \frac{123.94}{2\pi \times 50 \times 1000} = 394.51 \mu\text{F}$$

The new feeder current $VI = 200 \times 10^3$

$$I = \frac{200 \times 10^3}{1000}$$


$$\begin{aligned} \text{New feeder power loss} &= (200)^2 \times 0.8 \\ &= 32 \text{ kW.} \end{aligned}$$

© The source voltage is now set at 1kV.

With the capacitor still connected, the machine will now be a purely resistive load. We know that the packaging machine consumes 200kW with 1kV across it.

$$\text{Hence, } 200 \times 10^3 = \frac{(1000)^2}{R} \Rightarrow R = 5 \Omega$$

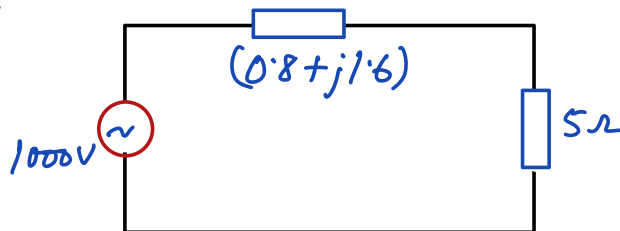We can therefore draw the following equivalent circuit:




The voltage across the machine terminal is:

$$= \frac{1000 \times 5}{|5.8 + j1.6|} = \frac{5000}{6.01} = 831.94 \text{ Volts.}$$

SECTION B

6 (short)

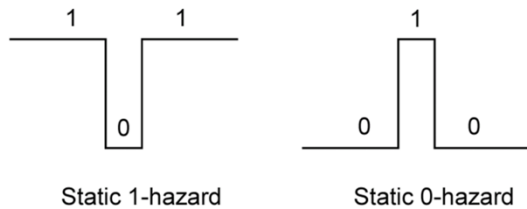(a) The signal exhibits a momentary state change when it is expected to stay intact primarily due to propagation delays in the circuit. Static 0 and 1 hazard occur when the signal is expected to stay at 0 and 1, respectively.



(b)


AB \ CD	00	01	11	10
00	1	1	0	0
01	1	1	1	1
11	0	0	1	1
10	0	0	0	0

This is the Karnaugh Map for function F . Clearly, for $D=1$ and $C=0$, $F = \bar{A} + A$ which corresponds to the static 1 hazard situation. To address this hazard, the terms corresponding to the red rectangle in the K-map above, i.e., $\bar{C}D$, could be added to the function F , i.e., $F = \bar{A}\bar{C} + AD + \bar{C}D$

Similarly, we can obtain the complement of the function to see if there is a static 0 hazard, i.e., $\bar{F} = \bar{A}C + A\bar{D} \rightarrow F = \overline{\bar{A}C + A\bar{D}} = \overline{\bar{A}C} \cdot \overline{A\bar{D}} = A \cdot \bar{A} = 0$ when $C=1, D=0$. Hence, there is a static 0 hazard. To mitigate it, the terms corresponding to the blue rectangle in the K-map, i.e., $C\bar{D}$ could be added to the complement of the function F , i.e., $\bar{F} = \bar{A}\bar{C} + AD + C\bar{D}$.

7 (short)

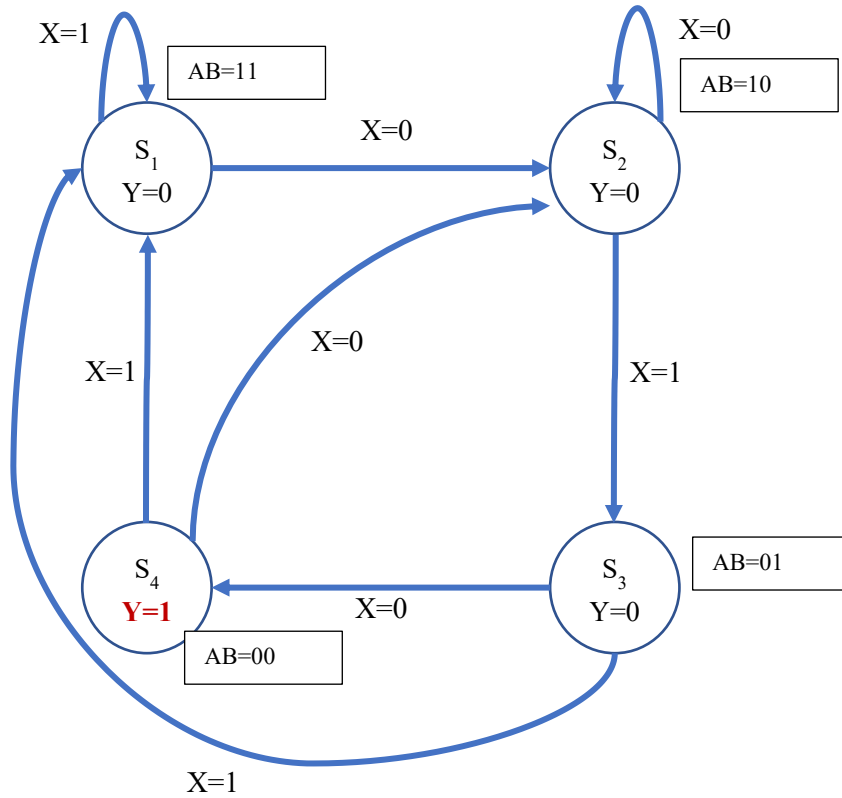(a) 4 states required as in the state diagram below and therefore 2 bistables will be sufficient to implement the circuit.



(b)

X	Current State		Next State		Bistable Inputs			
	A	B	A	B	J _A	K _A	J _B	K _B
0	1	1	1	0	X	0	X	1
1	1	1	1	1	X	0	X	0
0	1	0	1	0	X	0	0	X
1	1	0	0	1	X	1	1	X
0	0	1	0	0	0	X	X	1
1	0	1	1	1	1	X	X	0
0	0	0	1	0	1	X	0	X
1	0	0	1	1	1	X	1	X

8 (short)


(a) $2^{11} \times 8 \text{ bits} = 2048 \text{ bits} = 2 \text{ KBytes}$ is the capacity of the memory chip.

(b)

$D800_H \rightarrow 1101 \mid 1000 \mid 0000 \mid 0000$

$DFFF_H \rightarrow 1101 \mid 1111 \mid 1111 \mid 1111$
5-bits CS 11-bits the address space
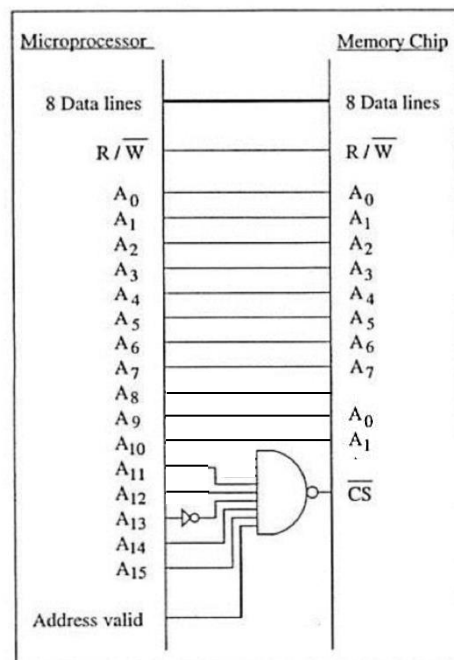
$$\rightarrow \overline{CS} = \overline{A_{15}A_{14}A_{13}A_{12}A_{11}}$$



9 (long)

(a)

Current State				Next State				J ₃	K ₃	J ₂	K ₂	J ₁	K ₁	J ₀	K ₀
Q ₃	Q ₂	Q ₁	Q ₀	Q ₃ ⁺	Q ₂ ⁺	Q ₁ ⁺	Q ₀ ⁺								
1	1	1	1	1	1	1	0	X	0	X	0	X	0	X	1
1	1	1	0	1	1	0	1	X	0	X	0	X	1	1	X
1	1	0	1	1	1	0	0	X	0	X	0	0	X	X	1
1	1	0	0	1	0	1	1	X	0	X	1	1	X	1	X
1	0	1	1	1	0	1	0	X	0	0	X	X	0	X	1
1	0	1	0	1	0	0	1	X	0	0	X	X	1	1	X
1	0	0	1	1	0	0	0	X	0	0	X	0	X	X	1
1	0	0	0	0	1	1	1	X	1	1	X	1	X	1	X
0	1	1	1	0	1	1	0	0	X	X	0	X	0	X	1
0	1	1	0	0	1	0	1	0	X	X	0	X	1	1	X
0	1	0	1	0	1	0	0	0	X	X	0	0	X	X	1
0	1	0	0	0	0	1	1	0	X	X	1	1	X	1	X
0	0	1	1	0	0	1	0	0	X	0	X	X	0	X	1
0	0	1	0	0	0	0	1	0	X	0	X	X	1	1	X
0	0	0	1	0	0	0	0	0	X	0	X	0	X	X	1
0	0	0	0	1	1	1	1	1	X	1	X	1	X	1	X

(b)

J₀

		Q ₁ Q ₀			
		00	01	11	10
Q ₃ Q ₂	00	1	X	X	1
	01	1	X	X	1
	11	1	X	X	1
	10	1	X	X	1

$$J_0 = 1$$

K₀

		Q ₁ Q ₀			
		00	01	11	10
Q ₃ Q ₂	00	X	1	1	X
	01	X	X	1	X
	11	X	1	1	X
	10	X	1	1	X

$$K_0 = 1$$

J_1

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	1	0	X	X
01	1	0	X	X
11	1	0	X	X
10	1	0	X	X

$$J_1 = \overline{Q_0}$$

 K_1

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	X	X	0	1
01	X	X	0	1
11	X	X	0	1
10	X	X	0	1

$$K_1 = \overline{Q_0}$$

 J_2

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	1	0	0	0
01	X	X	X	X
11	X	X	X	X
10	1	0	0	0

$$J_2 = \overline{Q_1} \cdot \overline{Q_0}$$

 K_2

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	X	X	X	X
01	1	0	0	0
11	1	0	0	0
10	X	X	X	X

$$K_2 = \overline{Q_1} \cdot \overline{Q_0}$$

 J_3

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	1	0	0	0
01	0	0	0	0
11	X	X	X	X
10	X	X	X	X


$$J_3 = \overline{Q_2} \cdot \overline{Q_1} \cdot \overline{Q_0}$$

 K_3


$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	0	0	0	0
10	1	0	0	0

$$K_3 = \overline{Q_2} \cdot \overline{Q_1} \cdot \overline{Q_0}$$

(c)

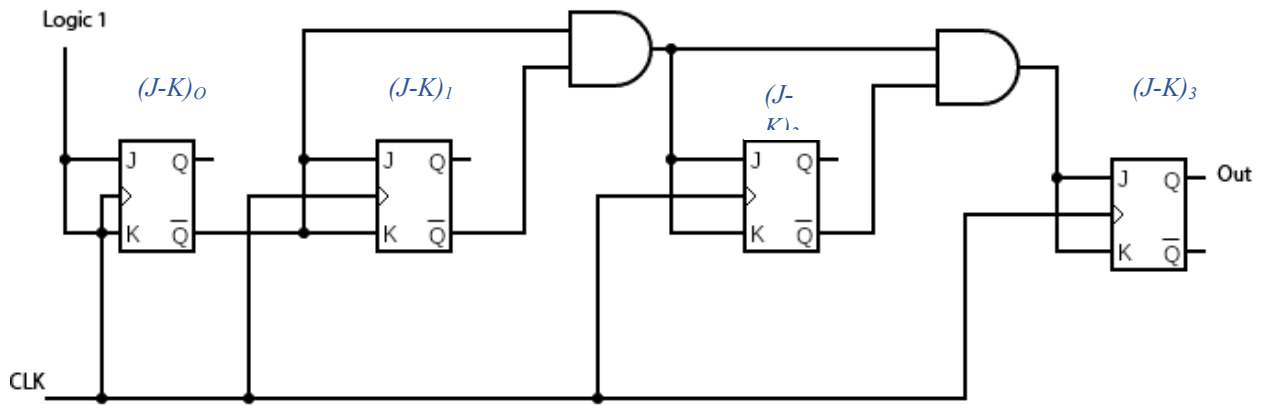


(d)

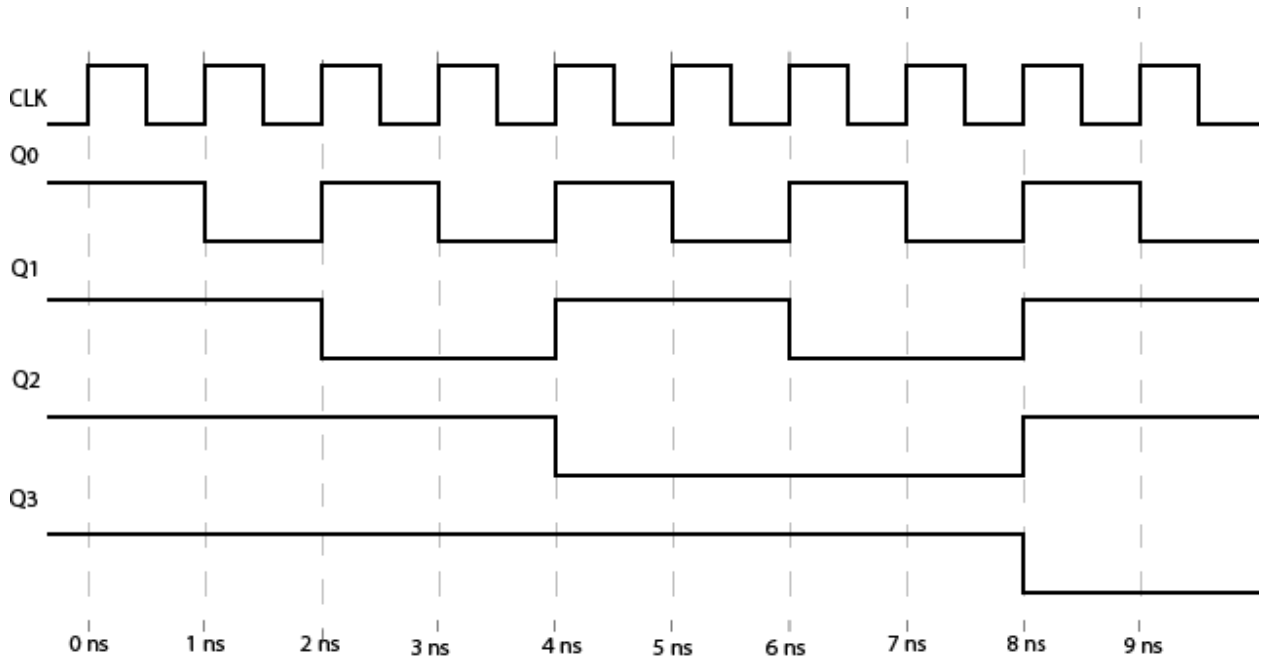

SECTION C

10 (short)

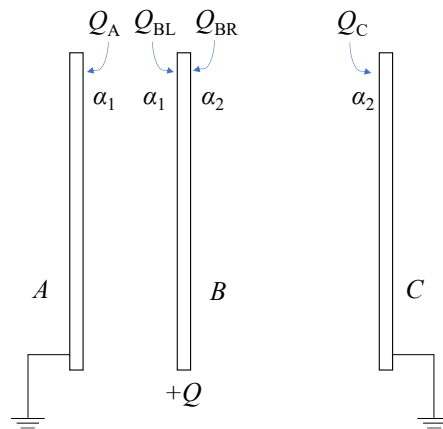

$$Q_{BL} + Q_{BR} = Q$$

$$Q_A = -Q_{BL}; Q_C = -Q_{BR}$$

$$(a) D_A * A = Q_A = \alpha_1 * A$$

$$\epsilon_r * E_{AB} = \alpha_1; \epsilon_r * E_{BC} = \alpha_2$$

$$V_{AB} = E_{AB} * d_1; V_{BC} = E_{BC} * d_2;$$

$$E_{AB} * d_1 = E_{BC} * d_2;$$


$$\frac{\alpha_1}{\alpha_2} = \frac{d_2}{d_1} = 2$$

$$Q_A = Q_{BL} = -2.0 \times 10^{-7} \text{ C}$$

$$Q_C = Q_{BR} = -1.0 \times 10^{-7} \text{ C}$$

$$(b) V_{AB} = V_{BC} = E_{AB} * d_1 = (\alpha_1 * d_1) / \epsilon_r = 2.3 \times 10^3 \text{ V}$$

11 (short)

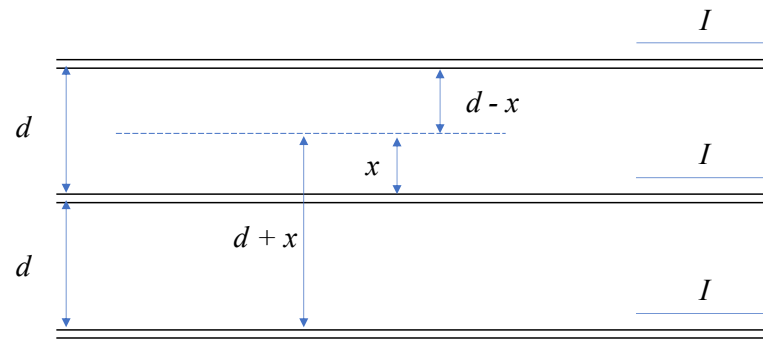

The location that $B=0$ must be within the same plane with the three wires. Assume the location that $B=0$ is x away from the central wire, and so the total B can be given by:

$$B_{\text{total}} = B_1 + B_2 + B_3$$

$$B_{\text{total}} = \frac{\mu_0 I}{2\pi x} + \frac{\mu_0 I}{2\pi(d+x)} - \frac{\mu_0 I}{2\pi(d-x)}$$

$$\text{Let } B_{\text{total}} = 0, x = \pm \frac{1}{\sqrt{3}}d = \pm 0.5773 d;$$

$x = 0$ would also be a solution.

12 (long)

(a) Electric field:

At $R=1.0$ cm, inside the conducting sphere, so $E=0$;

At $R=3.0$ cm,

$$E = \frac{Q}{4\pi\epsilon_0 R^2} = 3 \times 10^5 \text{ V/m}$$

At $R=6.0$ cm, outside the outer surface that got connected to earth,

So $E=0$.

(b) Capacitor of the concentric spheres:

$$Q = CV;$$

$$C = \frac{Q}{V}$$

$$V = \int \frac{Q}{4\pi\epsilon_0 R^2} dr = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{R_1} - \frac{1}{R_2} \right)$$

$$C = \frac{4\pi\epsilon_0}{\frac{1}{R_1} - \frac{1}{R_2}} = 4.49 \times 10^{-12} \text{ F}$$

(c) Total electrostatic energy:

$$W = \frac{1}{2} CV^2 = \frac{1}{2} QV = 1.01 \times 10^{-4} \text{ J}$$