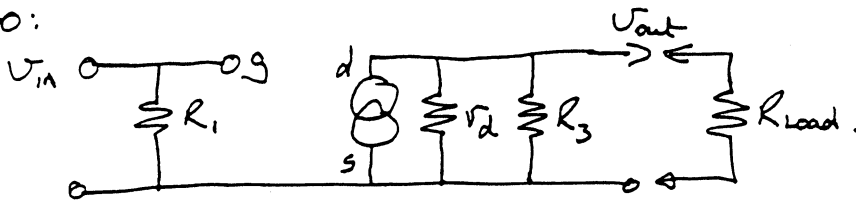


1. (a)  $V_{gs} = -3V$ , which must be voltage across  $R_2 = I_{DQ} R_2$  ie  $10^{-3} \cdot R_2 = 3$  or  $R_2 = 3k\Omega$ .

Voltage across :  $R_2 = 3V$   
 FET =  $10V$   
 $R_3 = 10k\Omega \cdot 1mA = 10V$

$R_1$  high  $\therefore V_{gs} = 23V$ .  $R_1 =$  e.g.  $1M\Omega$  to avoid absorbing signal, but low enough to take leakage.  
 (b) Capacitive impedances are negligible (ie 0)

so:




Input impedance =  $R_1$  ( $= 1M\Omega$ )

$R_o =$  Output impedance =  $r_d \parallel R_3 = \frac{50 \cdot 10}{50 + 10} k\Omega = 8.33 k\Omega$

Gain =  $g_m \cdot R_o = -5 \times 8.33 = 41.65$

c) For maximum power  $R_{Load} = R_o = 8.33k\Omega$ .

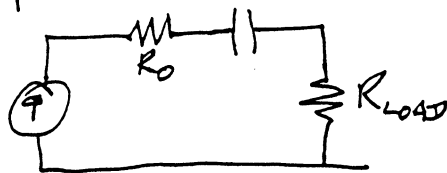d) At 3dB point, Thevenin equivalent of load circuit:



$$\therefore X_c = 2R_o \text{ or } \frac{1}{2\pi \cdot 100 \cdot C} = 16.66 \cdot 10^3$$

$$\text{or } C = \frac{1}{2\pi \cdot 100 \cdot 16.66 \cdot 10^3}$$

$$= 95.5 \text{ nF } (= 95.5 \cdot 10^{-9} \text{ F})$$

Q 2.

a) Perfect OP amp:


gain =  $\infty$  (at all frequencies)

input impedance =  $\infty$ , output impedance = 0

(also input offset voltage = 0, but not really required here; also other minor things)

To regard an amplifier as perfect, the input circuit impedance must be  $\ll$  amplifier input impedance, output circuit impedance  $\gg$  amplifier output impedance, and the circuit gain (with feedback)  $\ll$  amplifier gain at the operating frequency.

b)

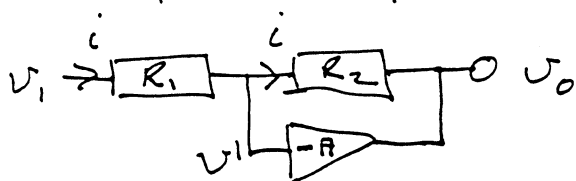

$$i = \frac{V_1 - V_0}{R_2} = \frac{V_1(1+A)}{R_2}$$

$$\text{or } V_1 = \frac{iR_2}{1+A} \text{ and } V_1 = iR_1 + \frac{iR_2}{1+A}$$

$$\text{or } R_{in} = R_1 + \frac{R_2}{1+A} = 10^3 + \frac{10^4}{101} = 1099 \Omega$$

$$V_0 = -AV_1 = \frac{-iAR_2}{1+A}$$

$$V_1 = iR_1 + \frac{iR_2}{1+A}$$


$$\therefore G = \frac{V_0}{V_1} = \frac{-AR_2}{R_1(1+A) + R_2} = \frac{-100 \cdot 10^4}{10^3 \cdot 101 + 10^4} = -9.01$$

c) Substitute  $R_1 = 2k\Omega$  in above eq. n

$$\therefore V_0 = \frac{-AR_2V_s}{R_1(1+A) + R_2} = \frac{-100 \cdot 10^4 V_s}{2 \cdot 10^3 \cdot 101 + 10^4} = -4.72 V_s$$

Q2 (cont)

d) equivalent c.c.t.

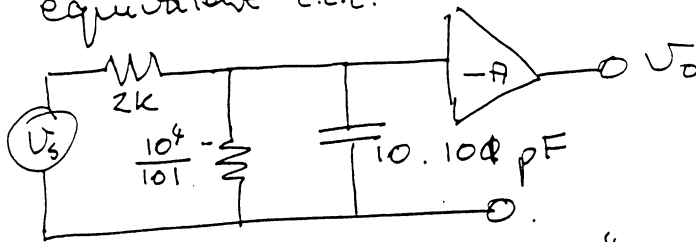

$$\text{Resistive impedance} = 2 \cdot 10^3 \parallel \frac{10^4}{101} \doteq 2 \cdot 10^3 \parallel 99 \\ = 94.3 \Omega$$



$$\text{Capacitive impedance} = 1010 \text{ pF}$$

$$\text{At 3dB point } R = \frac{1}{2\pi f C}$$

$$\text{or } f = \frac{1}{2\pi R C} = \frac{1}{2\pi \cdot 94.3 \cdot 1010 \cdot 10^{-12}} \\ = 1.67 \text{ MHz}$$

---

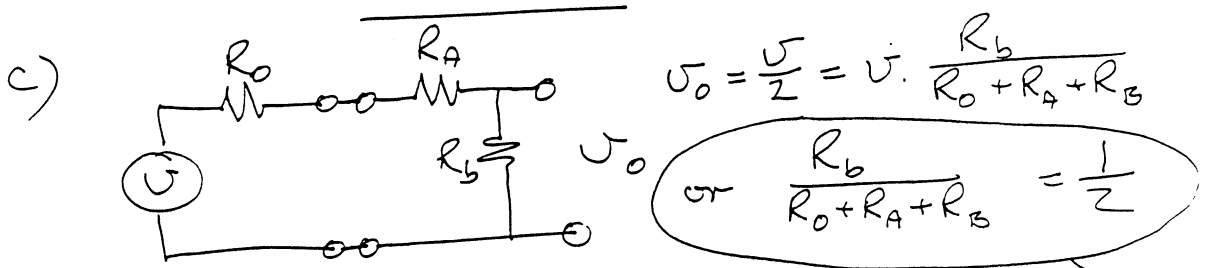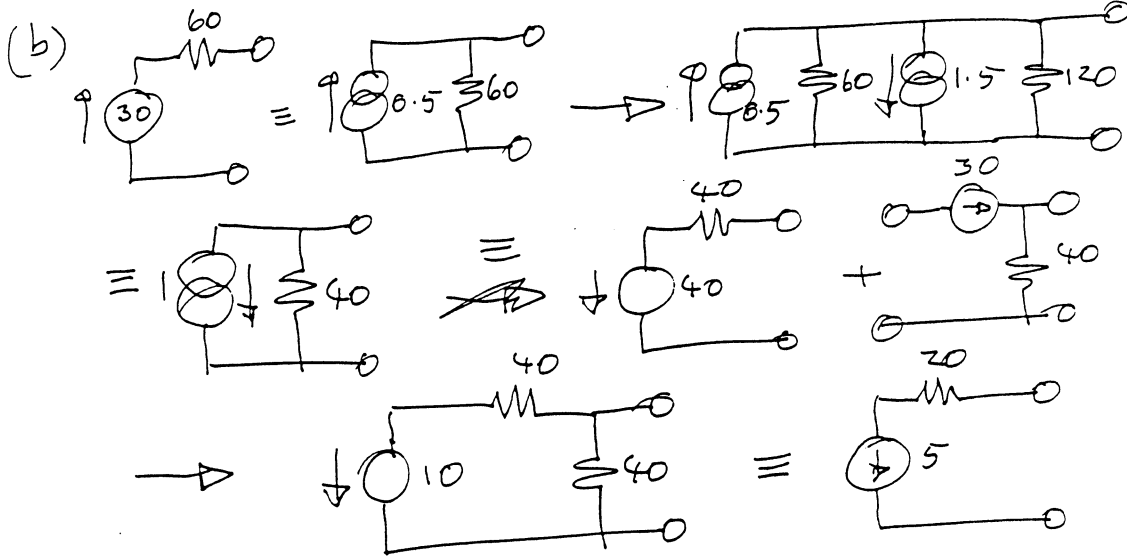3(a) any linear network can be expressed as:  
 a resistance with a series voltage source (Thevenin)  
 a resistance with a parallel current source (Norton)





Also  $Z_0 = R_0 = R_b \parallel (R_0 + R_A)$   
 $\therefore R_0 = \frac{R_b(R_0 + R_A)}{R_0 + R_A + R_b} = \frac{R_0 + R_A}{2}$  (using  $\frac{1}{2}$ )

$\therefore R_0 = R_A = 20 \Omega$

and  $2R_b = R_0 + R_0 + R_b$  or  $R_b = 2R_0 = 40 \Omega$

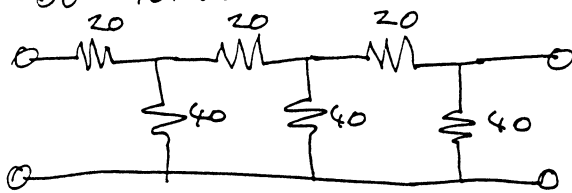d)  $8 = 2 \times 2 \times 2$ , and Thevenin impedance = constant  
 So network:



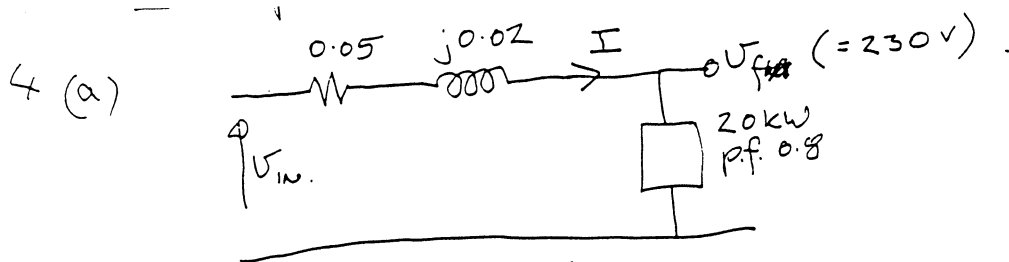

$$230 \cdot I \cdot \cos \phi = P$$

$$\therefore I = \frac{20 \cdot 10^3}{230 \cdot 0.8} = 108.7 \text{ A}$$

$$\frac{Q}{P} = \tan \phi \therefore Q_{\text{LOAD}} = P_{\text{LOAD}} \tan \phi = 20 \cdot 10^3 \cdot 0.75 = 15 \cdot 10^3 \text{ VAR}$$

$$P_{\text{LINE}} = I^2 R = 108.7^2 \cdot 0.05 = 590.8 \text{ W}$$

$$Q_{\text{LINE}} = I^2 X = 108.7^2 \cdot 0.2 = 2363 \text{ VAR}$$

$$\therefore \text{Input } P = 20 \cdot 10^3 + 590.8 = 20591 \text{ W}$$

$$\text{Input } Q = 15 \cdot 10^3 + 2363 = 17363 \text{ VAR}$$

$$\text{But } (\text{VA})^2 = P^2 + Q^2$$


$$\therefore \text{Input VA} = \sqrt{(20591^2 + 17363^2)} = 26934$$

$$\therefore \text{Input } V = \frac{\text{VA}}{I} = \frac{26934}{108.7} = 247.8 \text{ V}$$

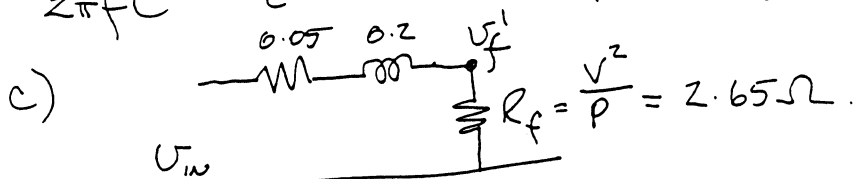b) Min. power in line when p.f. = 1

$$\text{Cancel load VARs: } \frac{V_{\text{LOAD}}}{X_c} = Q_L \text{ or } X_c = \frac{V_{\text{LOAD}}^2}{Q_L} = 3.53 \Omega$$

$$\frac{1}{2\pi f C} = X_c \text{ or } C = \frac{1}{2\pi f X_c} = 902 \mu\text{F}$$



$$V_f' = V_{\text{in}} \times \frac{R_f}{R_{\text{line}} + R_f + jX_L} = 241.9 - j17.9$$




$$\therefore |V_f'| = 242.6 \text{ volts}$$

## Section B

5.a) Truth table

Input	$I_2$	$I_1$	$I_0$	$O_2$	$O_1$	$O_0$
0	0	0	0	0	0	0
1	0	0	1	0	0	1
2	0	1	0	0	0	1
3	0	1	1	0	1	0
4	1	0	0	0	1	0
5	1	0	1	0	1	1
6	1	1	0	0	1	1
7	1	1	1	1	0	0

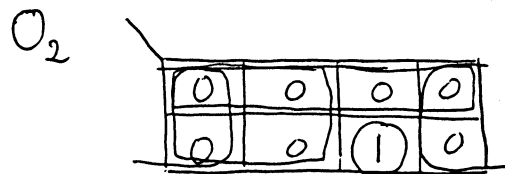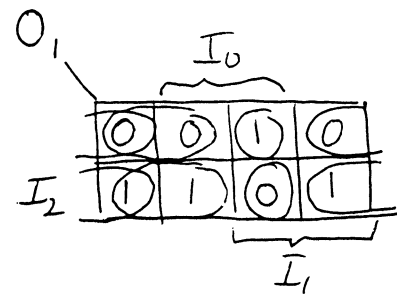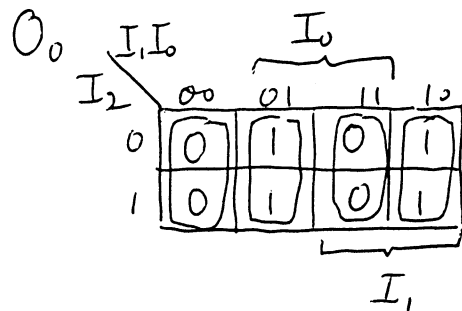b) Draw a 3 variable Karnaugh Map for each output (groups for zeros and ones shown)



For sum of products use mapping 1s

$$O_0 = \bar{I}_0 \bar{I}_1 + \bar{I}_0 I_1 \quad (= \text{XOR}(I_0, I_1))$$

$$O_1 = \bar{I}_1 I_2 + \bar{I}_0 I_2 + I_0 I_1 \bar{I}_2$$

$$O_2 = I_0 I_1 I_2$$

Product of sums (from mapping zeros)

$$\begin{aligned}
 O_0 &= (I_0 + I_1) \cdot (\bar{I}_0 + \bar{I}_1) \\
 O_1 &= (I_1 + I_2) \cdot (I_0 + I_2) \cdot (\bar{I}_0 + \bar{I}_1 + \bar{I}_2) \\
 O_2 &= I_0 I_1 I_2 \text{ (again)}
 \end{aligned}$$

c) NAND gate implementation

First convert product of sums to NAND form (De Morgan)

$$\begin{aligned}
 O_0 &= \overline{\overline{I_0 I_1} \cdot \overline{\bar{I}_0 \bar{I}_1}} \\
 O_1 &= \overline{\overline{\bar{I}_1 I_2} \cdot \overline{\bar{I}_0 I_2} \cdot \overline{I_0 I_1 \bar{I}_2}} \\
 O_2 &= \overline{\overline{I_0 I_1 I_2}}
 \end{aligned}$$

Here only 2-input NAND available

Hence convert expression for  $O_1, O_2$  to only require 2-input NAND gates.

$$O_1 = \overline{\overline{\bar{I}_1 I_2} \cdot \overline{\bar{I}_0 I_2} \cdot \overline{\overline{I_0 I_1} \cdot \bar{I}_2}}$$

and


$$O_2 = \overline{\overline{\overline{I_0 I_1} \cdot I_2}}$$

6 a) Unused states: states of bistables not taken up in the sequence used by the circuit. If the circuit initially enters such a state the subsequent behaviour may be undefined unless the designer has taken this into account.

b) Unused states: 0010  
0110  
1110  
1010

Draw state stable & required  $J_A, K_A, J_B, K_B$  inputs

State				Next State				$J_A$	$K_A$	$J_B$	$K_B$
A	B	C	D	A	B	C	D				
0	0	0	0	0	1	0	0	0	X	1	X
0	1	0	0	1	1	0	0	1	X	X	0
1	1	0	0	1	1	0	1	X	0	X	0
1	1	0	1	0	1	0	1	X	1	X	0
0	1	0	1	0	0	0	1	0	X	X	1
0	0	0	1	0	0	1	1	0	X	0	X
0	0	1	1	0	1	1	1	0	X	1	X
0	1	1	1	1	1	1	1	1	X	X	0
1	1	1	1	1	0	1	1	X	0	X	1
1	0	1	1	1	0	0	1	X	0	0	X
1	0	0	1	1	0	0	0	X	0	0	X
1	0	0	0	0	0	0	0	X	1	0	X

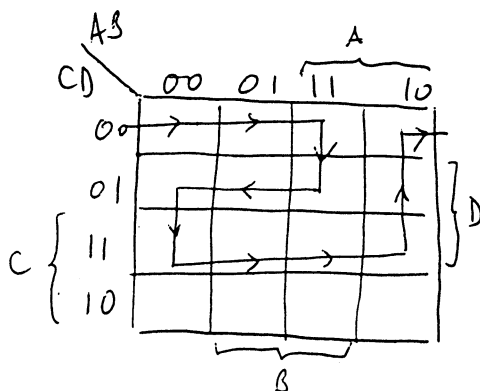

Use unit distance property of ~~map~~ code to make map easier to draw



## Bistable inputs

	JA		A	
	0	1	X	X
	0	0	X	X
C	0	1	X	X
	B		D	

$$J_A = Q_B Q_C + Q_B \bar{Q}_D$$

	KA		A	
	X	X	0	1
	X	X	1	0
C	X	X	0	0
	B		D	

$$K_A = \bar{Q}_B \bar{Q}_D + Q_B \bar{Q}_C Q_D$$

	JB		A	
	1	X	X	0
	0	X	X	0
C	1	X	X	0
	B		D	

$$J_B = \bar{Q}_A \bar{Q}_D + \bar{Q}_A Q_C$$

	KB		A	
	X	0	0	X
	X	1	0	X
C	X	0	1	X
	B		D	

$$K_B = \bar{Q}_A \bar{Q}_C Q_D + Q_A Q_C$$

c) If unused states occur two possibilities to return to correct sequence:

- i) At startup ensure that the clear input to all bistable is set so that they start in state 0000.
- ii) Add extra rows to the state table & ensure that count returns to 0000 (or some other point) on the next clock. This makes the expression for the bistable inputs more complex since we don't care states.

7 a) CCR contains following bits

- H - half carry
- I - interrupt mask
- N - negative (leading bit = 1)
- Z - zero (all bits zero)
- V - 2's complement overflow
- C - carry

The bits are set as a result of various instructions often in a data dependent way (e.g. the result of overflowed 2's complement range, or all bits zero). Branches examine combinations of CCR bits (set previously) to determine whether to take the branch. Arithmetic instructions can use e.g. carry bit to perform multiple precision arithmetic.

b) i)

CLC	; carry cleared
LDAB \$0900	; load number in range 1-15
	; to acc B
LDX #0A00	; load index reg with 0A00
LOOP: LDAA \$00, X	; load A from address in X
ADCA \$10, X	; A := A + value(\$X+10) + C
STAA \$20, X	; store A in X+20
INX	; X = X + 1
DECB	; B := B - 1
BNE LOOP	; if B > 0 GOTO LOOP

Carry is initially zero. ADCA will set if carry from addition and other instructions leave carry unchanged.

ii) It can be seen that the program performs multi-byte addition (via carry) of 2 1-15 byte numbers. The first (LS byte) is at \$0A00 & the second at

\$0A10 and the result at \$PA20.


iii) Timing

		# clock	
	CLC	2	
	LDAB \$0900	4	
	LDX # \$0A00	3	
LOOP:	LDAA \$00,X	5	} 26 per loop
	ADCA \$10,X	5	
	STAA \$20,X	6	
	INX	4	
	DECB	2	
	BNE LOOP	4	

$$\begin{aligned}
 \text{total cycles} &= 9 + 26 \times 3 \\
 &= 87 \text{ cycles.}
 \end{aligned}$$

$$\begin{aligned}
 \text{At } 8\text{MHz clock} &= \frac{87 \mu\text{s}}{8} \\
 &= \underline{10.9 \mu\text{s}}
 \end{aligned}$$

8a) i) S-R bistable

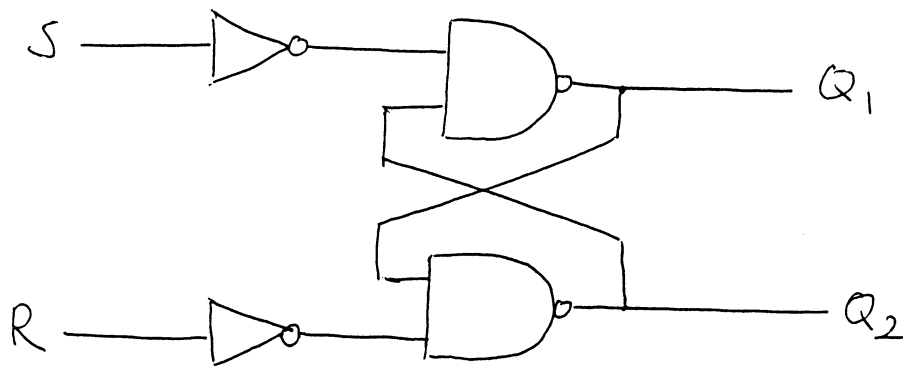


$S=1, R=0$  cause  $Q_1$  to go high (NAND if low)  
 $Q_2$  to go low  $\Rightarrow Q_2 = \overline{Q_1}$

$S=0, R=1$  cause  $Q_1$  to go low  
 $Q_2$  to go high (NAND if low)  $Q_2 = \overline{Q_1}$

$S=0, R=0$  no change  $Q_1, Q_2$  at previous state


$S=1, R=1$  forces both outputs high  
 $\Rightarrow Q_2 \neq \overline{Q_1}$  & this state normally disallowed

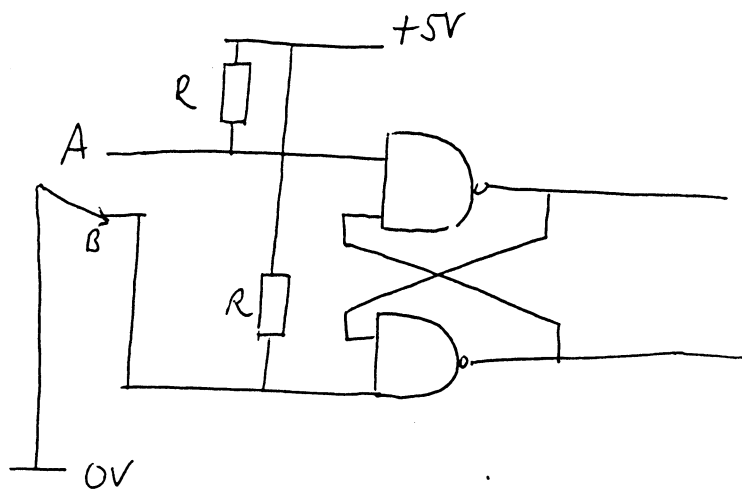For contact debouncing use the latter part of the above circuit



Typical waveform

Voltage at

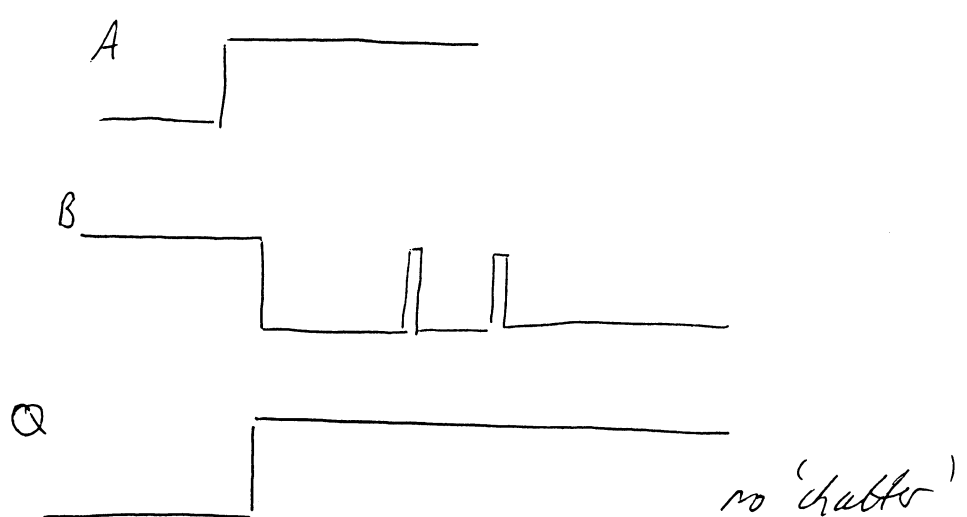

- b) R/W line : Describe the direction of the data bus (either reading from the device when high or writing to it when low)
- $\overline{CS}$  line : This is an enable (chip select). It must be low for the device to be selected & is typically used in address decoding.

Need 1 bistable per memory cell (bit)

13 address lines  $\Rightarrow 2^{13}$  locations  $\times$  8 bits/location  
 Hence  $2^{13} \times 2^3$  bits =  $2^{16}$  bistables  
 = 65536.


Number of addressable bytes is  $2^{13} = 8192 = 8k$  bytes

Hence to fill  $0000H \rightarrow 7FFFH = 32k$  bytes need  
 $\frac{32k}{8} = \underline{4}$  packages

Assuming upper 3 lines for address decoding & fully decoded to lower 32k

Package at		A <sub>15</sub>	A <sub>14</sub>	A <sub>13</sub>
0000H		0	0	0
2000H		0	0	1
4000H		0	1	0
6000H		0	1	1

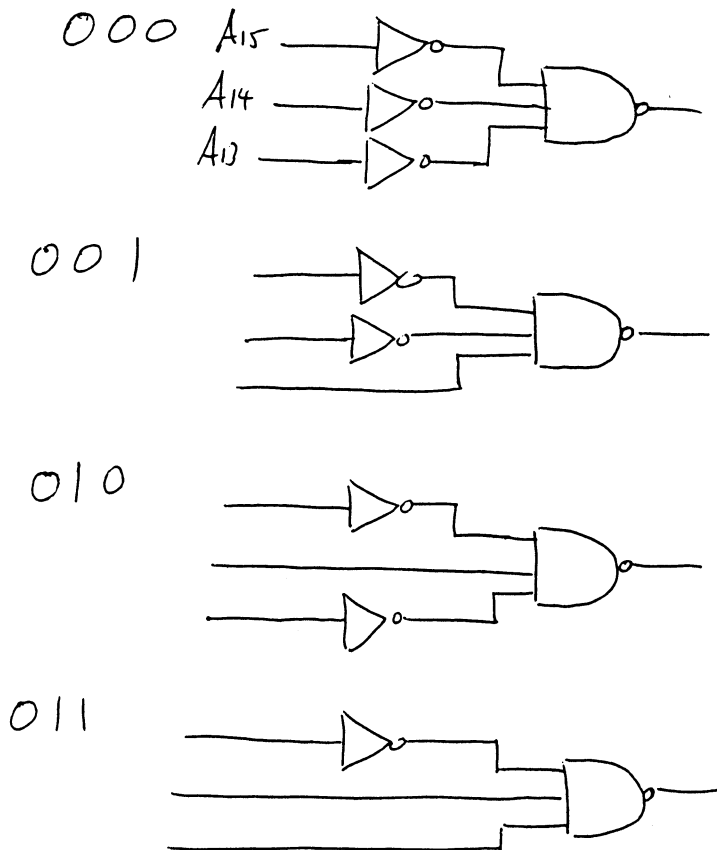For each of these packages typical circuitry (to connect to  $\bar{CS}$  on memory package)



Other schemes possible.

Question 9.

a) Gauss' Law states  $\oint \mathbf{D} \cdot d\mathbf{S} = Q$

or the electric flux leaving a volume is equal to the total enclosed charge.

b) Length  $L$  of rod, with charge  $Q$  on it:  
(Radial field only: ignore end effects)

Gauss:  $2\pi r \cdot D_r \cdot L = Q$

but assume linear dielectric of  $\epsilon$

$\therefore D_r = \epsilon E_r$

$\therefore E_r = \frac{D_r}{\epsilon} = \frac{Q}{2\pi r \epsilon L} \cdot \frac{1}{r}$


But voltage between  $R_1$  and  $R_2 = \int_{R_1}^{R_2} E_r dr$

$\therefore V = \frac{Q}{2\pi \epsilon L} \left[ \log_e r \right]_{R_1}^{R_2} = \frac{Q}{2\pi \epsilon L} \log_e \frac{R_2}{R_1}$

But  $C = \frac{Q}{V} \therefore C = \frac{2\pi \epsilon L}{\log_e \frac{R_2}{R_1}}$

air:  $\epsilon = \epsilon_0 \cdot 1 \rightarrow C = 8.03 \text{ pF}$

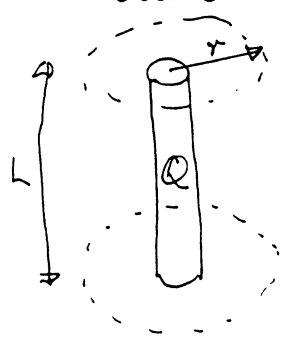liquid:  $\epsilon = \epsilon_0 \cdot 2 \quad C = 16.06 \text{ pF}$



c)  $C_d = (8 + 8 \cdot \frac{d}{200}) \text{ pF} \quad (d \text{ in mm})$   
 $= (8 + 0.04d) \text{ pF}$

d) Virtual work:  $S(\text{Electrical Stored Energy}) = S(\text{Potential Energy})$

Applying volts will tend to "suck" liquid into tube.

$SU_e = \frac{\partial C}{\partial h} \cdot Sh \cdot \frac{1}{2} V^2 \quad (SU_e = \frac{1}{2} SC \cdot V^2)$

$SU_p = g \cdot \rho \cdot A \cdot h \cdot Sh$

$A = \text{area in tube}$

$= \frac{\pi}{4} (R_2^2 - R_1^2) = \frac{\pi}{4} (8-1) \text{ mm}^2$   
 $= \pi (R_2^2 - R_1^2) = \pi \cdot 15 \text{ mm}^2$

$\therefore \frac{\partial C}{\partial h} \cdot \frac{1}{2} V^2 = g \rho A h$

$\left[ \frac{\partial C}{\partial h} = 40 \text{ pF/m}, g = 9.81, \rho = 10^3, A = 15 \cdot \pi \cdot 10^{-6} \right]$

$h = \frac{\frac{\partial C}{\partial h} \cdot \frac{1}{2} V^2}{g \rho A} = 4.3 \cdot 10^{-5} \text{ m} \text{ or } 0.043 \text{ mm}$

Question 10:

a) Assumptions: lines of flux circular  
all flux travels in toroid (none in air).  
linear materials so:

$$\oint H \cdot dl = NI \quad \text{and} \quad B = \mu H$$

So at radius  $R$

$$NI = \pi r \cdot H_1 + \pi r \cdot H_2$$

but  $B = \text{const.} \therefore H_1 = \frac{B}{\mu_1}, H_2 = \frac{B}{\mu_2}$

$$\therefore NI = \pi r B_r \left( \frac{1}{\mu_1} + \frac{1}{\mu_2} \right)$$



$$\text{or } B_r = \frac{NI}{\pi r \left( \frac{1}{\mu_1} + \frac{1}{\mu_2} \right)}$$

$$\begin{aligned} \oint B \cdot dA &= \frac{NI}{\pi \left( \frac{1}{\mu_1} + \frac{1}{\mu_2} \right)} \cdot d \cdot \int_{R_1}^{R_2} \frac{1}{r} dr \\ &= \frac{NI d}{\pi \left( \frac{1}{\mu_1} + \frac{1}{\mu_2} \right)} \log_e \frac{R_2}{R_1} \end{aligned}$$

but  $\oint = LI$  so inductance  $L = \frac{\Phi}{I} = \frac{N_1 d}{\pi \left( \frac{1}{\mu_1} + \frac{1}{\mu_2} \right)} \log_e \frac{R_2}{R_1}$

Makes no difference if coil shifted.

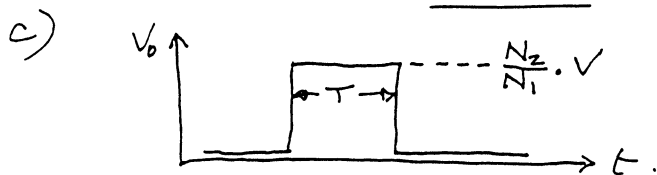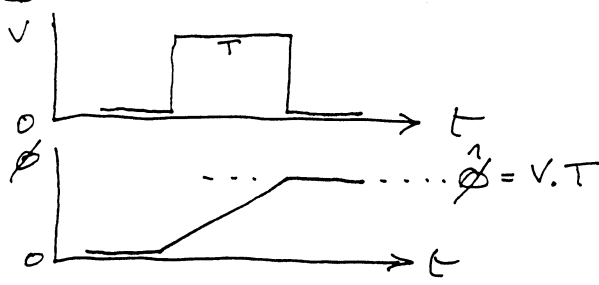b)  $\Phi = LI$  and  $V = L \frac{dI}{dt} \therefore V = \frac{d\Phi}{dt}$




d) If  $\mu_1, \mu_2 \gg 1$  as stated, all the flux is in the toroid, and none will be in the centre. (For uniformly wound toroid, any residual fields at the centre will cancel as well.)



Question 11

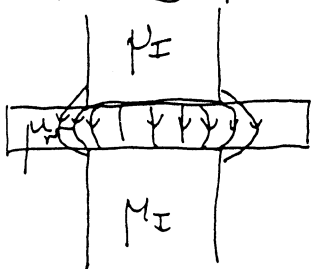a) If  $\mu_r < \mu_I$  (i.e. the relative permeability of the yoke & poles) then fringing is where the magnetic field lines "bulge" between the pole pieces, with consequent loss of uniformity for the field over the pole area.



Gets worse if:

- (i)  $t$  increases
- (ii)  $A$  decreases
- (iii)  $\mu_r$  decreases.

(proportionately).

b) Ampere's law:  $NI = H_I L + H_s t$

but  $B_I = B_s$  and  $B_s = \mu H_s$

so  $H_s = \frac{B_I}{\mu_0 \mu_r}$


$\therefore NI = H_I L + \frac{B_I \cdot t}{\mu_0 \mu_r}$

or  $B_I = NI \frac{\mu_0 \mu_r}{t} - H_I \cdot \frac{L}{t} \cdot \mu_0 \mu_r$

$= \frac{500 \cdot 0.1 \cdot 4\pi \cdot 10^{-7} \cdot 100}{10^{-2}} - H_I \cdot \frac{0.2}{0.01} \cdot 4\pi \cdot 10^{-7} \cdot 100$   
 $= 0.628 - H_I \cdot 2.51 \cdot 10^{-3}$


Use 4% Si: Fe curve in data book:

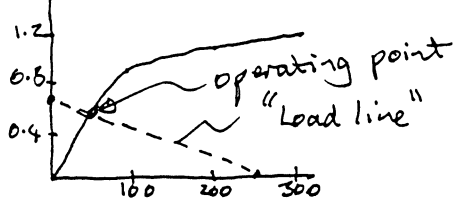$H = 0 : B = 0.63 \text{ Tesla} \quad B = 0 : H = \frac{0.63}{2.5 \cdot 10^{-3}} = 251 \text{ A/m}$



$B_{\text{sample}} = B_{\text{iron}} = 0.53 \text{ Tesla}$

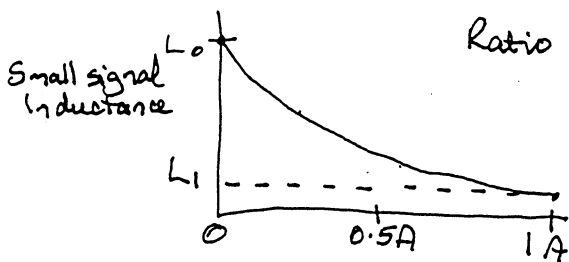c) If yoke + sample are doubled,  $\phi$  doubles (constant NI) hence  $L$  doubles (non linearity doesn't matter).



Ratio  $\frac{L_0}{L_1} = \frac{B-H \text{ Slope at } H=0}{B-H \text{ Slope, } H=\text{large}}$

could calculate new H as in part b)