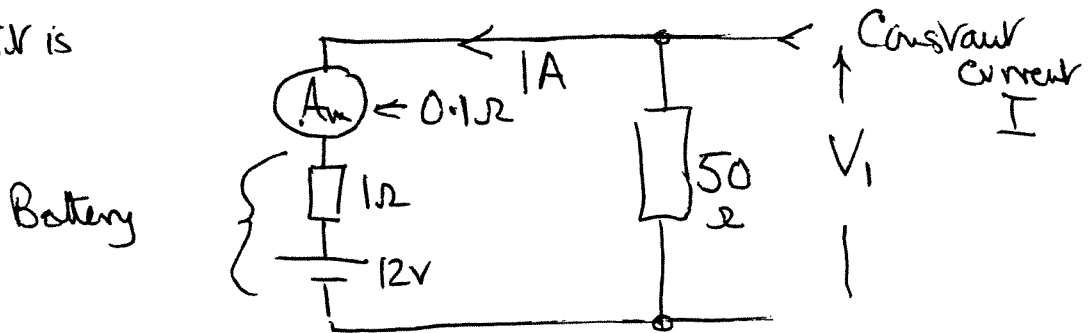


Answers

✓ Ammeter A_m , dropping 1V and on its 10A f.s.d range is modelled as a 0.1Ω resistance.

Circuit is



So when A_m reads 1A, for left hand circuit, KVL:

$$V_1 = 12 + 1(1 + 0.1) = 13.1 \text{ V}$$

So current in 50Ω resistor = $13.1/50 = 0.262 \text{ A}$

$$\text{So } \underline{I = 1.262 \text{ A}} = \text{Constant current supply}$$

$$\text{Power input to battery} = 12 \times 1 = 12 \text{ W}$$


$$\text{Power in battery as heat} = 1^2 \times 1\Omega = 1 \text{ W}$$

$$\text{Power lost in Ammeter} = 1^2 \times 0.1 = 0.1 \text{ W}$$

$$\text{Power in } 50\Omega = I^2 R = 0.262^2 \times 50 = 3.43 \text{ W}$$

$$\text{Total Power in} = \underline{16.53 \text{ W}} \quad \left\{ \begin{array}{l} \text{Check} \\ = 13.1 \times 1.262 \end{array} \right.$$
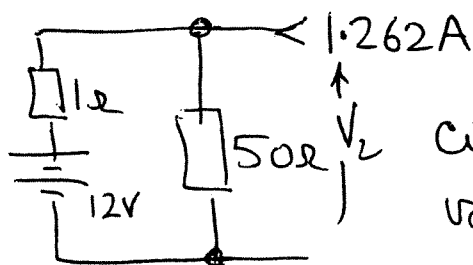
$$\text{Efficiency} = \frac{12}{16.53} = 0.726 \text{ or } \underline{72.6\%}$$




With the Ammeter replaced, the circuit becomes as shown. The new voltage V_2 across the circuit given by

$$\text{KCL: } \frac{V_2}{50} + \frac{V_2 - 12}{1} = 1.262 \quad \text{so } 0.02V_2 + V_2 = 13.262$$

$$\text{so } V_2 = \frac{13.262}{1.02} = 13.002 \text{ V.}$$

$$\text{Current into battery} = \frac{13.002}{1} = 1.002 \text{ A.}$$

(2)

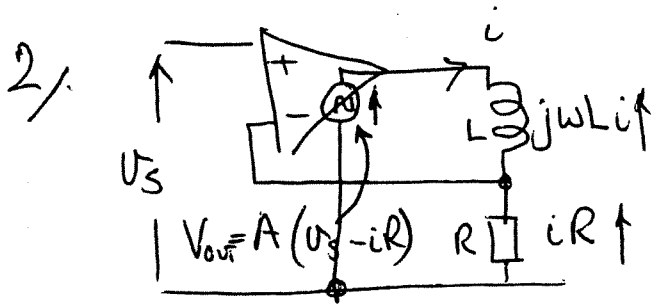

For the output current i , voltages are shown as from

the Data Book, $V_{out} = i(j\omega L + R) = A(v_s - iR)$ — (1)

So $v_s = iR + \frac{i(j\omega L + R)}{A}$ — (2) $= iR$ when A is large.

So conductance $= i/v_s = \underline{\underline{1/R}}$

If A is finite, equation (2) gives :-

$$\text{Conductance} = i/v_s = \frac{1}{R + \frac{j\omega L + R}{A}} = \underline{\underline{\frac{1}{(R + \frac{R}{A}) + j \frac{\omega L}{A}}}}$$

If $A = 100/j + jf/f_c$, $\frac{1}{\text{Conductance}} = R + \frac{1}{100} (1 + j \frac{f}{f_c}) (R + j\omega L)$

-3dB point is when Real = Imag parts; i.e. when

$$100R + R - \omega L \cdot \frac{f}{f_c} = \frac{f}{f_c} \cdot R + \omega L$$

But $\frac{f}{f_c} = \omega/\omega_c$, so $101R - \frac{\omega^2 L}{\omega_c} = \frac{\omega}{\omega_c} \cdot R + \omega L$

As $\omega_c = R/L$ or $L = R/\omega_c$, $101R - \frac{\omega^2 R}{\omega_c^2} = \frac{\omega R}{\omega_c} + \omega \frac{R}{\omega_c} = \frac{2\omega R}{\omega_c}$


Or $\omega^2 + 2\omega\omega_c - 101\omega_c^2 = 0$.

So $\omega = -\omega_c \pm \sqrt{\omega_c^2 + 101\omega_c^2} = \underline{\underline{9.1\omega_c}}$
as the positive answer.

So $f = 9.1 f_c$ is the turnover frequency


(i.e. 9.1 times better than that derived by the basic LR circuit).

3

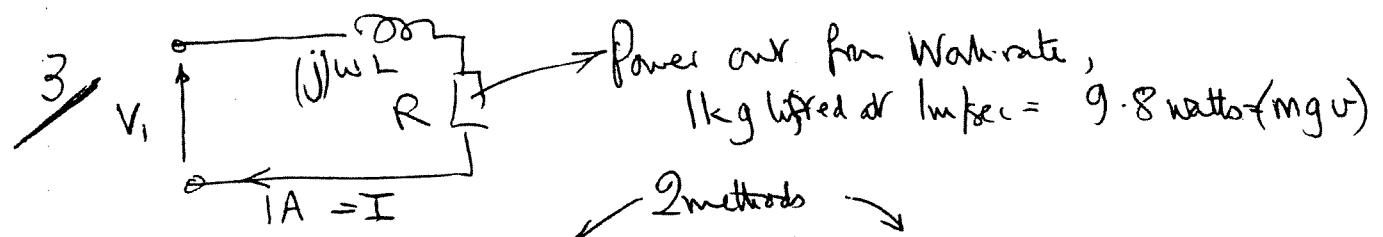

As $\omega L = 2\pi \cdot f \cdot L = 2\pi \times 50 \times 50 \times 10^{-3} = 15.708 \Omega$

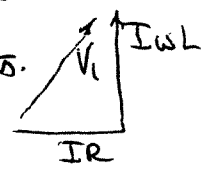$\omega L I = 15.708 \text{ Volts}$
 $IR = 9.8 \text{ Volts}$



So $V_1 = \sqrt{9.8^2 + 15.708^2} = 18.51 \text{ V}$

From power $P = V_1 I \cos\phi$

$\cos\phi = \frac{9.8}{18.51} = 0.53$

2 methods

or Watts out = 9.8

$\text{VARs} = I^2 \cdot \omega L = 1^2 \cdot 15.708 = 15.708$

$\text{VA in circ} = \sqrt{W^2 + \text{VAR}^2} = 18.51$

$\propto \text{power factor} = \frac{\text{Watts}}{\text{VA}} = 0.53$

Transformer ratio 20:1 means $\frac{1}{20} \text{ A} =$ current in for 1 A out of transformer
 Input voltage = $20 \times V_1 = 370.2 \text{ V}$

A capacitor C in parallel across the input has

$\text{VARs} = V^2 / \omega C = 370.2^2 \cdot 2\pi \cdot 50 \cdot C = 15.71$
 for zero power factor.

Hence $C = 3.65 \times 10^{-7}$ or $0.365 \mu\text{F}$


As watts & VARs are conserved, Power in = $3 + 9.8 = 12.8$

$\text{VARs in} = 4 + 15.71 = 19.71$


So $\text{VA in} = \sqrt{W^2 + \text{VAR}^2} = 23.50$

As current in = $\frac{1}{20} \text{ A}$, Volts in = 4700

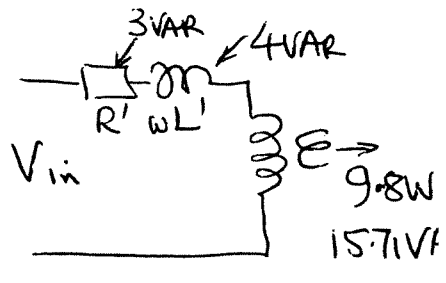Input Power factor = $\frac{\text{Watts}}{\text{Var Amps}} = \frac{12.8}{23.50} = 0.545$



4

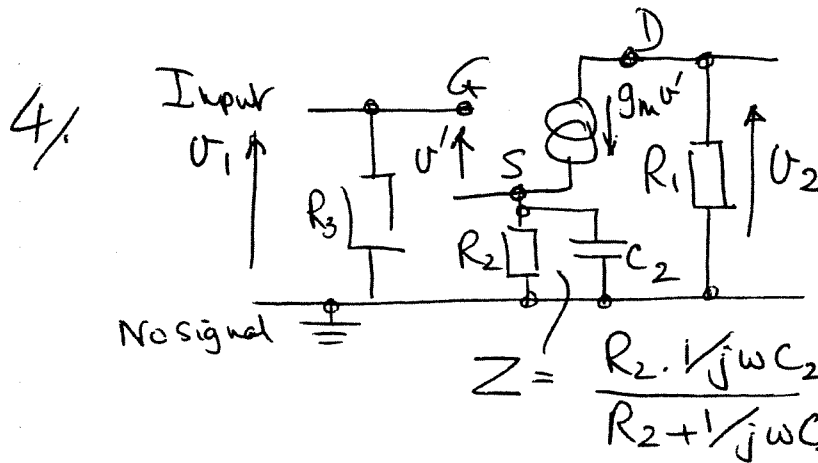

At a freq ω_s

$$Z = \frac{R_2 \cdot 1/j\omega C_2}{R_2 + 1/j\omega C_2} = \frac{R_2}{1 + j\omega C_2 R_2}$$

KVL at input: $v_i = v' + g_m v' \cdot \frac{R_2}{1 + j\omega C_2 R_2}$ so $v' = \frac{v_{in}}{1 + \frac{g_m R_2}{1 + j\omega C_2 R_2}}$ ①

KVL at output: $v_{out} = -g_m v' R_1 = \frac{-g_m R_1 v_{in}}{1 + (g_m R_2)/(1 + j\omega C_2 R_2)}$

Hence the given gain expression.

If C_2 is very large - second term in denominator = 0, —
So gain = $-g_m R_1$ (Simple amp)

If $\omega \rightarrow 0$ or DC, Gain = $-g_m R_1 / (1 + g_m R_2)$

From the equation, putting in values :-

$$\text{Gain} = \frac{-0.05 \times 1000}{1 + 50 / (1 + j \cdot 2\pi \cdot 10^3 \times 300 \times 10^{-9} \cdot 1000)}$$

$$= \frac{-50}{1 + 50 / (1 + j1.885)} = \frac{-50}{1 + 10.98 - j20.7} \quad \otimes$$


$$= \frac{-50}{12 - j20.7} = -1.05 - 1.81j = 2.09 \angle -120.0^\circ \quad \otimes$$

Step \otimes Use calculator in Complex mode


So Gain = 2.09 in magnitude and phase change is -120°

SECTION B PAPER 3

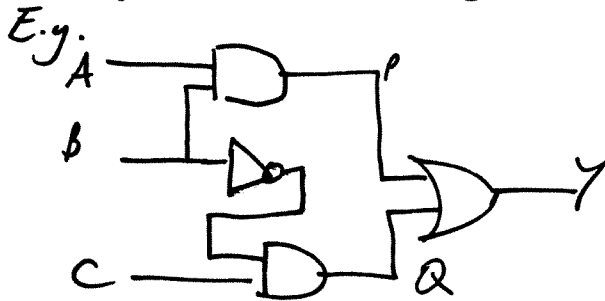
5. a) Let there be two input states to a combinational logic circuit q^1 & q^2 which both have the same output state $b^1 = b^2 = b$. When the logic input change from q^1 or q^2 to the other it is possible to momentarily change q to \bar{b} , for certain logic designs. This is a static hazard.



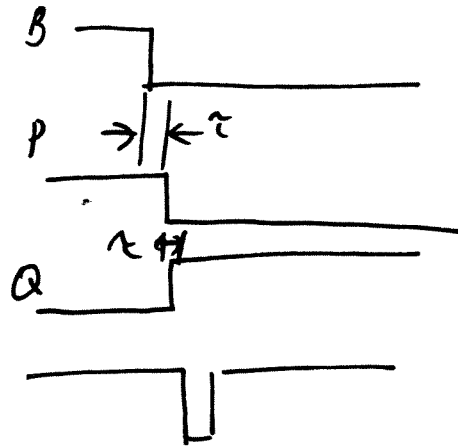This circuit exhibits a static one hazard when $A=C=1$ & B change $1 \rightarrow 0$



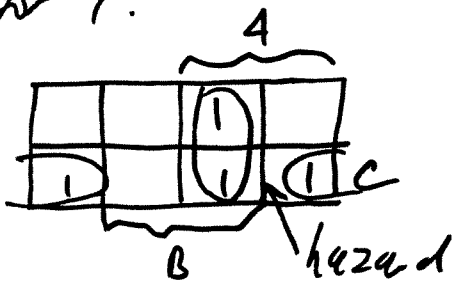
To eliminate a static-hazard draw the k-map for Y.



Fix hazard by adding an extra gate $A.C$ to the circuit so that there is "overlap" in k-map.

i.e. $F = AB + A.C + \bar{B}C$.

b) i)

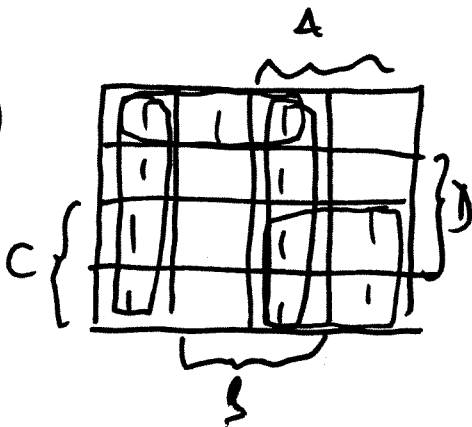


terms $A.B$ & $\bar{A}.B$ is all solutions

for F, also have $A.C$ & $B.C.\bar{D}$


as shown here.

6

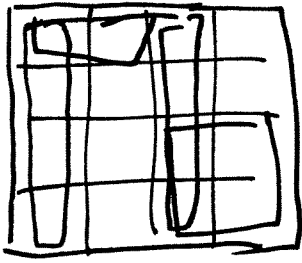
5(b) ii) Also other ~~two~~ combination
(Cont'd)


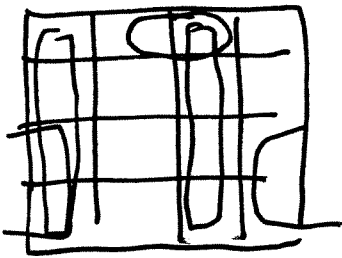
$$AB + \bar{A}\bar{B} + AC + \bar{A}\bar{C}D$$


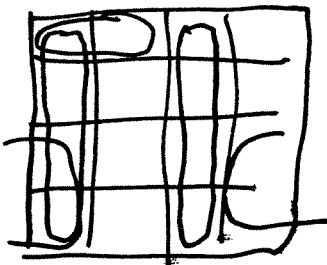
$$\bar{A}\bar{B} + AB + B\bar{C}\bar{D} + \bar{B}C$$



$$\bar{A}B + AB + \bar{A}\bar{C}\bar{D} + \bar{B}C$$

They all have potential for static hazards, as not all terms overlapped.

iii)

$$F_1 = \overline{A \cdot B + \bar{A}\bar{B} + AC + B \cdot \bar{C}\bar{D}}$$

$$F_1 = \overline{\bar{A} \cdot \bar{B} + A \cdot \bar{C} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D}}$$

Need in 2 Input form

$$\overline{x \cdot y \cdot z} \Rightarrow \overline{\overline{\overline{x \cdot y \cdot z}}}$$

$$\overline{w \cdot x \cdot y \cdot z} \Rightarrow \overline{\overline{\overline{\overline{w \cdot x \cdot y \cdot z}}}}$$

Hence Also $\bar{x} = \text{---} \square \text{---}$

Hence cct.

6 a) An unused state is a state of the logic that is not used in the normal operation of the circuit.

Circuits can be designed so that, should an unused state occur [see b(iii)] it will return to normal operation on the next clock pulse. If this is not done the subsequent operation is not defined by the required logic sequence & is therefore arbitrary. This would often lead to malfunction.

b) i)

CURRENT A B C D	NEXT A B C D	J_A	K_A	J_B	K_B	J_C	K_C	J_D	K_D
0011	0100	0	X	1	X	X	1	X	1
0100	0100	0	X	X	0	0	X	1	X
0101	0110	0	X	X	0	1	X	X	1
0110	0000	0	X	X	0	X	0	1	X
0111	1000	1	X	X	1	X	1	X	1
1000	1001	X	0	0	X	0	X	1	X
1001	1010	X	0	0	X	1	X	X	1
1010	1011	X	0	0	X	X	0	1	X
1011	1100	X	0	1	X	X	1	X	1
1100	0011	X	1	X	1	1	X	1	X

b ii) J_B

	A		
	X	X	0
	X		0
C	1	X	1
	X		0
	B		

$J_B = C \cdot D$

K_B

	A		
	0	1	X
	0		X
C	X	1	X
	0		X
	B		

$K_B = C \cdot D + A$

	0	1	0
	1		1
C	X	X	X
	X		X
	B		

$J_C = A \cdot B + D$

	X	X	X
	X		X
C	1	1	1
	0		0
	B		

$K_C = C \cdot D$

9)
6 b) iii)

Either redesign based on full (16 line) state table resulting in complete K-maps & giving a ct that will return to the correct sequence from all unused states

or

Build logic to detect unused states & use preset & clear inputs to the bitable to reset them to e.g. ABCD = 0011

Alternatively could just do the above on power up as this is the most locked time when there is a problem of this type.

7 a) Addressing modes determine where the operands (the data) for an instruction come from

- ADDA #12 IMMEDIATE - load A with 12
- ADD A \$12 DIRECT - load A from 2 byte address 12H
- ADDA \$1200 EXTENDED - load A from 2 byte address 1200H
- ADDA X,0 INDEXED - load A with number stored in X

	<u>Cycles</u>			
	b) i) 3	LOOP A :	LDX # \$1000	load X with value \$1000H.
21x64	5	LOOP B :	LDA X,0	load Acc A from address in X
			STAA \$E000	store A to DAC
			INX	inc X
			CPX # \$1040	compare X to \$1040
			BNE LOOPB	branch if compare not true
	3		LDX # \$1000	ld X with \$1000
23x64	2	LOOP C :	CLRA	clear Acc A
			SUBA X,0	subtract value at X from A → A i.e. A → -A
			STAA \$E000	store to DAC
			INX	next value to X
			CPX # \$1040	compare X to \$1040
	4		BNE LOOPC	to next value in loop
	3		BRA LOOPA	start again

Loop C outputs the negative half cycle of the waveform.

ii) From cycle in above figure total through loop A

$$\begin{aligned} &= 3 + 21 \times 64 + 23 \times 64 + 4 + 3 \\ &= 10 + 44 \times 64 \\ &= 2826 \end{aligned}$$

This takes 0.353 ms at 8 MHz clock.

iii) For 0.353 ms / 128 sample \Rightarrow 362.35 kHz
av. sampling freq.

iv) For 8 kHz need 1 sample every 1000 cycles. Therefore add a delay loop [eg loop of NOP's] in appropriate place.


In loop B add a delay of $1000 - 21 = 979$ cycles

In loop C of $1000 - 23 = 977$ sample.


Add these after each sample has been stored.

8 a) i) A shift register is a set of storage [1 bit] element arranged in series so that the content move one bit on each clock & the (n+1)th bistable take on the value of the nth from the one before.

From J-K bistables:

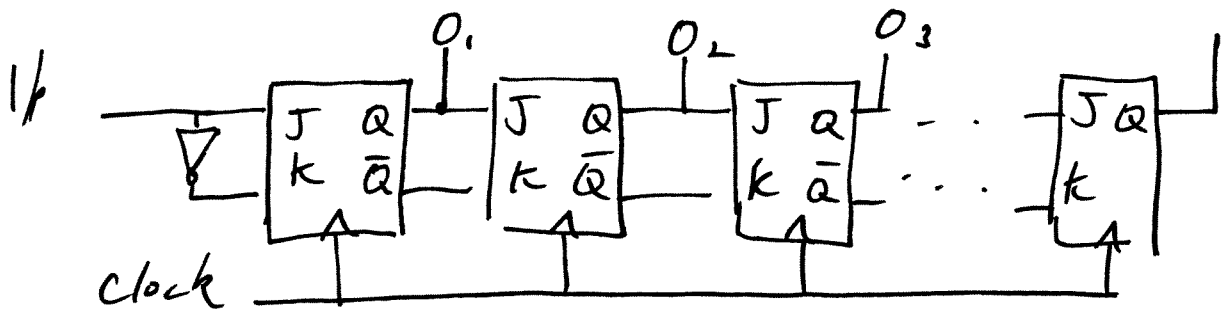

ii)

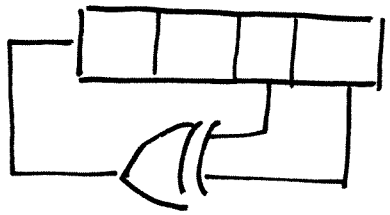

Sequence . 0000

- 1111
- 0111
- 0011
- 0001
- 1000
- 0100
- 0010
- 1001
- 1100
- 0110
- 0101
- 1010
- 1101
- 1110

15 long sequence. This is the longest sequence.

b) i) 64 kbit $2 = 2^{16}$ bit
 4 data line $= 2^2$
 hence $2^{(16-2)}$ locations $\Rightarrow 2^{14}$ location
 $\Rightarrow 14$ address line.

4 data line, 14 address
 \bar{CS} - chip select
 R/\bar{W} - read, not write.


ii) 32 kbytes $= 32 \times 2^3$ bit i.e. 2^{18} bit.
 Hence $2^{18} / 2^{16}$ device $= 2^2 = 4$

iii) 32 kbytes, 8 data line
 Each chip has 16k, 4 bit addresses.

Use same decoding for low address range to 2

				chip - $[\$0000 \rightarrow \$3FFF]$	
				$[\$4000 \rightarrow \$7FFF]$	
high range	A_{15}			A_0	
$\$0000$	0000	0000	0000	0000] low range
$\$3FFF$	0011	1111	1111	1111	
$\$4000$	0100	0000	0000	0000	
$\$7FFF$	0111	1111	1111	1111	

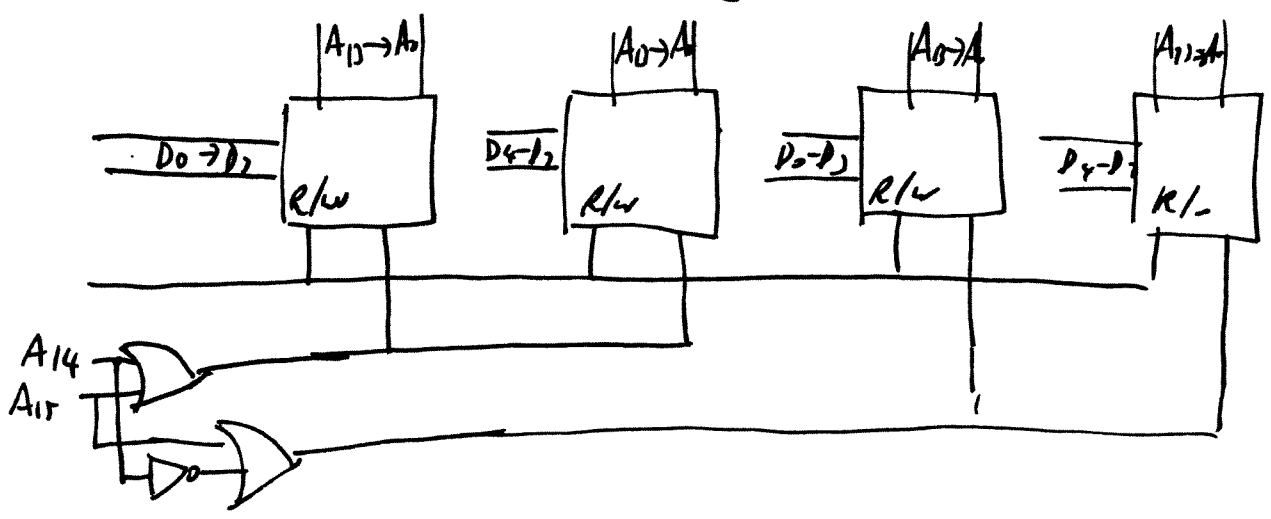i.e. need low A_{15} , low A_{14} for low range
 ... , high A_{15} ... high range.



Question 9, paper 3 - Electrical and Information Engineering

$$a) \quad r := 10 \cdot \text{cm} \quad \epsilon_0 := 8.854 \cdot 10^{-12} \cdot \frac{\text{farad}}{\text{m}}$$

$$d := 2 \cdot r$$

$$E := \frac{q}{4 \cdot \pi \cdot \epsilon_0 \cdot r^2}$$

$$V := \int_r^{\infty \cdot \text{cm}} E \, dr$$

$$V := \frac{q}{(4 \cdot \pi \cdot \epsilon_0 \cdot r)}$$

$$q := \left((4 \cdot \pi \cdot \epsilon_0 \cdot r) \right) \cdot 100 \cdot 10^3 \cdot \text{volt}$$

$$q = 1.113 \cdot 10^{-6} \cdot \text{coul}$$

b)

$$F := q \cdot E$$

$$F := \frac{q^2}{4 \cdot \pi \cdot \epsilon_0 \cdot d^2}$$

$$F = 0.278 \cdot \text{newton}$$

c) Use method of images and then the time taken to fall is time taken for force between balloon and its image to drop to the weight of the balloon

$$\text{Balloon_weight} := 5 \cdot 10^{-3} \cdot \text{kg} \cdot 9.81 \cdot \text{m} \cdot \text{sec}^{-2}$$

$$\text{Charge_at_drop_off} := \left(\text{Balloon_weight} \cdot 4 \cdot \pi \cdot \epsilon_0 \cdot d^2 \right)^{0.5}$$

$$\text{Charge_at_drop_off} = 4.672 \cdot 10^{-7} \cdot \text{coul}$$

$$\text{time} := \frac{q - \text{Charge_at_drop_off}}{10^{-9} \cdot \text{coul} \cdot \text{sec}^{-1}}$$

$$\text{time} =$$

Question 10, paper 3 - Electrical and Information Engineering

a) Use ampere's law to integrate round the central core one half of the C chape and across the gap between the C and the core. Don't forget that the H in the central core is split left and right round the core and therefore needs to be multiplied by 2

$$N := 500 \quad I := 0.5 \cdot \text{amp} \quad \mu_0 := 4 \cdot \pi \cdot 10^{-7} \cdot \frac{\text{henry}}{\text{m}}$$

$$H_{\text{central}} := \frac{2 \cdot N \cdot I}{(25 + 30 + 20 + 30 \cdot 2 + 2.5 \cdot \mu_r) \cdot \text{mm}}$$

$$H_{\text{central}} = 189.753 \cdot \frac{\text{amp}}{\text{m}}$$

b)

H (and B) need to be recalculated because the gap has changed

$$B := \frac{\mu_r \cdot \mu_0 \cdot 2 \cdot N \cdot I}{(25 + 30 + 20 + 2 \cdot 29 + 2 \cdot \mu_r \cdot 1 + 2.5 \cdot \mu_r) \cdot \text{mm}}$$

$$B = 0.136 \cdot \text{tesla}$$

energy per unit volume is given by:

$$B = \mu_0 \cdot H$$

$$\text{Energy} = \int B \, dH$$

$$\text{Energy} := \frac{B^2}{2 \cdot \mu_0}$$

$$\text{Energy} = 7.318 \cdot 10^3 \cdot \text{m}^{-3} \cdot \text{joule}$$

c) the force is simply the energy per unit volume multiplied by the area. But note the question asks for the force to pull out hence we must use the results from part a not part b

$$B := H_{\text{central}} \cdot (\mu_0 \cdot \mu_r) \quad \text{area} := 5 \cdot \text{mm} \cdot \text{mm}$$

$$B = 0.238 \cdot \text{tesla}$$

$$\text{force} := \frac{B \cdot B \cdot \text{area}}{2 \cdot \mu_0}$$

$$\text{force} = 0.113 \cdot \text{newton}$$

9) Question 11 paper No. 3.

a) From the Maxwell-Ampere equation (databook p11)

$$\oint_c \underline{H} \cdot d\underline{l} = \int_s (\underline{J} + \dot{\underline{D}}) \cdot d\underline{s}$$

But the displacement current $\dot{\underline{D}}$ is zero. Hence the right hand side is the current I and the solution is:

$$H = \frac{I}{2\pi r}$$

b)

The EMF is simply the rate of change of flux:

$$emf = -\dot{\phi}$$

Hence the voltage is:

$$V = -\frac{d\phi}{dt}$$

c) The total flux is given by:

$$\phi = \int_s \underline{B} \cdot d\underline{S} = l\mu_0 \int_a^b H(r) dr$$

Hence from part a)

$$\phi = l\mu_0 \int_a^b \frac{I}{2\pi r} dr = \frac{l\mu_0}{2\pi} I \ln(b/a)$$

from which

$$\dot{\phi} = \frac{l\mu_0}{2\pi} \dot{I} \ln(b/a)$$

Hence from b) we get

$$V = -\frac{l\mu_0}{2\pi} \dot{I} \ln(b/a)$$

and the inductance per unit length

$$= \frac{V}{\dot{I}l} = \frac{l\mu_0}{2\pi} \ln(b/a)$$