


1. i) Open loop gain A is infinite.
 Input resistance is infinite.
 Output resistance is zero.

ii) Ideal op-amp so $v_- = v_+ = 0$ by virtual earth principle. Also no current flows into the inverting input since input resistance is infinite. Therefore:

$$v_i/600 + v_o/12000 = 0 \text{ and so Gain} = v_o/v_i = -12000/600 = -20$$

$$\text{Input current } i_{in} = v_i/600 \text{ Input resistance} = v_i/i_{in} = 600 \Omega$$

iii)

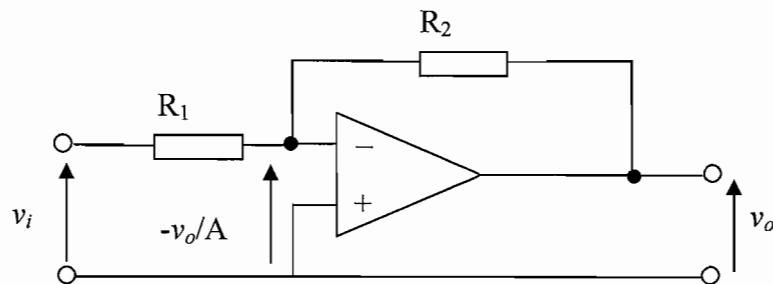

Summing currents at the inverting input:

$$v_i - (-v_o/A)/R_1 + v_o - (-v_o/A)/R_2 = 0$$


$$v_o(R_2 + R_1 + AR_1) = -R_2Av_i$$

$$v_o/v_i = -AR_2/(R_2 + R_1 + AR_1) \text{ Check: As } A \rightarrow \infty \text{ } v_o/v_i \rightarrow -R_2/R_1 \text{ as required.}$$

Putting in numbers gives $v_o/v_i = -19.96$


$$i_{in} = (v_i - (-v_o/A))/R_1 = (v_i - 19.96v_i/10^4)/600 \text{ } R_{in} = v_i/i_{in} = 600/(1 - 19.96 \times 10^{-4}) = 601.2 \Omega$$

iv)

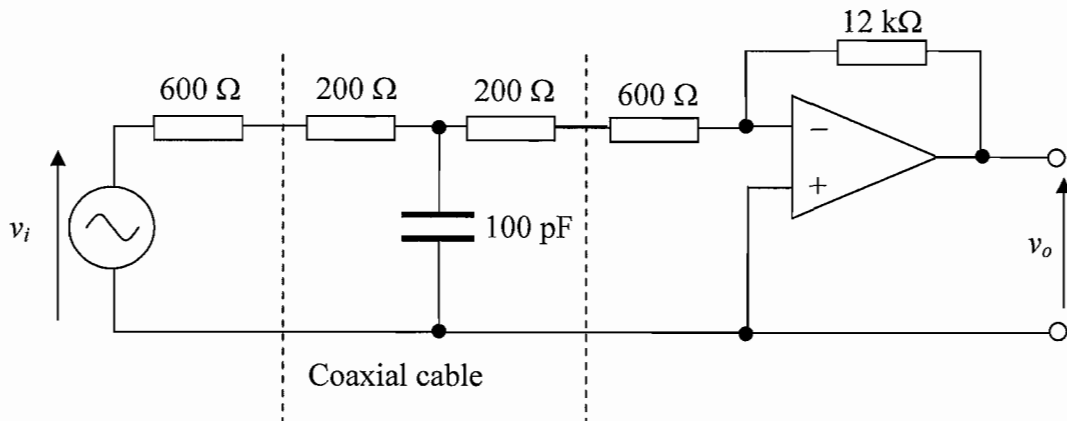

The mid-band voltage gain assumes that ω is low enough so that the 100 pF capacitor is an open-circuit. In this case all the series resistors in the circuit above may be lumped together to give 1600 Ω . Using earlier results:
 Mid-band voltage gain $v_o/v_i = -12000/1600 = -7.5$

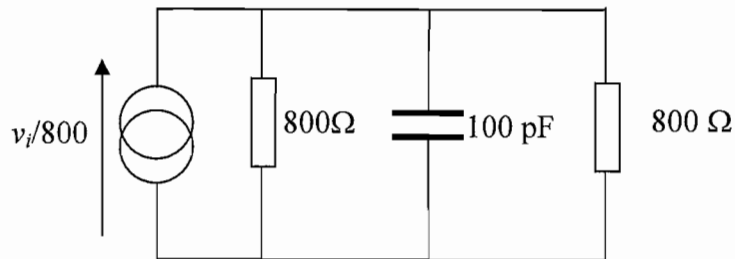For -3 dB frequency the voltage across the 100 pF capacitor needs to fall to $1/\sqrt{2}$ of its mid-band value (since the output voltage is proportional to the capacitor voltage). To obtain this voltage, convert left-hand side of circuit to Norton equivalent and use the fact that the inverting input of the op-amp is at 0 V by virtual earth principle:




The two 800 Ω resistors may be combined in parallel to give 400 Ω . Denoting $R = 400\Omega$ and $C = 100$ pF the capacitor voltage, v_c , is:

$$v_c = (R \times 1/j\omega C) / (R + 1/j\omega C) \times v_i/2R = R / (1 + j\omega CR) \times v_i/2R = v_i / (2(1 + j\omega CR))$$

-3dB frequency is found by equating the magnitudes of the real and imaginary parts of the denominator:


$$\omega CR = 1 \text{ so } f_{3dB} = 1/(2\pi CR) = 3.98 \text{ MHz}$$

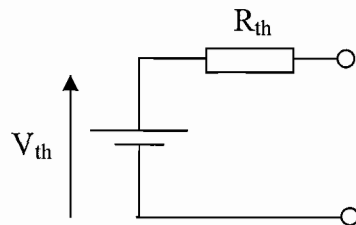2. a) Thevenin's theorem: Any linear circuit, insofar as the load connected to it is concerned, may be represented as a voltage, V_{th} , in series with a resistance, R_{th} :




where V_{th} is the open-circuit voltage of the linear circuit, V_{OC} , and $R_{th} = V_{OC}/I_{SC}$ where I_{SC} is the short-circuit current of the linear circuit.

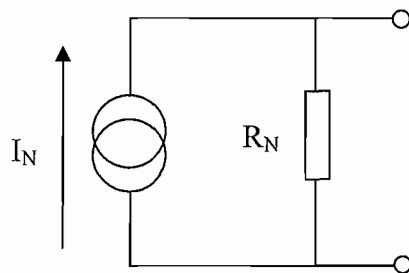Norton's theorem: Any linear circuit, insofar as the load connected to it is concerned, may be represented as a current source, I_N , in parallel with a resistance R_N :




where $I_N = I_{SC}$ and $R_N = V_{OC}/I_{SC}$

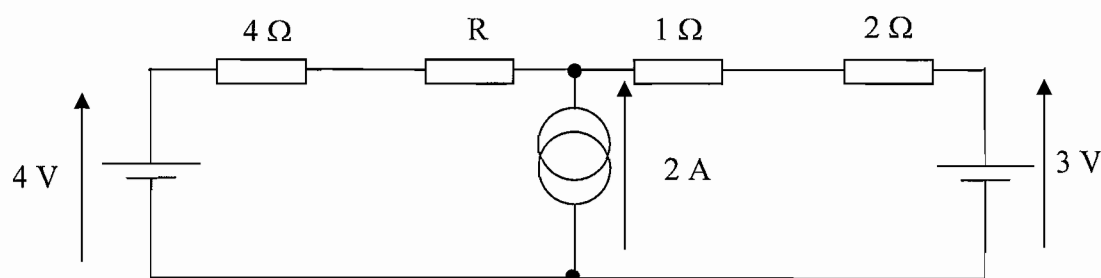b) Convert left-hand side of the circuit to Thevenin equivalent, and do the same to the right-hand side:




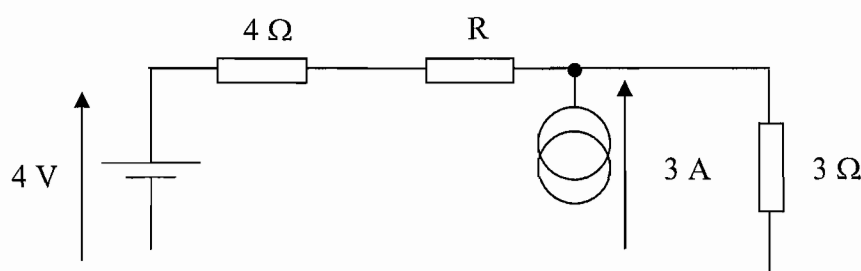Now convert right-hand side to Norton to give a 1 A current source in parallel with a 3 Ω resistor, and combine this 1 A current source with the 2 A current source by adding (since they are in parallel):





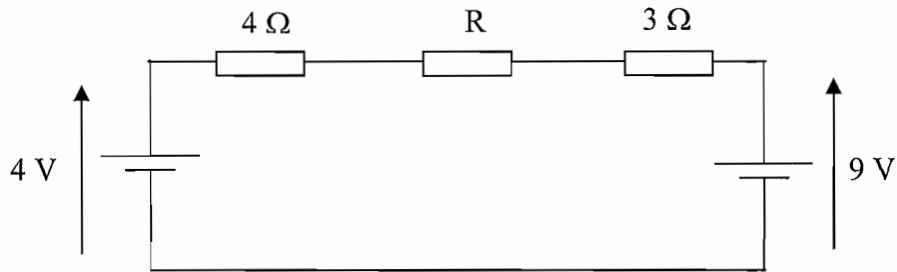Finally, convert the right-hand side of the circuit back to Thevenin to give:



i) $R = 13 \Omega$ $I = (9-4)/20 = 0.25 \text{ A}$

ii) $R = 3 \Omega$ $I = (9-4)/10 = 0.5 \text{ A}$

c) i) Find the total impedance as seen by the 240 V voltage source:

Impedance of the series combination of the capacitor, inductor and 1Ω resistor is

$$1 + j\omega L + 1/j\omega C = 1 + j(3.14 - 6.77) = 1 - j3.63$$


Combine this in parallel with the 1Ω resistor and add the series 1Ω resistor:

$$Z = 1 + 1 \times (1 - j3.63) / (1 + 1 - j3.63) = 1.884 - j 0.211$$

$$\text{Finally } I = 240/Z = 126.6 \angle +6.4^\circ$$

Examiner's comment: A common mistake here was to convert to Thevenin and find the current. This gives the current flowing in the inductor/capacitor ie the 'load' current, but not the supply current as asked for.

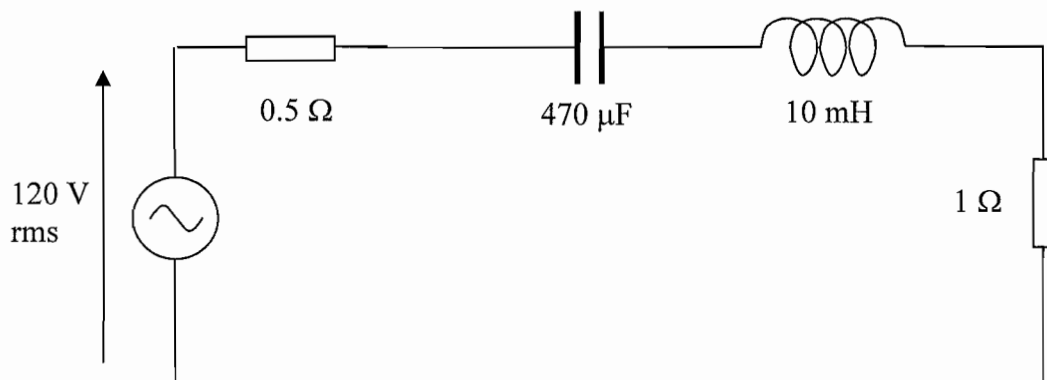ii) Convert left-hand side of circuit to Thevenin:



ii) Resonant frequency $\omega_0 = 1/\sqrt{LC}$ and $f_0 = \omega_0/2\pi$ giving 73.4 Hz

At resonance the impedance of the capacitor and inductor cancel out so that the only impedance is the 1.5Ω of resistance. Therefore:

$$I = 120/1.5 = 80 \text{ A } \angle 0$$

$$\begin{aligned} \text{Capacitor voltage } V_c &= X_C \times I \text{ where } X_C \text{ is the reactance of the capacitor} \\ &= 80/\omega C = 369 \text{ V } \angle -90 \end{aligned}$$

$$Q = \omega_0 L/R = 4.61/1.5 = 3.07$$


3. i) For $V_{GS} = 4 \text{ V}$ by potential divider:

$$10000 \times 20 / (10000 + R_1) = 4 \text{ giving } R_1 = 40 \text{ k}\Omega$$

For $V_{DS} = 10 \text{ V}$, 10 V must be dropped across R_2 with 5 mA flowing through it:

$$10 / R_2 = 0.005 \text{ giving } R_2 = 2 \text{ k}\Omega$$

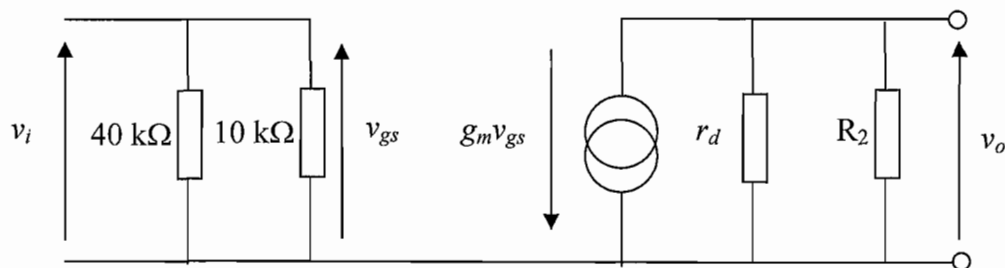
ii) To construct small-signal circuit valid at mid-band, treat all capacitors as short circuits and short-circuit all points at fixed voltage ie 20 V supply rail to ground:



$$v_{gs} = v_i$$

$$v_o = g_m v_{gs} r_d R_2 / (r_d + R_2) \text{ giving } v_o / v_i = -9.375$$

4.

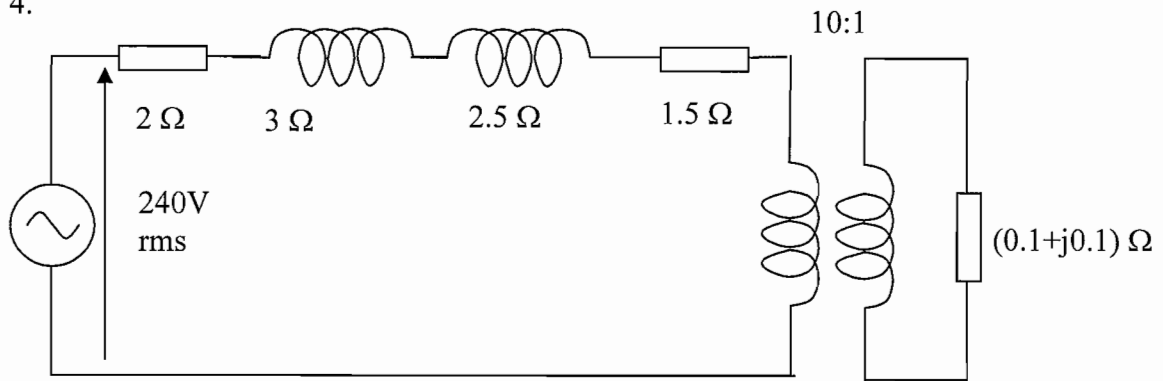

i) Load referred to primary = $(N_1/N_2)^2 Z_L = 100 (0.1 + j0.1) = (10 + j 10) \Omega$

ii) $I_L' = 240 / (13.5 + j 15.5) = 11.7 \text{ A in magnitude.}$

This is the load current referred to the primary.

$I_L = 10 I_L' = 117 \text{ A in magnitude.}$

Examiner's comment: A common mistake here was to forget to calculate the actual load current as opposed to the load current referred to the primary.

iii) $P_{\text{LOAD}} = 11.7^2 \times 10 = 1369 \text{ W}$

$P_{\text{LOSS}} = 11.7^2 \times (2 + 1.5) = 479 \text{ W}$

Therefore input power, $P_{\text{IN}} = P_{\text{LOAD}} + P_{\text{LOSS}} = 1848 \text{ W}$

Efficiency = $P_{\text{LOAD}} / P_{\text{IN}} = 1369 / 1848 = 74.1 \%$

5. i) Total impedance, $Z_T = 0.5 + j2 + 10 + j5 = (10.5 + j7) \Omega$

$I = 240 / (10.5 + j7) = 19 \text{ A in magnitude}$

$P_{\text{LOAD}} = 19^2 \times 10 = 3.62 \text{ kW}$ $Q_{\text{LOAD}} = 19^2 \times 5 = 1.81 \text{ kVAr}$

ii) Need to find total reactive power supplied

$Q_{\text{TOTAL}} = 19^2 \times 7 = 2.53 \text{ kVAr}$

Capacitor reactive power must equal total reactive power to correct power factor to unity:

$240^2 / X_C = 2530$ where X_C is the capacitor reactance at the supply frequency of 50 Hz

$X_C = 22.75 \Omega = 1 / (100\pi C)$ giving $C = 140 \mu\text{F}$

Engineering Tripos Part 1A 2006 - Paper 3 - Sections B and C answers

A R L Travis

q 6

C	A=00	01	11	10
B=00	00001	00001	00001	00001
01	00000	00001	00011	00010
11	00000	00001	11011	01000
10	00000	00001	01001	00100

C₄	A=00	01	11	10
B=00	0	0	0	0
01	0	0	0	0
11	0	0	1	0
10	0	0	0	0

C₃	A=00	01	11	10
B=00	0	0	0	0
01	0	0	0	0
11	0	0	1	1
10	0	0	1	0

C₂	A=00	01	11	10
B=00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	1

C₁	A=00	01	11	10
B=00	0	0	0	0
01	0	0	1	1
11	0	0	1	0
10	0	0	0	0

C₀	A=00	01	11	10
B=00	1	1	1	1
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

So:

$$C_4 = A_1 A_0 B_1 B_0$$

$$C_3 = A_1 A_0 B_1 + A_1 B_1 B_0$$

$$C_2 = A_1 \bar{A}_0 B_1 \bar{B}_0$$

$$C_1 = A_1 A_0 B_0 + A_1 \bar{B}_1 B_0$$

$$C_0 = A_0 + \bar{B}_1 \bar{B}_0$$

(b)


$$C_4 = \overline{\overline{A_1 A_0 B_1 B_0}}$$

$$C_3 = \overline{\overline{A_1 A_0 B_1} \cdot \overline{A_1 B_1 B_0}}$$


$$C_2 = \overline{A_1 \bar{A}_0 B_1 \bar{B}_0}$$

$$C_1 = A_1 A_0 B_0 + A_1 \bar{B}_1 B_0 = \overline{\overline{A_1 + A_0 + B_0} + \overline{A_1 + B_1 + B_0}}$$
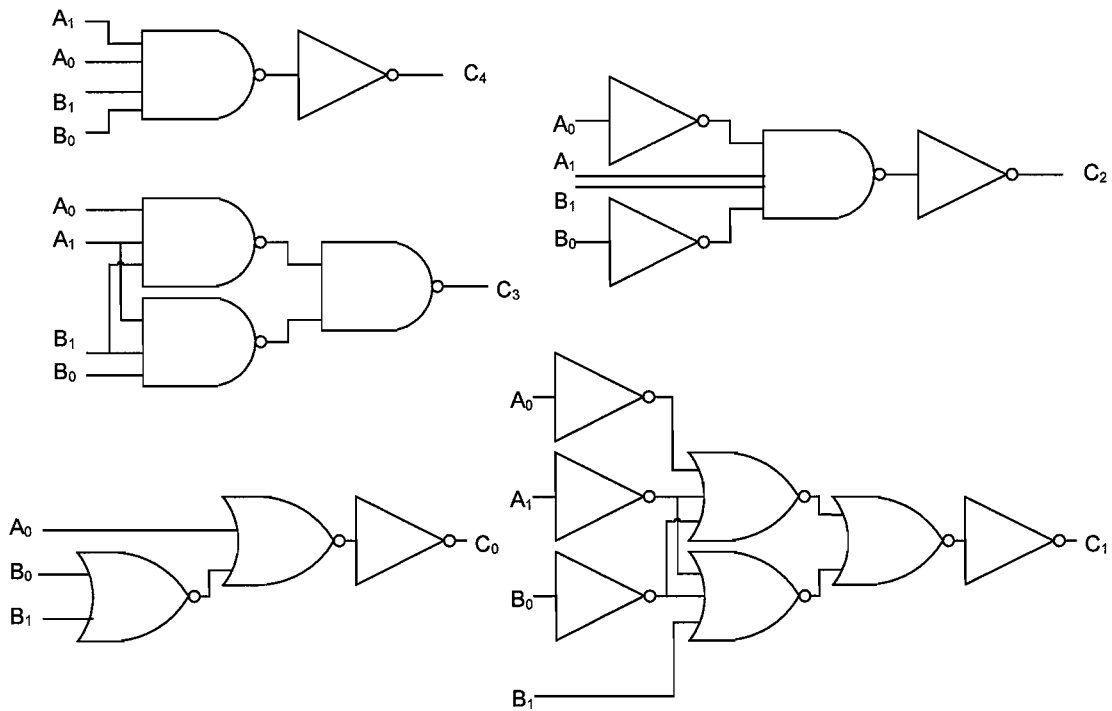
$$C_0 = A_0 + \bar{B}_1 \bar{B}_0 = \overline{\overline{A_0 + B_1 + B_0}}$$



q 7

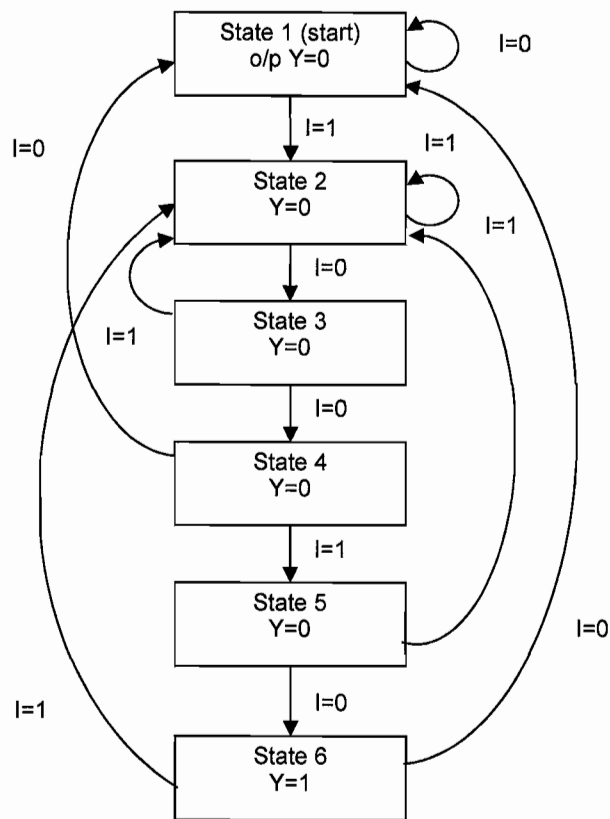

There are 6 states so 3 bistables are required to implement the system

- q 8 (i) $A \leftarrow \#FC = 11111100B$
 $B \leftarrow \#3D = 00111101B$
 $A \leftarrow \text{sum} = 00111001B + \text{carry}$

The carry into bit 7 equals the carry out of bit 7, so V is not set
 There has been a carry so C is set
 The result is not a negative number so N is not set
 The result is not zero so Z is not set
 The contents of B are 3DH
 The contents of A are 00111001B

- (ii) Sum of clock cycles per instruction = $2+2+2+2+2 = 10$ so code takes 10 microsecond.

q 9

A	B	C	D	E	F	G	H	I	J	K	L	M	N
0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110
√				√	√		√	√		√	√	√	√

C	X₁X₀=00	01	11	10
X₃X₂=00	X	1	0	0
01	0	1	0	1
11	1	1	X	1
10	1	1	1	0

$$C = \bar{X}_1 X_0 + X_3 \bar{X}_1 + X_3 X_0 + X_2 X_1 \bar{X}_0$$

q 10 By symmetry, around any circle concentric with the annulus, H is constant. Ampère's Law states that $NI = H2\pi r$

Now $\mathbf{B} = \mu_r \mu_0 \mathbf{H}$ so:

$$\mathbf{B} = \mu_r \mu_0 \frac{NI}{2\pi r} \mathbf{e}_\theta$$

where \mathbf{e}_θ is the tangential unit vector. So:

$$(a) \mathbf{B} = 100 \times 4\pi \times 10^{-7} \frac{100 \times 1}{2\pi r} \mathbf{e}_\theta$$

$$(b) \mathbf{B} = 4\pi \times 10^{-7} \frac{100 \times 1}{2\pi r} \mathbf{e}_\theta = \frac{2 \times 10^{-5}}{r} \mathbf{e}_\theta$$

$$\begin{aligned} \phi &= \int_S \mathbf{B} \cdot d\mathbf{A} = \int_{r_1}^{r_2} \left(\frac{2 \times 10^{-5}}{r} \mathbf{e}_\theta \right) \cdot (t dr \mathbf{e}_\theta) = 2 \times 10^{-5} t \int_{r_1}^{r_2} \frac{dr}{r} = 2 \times 10^{-5} t \ln \frac{r_2}{r_1} = 2 \times 10^{-8} \ln \frac{30}{20} \\ &= 8.1 \times 10^{-9} \text{ Wb} \end{aligned}$$

$$(c) L = \phi / I = 8.1 \times 10^{-9} \text{ H}$$

(d) The relationship between B and H is non-linear in both Permalloy and Columax

q 11 $Q = C_1 V_1 = C_2 V_2$ so:

$$\begin{aligned} V_2 &= \frac{C_1}{C_2} V_1 \\ &= \frac{r_1}{r_2} V_1 \\ &= 200 \text{ kV} \end{aligned}$$

$$E_2 - E_1 = \frac{1}{2}(C_2 V_2^2 - C_1 V_1^2) = \frac{1}{2}4\pi\epsilon_0(r_2 V_2^2 - r_1 V_1^2) = 2\pi\epsilon_0(\frac{1}{2} \times 4 \times 10^9 - 10^9) = 2\pi\epsilon_0 \times 10^9$$

q 12 By symmetry, the direction of the electric flux must be radial.

According to Gauss:

$$\begin{aligned} D4\pi r^2 &= \int ar \times 4\pi r^2 dr \\ D4\pi r^2 &= \pi ar^4 \\ D &= ar^2/4 \end{aligned}$$

$$\text{Energy stored within a small volume, } V = \int_V \mathbf{B} \cdot d\mathbf{H} = \frac{1}{2} \mu_r \mu_0 H^2$$

$$\begin{aligned} \text{Energy stored within one annulus} &= \frac{1}{2} \mu_r \mu_0 \times 2\pi \times t \times \int_{r_1}^{r_2} H^2 dr \\ &= \frac{\mu_r \mu_0 2\pi t}{2} \times \left(\frac{NI}{2\pi}\right)^2 \times \int_{r_1}^{r_2} \frac{1}{r^2} dr \\ &= \frac{\mu_r \mu_0 t N^2 I^2}{4\pi} \times \left(\frac{1}{r_2^3} - \frac{1}{r_1^3}\right) \end{aligned}$$