



Short Answers-Paper 3, PartIA, 2009

1(a) Textbook;

$$\text{1(b)} \quad R_{in} = 2198\Omega; \quad G = -9.01$$

2(a) Textbook;


2(b)

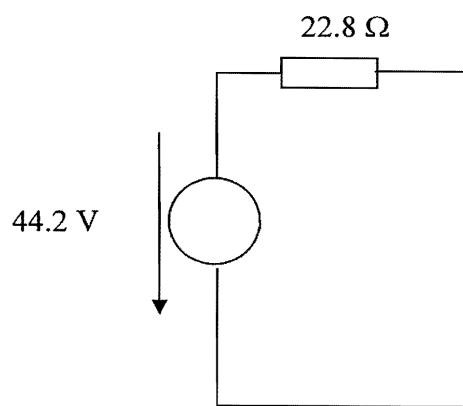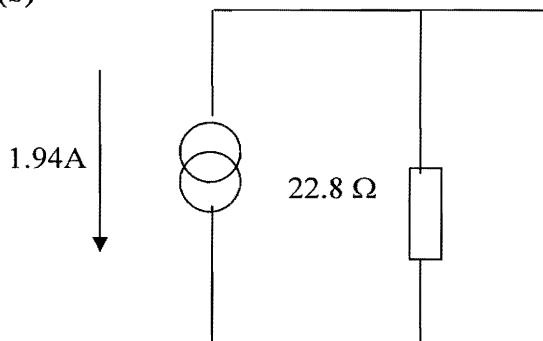

$$\text{3} \quad \overline{Z_r} = (8 + j2)\Omega; \quad \overline{I} = 29.1 \angle -14^\circ A$$

$$\text{4(a)} \quad R_1 = 63.3k\Omega; \quad R_2 = 10k\Omega$$

4(b)

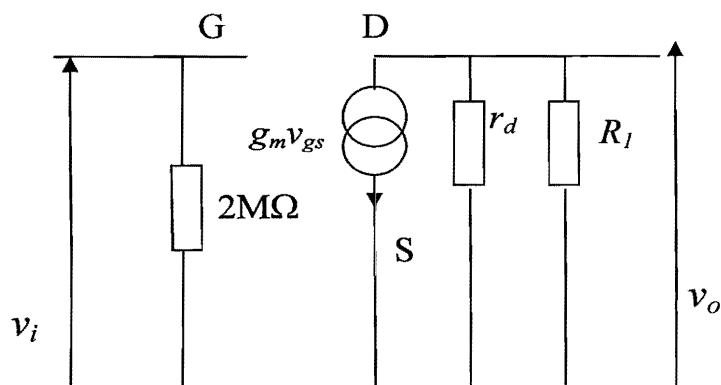

$$4(c) \text{ } Gain = \frac{-g_m R_1 r_d}{R_1 + r_d} = 48.1; \text{ } R_{out} = \frac{R_1 r_d}{R_1 + r_d} = 41.8 k\Omega$$

$$4(d) C_1 = 182.6 \text{nF}$$

5(a) Textbook

$$5(b) \bar{I} = 6.26 \angle -80^\circ A; \cos\Phi = 0.178 \text{ lag}$$

5(c) Motor Power=182.6W; Motor VARs=1454VARs; Cable power loss=78.4W

$$5(d) C = 84.4 \mu F$$

Section B Digital

6 (a) 2 bistables (c) If Q_A and Q_B are MSB and LSB respectively then $J_A = Q_B$ $K_A = \overline{Q_B}$

$$J_B = \overline{Q_A} \quad K_B = Q_A$$

7 (b) Sawtooth waveform of period 2811 clock cycles = 351.4 μs.

8 (b) Output voltage = 0.8789 V (c) Output voltage = 2.49 V

9 (a) (i) $Z = A \cdot C + B \cdot \overline{C}$ (ii) Z = 1 independent of C (iii) Static 1 hazard between 2μs and 3μs

(iv) Remove hazard by adding term A.B term.

(b) $O_0 = A_0$, $O_1 = A_1 \oplus A_0$, $O_2 = A_1 \cdot \overline{A_0}$, $O_3 = A_1 \cdot A_0$ NAND gate implementation is

$$O_3 = \overline{\overline{A_1} \cdot \overline{A_0}} \quad O_2 = \overline{A_1 \cdot \overline{A_0}} \quad O_1 = \overline{\overline{A_1} \cdot \overline{\overline{A_0} \cdot \overline{A_1} \cdot \overline{A_0}}}$$

Section C Electromagnetics

10 (c) $C = 0.163 \text{ nFm}^{-1}$

$$11 \text{ (c)} \quad L = \frac{\mu_0}{\pi} \ln \frac{2a-b}{b} \approx \frac{\mu_0}{\pi} \ln \frac{2a}{b}$$

12 (a) $R = 2.45 \Omega$ (b) $L = 0.11 \text{ H}$ (c) $Z = (2.45 + j34.6)\Omega$ $I = 2.89 \text{ A}$

(d) $B = 1.8 \text{ T}$ gives $H = 500 \text{ Am}^{-1}$ and $I = 1.4 \text{ A}$, $B = 0.9 \text{ T}$ gives $H = 25 \text{ Am}^{-1}$ and $I = 0.07 \text{ A}$ so

input current is very 'peaky' owing to core saturation.