

PART 1A
2011 Paper 3 SECTION A

2 (a) $R_2 = 2k\Omega$

$$V_{DD} = 37V$$

(b) Input impedance = $1M\Omega$
Output impedance = $11.1k\Omega$
Gain = -111.1

(c) $R_{LOAD} = 11.1k\Omega$

(d) $C = 36nF$

3 (a) $P_{LINE} = 2355W$

$$V = 251.2V$$

(b) $P_{Line} = 1.701 kW$

4 (b) $R_o = 1352\Omega$

$$X_o = 457.5\Omega$$

$$\text{Turns Ratio} = 2$$

$$R_t = 1.39\Omega$$

$$X_t = 8.21\Omega$$

5 (a) $V_{th} = V_{OC} = \frac{R_2}{R_1 + R_2} V$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

(b) $\bar{I} = 20.26 \angle 80.25^\circ A$

$$\hat{I}_C = 28.65 A$$

Section B

6. a) $F = B \cdot \bar{C} \cdot \bar{D} + A \cdot D + \bar{B} \cdot D$

c) $F = B \cdot \bar{C} \cdot \bar{D} + A \cdot D + \bar{B} \cdot D + A \cdot B \cdot \bar{C}$

7. a) 2 bistables

c) $I_A = \bar{Q}_B, J_B = 1, K_A = \bar{Q}_B, K_B = 1$

8 a) i) 00, 7F, 1, 1, 1

ii) FF, 7F, 0, 0, 0

b) 900 ns

9 a)

$Z_1 = 0 \iff Y_1 = 0, Z_1 = 1 \iff X_1 = 0 \cdot (Y_1 = 1) + (X_1 = 0) \cdot Y_1 = 1, Z_1 = 1$

b) $Z_2 = (X_1 + X_0) \cdot (X_1 + Y_1) \cdot (\bar{X}_1 + \bar{X}_0 + \bar{Y}_1)$

c)

$Z_1 = 0 \iff Y_1 = 0, Z_1 = 1 \iff (Y_1 = 0 \cdot (Y_1 = 1)) \cdot (X_1 = 0 \cdot Y_1 = 1)$

Section C

10 b) 0.031 m

11 a) 3.14 T

b) 1.3 T

12 a) i) $\frac{2}{3} \pi \rho_0 R^3$

ii) $\frac{\rho_0 R^3}{6 \epsilon_0 r^2}, \frac{\rho_0}{\epsilon_0 \epsilon_r} \left(\frac{1}{3} + \frac{r}{6R} \right) r$

b) i) 1.4 pF

ii) 0.31 nC