

Cambridge University Engineering Department
1997 Part 1B Paper 5 "Electrical Engineering"
ANSWERS

1 (a) (i) -196 (ii) 714 Ω (iii) 1961 Ω

(b) (i) -5.83 (ii) 2330 Ω

2 (b) (i) $R = 1 \text{ k}\Omega$

(ii) open-loop gain: $\frac{4 \times 10^4}{1 + j \frac{f}{120}}$; closed-loop gain: $\frac{4 \times 10^4}{3078 + j \frac{f}{120}}$; -3 dB frequency: 369.36 kHz

(c) (i) -6.8 (ii) -47.6

3 (b) (i) 13,122 A (ii) 9067 V (iii) 20.3 $^\circ$ last part: 27.6 $^\circ$


4 (b) (i) 4006 A (ii) 1002 A (iii) 229 MVA last part 0.7 Ω

5 (b) (i) $X_m = 184 \Omega$, $R_0 = 861 \Omega$, $R_2' = 3.2 \Omega$, $X_1 = X_2' = 1.95 \Omega$

(c) (i) 0.01333 (ii) $(47.9 + j 70.1) \Omega$ (iii) 8.5 A (iv) 20.9 Nm


6 (a) characteristic impedance: 50 Ω Transmission frequency: 781.25 kHz

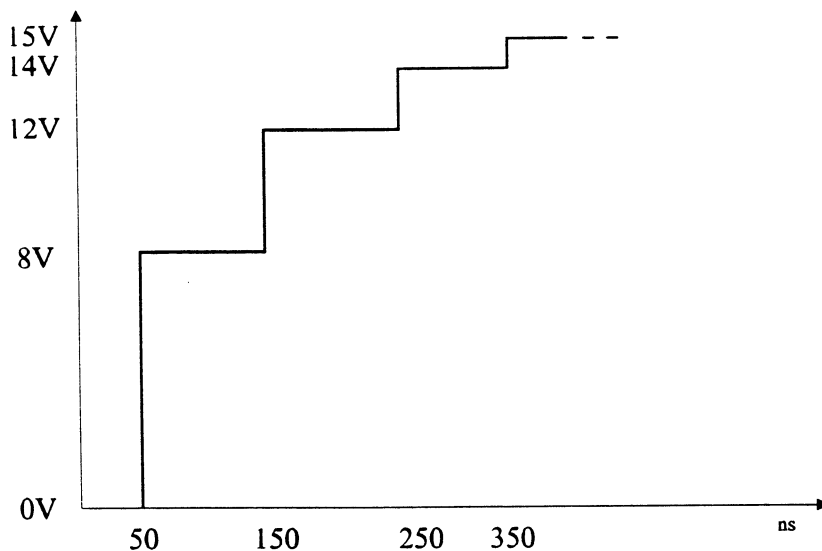(b) first incident wave: 8V (i) 1.28 W (ii) 1.28 W (iii) 0 W



7 (a) 6.37 pW m^{-2} (i) 12.7 pW (ii) 0.504 μA

(1) (a)

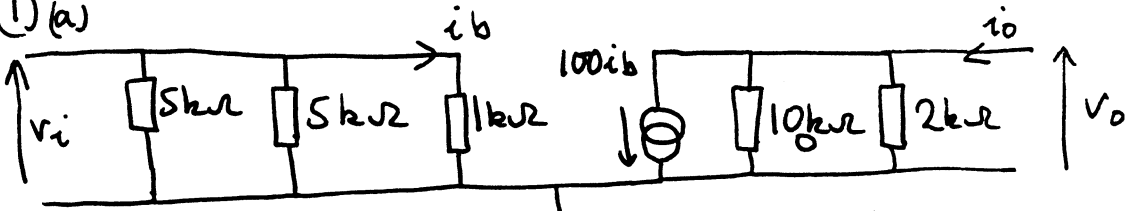

$$\frac{1}{h_{oe}} = \frac{1}{10 \times 10^{-6}} = 100k\Omega$$


$$(i) v_o = -100i_b \times 100k\Omega // 2k\Omega = -100i_b \times \left(\frac{100 \times 2}{100+2}\right) \times 10^3$$

$$i_b = \frac{v_i}{1000} \Rightarrow v_o = -\frac{100v_i}{1000} \times \frac{200}{102} \times 10^3 = -196v_i$$

$$\therefore \text{gain} = \frac{v_o}{v_i} = -196 \quad (ii) r_{in} \text{ is clearly (by inspection)} \\ = 5k\Omega // 5k\Omega // 1k\Omega = \underline{\underline{714\Omega}}$$


(iii) short-circuit input $\Rightarrow v_i = 0 \Rightarrow i_b = 0 \Rightarrow h_{fe}i_b = 0$

circuit becomes

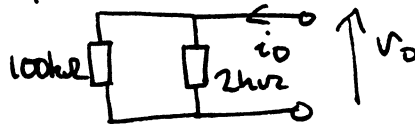

$$\Rightarrow \frac{v_o}{i_o} = R_{out} = 100k\Omega // 2k\Omega = \underline{\underline{1961\Omega}}$$

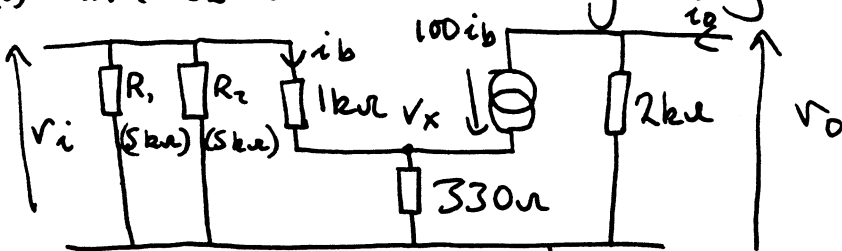(b) with CE omitted and neglecting \$h_{oe}\$:-



sum currents at output (\$i_o = 0\$):

$$\frac{v_o}{2000} = -100i_b \quad (1) \quad \frac{v_i - v_x}{1000} = i_b \quad (2)$$

$$i_b(1+100) = \frac{v_x}{330} \quad (3); \quad (2) \Rightarrow v_i = v_x + 1000i_b$$

$$\text{so } v_i = 330i_b \times 101 + 1000i_b \text{ using (3)}$$

$$\Rightarrow v_i = 34330i_b \text{ sub. in (1)} \Rightarrow v_o = -2000 \times 100i_b$$

$$(i) \text{ so } \frac{v_o}{v_i} = -5.83 = \frac{-200000v_i}{34330}$$

R_E - provides a stable operating point (dc conditions)
 C_E - "bypass" capacitor ensures high ac gain by providing a short-circuit path for ac signals to ground

(b)(ii) ^{4.4} we already have $v_i = 330 i_b \times 101 + 1000 i_b$

$$\Rightarrow i_b = \frac{v_i}{330 \times 101 + 1000}$$

$$\left[\text{so } \frac{v_i}{i_b} = 34.33 \text{ k}\Omega \right]$$

$\frac{v_i}{i_{in}}$ is $\therefore R_1 // R_2 // 34.33 \text{ k}\Omega$

i.e. $r_{in} = 2.5 \text{ k}\Omega // 34.33 \text{ k}\Omega$

$$\doteq \underline{\underline{2.33 \text{ k}\Omega}}$$

(2) (a) Common mode gain: 2 inputs of amp. at same voltage $V_1 = V_2 = V_c$
 output voltage = $A_c V_c$ where A_c is c.m. gain.

Differential gain: the factor by which an amplifier multiplies
 the difference between the 2 inputs. $V_1 = V_2 = V_d/2$

$V_o = A_d v_d$ where $v_d = v_1 - v_2$; A_d is diff. gain.

High CMRR: small differential signal from transducer
 has superimposed 50Hz mains noise on top of each
 inputs to amp (i.e. common mode signal). High CMRR
 will attenuate this 50Hz noise, but amplify transducer
 signal. (e.g.)

(b) Ideal op-amp: $V_+ = V_-$ so $V_i = \frac{R}{12+R} V_o \Rightarrow \frac{V_o}{V_i} = \frac{12+R}{R} = 1 + \frac{12}{R}$

for gain of 13, $\Rightarrow 13 = 1 + \frac{12}{R} \Rightarrow \underline{\underline{R = 1k\Omega}}$.

$$A = \frac{A_o}{1 + jf/120} \quad (\text{open-loop})$$

$$\Rightarrow \text{closed loop gain} = \frac{A}{1 + AB}$$

$$\text{where } B = \frac{R}{12+R}; \quad \text{closed-loop gain} = \frac{A_o}{(1 + jf/120)}$$

$$\therefore B = \frac{1}{12+1} = 1/13$$

$$1 + \frac{A_o B}{(1 + jf/120)}$$

$$= \frac{A_o}{(1 + A_o B) + jf/120} = \frac{4 \times 10^4}{1 + 4 \times 10^4 \cdot \frac{1}{13} + jf/120}$$

$$= \frac{4 \times 10^4}{3078 + jf/120}$$

$$= \frac{13}{1 + jf/120 \times 3078}$$

$$= \frac{13}{1 + jf/369360}$$

$$\Rightarrow \underline{\underline{f_{3dB} = 369.36 \text{ kHz}}}$$

(c) (i) $V_+ = \frac{R_2}{R_1 + R_2} \cdot V_4 = V_-$. Summing currents at "-" termin

$$\frac{V_x - V^-}{R_1} = -\frac{V_o - V^-}{R_2} \therefore \left(\frac{V_x - \frac{R_2}{R_1 + R_2} \cdot V_4}{R_1} \right) = \left(\frac{-V_o + \frac{R_2}{R_1 + R_2} \cdot V_4}{R_2} \right)$$


$$\therefore \frac{(R_1 + R_2)V_x - R_2 V_4}{R_1} = \frac{-V_o(R_1 + R_2) + R_2 V_4}{R_2}$$

$$\therefore R_2(R_1 + R_2)V_x - R_2^2 V_4 = -V_o R_1(R_1 + R_2) + R_1 R_2 V_4$$

$$\text{so } R_2(R_1 + R_2)[V_x - V_4] = -V_o R_1(R_1 + R_2)$$

$$\Rightarrow \frac{V_o}{V_x - V_4} = -\frac{R_2}{R_1} = -\frac{68}{10} = \underline{\underline{-6.8}}$$

(2) (c) (ii) Consider $1/2$ circuit:-

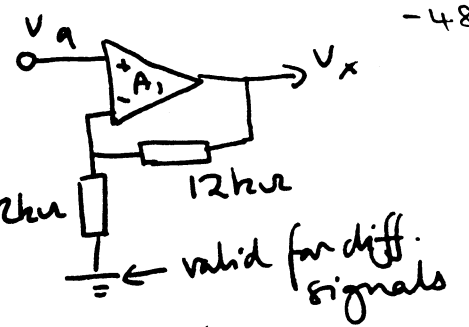


as before, $\frac{V_x}{V_a} = 1 + \frac{12}{2} = +7$

$\frac{4k\Omega}{2} = 2k\Omega$ ← valid for diff. signals.


so overall gain $\frac{V_o}{V_a} = +7 \times -6.8 = \underline{\underline{-47.6}}$

First stage gives v. high input impedance (and reduces problems due to resistor mismatches in 2nd stage)

(3) (a)

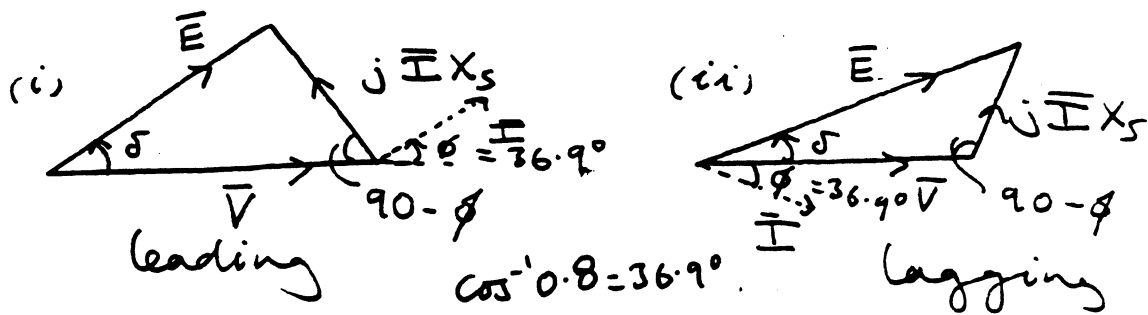

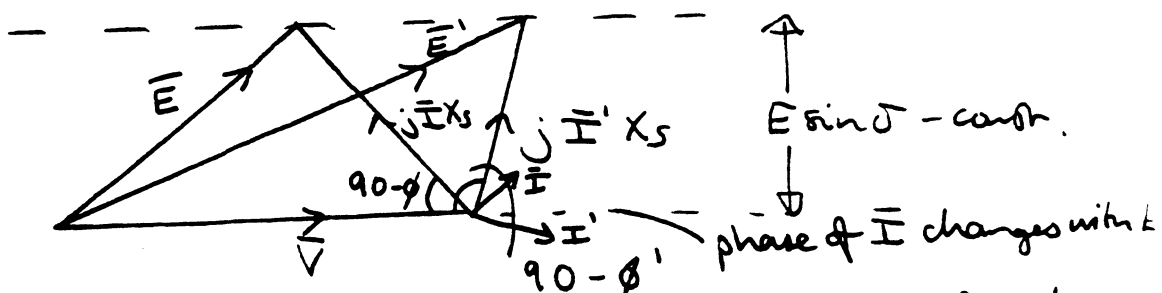for constant power, $E \sin \delta$ is constant



by changing excitation voltage using field regulator, the shape of the diagram changes and so ϕ varies. Hence for constant power, Q varies because of change in p.f.

(b) (i) $\frac{\sqrt{3} V_L I_L}{\cos \phi} = 300 \times 10^6 \Rightarrow I_L = \frac{300 \times 10^6}{0.6 \times \sqrt{3} \times 22 \times 10^3} = 13,12$

(ii) using phasor diagram above and cosine rule:-
 $E^2 = V^2 + (IX_s)^2 - 2V(I X_s) \cos(90 - \phi)$

$\Rightarrow E^2 = \frac{(22 \times 10^3)^2}{3} + (13122 \times 0.4)^2 - \frac{2 \times 22 \times 10^3 \times (13122 \times 0.4)}{\sqrt{3}} \sin \phi$

$\Rightarrow \underline{E = 9067V \text{ per phase}}$

(iii) using sine rule: $\frac{\sin \delta}{IX_s} = \frac{\sin(90 - \phi)}{E}$

$\Rightarrow \sin \delta = \frac{IX_s \cos \phi}{E} = \frac{13122 \times 0.4 \times 0.6}{9067} \Rightarrow \underline{\delta = 20.3}$

for increase in power, $\frac{\sin \delta_2}{\sin \delta_1} = \frac{400}{300} \Rightarrow \delta_2 = \sin^{-1} \left[\frac{4}{3} \times \sin 20 \right]$
 $\Rightarrow \underline{\delta_2 = 27.6^\circ}$

(4)(a) "fast acting": to prevent damage to equipment and danger - 50-
 "resettable": automatic clearing of faults - breakers reclose
 after fault has gone
 "redundancy": tripping one part of a system doesn't
 adversely affect another part (multiple trips etc.)
 (others)

(b) $MVA_b = 100 \text{ MVA}$.

generator: $1.0 \text{ pu volts}, j0.3$

200 MVA transf: $j \frac{0.05 \times 100}{200} = j0.025 \text{ pu}$

line: $j50 \times 0.2 \mu = j1 \mu \Rightarrow j \frac{10}{132^2/100} = j0.057 \text{ kpu}$

150 MVA transf: $j \frac{0.08 \times 100}{150} = j0.05333 \text{ pu}$

one-line diagram is:



$$I_f = \frac{1}{j(0.3 + 0.025 + 0.057k + 0.05333)} = j2.29 \text{ pu}$$

base current at 33kV bus = $\frac{100 \times 10^6}{\sqrt{3} \times 33 \times 10^3} = 1749.5 \text{ A}$
 (in bus)

(i) $S_0 I_f = 2.29 \times 1749.5 = \underline{\underline{4006 \text{ A}}}$

(ii) $I_f' \text{ (in line)} = 2.29 \times \frac{100 \times 10^6}{\sqrt{3} \times 132 \times 10^3} = \underline{\underline{1002 \text{ A}}}$

(iii) fault MVA = $1 \text{ pu} \times 2.29 = 2.29 \text{ pu} \Rightarrow 2.29 \times 100 = \underline{\underline{229 \text{ MVA}}}$
 (breaker rating)

For 3500 A in bus, $\Rightarrow \frac{3500}{1749.5} = 2 \text{ pu}$.


so $2 \text{ pu} = \frac{1}{x} \Rightarrow x = 0.5$ so extra reactance (pu)

is $0.5 - 0.43573 = 0.06427 \text{ pu}$


$\Rightarrow 0.06427 \times \left(\frac{33^2}{100}\right) = \underline{\underline{0.7 \Omega}}$

$Z_{\text{base at bus}}$

- (5) (a) R_1 : stator winding resistance
 R_2' : referred rotor resistance
 X_m : three phase magnetizing reactance
 X_1 : stator leakage reactance :-
 X_2' : referred rotor leakage reactance :-
 R_0 : iron loss resistance

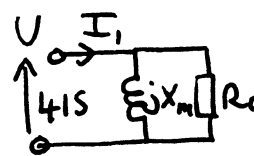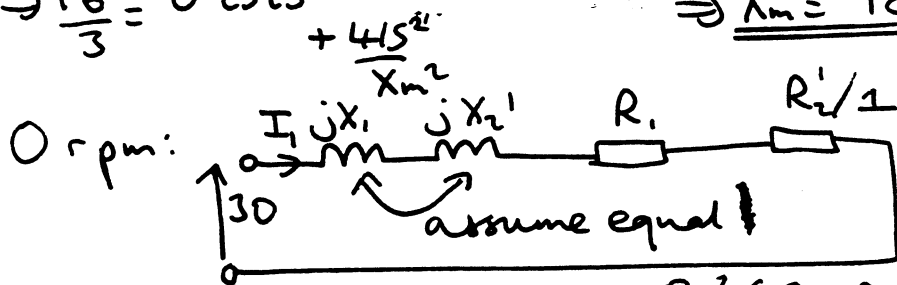(b) 1500 rpm:  $\frac{3 \times V_1^2}{R_0} = 600 \Rightarrow \frac{3 \times 415^2}{R_0} = 600$
 $\Rightarrow R_0 = 861 \Omega$

Currents in quadrature
 so $I_1^2 = I_{X_m}^2 + I_{R_0}^2 \therefore \left(\frac{4}{\sqrt{3}}\right)^2 = \left(\frac{415}{861}\right)^2 + \left(\frac{415}{X_m}\right)^2$
 $\Rightarrow \frac{16}{3} = 0.2323 \Rightarrow X_m = 184 \Omega$



$3I_1^2 (R_1 + R_2') = 333 \Rightarrow \left(\frac{8}{\sqrt{3}}\right)^2 (2 + R_2') = 111$
 $\Rightarrow R_2' = 3.2 \Omega$

$\frac{30^2}{(X_1 + X_2')^2} + (2 + 3.2)^2 = \left(\frac{8}{\sqrt{3}}\right)^2 \Rightarrow \frac{900}{5.2^2 + 4X_1^2} = \frac{64}{3} \Rightarrow X_1 = X_2' = 1.95 \Omega$

(c) $\delta = \frac{1500 - 1480}{1500} = \frac{20}{1500} = 0.01333$

(ii) $\bar{Z}_1 = R_1 + jX_1 + \frac{jX_m (jX_2' + R_2'/s)}{j(X_m + X_2') + R_2'/s}$

$\therefore \bar{Z}_1 = 2 + j1 + \frac{j100 \left(\frac{2}{0.01333} + j1\right)}{j101 + 20 \cdot 0.01333} = (47.9 + j70.1) \Omega$

(iii) $I_L = \frac{\sqrt{3} \times 415}{1.2 \cdot 9 + j70.1} = \frac{\sqrt{3} \times 4.89}{\dots} = 8.5 \text{ A}$

(d)(c) (iv) using current divider rule:-

$$I_2' = \frac{4.89 |j100|}{|j100 + j1 + \frac{2}{0.0133}|} = 2.7 \text{ A.}$$

$$T_e = \frac{3 I_2'^2 R_2'}{8 \text{ Ws}} = \frac{3 \times 2.7^2 \times 2}{\pi \times \frac{1500}{60} \times 0.0133} = \underline{\underline{20.9 \text{ Nm}}}$$

(3)(a) Z_0 : The ratio between the voltage and current of a unidirectional wave on a transmission line at any point.

$$\epsilon = 80 \times 10^{-12} \text{ F m}^{-1}, \quad \mu = 2 \times 10^{-7} \text{ H m}^{-1}$$

$$\text{so } Z_0 = \sqrt{\frac{\mu}{\epsilon}} = \sqrt{\frac{2 \times 10^{-7}}{80 \times 10^{-12}}} = \underline{\underline{50 \Omega}}$$

$$\lambda = \frac{2\pi}{\beta} \text{ where } \beta = \omega \sqrt{\mu\epsilon} \text{ so for } \lambda = 16 \times 20 \text{ m}$$

$$\Rightarrow 20 \times 16 = \frac{2\pi}{2\pi f \sqrt{\mu\epsilon}} = \frac{1}{f \sqrt{\mu\epsilon}} \text{ so } f = \frac{1}{20 \times 16 \times \sqrt{2 \times 10^{-7} \times 80 \times 10^{-12}}} \\ = \underline{\underline{781.25 \text{ kHz}}}$$

(b) $e_L = \frac{Z_L - Z_0}{Z_L + Z_0} \Rightarrow$ (i) for $Z_L \rightarrow \infty, e_L \rightarrow +1 \Rightarrow |e_L|^2 \rightarrow 1$.

incident wave is $\frac{Z_0}{Z_0 + Z_G} \times 32 = \frac{50}{50 + 150} \times 32 = \underline{\underline{8V}}$

so incident power = $\frac{8^2}{Z_0} = \frac{8^2}{50} = \underline{\underline{1.28W}}$ = reflected power since $|e_L|^2 = 1$.

(ii) $e_L = \frac{0 - Z_0}{0 + Z_0} = -1 \Rightarrow |e_L|^2 = 1 \Rightarrow$ reflected power = 1.28W


(iii) $e_L = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0 \Rightarrow |e_L|^2 = 0 \Rightarrow$ reflected power = 0W

(because line is "matched" or "correctly terminated",
∴ no reflections)

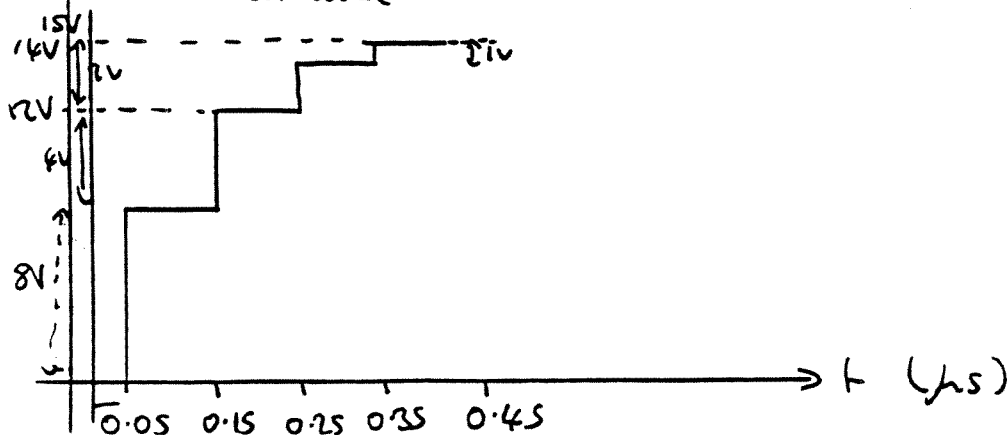(c) propagation time = $\frac{20}{2 \times 10^8} = 0.1 \mu\text{s}$

if $Z_L = 150 \Omega \Rightarrow e_L = \frac{150 - 50}{150 + 50} = 0.5; Z_G = 150 \Omega$ also so $e_G = 0.5$

all reflections ∴ produce an attenuation by a factor of 0.5 (at load and source). First incident wave is ~~32V~~ 8V
1st reflected is 4V, then 2V at source etc.



(7) (a) The gain of an antenna is the factor by which the maximum radiated intensity exceeds that of an isotropic antenna if they emit equal power from an equal distance.

$$\text{peak intensity} = \frac{G \times \text{Power}}{4\pi r^2} = \frac{2000 \times 25}{4\pi \cdot (25 \times 10^3)^2} = \frac{0.37}{\text{m}^2} \text{ W}$$

(i) peak power received = $A_{\text{eff}} \times \text{intensity}$
 $= 2 \times 0.37 = \underline{\underline{12.7 \text{ W}}}$

(ii) perfect matching \Rightarrow all power received goes to receiving electronics

so $12.7 \times 10^{-1} \text{ W} = \frac{1}{2} V I = \frac{1}{2} I^2 Z_0$
 $\Rightarrow I^2 = \frac{2 \times 12.7 \times 10^{-1}}{Z_0} = 713 \text{ A}^2 \Rightarrow \text{RMS } I = \underline{\underline{504 \text{ A}}}$

(b) $\text{curl } \underline{\underline{H}} = \frac{\partial \underline{\underline{D}}}{\partial t} = \epsilon_0 \frac{\partial \underline{\underline{E}}}{\partial t} = j\omega \epsilon_0 \underline{\underline{E}}$ for sinusoids.
 so $\text{curl } \underline{\underline{H}} = j\omega \epsilon_0 \underline{\underline{E}}$

$$\text{curl } \underline{\underline{H}} = \begin{vmatrix} \hat{u}_x & \hat{u}_y & \hat{u}_z \\ \partial/\partial x & \partial/\partial y & \partial/\partial z \\ 0 & H_0 e^{-j\beta z} & 0 \end{vmatrix} = -\hat{u}_x \frac{\partial (H_0 e^{-j\beta z})}{\partial z} + \hat{u}_z \frac{\partial (H_0 e^{-j\beta z})}{\partial x} \rightarrow 0$$

so $\text{curl } \underline{\underline{H}} = -\hat{u}_x H_0 (-j\beta) e^{-j\beta z}$
 $= \hat{u}_x j\beta H_0 e^{-j\beta z}$

$\Rightarrow \hat{u}_x j\beta H_0 e^{-j\beta z} = j\omega \epsilon_0 \underline{\underline{E}}$

so $\underline{\underline{E}} = \frac{\hat{u}_x \beta}{\omega \epsilon_0} H_0 e^{-j\beta z}$

$\text{with } \left[\frac{\beta}{\omega} \right] = \sqrt{\mu_0 \epsilon_0}$
 \uparrow
 reciprocal of prop. vel.

so $\underline{\underline{E}} = \frac{\hat{u}_x \sqrt{\mu_0 \epsilon_0}}{\epsilon_0} H_0 e^{-j\beta z}$
 $= \hat{u}_x \sqrt{\frac{\mu_0}{\epsilon_0}} H_0 e^{-j\beta z} \leftarrow \eta_0$

reintroduce implied sinusoidal time variation

$\Rightarrow \underline{\underline{E}}(z,t) = \hat{u}_x \eta_0 H_0 e^{+j(\omega t - \beta z)}$