

IB Paper 5 June 1998 - Crib.


Section A

1. $\delta I_c \Rightarrow i_c$, $\delta I_B \Rightarrow i_b$, $\delta V_{CE} \Rightarrow V_{ce}$, $\delta V_{BE} \Rightarrow V_{be}$

$\frac{\partial I_c}{\partial I_B} = h_{fe}$, $\frac{\partial I_c}{\partial V_{CE}} = h_{oe}$, $\frac{\partial V_{BE}}{\partial I_B} = h_{ie}$, $\frac{\partial V_{BE}}{\partial V_{CE}} = h_{re}$

$\Rightarrow i_c = h_{fe} i_b + h_{oe} V_{ce}$ ①

$V_{be} = h_{ie} i_b + h_{re} V_{ce}$ ②

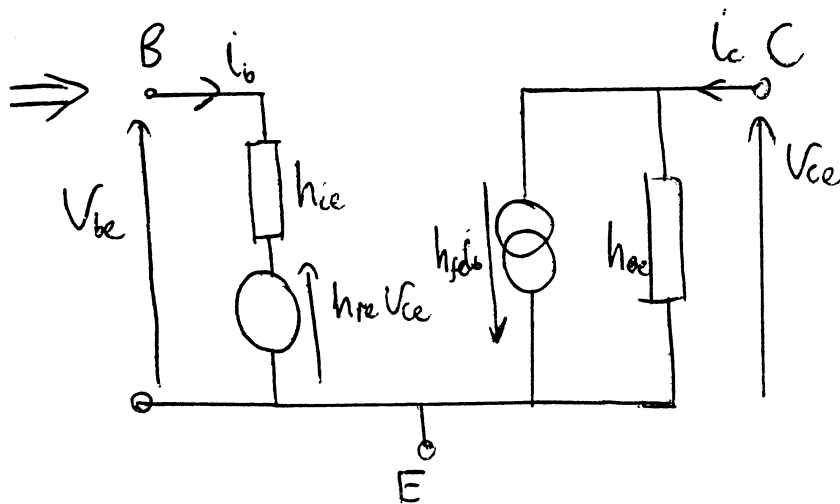

It is seen that the circuit linking C to E represents ①, that linking B to E represents ②

a) Voltage across R_c is $20 - V_{CE} = 10V$ (R_c is ignored in bias analysis because of C_2)
 $\therefore I_c = \frac{10}{R_c} = 25 \text{ mA}$


$\Rightarrow \underline{R_c = 400 \Omega}$

$$h_{FE} = 200 = \frac{I_c}{I_b} \Rightarrow I_b = \frac{I_c}{200} = 125 \mu A$$


Quiescent voltage across $R_B = 20 - V_{BE} = 19.3 V$

$$\therefore \frac{19.3}{R_B} = 125 \mu A \Rightarrow \underline{\underline{R_B = 154.4 k\Omega}}$$

b)

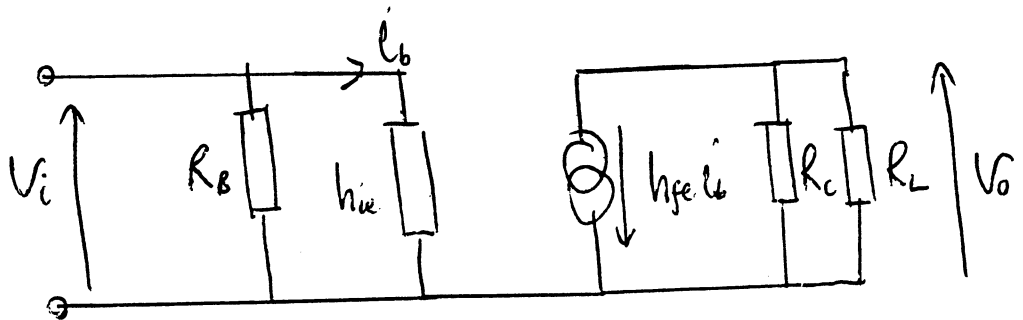

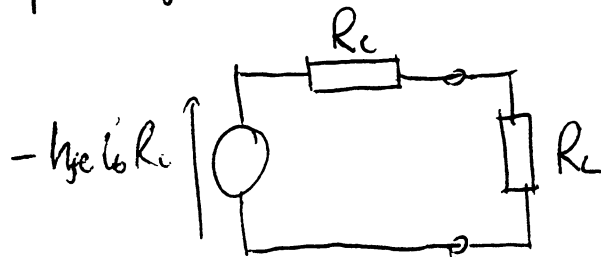Replace $h_{fe} i_b \parallel R_C$ with Thevenin equivalent




By maximum power transfer theorem $R_L = R_C$

$$\Rightarrow \underline{\underline{R_L = 400 \Omega}}$$

$$i_b = \frac{V_i}{h_{ie}}, \quad V_o = -h_{fe} i_b R_C \parallel R_L$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{h_{fe}}{h_{ie}} R_C \parallel R_L = -\frac{200}{300} \times 200 = \underline{\underline{-50}}$$

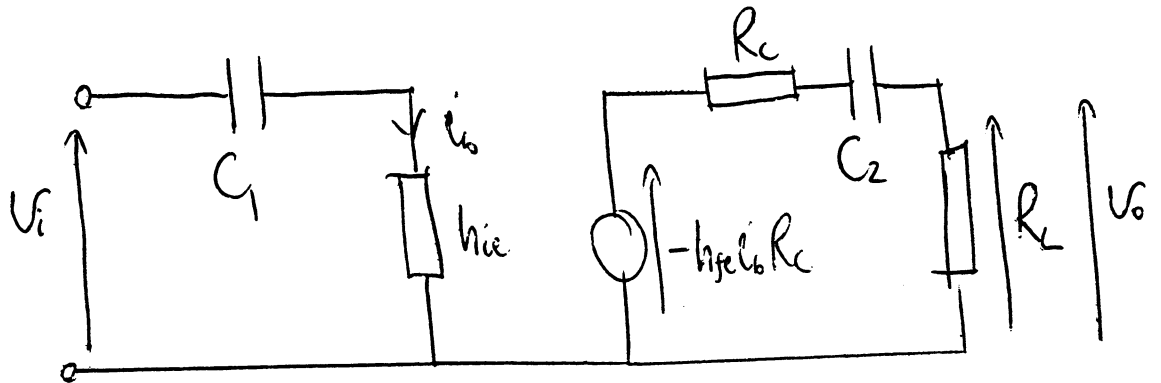- c) At low frequencies the reactances of C_1 and C_2 increase. C_1 will reduce the base current, and C_2 is effectively in series with R_c . Both of these will cause the gain to be reduced.



As before, replace $h_{fe} i_b // R_c$ with $-h_{fe} i_b R_c$ in series with R_c

$$i_b = \frac{V_i}{h_{ie} + 1/j\omega C_1} \quad V_o = \frac{R_L}{R_L + R_c + 1/j\omega C_2} \times (-h_{fe} i_b R_c)$$

$$\frac{V_o}{V_i} = \frac{-h_{fe} R_c R_L}{(h_{ie} + 1/j\omega C_1)(R_L + R_c + 1/j\omega C_2)}$$

Check $\omega \rightarrow \infty$, $\frac{V_o}{V_i} \rightarrow \frac{-h_{fe}}{h_{ie}} \frac{R_c R_L}{R_c + R_L} = \frac{-h_{fe} R_c // R_L}{h_{ie}}$

ie tends towards mid-band gain.

- d) Notice that $h_{ie} = R_L + R_c$, and $C_1 = C_2$. For half-power,

$$\left(h_{ie}^2 + \left(\frac{1}{\omega C_1} \right)^2 \right)^{1/2} = \left((R_L + R_c)^2 + \left(\frac{1}{\omega C_2} \right)^2 \right)^{1/2} = \sqrt{2} h_{ie} (R_L + R_c)$$

$$\Rightarrow h_{ie}^2 + \left(\frac{1}{\omega C_1} \right)^2 = \sqrt{2} h_{ie}^2$$

$$\frac{1}{\omega C_1} = h_{ie} (\sqrt{2} - 1)^{1/2} \quad \omega = 47.1 \quad f = 15.5 \text{ Hz.}$$

2/ Two signals V_1 and V_2 can always be broken down as:-

$$V_1 = V_c + \frac{V_d}{2} \quad , \quad V_2 = V_c - \frac{V_d}{2}$$

where V_c is the average, or common-mode component of the signals


V_d is the difference between, or the differential components of the signals.

∴ The common-mode signal is of the form $V_1 = V_2$

The differential signal is of the form $V_1 = -V_2$.

In this application, the thermocouple signal is a differential signal of one order magnitude less than the mains interference, which is a common-mode signal. A differential amplifier is designed to have a much higher gain for differential than for common-mode signals, as required here.

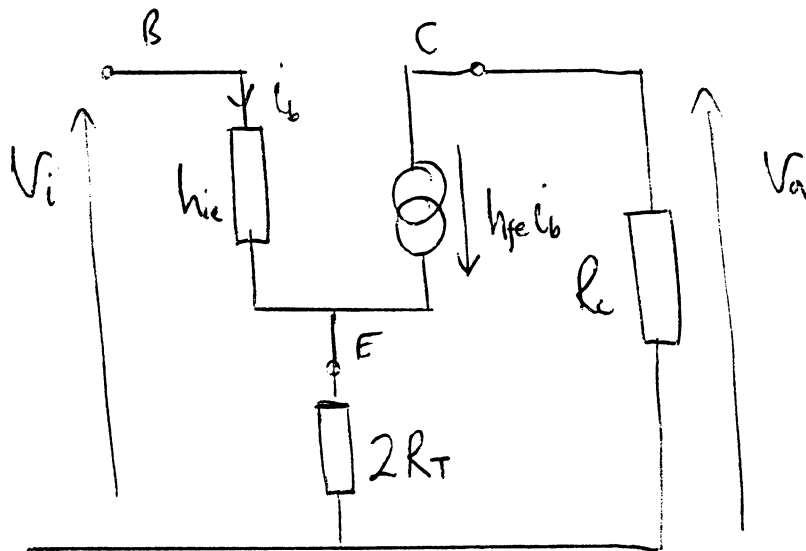b) $V_1 = V_2 \Rightarrow i_{e1} = i_{e2} \Rightarrow$ need to include R_T . To use half-circuit principles, replace R_T with two parallel resistors of value $2R_T$.



$$V_i = h_{ie} i_b + 2R_T (h_{fe} + 1) i_b$$

$$V_o = -h_{fe} i_b R_c$$

$$\underline{\underline{\frac{V_o}{V_i} = \frac{-h_{fe} R_c}{h_{ie} + 2R_T (h_{fe} + 1)}}}$$

Differential gain $\Rightarrow V_1 = -V_2 \Rightarrow i_{e1} = -i_{e2}$ so no small signal current in R_T , so emitters of transistors are at small-signal earth. \therefore Circuit for differential signal as above, but with $2R_T = 0$.

\therefore Find differential gain from common-mode gain, but with $R_T = 0$

$$\frac{V_o - V_b}{V_1 - V_2} = \underline{\underline{\frac{-h_{fe} R_c}{h_{ie}}}}$$

$$CMRR = \frac{A_{diff}}{A_{common-mode}} = \frac{-h_{fe} R_c / h_{ie}}{-h_{fe} R_c / (h_{ie} + 2R_T (h_{fe} + 1))} = \underline{\underline{\frac{h_{ie} + 2R_T (h_{fe} + 1)}{h_{ie}}}}$$

$$A_{diff} = 1000 = \frac{h_{fe} R_c}{h_{ie}} = \frac{200 R_c}{10^3}$$

$$\Rightarrow \underline{R_c = 5 \text{ k}\Omega}$$

$$CMRR = 2000 = \frac{h_{ie} + 2(h_{fe} + 1) R_T}{h_{ie}} = \frac{10^3 + 2(201) R_T}{10^3}$$

$$\Rightarrow \underline{R_T = 4973 \Omega}$$

- c) The new small-signal circuit valid for differential signals is the same as that for common-mode signals, except with $2R_T$ replaced by R_E .

$$\therefore \underline{A_{diff} = -\frac{h_{fe} R_c}{h_{ie} + R_E (h_{fe} + 1)}}$$

$$\text{Gain reduction factor} = \frac{-h_{fe} R_c / h_{ie}}{-h_{fe} R_c / (h_{ie} + R_E (h_{fe} + 1))}$$

$$= \frac{h_{ie} + R_E (h_{fe} + 1)}{h_{ie}}$$

$$= 1 + \frac{R_E (h_{fe} + 1)}{h_{ie}}$$

- d) Applying ideas from Theory of negative feedback, open-loop gain is reduced by factor " $1+AB$ " \Rightarrow input resistance is increased by the same factor

$$\therefore 1 + \frac{R_E (h_{fe} + 1)}{h_{ie}} = 10 \quad \underline{R_E = 44.8 \Omega}$$

4/ Generate as a.c. because transformers can be used to step up the voltage for transmission, enabling less losses (high voltage \Rightarrow low current \Rightarrow reduced I^2R losses in lines)

Three-phase is chosen to increase power output for given size of generator, but without excessive conductors needed to transmit the power.

i) Δ load: $V_{ph} = V_{line} = 415V$

$$P_{\Delta} = \frac{3V_{ph}^2}{R} = \frac{3 \times 415^2}{10} = \underline{51.7 \text{ kW}}$$

$$Q_{\Delta} = \frac{3V_{ph}^2}{X_L} = \frac{3 \times 415^2}{10} = 51.7 \text{ kVAR}$$

λ load: $V_{ph} = V_{line} / \sqrt{3} = 240V$

$$I_{ph} = \frac{V_{ph}}{|Z|} = \frac{240}{(10^2 + 5^2)^{1/2}} = 21.43 \text{ A}$$

$$P_{\lambda} = 3I_{ph}^2 R = \underline{13.8 \text{ kW}}$$

$$Q_{\lambda} = -3I_{ph}^2 X_c = -6.9 \text{ kW}$$

ii) \oint Total power = $P_{\Delta} + P_{\lambda} = 65.5 \text{ kW}$

$$\text{Total reactive power} = Q_{\Delta} + Q_{\lambda} = 44.8 \text{ kVAR}$$

$$\therefore \text{Total apparent power} = (P^2 + Q^2)^{1/2} = 79.4 \text{ kVA}$$

$$S = \sqrt{3} V_L I_L \Rightarrow I_L = \frac{79.4 \times 10^3}{\sqrt{3} \times 415} = \underline{110.4 \text{ A}}$$

$$iii) \cos\phi = \frac{P}{S} = \frac{65.5}{79.4} = \underline{\underline{0.825 \text{ lagging}}}$$

$$\text{Star-connected capacitors} \Rightarrow V_{cap} = V_L / \sqrt{3} = 240 \text{ V}$$

$$Q_{cap} = 3 \frac{V_{ph}^2}{X_c} = \frac{3 \times (415/\sqrt{3})^2}{1/\omega C} = \omega C \times 415^2$$

$$= 100\pi \times 415^2 \times C = 54.1 \times 10^6 \text{ C.}$$

$$\text{For unity power factor, } Q_{cap} = Q_{load} = 44.8 \times 10^3$$

$$\therefore \underline{\underline{C = 828 \mu\text{F}}}$$

$$\text{Now, } S = P \text{ since } Q = 0 \text{ i.e. } S = 65.5 \text{ kVA}$$

$$S = \sqrt{3} V_L I_L \Rightarrow I_L = 91.1 \text{ A.}$$

$$\% \text{ reduction} = \frac{110.4 - 91.1}{110.4} \times 100 = \underline{\underline{17.5\%}}$$

For 0.95 lagging power factor, new total reactive power = $P \tan\phi$

$$\text{where } \cos\phi = 0.95 \Rightarrow Q_{total} = 21.5 \text{ kVAR}$$

$$\therefore Q_{cap} = 44.8 \text{ kVAR} - 21.5 \text{ kVAR} = 23.3 \text{ kVAR}$$

$$= 54.1 \times 10^6 \text{ C}$$

$$\underline{\underline{C = 430 \mu\text{F}}}$$

$$S = (P^2 + Q^2)^{1/2} = (65.5^2 + 21.5^2)^{1/2} = 68.9 \text{ kVA}$$

$$\sqrt{3} V_i I_i = 68.9 \times 10^3 \Rightarrow I_i = 95.9 \text{ A.}$$


$$\% \text{ reduction} = \frac{110.4 - 95.9}{110.4} \times 100\% = 13.1\%$$

Correcting p.f. from 0.825 \rightarrow 0.95 reduces losses in transmission by $\left(\frac{95.9}{110.4}\right)^2 = 75.5\%$


Correcting p.f. from 0.825 \rightarrow 1 reduces losses in transmission by $\left(\frac{91.1}{110.4}\right)^2 = 68.1\%$, but requires almost twice the size of capacitance.

\therefore For an ^{extra} reduction in losses of 7.4%, the power factor correction capacitors will cost twice as much, and the 'pay-back' period therefore may not justify correction to unity.

4 a)

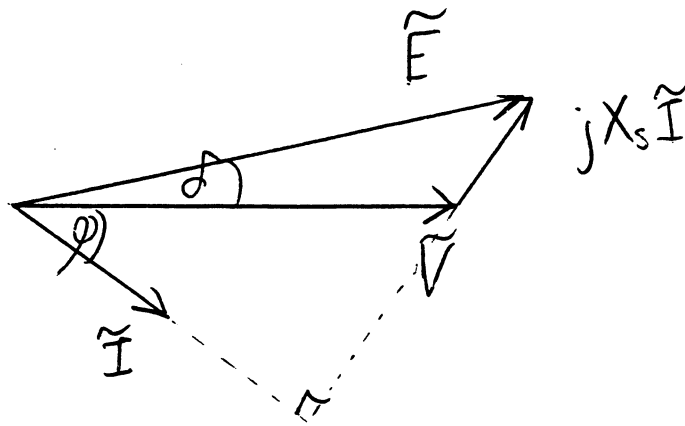

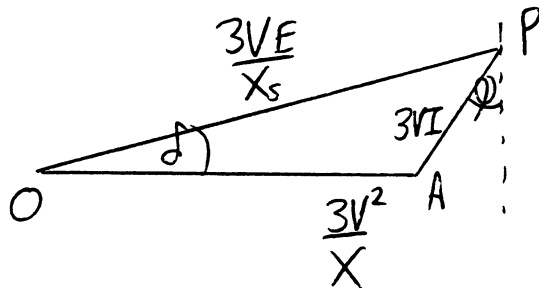Phasor diagram for a typical operating point when generating has its sides scaled by $3V/X_s$:



Now the limits on P_{max} , VA, excitation and stability can all be marked on to give the operating chart.

b) $V = 60 \text{ kV line} \Rightarrow V_{ph} = \frac{60 \text{ kV}}{\sqrt{3}} = 34.6 \text{ kV}$

OA is fixed at $\frac{3V^2}{X_s} = \frac{3 \times (34.6 \times 10^3)^2}{5} = 720 \times 10^6$


Maximum possible length $AP_{max} = 1000 \times 10^6$, since $AP = 3VI$, and $3VI$ has a maximum value equal to the generator VA rating.

$$E_{max} = 135 \text{ kV line} = \frac{135}{\sqrt{3}} \text{ kV phase} = 77.9 \text{ kV}$$

$$\therefore \text{Maximum length of OP} = \frac{3VE_{max}}{X_s} = \frac{3 \times 34.6 \times 10^3 \times 77.9 \times 10^3}{5}$$

$$= 1620 \times 10^6$$

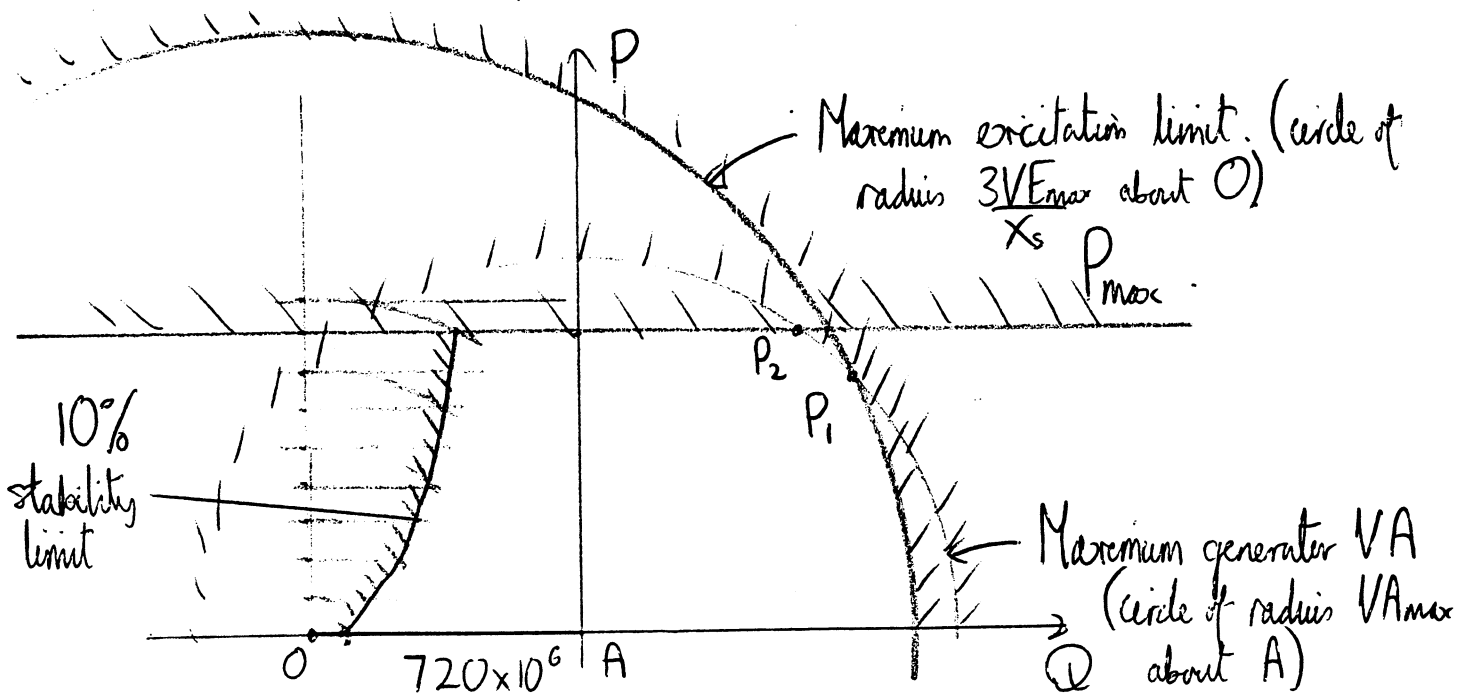Choose scale of 1 cm $\equiv 200 \times 10^6$



$P_{max} = 800 \text{ MW} \Rightarrow$ horizontal line at 800×10^6 since $P = 3VI \cos \phi$, which is the vertical projection of the point P.

10% stability limit $\Rightarrow \Delta P = 10\% \times \text{rated VA} = 100 \text{ MW}$ without losing synchronism.

ii) Circle of radius $V A_{max}$ about A - limit is due to the maximum value of current in the stator windings which can occur before the winding overheats due to $I^2 R$ losses

Circle of radius $3V E_{max} / X_s$ about O - limit due to maximum excitation voltage, which in turn is limited by the maximum field current which can flow in the rotor winding before it overheats due to $I^2 R$ losses.

Horizontal line at P_{max} is a limit on the maximum real power which the generator can produce, which in turn is limited by the prime-mover.


Stability margin - this prevents the generator losing synchronism when a step change in demanded power occurs, by allowing the load angle δ to swing to 90° .

iii) Rated MVA can be delimited over power factors ranging from the point P_1 to the point P_2 .

P_2 corresponds to the intersection of $(3VI)_{max}$ and P_{max}

$$\Rightarrow S = 1000 \text{ MVA}, P = 800 \text{ MW} \therefore \cos \phi = \frac{P}{S} = \underline{\underline{0.8 \text{ lagging}}}$$


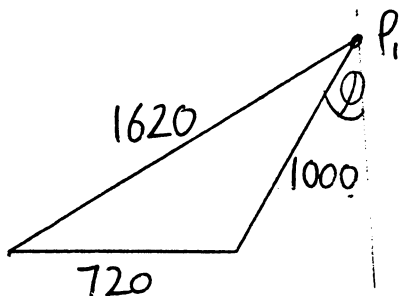
P_1 is the intersection of $(3VI)_{max}$ with $\left(\frac{3VE}{X_s}\right)_{max}$



Pythagoras:

$$1620^2 = (1000 \cos \phi)^2 + (720 + 1000 \sin \phi)^2$$
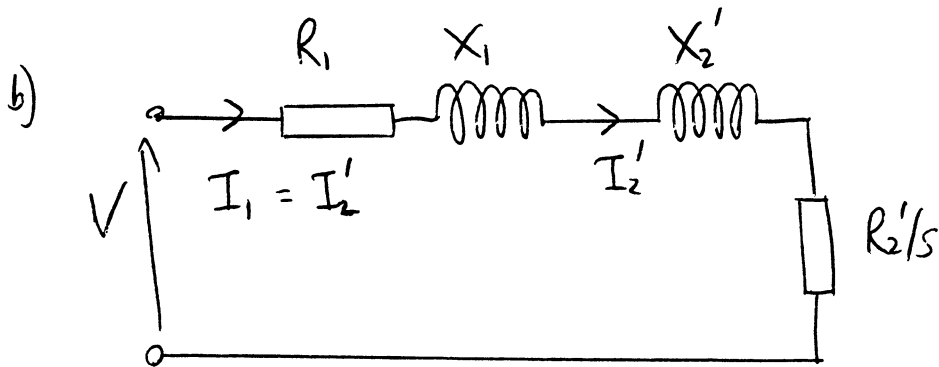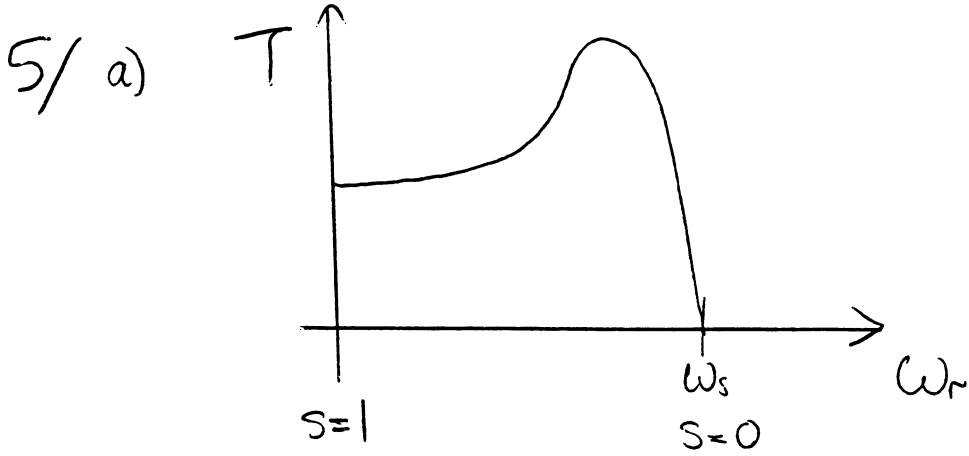
$$\Rightarrow \cancel{\cos \phi} \quad \sin \phi = 0.768 \quad \underline{\underline{\cos \phi = 0.64 \text{ lagging.}}}$$



$$P_{in} = 3 I_2'^2 (R_1 + R_2'/s)$$

$$P_{loss} = 3 I_2'^2 (R_1 + R_2')$$

$$\therefore P_{out} = P_{in} - P_{loss} = 3 I_2'^2 R_2' \frac{(1-s)}{s}$$

This output power is the power which is converted to mechanical power

$$\Rightarrow T \omega_r = T (1-s) \omega_s = 3 I_2'^2 R_2' \frac{(1-s)}{s}$$

$$\Rightarrow T = \frac{3 I_2'^2 R_2'}{\omega_s s}$$

$$I_2'^2 = \frac{V^2}{(R_1 + R_2'/s)^2 + (X_1 + X_2')^2} \Rightarrow T = \frac{3V^2}{\omega_s (R_1 + R_2'/s)^2 + (X_1 + X_2')^2} \times$$

c) Maximum torque occurs when maximum power is 'consumed' in R_2'/s .

By maximum power transfer theorem, source impedance = load resistance

$$\Rightarrow (R_1^2 + (X_1 + X_2')^2)^{1/2} = \frac{R_2'}{s_{max}}$$

$$s_{max} = \frac{R_2'}{(R_1^2 + (X_1 + X_2')^2)^{1/2}}$$

d)
$$s_{max} = \frac{1.4}{(1^2 + (2 + 2.4)^2)^{1/2}} = 0.31$$

4 pole motor \Rightarrow synchronous speed = $\frac{60f}{p} = \frac{60 \times 50}{2} = 1500 \text{ rpm}$

$\therefore N = (1-s)N_s = (1-0.31) \times 1500 = \underline{1035 \text{ rpm}}$

Maximum torque is the torque evaluated at $s = s_{max}$. $V = V_{ph} = \frac{415}{\sqrt{3}}$
 = 239.6 V (star-connected)

$$\therefore T_{max} = \frac{3 \times (415/\sqrt{3})^2}{(1 + 1.4/0.31)^2 + (2 + 2.4)^2} \times \frac{1.4}{0.31} \times \frac{1}{1500 \times 2\pi/60}$$

$$= \underline{99.5 \text{ Nm}}$$

e) Need s_{max} to occur at 1, since $s=1$ at starting

$$\Rightarrow 1 = \frac{R_2' + R_{extra}}{(R_1^2 + (X_1 + X_2')^2)^{1/2}} = \frac{1.4 + R_{extra}}{4.51}$$

$$R'_{extra} = 3.11 \Omega$$

This is the extra resistance referred to the stator.

$$N_s : N_r = 2 : 1$$

$$\Rightarrow R_{extra} = \left(\frac{N_r}{N_s}\right)^2 R'_{extra} = \left(\frac{1}{2}\right)^2 \times 3.11 = \underline{\underline{0.778 \Omega}}$$

A cage induction motor does not have slip-rings and brushes, which enable extra resistance to be added in series. To increase starting resistance, cage motors use specially shaped slots which exploit skin effect to give a high starting resistance (since rotor currents are at supply frequency when $S=1$), or alternatively, a double cage, with a high resistance starting cage, and a low resistance running cage.

$$G/a) \quad v = \frac{1}{\sqrt{LC}} \quad 2.5 \times 10^8 = \frac{1}{\sqrt{80 \times 10^{-12} \times L}}$$

$$\underline{L = 0.2 \mu\text{H/m.}}$$

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{0.2 \times 10^{-6}}{80 \times 10^{-12}}} = \underline{50 \Omega}$$

$$v = f \lambda \quad 2.5 \times 10^8 = 100 \times 10^6 \lambda$$

$$\underline{\lambda = 2.5 \text{ m}}$$

- b) These equations mean that the transmission line supports forwards- and backwards-travelling voltage and current waves, of angular frequency ω , and wavelength $2\pi/\beta$.

At the load, $x = 0$

$$\bar{V}(0, t) = (\bar{V}_f + \bar{V}_r) e^{j\omega t} \quad (1)$$

$$\bar{I}(0, t) = (\bar{I}_f + \bar{I}_r) e^{j\omega t} \quad (2)$$

$$\bar{I}_f = \frac{\bar{V}_f}{Z_0}, \quad \bar{I}_r = -\frac{\bar{V}_r}{Z_0}$$

Substitute for \bar{V}_f and \bar{V}_r in (1)

$$\bar{V}(0, t) = (Z_0 \bar{I}_f - Z_0 \bar{I}_r) e^{j\omega t}$$

Ohms law for the load:

$$\bar{I}(0, t) = \frac{\bar{V}(0, t)}{\bar{Z}_L} \Rightarrow (\bar{I}_f + \bar{I}_r) e^{j\omega t} = \frac{(Z_0 \bar{I}_f - Z_0 \bar{I}_r) e^{j\omega t}}{\bar{Z}_L}$$

$$\bar{Z}_L \bar{I}_f + \bar{Z}_L \bar{I}_r = Z_0 \bar{I}_f - Z_0 \bar{I}_r$$

$$\frac{\bar{I}_r}{\bar{I}_f} = \bar{\rho}_I = \frac{Z_0 - \bar{Z}_L}{Z_0 + \bar{Z}_L}$$

$$\bar{\rho}_V = \frac{\bar{Z}_L - Z_0}{\bar{Z}_L + Z_0} \quad (\text{Data-book})$$

$$c) \quad \bar{V}(x,t) = \bar{V}_f e^{j(\omega t - \beta x)} + \bar{\rho}_V \bar{V}_f e^{j(\omega t + \beta x)}$$

$$\bar{I}(x,t) = \bar{I}_f e^{j(\omega t - \beta x)} + \bar{\rho}_I \bar{I}_f e^{j(\omega t + \beta x)}$$

$$\begin{aligned} \frac{\bar{V}(x,t)}{\bar{I}(x,t)} &= \bar{Z}(x) = \frac{\bar{V}_f}{\bar{I}_f} \frac{(e^{j\beta x} + \bar{\rho}_V e^{j\beta x}) e^{j\omega t}}{(e^{-j\beta x} + \bar{\rho}_I e^{j\beta x}) e^{j\omega t}} \\ &= Z_0 \frac{e^{-j\beta x} + \bar{\rho}_V e^{j\beta x}}{e^{-j\beta x} + \bar{\rho}_I e^{j\beta x}} \end{aligned}$$

$$d) \quad \text{Find } \bar{Z}(-2.5) \quad \beta = \frac{2\pi}{\lambda}, \text{ and } \lambda = 2.5 \text{ m}$$

$$\therefore \beta x = -2\pi$$

$$\therefore \bar{Z}(-2.5) = Z_0 \frac{e^{j2\pi} + \bar{\rho}_V e^{-j2\pi}}{e^{j2\pi} + \bar{\rho}_I e^{-j2\pi}}$$

$$= 50 \frac{(1 + \bar{\rho}_V)}{(1 + \bar{\rho}_I)}$$

$$= 50 \frac{\left(1 + \frac{\bar{Z}_L - Z_0}{\bar{Z}_L + Z_0}\right)}{1 + \frac{Z_0 - \bar{Z}_L}{Z_0 + \bar{Z}_L}}$$

$$= 50 \cdot \frac{2\bar{Z}_L}{2Z_0} = \bar{Z}_L = (30 + j40) \Omega.$$

i.e. If the length of the transmission line is equal to a wavelength (or multiple of a wavelength), the impedance presented by the line plus load at the start of the line is equal to the load impedance.

$$7/ \quad \underline{E} = \underline{u}_x E_0 e^{j(\omega t - \beta z)}$$

$$\frac{\partial \underline{E}}{\partial z} = (-j\beta) \underline{u}_x \underline{E}, \quad \frac{\partial^2 \underline{E}}{\partial z^2} = -\beta^2 \underline{E}$$

$$\frac{\partial \underline{E}}{\partial t} = -j\omega \underline{E}, \quad \frac{\partial^2 \underline{E}}{\partial t^2} = -\omega^2 \underline{E}$$

∴ For \underline{E} to be a solution:-


$$-\beta^2 \underline{E} - \epsilon_0 \mu_0 (-\omega^2 \underline{E}) = 0$$

$$\omega^2 \epsilon_0 \mu_0 = \beta^2$$

$$\underline{\omega / \beta = 1 / \sqrt{\epsilon_0 \mu_0}}$$

But, ω / β is the speed of propagation of the wave
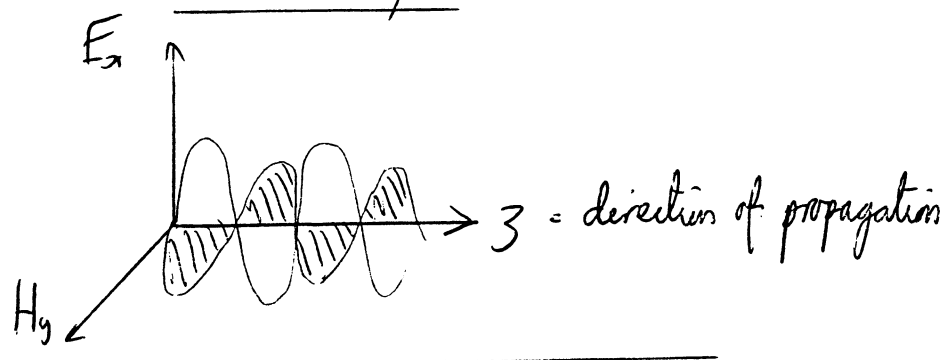
$$\Rightarrow \underline{v = 1 / \sqrt{\epsilon_0 \mu_0}}$$



$$\underline{\rho_0 = \frac{|E|}{|H|} = \sqrt{\frac{\mu_0}{\epsilon_0}}}$$

$$\underline{\therefore \underline{H} = \underline{u}_y \frac{E_0}{\rho_0} e^{j(\omega t - \beta z)}}$$

$$\text{Power pu area} = \left| \text{Re} \left\{ \frac{1}{2} \underline{E} \times \underline{H}^* \right\} \right|$$

$$= \left| \text{Re} \left\{ \frac{1}{2} \underline{u}_3 \underline{E}_0 e^{j(\omega t - \beta z)} \times \underline{u}_y \frac{\underline{E}_0}{\eta_0} e^{-j(\omega t - \beta z)} \right\} \right|$$

$$= \left| \underline{u}_3 \frac{\underline{E}_0^2}{2\eta_0} \right| = \underline{\underline{\frac{\underline{E}_0^2}{2\eta_0}}}$$

$$\text{Power pu. area} = \frac{10^{-3}}{\pi \times (0.5 \times 10^{-3})^2} = 1273 \text{ Wm}^{-2} = \frac{\underline{E}_0^2}{2\eta_0}$$

$$\eta_0 = \sqrt{\frac{\mu_0}{\epsilon_0}} = \sqrt{\frac{4\pi \times 10^{-7}}{8.85 \times 10^{-12}}} = 376.8 \Omega$$

$$\therefore 1273 = \frac{\underline{E}_0^2}{2 \times 376.8} \Rightarrow \underline{E}_0 = \underline{\underline{980 \text{ Vm}^{-1}}}$$

$$\underline{H} = \frac{\underline{E}_0}{\eta_0} = \frac{980}{376.8} = \underline{\underline{2.6 \text{ Am}^{-1}}}$$

$$\begin{aligned} \text{Power reflection coefficient} &\equiv \rho_V^2 = \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right)^2 = \left(\frac{\eta_L - \eta_0}{\eta_L + \eta_0} \right)^2 \\ &= \left(\frac{\sqrt{\frac{\mu_0}{3\epsilon_0}} - \sqrt{\frac{\mu_0}{\epsilon_0}}}{\sqrt{\frac{\mu_0}{3\epsilon_0}} + \sqrt{\frac{\mu_0}{\epsilon_0}}} \right)^2 = \left(\frac{1/\sqrt{3} - 1}{1/\sqrt{3} + 1} \right)^2 = 0.072 \end{aligned}$$

$$\therefore \text{Reflected power} = 0.072 \text{ mW}, \text{ transmitted power} = 0.928 \text{ mW.}$$

$$\therefore \text{Transmitted power pu area} = \frac{0.928 \times 10^{-3}}{\pi \times (0.5 \times 10^{-3})^2} = \underline{\underline{1182 \text{ Wm}^{-2}}}$$

$$\text{Power p.u. area} = \frac{E^2}{2\eta_L}$$

$$\eta_L = \sqrt{\frac{\mu_0}{3\epsilon_0}} = \sqrt{\frac{4\pi \times 10^{-7}}{3 \times 8.85 \times 10^{-12}}}$$
$$= 217.6 \Omega$$

$$\therefore 1182 = \frac{E^2}{2 \times 217.6} \Rightarrow \underline{E = 717 \text{ Vm}^{-1}}$$

$$H = \frac{E}{\eta_L} = \frac{717}{217.6} = \underline{3.30 \text{ Am}^{-1}}$$

T Rack

June 1998

1998 Part 1B - PAPER 5 - ANSWERS

1. a) $i_c = h_{fe}i_b + h_{oe}v_{ce}$ $v_{be} = h_{ie}i_b + h_{re}v_{ce}$ b) $R_C = 400 \Omega$; $R_B = 154 \text{ k}\Omega$

c) $R_L = 400 \Omega$; Mid-band gain $\frac{v_o}{v_i} = -\frac{h_{fe}R_C R_L}{h_{ie} + R_C + R_L} = -50$

d) $\frac{v_o}{v_i} = -\frac{h_{fe}R_C R_L}{(h_{ie} + 1/j\omega C_1)(R_L + R_C + 1/j\omega C_2)}$ e) $f_{3dB} = 15.5 \text{ Hz}$


2. b) Common mode gain $= -\frac{h_{fe}R_C}{h_{ie} + 2R_T(h_{fe} + 1)}$; Differential gain $= -\frac{h_{fe}R_C}{h_{ie}}$;

$R_C = 5 \text{ k}\Omega$; $R_T = 4.97 \text{ k}\Omega$ c) Differential gain $= -\frac{h_{fe}R_C}{h_{ie} + R_E(h_{fe} + 1)}$;

Gain reduction factor $= 1 + \frac{R_E(h_{fe} + 1)}{h_{ie}}$ d) $R_E = 44.8 \Omega$

3. b) (i) $P_{\text{delta}} = 51.7 \text{ kW}$; $P_{\text{star}} = 13.8 \text{ kW}$ (ii) $I_{\text{line}} = 110.4 \text{ A}$
 (iii) Power factor = 0.825 lagging c) (i) $828 \mu\text{F}$; (ii) $430 \mu\text{F}$; 17.5 % and 13.1 %
 reduction in line current respectively.

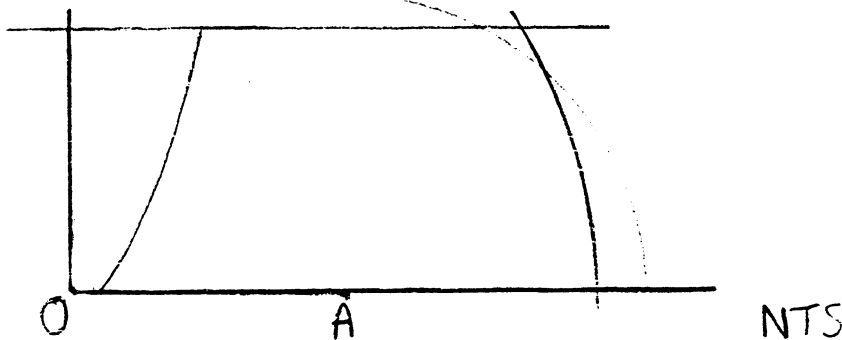4. b) i) Prime-mover limit - horizontal line at 800×10^6 ; Stator heating limit - circle of radius 1000×10^6 , centre A; Rotor heating limit - circle of radius 1620×10^6 , centre O; Length OA = 720×10^6 ; Stability limit - intersection of circles and horizontal lines drawn at increments of 10 % of rated MVA = 100×10^6 .



- (iii) Power factor between 0.64 and 0.8 lagging.

5. d) $T_{\text{max}} = 99.5 \text{ Nm}$; $N = 1035 \text{ rpm}$ e) Extra rotor resistance = 0.778Ω

6. a) $L = 0.2 \mu\text{Hm}^{-1}$; $Z_0 = 50 \Omega$; Wavelength = 2.5 m d) $Z_{\text{in}} = Z_L = (30 + j40) \Omega$ -
 this is because the transmission line is exactly one wavelength long.

7. a) $\omega^2 \epsilon_0 \mu_0 = \beta^2$ b) \mathbf{E} , \mathbf{H} and direction of propagation mutually orthogonal, such

that $\mathbf{E} \times \mathbf{H}$ gives direction of propagation; $\eta_0 = \frac{|\mathbf{E}|}{|\mathbf{H}|} = \sqrt{\frac{\mu_0}{\epsilon_0}}$; $\bar{\mathbf{H}} = \mathbf{u}_y \frac{E_0}{\eta_0} \exp j(\omega t - \beta z)$

c) $\mathbf{E} = 980 \text{ Vm}^{-1}$; $\mathbf{H} = 2.6 \text{ Am}^{-1}$ d) Power pu area = 1182 Wm^{-2} ; $\mathbf{E} = 717 \text{ Vm}^{-1}$;
 $\mathbf{H} = 3.30 \text{ Am}^{-1}$