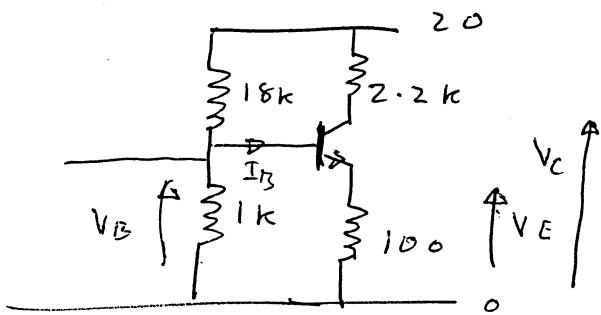


1 (a) $h_{FE} = \infty, I_B = 0$

$$V_B = 1.0526$$

$$V_E = \underline{\underline{3.52 V}}$$

$$I_E = I_C = 3.52 \text{ mA}$$



$$V_C = 20 - 2.2 \times 3.52$$

$$= \underline{\underline{12.256 V}}$$

(b) $V_B = 1.0526 - 18k \parallel 1k \cdot I_B = 1.0526 - 9474 I_B$
 $I_B \text{ in mA.}$

$$I_E = \frac{10 V_E}{101}, I_B = \frac{V_E}{10} = \frac{10 V_E}{101}$$

$$V_E = 1.0526 - \frac{9474 V_E \times 10}{101} = 0.7$$

$$V_E = \frac{0.352}{1 + 0.9474 \times 10} \quad V_E = \underline{\underline{3.218 V}}$$

$$V_C = 20 - 2.2 \times 3.218 = \underline{\underline{12.920}}$$

(c). The maximum gain available (modulus) if R_E is not bypassed is 22 ($h_{FE} = \infty$). With a bypass capacitor (not shown in original!) the gain ~~will~~ will be much higher at m.f.

(d). With R_E bypassed, $i_B = \frac{V_1}{h_{FE}} = \frac{V_1}{200} \text{ mA}$

$$\frac{V_2}{V_1} = -2.2 \frac{V_1}{2} \times 150$$

$$= \underline{\underline{-1.65 \times 10^3}} = \underline{\underline{64 \text{ dB}}}$$

2 (a). Strictly depends on f. b. used. Ideal(?) answer:

- i. Gain made independent of exact parameters of Evans / Op amp.
- ii. Non linearity greatly reduced.
- iii. Bandwidth extended.
- iv. Affects input & output impedance.

Voltage f.b. at input R_i is High

Voltage f.b. at output R_o is Low

Current f.r. at input R_i is Low

Current f.r. at output R_o is High

(b). 3dB point when $\omega T = 1$, $\omega = \frac{1}{\sqrt{T}}$

\therefore 3dB b.w. is $\frac{1}{2\pi\sqrt{T}}$.

(c) Gen expression for gain with f.b. is

$$\begin{aligned}
 G &= \frac{A}{1 + BA} = \frac{A_0/(1+j\omega T)}{1 + BA_0/(1+j\omega T)} \\
 &= \frac{A_0}{1 + j\omega T + BA_0} = \frac{A_0/(1+BA_0)}{1 + \frac{j\omega T}{1+BA_0}} \\
 &= \frac{G_0}{1 + j\omega T/(1+BA_0)}
 \end{aligned}$$

\therefore B.w. increased by a factor of $1 + BA_0$.

$$\frac{1}{2\pi\sqrt{T}} = 10 \text{ Hz}$$

$$\text{Ans(1). } \underline{\underline{10_{m0}(001) \text{ kHz}}}$$

$$\text{Ans(2). } \underline{\underline{1.01 \text{ kHz}}}$$

2 | cont - (d)

(1). $B = 0.1$; gain at 3dB point = 67.07

With amplitude v_i at 100 kHz (approx),

$$\text{output slew rate} = 7.07 \times 2\pi \times v_i \times 100,000 = 10^5$$

$$\therefore v_i = 22.5 \text{ mV}. \quad \text{Gain} \times 22.5 \text{ mV} \ll 15 \text{ V}$$

\therefore slew-rate limited + max input signal is $\approx \underline{\underline{4.5 \text{ mV}_\text{p-p}}}$

(2) $B = .001$; gain at 3dB point = 7.07

slew rate limitation has same $\frac{\text{input}}{\text{p-p/voltage}}$ as

above but ~~gates~~ is ~~not~~ output is now $\approx 32 \text{ V}$

p-p. \therefore slew rate unimportant. Maximum p-p


input is $\therefore < \frac{20}{7.07} \text{ V}$, i.e. $< \underline{\underline{2.8 \text{ mV p-p}}}$

- 3 (a) i. Lots of room for 3 sets of coils in a generator.
 Power required over a cycle constant. Smooth running.
 ii. Since most loads are approximately balanced can
 get away with 3 heavy cables + one lighter one.
 c.f. 6 heavy cables for 3x single phase supplies.

(b).

$$I_{\Delta} = \frac{415}{15 + j20}; |I_{\Delta}|^2 = 276 A^2$$

$$I_{\lambda} = \frac{240}{10 + 10j}; |I_{\lambda}|^2 = 288 A^2$$

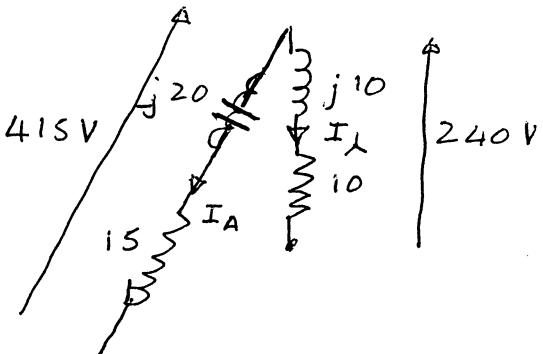

Evaluate Power + VARs for each.

$$\Delta \quad P = 4140 \text{ W} \quad VARS = -5520 \text{ VARs}$$

$$\lambda \quad \underline{P = 2880 \text{ W}} \quad \underline{VARS = 2880 \text{ VARs}}$$

$$7020 \text{ W} \quad - 2640 \text{ VARs}$$


$$\therefore \text{Total power} = 3 \times 7020 = \underline{\underline{21.06 \text{ kW}}}$$

$$\text{Per phase, VA} = \sqrt{P^2 + Q^2} = 7500 \text{ VA.}$$

$$\text{Line current} = \frac{7500}{240} = \underline{\underline{31.25 \text{ A.}}}$$

$$\text{P.F.} = \cos \tan^{-1} \frac{2640}{7020} = \underline{\underline{0.936}}$$

(c).

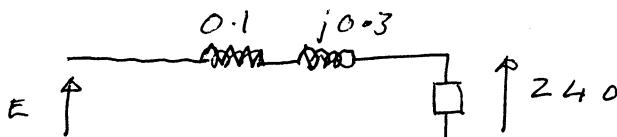


From conservation of Watt + VARs:

$$(E \times 31.25)^2 = (7020 + 31.25^2) + (-2640 + (3 \times 31.25^2))$$

$$E \times 31.25 = 7989.6, E = 256 \text{ V}$$

$$\therefore \text{Line voltage} = \underline{\underline{443 \text{ V}}}$$

4 (a). Book work, but

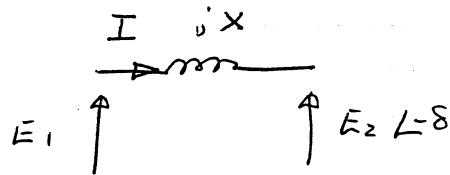

$$I = \frac{E_1 - E_2(\cos\delta - j\sin\delta)}{jX}$$

Power to E_2 = power from E_1 - pure reactance.

$$\text{Power from } E_1 = R \{ E_1 I^* \} = R \left\{ \frac{E_1^2 - E_1 E_2 (\cos\delta + j\sin\delta)}{-jX} \right\}$$

Only R.P. from 2nd term in bracket

$$= \underline{\underline{\frac{E_1 E_2 \sin\delta}{X}}}$$

(b).

Per phase: 100 MW ; $\frac{33}{\sqrt{3}}$ kV at unity p.f. \rightarrow

$$|I| = 4249 \text{ A.}$$

$$E = 19.05 \text{ kV} + j 4249 ; |E| = \underline{\underline{19.52 \text{ kV}}}$$

$$\sin\delta \text{ from } \frac{19.52 \times 19.05 \times 10^6 \times \sin\delta}{|I|} = 10^8$$

$$\underline{\underline{\delta = 15.6^\circ}}$$

$$(c). \text{ New } E = 19.52 \times 1.15 = 22.45 \text{ kV.}$$

$$\text{New } \sin\delta \text{ from } \frac{22.45 \times 19.05 \times 10^6}{|I|} = 120 \times 10^6$$

$$\underline{\underline{\delta = 16.3^\circ}}$$

$$\text{From (a), } I = \frac{22.45 - 19.05(\cos 16.3 - j \sin 16.3)}{jX} \text{ kA}$$

$$|I| = \sqrt{14.165 + j 5.345} = \underline{\underline{6776 \text{ A}}}$$

$$\text{New p.f.} = \frac{120 \text{ MW}}{19.05 \text{ kV} \times 6776 \text{ A}} = 0.9296.$$

Bonus*: From above, I lags E by $52.1^\circ - 90^\circ = 37.9^\circ$.
 V lags E by $16.3^\circ \therefore I$ lags V by $21.6^\circ - \cos\phi = 0.9296 \text{ lag}$.

5) a) The table giving $V_a(V)$ vs $I_f(A)$ is the open-circuit characteristic of the motor, and enables $K\phi(I_f)$ to be found:-

On open-circuit $E_a = V_a = K\phi\omega$

$$\Rightarrow K\phi = V_a/\omega \text{ where } \omega \text{ is the speed at which the test was carried out} = 1200 \times 2\pi/60 = 125.7 \text{ rad s}^{-1}$$

With $I_f = 4A$, $K\phi = 300/125.7 = 2.39 \text{ Vs.}$

$$E_{12} = K\phi\omega = 300 \text{ V at } 1200 \text{ rpm}$$

$$i_a = \frac{V_a - E_a}{R_a} = \frac{350 - 300}{1} = 50 \text{ A.}$$

$$T = K\phi i_a = 2.39 \times 50 = \underline{119.4 \text{ Nm}}$$

b) Use linear interpolation to find V_a at $I_f = 7A$ from o.c. dat

$$V_a = 420 + \frac{510 - 420}{2} = 465 \text{ V}$$

$$K\phi = 465/2.39 \times 125.7 = 3.70$$

$$T = K_P i_a = 119.4 \quad (\text{same as part a})$$

$$\Rightarrow i_a = \frac{119.4}{3.7} = 32.3 \text{ A}$$

$$E_a = V_a - i_a R_a = 350 - 1 \times 32.3 \\ = 317.7$$

$$Q_a = K_D \omega \Rightarrow \omega = \frac{317.7}{3.70} = 85.9 \text{ rad s}^{-1} = 820 \text{ rpm}$$

To reduce speed, increase I_f . However, K_D is limited by saturation to approx $600/125.7 = 4.77$ (taking maximum I_f from O.C. characteristic). - other answers possible e.g. use $K_D = \frac{615}{125.7}$ at $I_f = 14 \text{ A}$

$$i_a = T/K_P = 119.4/4.77 = 25.0 \quad = 4.89$$

$$E_a = 350 - 25 \times 1 = 325 = K_D \omega$$

$$\Rightarrow \omega = \frac{325}{4.77} = 68.1 \text{ rad s}^{-1} = 651 \text{ rpm.}$$

To reduce speed further use armature voltage control or reduce armature voltage.

6 (a). $v = \frac{1}{\sqrt{LC}} = \underline{\underline{2.11 \times 10^8 \text{ m/s}}}$

$$Z = \sqrt{\frac{L}{C}} = \underline{\underline{63.2 \Omega}}$$

$$\sqrt{\epsilon_r} = \frac{3}{2.11} \quad \text{assuming } \mu_r = 1$$

$$\therefore \underline{\underline{\epsilon_r = 2.02}}$$

(b). A length of line of $\lambda/4$ will present an open circuit.

At 300 MHz, $\lambda = 703 \text{ mm}$

$$\therefore (1) \quad \underline{\underline{175.8 \text{ mm}}}$$

A length of line of $\lambda/2$ will present a s/c (ignore the trivial case of $L=0$)

$$\therefore (2) \quad \underline{\underline{351.7 \text{ mm}}}.$$

(c). The length of line beyond the resistor looks like an o.c. so the load looks like a $\lambda/4$ section terminated in 100Ω .

$$P = \frac{100 - 63.2}{100 + 63.2} = .2255, \text{ real.}$$


$$\text{The V.S.W.R.} = \frac{1 + .2255}{1 - .2255} = \frac{100}{63.2} = \underline{\underline{1.582.}}$$

(d). The input resistance of the line is $\frac{63.2^2}{100} = 39.9 \Omega$

$$\therefore \text{Input voltage} = \frac{100 \times 39.9}{63.2 + 39.9} = \frac{100}{100} = 38.7 \text{ V.}$$

$$\therefore \text{Power to line and also load} = \frac{38.7^2}{63.2} \text{ W} = \underline{\underline{23.7 \text{ W}}}$$

6

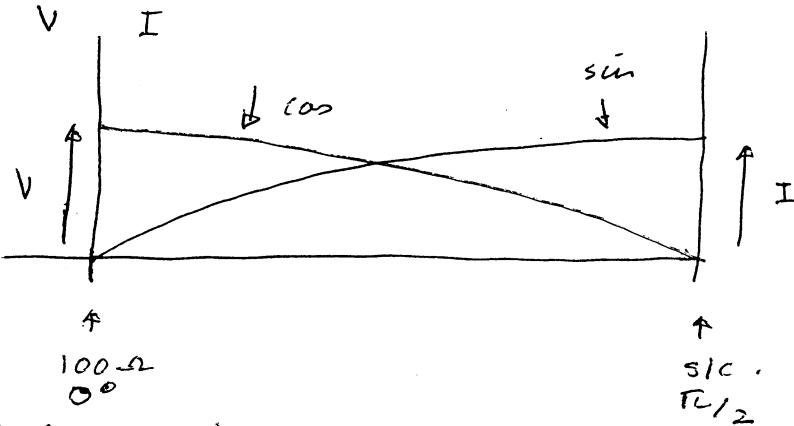

Standing waves as shown.

$$\text{For a series, } V = \sqrt{23.7 \times 100} = \underline{\underline{48.7V}}$$

$$I = \frac{48.7}{63.2} = \underline{\underline{.77A}}$$

7 (a) From $\nabla \times \underline{E} = - \frac{\partial \underline{B}}{\partial t} = - j\omega \mu_0 \underline{H}$

$\nabla \times \underline{E}$ has only one component $\rightarrow -i \cdot \frac{d \underline{E}_y}{dz}$; in x direction

$$\therefore -j\omega \mu_0 \underline{H} = -i \cdot -jB E_0 \exp(j(\omega t - Bz))$$

$$\therefore H_x = -\frac{i}{\mu_0 c} E_0 \exp(j(\omega t - Bz)) = -\frac{E_0}{Z_0} \exp(j(\omega t - Bz))$$

where $Z_0 = \sqrt{\frac{\mu_0}{\epsilon_0}}$.

$$\text{Mean power} = \text{Re} \left\{ \underline{E} \times \underline{H}^* \right\} = \frac{-E_0^2 \cdot i \times i}{Z_0} = \frac{E_0^2}{Z_0} k \quad \text{if } i \times i = -k$$

(b) Loop is \perp to direction of H \therefore |flux| through loop

$$= \frac{\pi a^2}{4} \cdot \mu_0 \frac{E_0}{Z_0} + |E_m| = \frac{\pi a^2 E_0}{4} \frac{\omega \mu_0}{Z_0}$$

$$= \frac{\pi a^2 E_0 \omega \sqrt{\mu_0 \epsilon_0}}{4} = \frac{\pi^2 a^2 E_0}{2\lambda}.$$

P is peak?

$$(c) \text{Power density at a distance } r = \frac{P}{2\pi r^2} = \frac{E_0^2}{Z_0} = \frac{E_0^2}{120\pi}$$

$$\therefore E_0^2 = \frac{60P}{r^2}.$$

Induced e.m.f. must be, in absence of receiver, given by

$$\frac{V_o^2}{4 \times 75} = 4 \times 10^{-9}; \quad V_o^2 = 1.2 \times 10^{-6} \quad V^2 = \left(\frac{\pi^2 a^2}{2\lambda} \right)^2 \cdot \frac{60P}{r^2}$$

$$2\lambda = 1 \text{ m}, \quad a = 0.15 \text{ m}, \quad P = 1 \text{ kW}$$

$$\therefore r^2 = \left(\frac{\pi^2 a^2}{2\lambda^2} \right)^2 \cdot \frac{6 \times 10^4}{1.2 \times 10^{-6}}, \quad r = \underline{\underline{49.6 \text{ km}}}.$$

(d) Can reduce induced e.m.f. by 2 \therefore can tilt by 60° .