

10/2/2000


IB Paper 5 June 2000 CRIB.

1/ a) Choose $V_{CE} = 10V$ since it's midway between 0V and 20V, and therefore allows equal output voltage swings in the positive and negative directions.

$$\frac{20 - V_{CE}}{R_L} = I_C \Rightarrow R_L = \frac{20 - 10}{20 \text{ mA}} = \underline{\underline{500 \Omega}}$$

$$\frac{20 - V_{BE}}{R_B} = I_B = \frac{I_C}{h_{FE}} \Rightarrow R_B = \frac{20 - 0.7}{20 \times 10^{-3} / 100} = \underline{\underline{96.5 \text{ k}\Omega}}$$

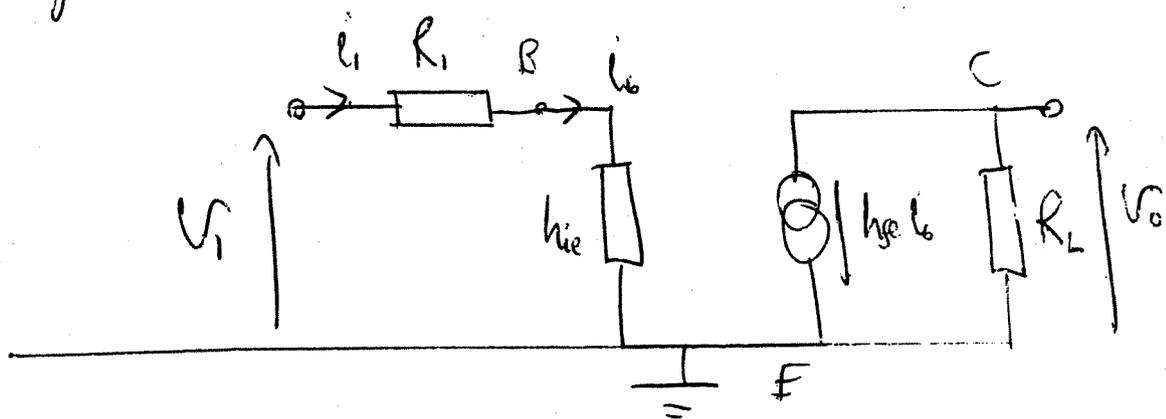b) Mid-band frequencies \Rightarrow assume $\frac{1}{j\omega C_1} \approx 0$. Also $R_S \Rightarrow h_{ie}$, so ignore R_S .



$$i_b = \frac{V_i}{R_1 + h_{ie}} \quad V_o = -h_{fe} i_b R_L = -\frac{h_{fe} V_i R_L}{R_1 + h_{ie}}$$

$$\Rightarrow \text{Gain} = \frac{V_o}{V_i} = \frac{-h_{fe} R_L}{R_1 + h_{ie}} = \frac{-100 \times 500}{5000} = \underline{\underline{-10}}$$

$$R_{in} = \frac{V_i}{i_i} = R_1 + h_{ie} = \underline{\underline{5 \text{ k}\Omega}}$$

$$R_o = \frac{V_o}{I_o/V_i=0} = R_L = \underline{\underline{500\Omega}}$$


c) At low frequencies capacitive reactance of C_1 is large, so I_b is reduced, thus reducing $h_{fe} I_b$ and therefore V_o .

$$I_b = \frac{V_i}{R_i + h_{ie} + \frac{1}{j\omega C_1}}$$

$\frac{V_o}{V_i}$ -3dB point is also when I_b is -3dB compared to mid-band value

$$\therefore R_i + h_{ie} = \frac{1}{\omega C}$$
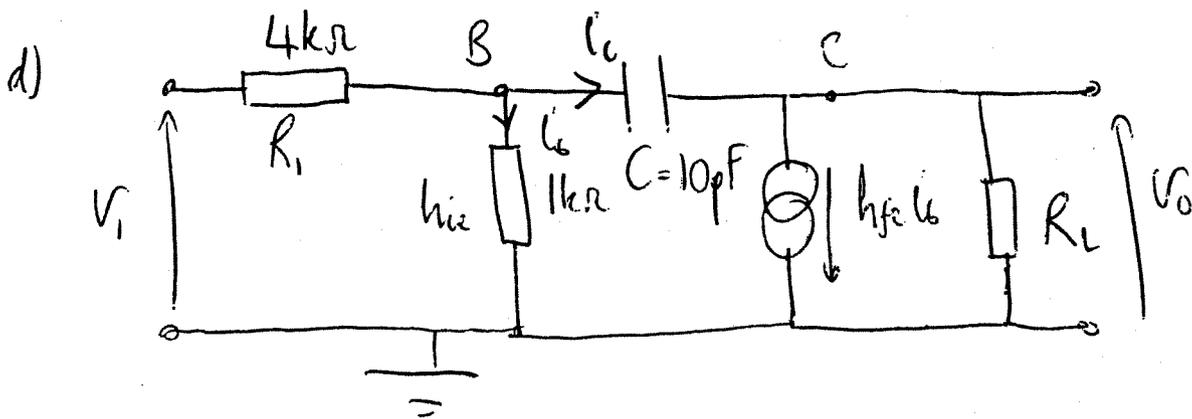
$$5 \times 10^{-3} = \frac{1}{2\pi \times 20 \text{ C}} \Rightarrow C = 1.59 \mu\text{F}$$



At high frequencies $\frac{1}{j\omega C}$ is small, and so I_b is reduced owing to shunting effect of C . In turn, $V_o \propto I_b$, and so gain is reduced.

Ignore capacitor current I_c in terms of its effect on the output, since $I_c \ll h_{fe} I_b$
 Ignore R_B as before since $\gg h_{ie}$.

Kirchoff's current law at B

$$\frac{V_i - h_{ie} i_b}{R_1} = i_b + i_c$$

$$i_c = \frac{h_{ie} i_b - (-h_{fe} i_b R_L)}{1/j\omega C} = j\omega C (h_{ie} + h_{fe} R_L) i_b$$

$$\Rightarrow V_i = (R_1 + h_{ie}) i_b + j\omega C R_1 (h_{ie} + h_{fe} R_L) i_b$$

$$i_b = \frac{V_i}{R_1 + h_{ie} + j\omega C R_1 (h_{ie} + h_{fe} R_L)}$$

-3dB point for V_o/V_i corresponds to -3dB point for i_b , since $V_o = -h_{fe} i_b R_L$

$$\Rightarrow R_1 + h_{ie} = \omega_{3dB} C R_1 (h_{ie} + h_{fe} R_L)$$

$$5 \times 10^3 = 2\pi f_{3dB} \times 10 \times 10^{-12} \times 4000 (1000 + 100 \times 500)$$

$$\underline{\underline{f_{3dB} = 390 \text{ kHz}}}$$


4a) Differential amplifier has much greater gain for differential input signals than common-mode signals. \therefore Only the desired 5 kHz signal will be amplified significantly, whilst the 50 Hz unwanted component will not be.

$$V_{o_{diff}} = A_{diff} \times 1 \text{ mV}$$

$$V_{o_{com}} = A_{com} \times 100 \text{ mV}$$

$$\frac{V_{o_{diff}}}{V_{o_{com}}} = 1000 = \frac{A_{diff}}{A_{com}} \times \frac{1}{100} = \frac{CMRR}{100}$$

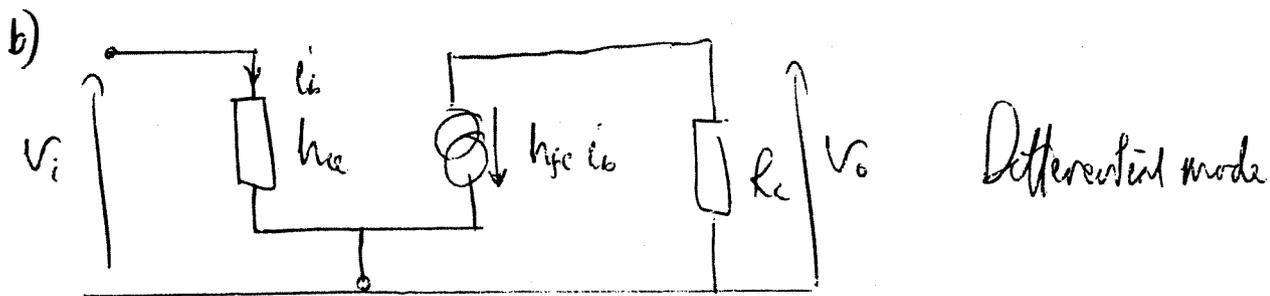
$$\therefore CMRR = 1000 \times 100 = 10^5 \approx 100 \text{ dB.}$$



Use half-circuit for differential input, with R_T a short-circuit since there is no small-signal voltage across it.

$$i_b = \frac{V_i}{h_{ie}} \quad V_o = -h_{fe} i_b R_c = -h_{fe} \frac{V_i}{h_{ie}} R_c$$
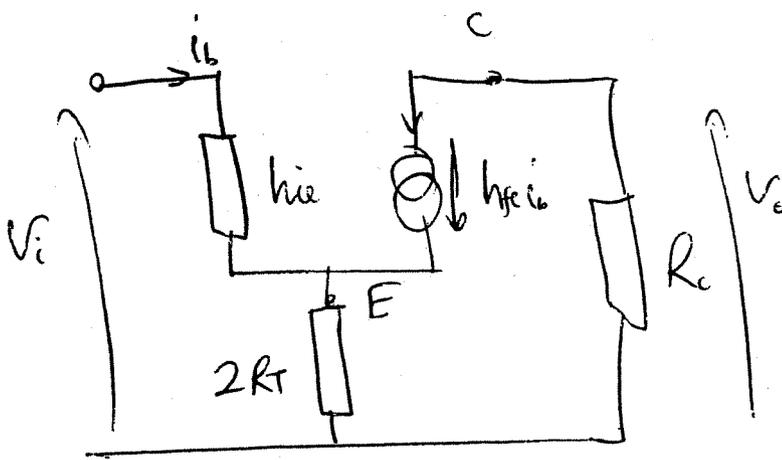
$$\Rightarrow \underline{\underline{\frac{V_o}{V_i} = -\frac{h_{fe} R_c}{h_{ie}}}}$$



Common-mode
N.B. R_T appears as $2R_T$ in half-circuit.

$$V_i = i_b h_{ie} + 2R_T (h_{fe} + 1) i_b$$

$$V_o = -R_C h_{fe} i_b$$

$$\underline{\underline{\frac{V_o}{V_i} = \frac{-h_{fe} R_C}{h_{ie} + 2R_T (h_{fe} + 1)}}}$$

$$\begin{aligned} \text{CMRR} &= \frac{A_{diff}}{A_{common}} = \frac{-h_{fe} R_C}{h_{ie}} \bigg/ \frac{-h_{fe} R_C}{h_{ie} + 2R_T (h_{fe} + 1)} \\ &= \frac{h_{ie} + 2R_T (h_{fe} + 1)}{h_{ie}} \end{aligned}$$

$$\text{For } A_{diff} = 40 \text{ dB} = 100 \Rightarrow \frac{h_{fe} R_C}{h_{ie}} = 100$$

$$\frac{200 R_C}{1000} = 100 \quad \underline{\underline{R_C = 500 \Omega}}$$

$$\text{CMRR} = 60 \text{ dB} = 1000 = \frac{1000 + 2R_T (201)}{1000}$$


$$\Rightarrow \underline{\underline{R_T = 2.49 \text{ k}\Omega}}$$

$$\begin{aligned}
 e) \quad V_{CC} &= 0 - V_{BE} + V_{CE} + I_C R_C \\
 &= -0.7 + 10 + 20\text{mA} \times 0.5\text{k}\Omega \\
 &= \underline{\underline{19.3\text{V}}}
 \end{aligned}$$

$$\begin{aligned}
 -V_{EE} &\approx -V_{BE} - 2I_E R_T \\
 &\approx -0.7 - 2 \times 20\text{mA} \times 2.49\text{k}\Omega \\
 &= 100.3
 \end{aligned}$$

$$\Rightarrow \underline{\underline{V_{EE} \approx 100.3\text{V}}}$$

d) Replace R_T with

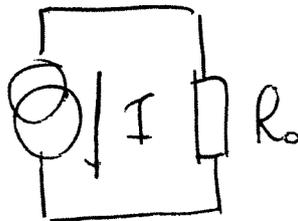


avoids excessive V_{EE} whilst retaining high effective R_T and hence CMRR.

$$I \approx 2I_C = 40\text{mA}$$

$$\underline{\underline{R_0 = R_T = 2.49\text{k}\Omega}}$$

3/a)

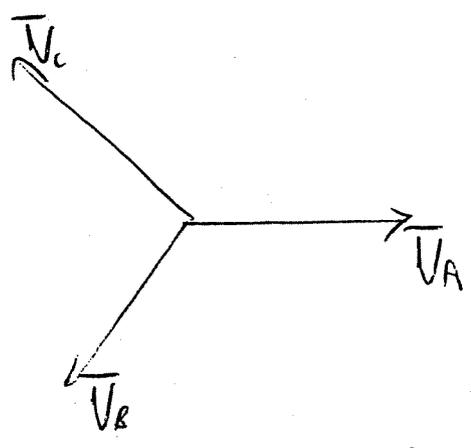

Reverse \bar{V}_B and sum :- $\bar{V}_{1\phi} = \bar{V}_A - \bar{V}_B + \bar{V}_C$

$$= V e^{j0} - V e^{-j2\pi/3} + V e^{j2\pi/3}$$


$$= V \left(1 - \left(0.5 - j\frac{\sqrt{3}}{2} \right) + 0.5 + j\frac{\sqrt{3}}{2} \right)$$

$$= V (1 + j\sqrt{3})$$

$$\therefore |\bar{V}_{1\phi}| = V (1+3)^{1/2} = \underline{2V}$$

Maximum o/p power of 1 ϕ generator is $2V I_{max}$ of $3V I_{max}$ for 3 ϕ . Increasing phases beyond 3 bring negligible benefits, but increases cost & complexity.

b)

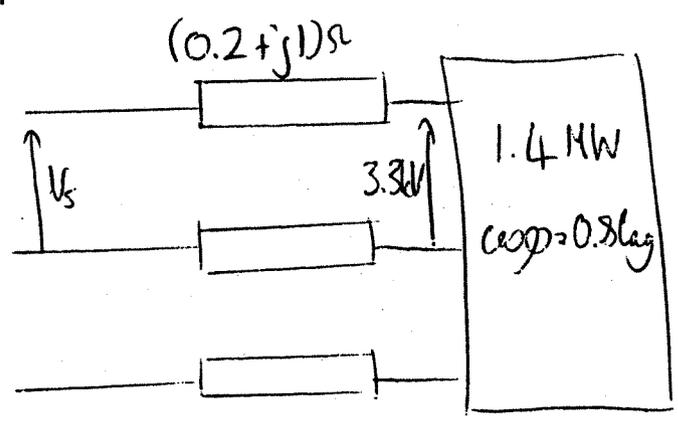

$$P_2 = 1.4 \text{ MW}, \quad Q_2 = P_2 \tan \phi_2 = 1.05 \text{ MVAR}$$

$$S_2 = (P_2^2 + Q_2^2)^{1/2} = 1.75 \text{ MVA} = \sqrt{3} V_L I_L$$

$$\Rightarrow I_L = 306.2 \text{ A}$$

$$P_{\text{line}} = 3 I_c^2 R = 3 \times 306.2^2 \times 0.2 = \underline{\underline{56.2 \text{ kW}}}$$

$$Q_{\text{line}} = 3 I_c^2 X_L = 3 \times 306.2^2 \times 1 = 281.2 \text{ kVAR}$$

$$P_{\text{source}} = 1.4 \text{ MW} + 0.0562 \text{ MW} = 1.456 \text{ MW}$$

$$Q_{\text{source}} = 1.05 \text{ MVAR} + 0.281 \text{ MVAR} = 1.331 \text{ MVAR}$$

$$S_{\text{source}} = (P^2 + Q^2)^{1/2} = 1.973 \text{ MVA} = \sqrt{3} V_s I_c$$

$$\Rightarrow \underline{\underline{V_s = 3.72 \text{ kV}}}$$

c) P_{load} unaffected, find new Q

$$\tan \phi = \frac{Q}{P}, \quad Q = P \tan \phi = 1.4 \tan(\cos^{-1} 0.9) \\ = 0.678 \text{ MVAR}$$

$$\text{Old } Q = 1.05 \text{ MVAR}$$

\therefore Capacitors must generate 0.372 MVAR

$$3 \frac{V_{ph}^2}{X_c} = 372 \times 10^3$$

$$\frac{V_c^2}{X_c} = 372 \times 10^3 \Rightarrow X_c = \frac{(3.3 \times 10^3)^2}{372 \times 10^3}$$

$$\frac{1}{\omega C} = X_c = 29.3 \Omega \quad \underline{\underline{C = 109 \mu\text{F}}}$$

$$\text{New load } S = \frac{P}{\cos \phi} = \frac{1.4}{0.9} = 1.56 \text{ MVA} = \sqrt{3} V_c I_c$$

$$\underline{\underline{I_c = 272.2 \text{ A}}}$$

$$d) Q_{cap} = -\frac{3 V_L^2}{X_c} = -\frac{3 \times (3.3 \times 10^3)^2}{29.3} = -1.12 \text{ MVAR}$$

$$P = 1.4 \text{ MW}, Q = 1.05 - 1.12 \text{ MVAR} = -65 \text{ kVAR}$$


$$\cancel{app} S = (1.4^2 + (0.065)^2)^{1/2} = 1.402 \text{ MVA}$$

$$\cancel{app} \cos \phi = \frac{P}{S} = 0.999 \text{ leading.}$$

$$\therefore I_{line} = S / \sqrt{3} V_L = 245 \text{ A.}$$

Power factor improved even more, resulting in an even lower line current \Rightarrow good. However, capacitors may not be adequately rated.

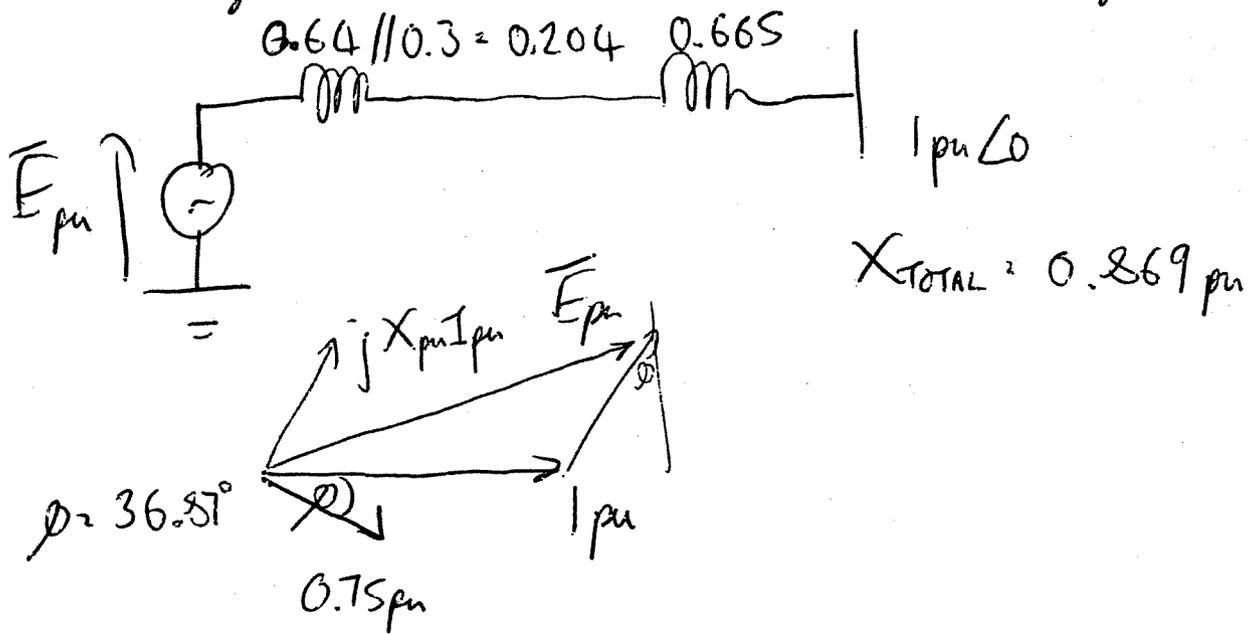Since generator excitations are identical, can connect together :-



$$\begin{aligned} \text{Re}(\bar{E}_{pu}) &= 1 + X I \sin\phi \\ &= 1 + 0.75 \times 0.869 \times 0.6 = 1.391 \end{aligned}$$

$$\text{Im}(\bar{E}_{pu}) = X I \cos\phi = 0.75 \times 0.869 \times 0.8 = 0.521$$

$$\bar{E}_{pu} = 1.49 \angle 20.5^\circ$$

$$\text{For } 11 \text{ kV generator, } \underline{\underline{E = 16.39 \text{ kV} \angle 20.5^\circ}}$$

$$\text{For } 33 \text{ kV generator, } \underline{\underline{E = 49.17 \text{ kV} \angle 20.5^\circ}}$$

- iii) Control prime-mover input power to control output electrical power
 Control rotor field current to control output VARs.

$$/ a) T = \frac{3 I_2'^2 R_2'}{5 \omega_s}$$

$$I_2'^2 = \frac{V^2}{(X_1 + X_2')^2 + (R_1 + R_2'/s)^2}$$

$$\therefore T = \frac{3 V^2 R_2'}{5 \omega_s ((R_1 + R_2'/s)^2 + (X_1 + X_2')^2)}$$

b) i) At $\omega_r = 0$, $s = 1$ $\omega_s = \omega/p = 2\pi \times 50/2 = 157.1 \text{ rad s}^{-1}$

$$\therefore T = \frac{415^2 \times 0.5}{1 \times 157.1 ((0.7 + 0.5)^2 + 1.8^2)} = \underline{\underline{117 \text{ Nm.}}}$$

ii) $160 = \frac{415^2 \times 0.5}{157.1 ((0.7 + 0.5/s)^2 + 1.8^2)} s$

$$= \cancel{86112.5} \frac{548.1 s^3}{0.49 s^2 + 0.7 s + 0.25 + 3.24 s^2}$$

$$3.73 s^2 + 0.7 s + 0.25 = 3.43 s^3$$


$$0.304 s^2 + 0.7 s + 0.25 = 0$$

$$s = \frac{-0.7 \pm \sqrt{0.7^2 - 4 \times 0.304 \times 0.25}}{2 \times 0.304} = -0.7 \pm$$

$$3.73 s^2 - 2.73 s + 0.25 = 0$$

$$s = \frac{2.73 \pm \sqrt{2.73^2 - 4 \times 3.73 \times 0.25}}{2 \times 3.73} = \frac{2.73 \pm 1.93}{7.46}$$
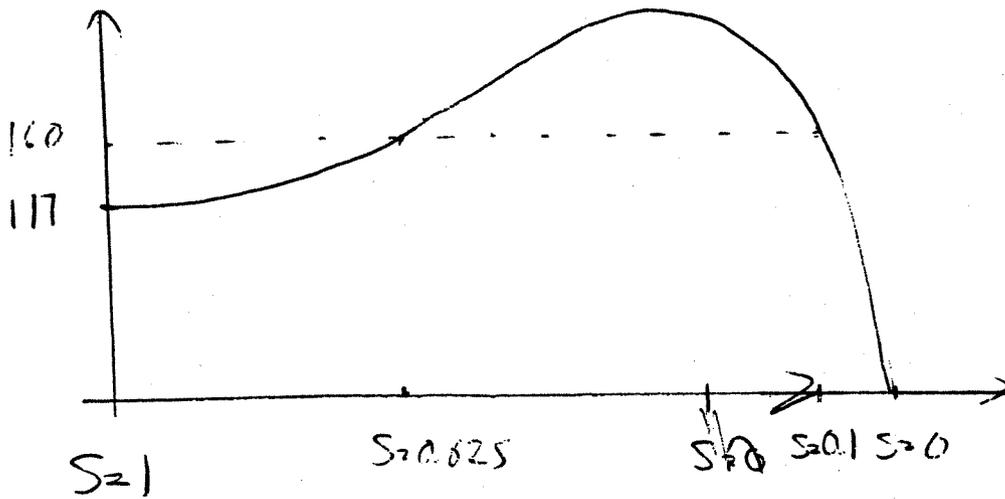
$$S = 0.625 \text{ or } s = 0.108 \Rightarrow \omega = 562.5 \text{ rpm or } 1338 \text{ rpm}$$



$$d) \quad \eta = \frac{P_{out}}{P_{in}} = \frac{P_{in} - P_{loss}}{P_{in}}$$

$$P_{in} = 3I^2 \left(R_1 + \frac{R_2'}{s} \right) \quad P_{loss} = 3I^2 (R_1 + R_2')$$

$$I = \frac{V}{\left(R_1 + \frac{R_2'}{s} \right)^2 + (X_1 + X_2')^2}^{1/2}}$$

$$\eta = \frac{3I^2 \left(R_1 + \frac{R_2'}{s} \right) - 3I^2 (R_1 + R_2')}{3I^2 \left(R_1 + \frac{R_2'}{s} \right)}$$

$$= \frac{R_1 + \frac{R_2'}{s} - (R_1 + R_2')}{R_1 + \frac{R_2'}{s}} = \frac{\frac{R_2'}{s} - R_2'}{R_1 + \frac{R_2'}{s}} = \frac{R_2' (1-s)}{R_2' + sR_1}$$

$$= \frac{(1-s)}{1 + sR_1/R_2'}$$

$$\therefore \eta_1 = \frac{1-s}{1 + s \times 1.4}$$

$$\eta_1 = \frac{1 - 0.108}{1 + 0.108 \times 1.4} = 77.5\%$$

$$\eta_2 = \frac{1 - 0.625}{1 + 0.625 \times 1.4} = 20\%$$

Clearly, the low slip condition is best at 1338 rpm.

- d) 117 Nm starting torque means motor cannot accelerate load unless additional rotor resistance is used. This can be done since the motor is a slip-ring machine, and usually, the peak motor torque is available at all speeds up to the speed corresponding to peak torque with no external resistance added.

$$6/a) \quad Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{250 \times 10^{-9}}{100 \times 10^{-12}}} = \underline{\underline{50 \Omega}}$$

$$v = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{250 \times 10^{-9} \times 100 \times 10^{-12}}} = 2 \times 10^8 \text{ ms}^{-1}$$

$$\therefore \tau = \frac{5}{2 \times 10^8} = \underline{\underline{25 \text{ ns}}}$$

b) Incident voltage = V_+ , reflected = V_-

$$I_+ = \frac{V_+}{Z_0}, \quad I_- = -\frac{V_-}{Z_0}$$

$$\text{Current in } R_L = I_+ + I_- = \frac{V_+ + V_-}{R_L}$$

$$\therefore \frac{V_+}{Z_0} - \frac{V_-}{Z_0} = \frac{V_+ + V_-}{R_L}$$

$$R_L(V_+ - V_-) = Z_0(V_+ + V_-)$$

$$V_-(R_L + Z_0) = V_+(R_L - Z_0)$$

$$\frac{V_-}{V_+} = \rho_V = \underline{\underline{\frac{R_L - Z_0}{R_L + Z_0}}}$$

$$\text{At source end, } \rho_{V_S} = \frac{200 - 50}{200 + 50} = \underline{\underline{0.6}}$$

$$\text{At logic gate end, } \rho_{V_L} = \frac{1000 - 50}{1000 + 50} = \underline{\underline{0.905}}$$

c)
$$\frac{V_{dc} - V_+}{2000 R_0} = \frac{V_+}{Z_0} \quad (\text{Continuity of current at start of transmission line})$$

$$V_+ = \frac{Z_0}{Z_0 + R_0} V_{dc}$$

∴ Initial $V_+ = \frac{50}{250} V_{dc} = 1 \text{ V}$

Reflected voltage = $\rho_{V_L} \times V_+ = 0.905 \text{ V}$

$\Gamma = 25 \text{ ns}$,
 $V = V_+ + V_- = 1.905 \text{ V}$

Voltage reflected from source = $0.6 \times 0.905 = 0.543 \text{ V}$


Reflected voltage at gate = $0.905 \times 0.543 = 0.491$

$= 0.6 \times 0.491 = 0.295 \text{ V}$

$= 0.905 \times 0.295 = 0.267 \text{ V}$

3 ns
 $\Gamma = 75 \text{ ns}$
 $V = 2.94 \text{ V}$

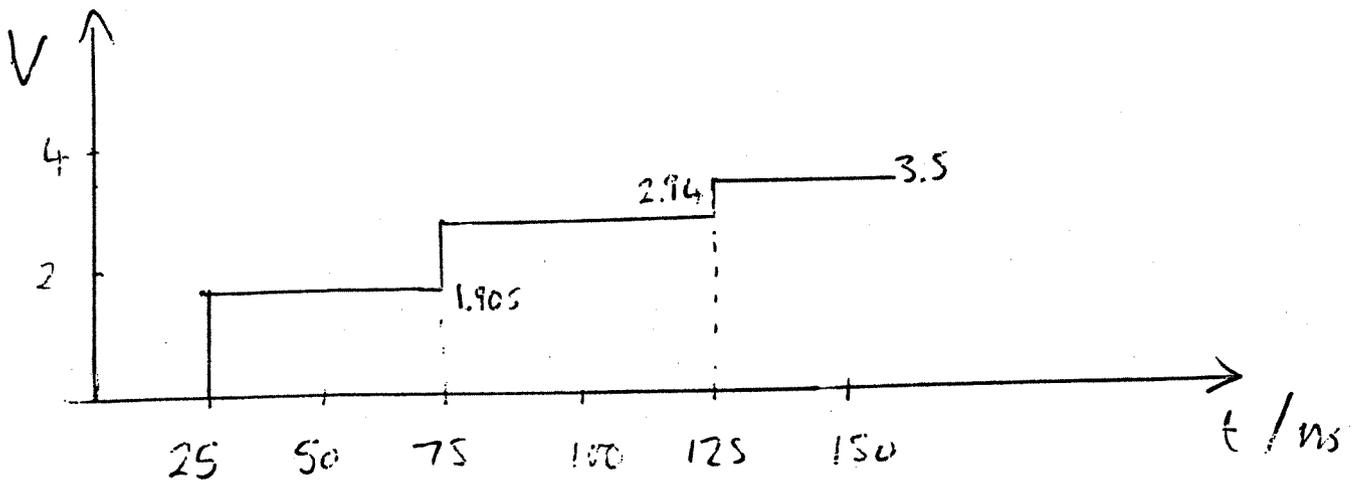5 ns
 $\Gamma = 125 \text{ ns}$
 $V = 3.5 \text{ V}$



$$d) \quad V = V_{t_0} + \rho_{V_L} V_{t_0} + \rho_{V_S} \rho_{V_L} V_{t_0} + \rho_{V_S}^2 \rho_{V_L}^2 V_{t_0} + \rho_{V_S}^3 \rho_{V_L}^3 V_{t_0} + \rho_{V_S}^4 \rho_{V_L}^4 V_{t_0} + \dots$$

$$= V_{t_0} (1 + \rho_{V_L}) \underbrace{\left(1 + \rho_{V_S} \rho_{V_L} + (\rho_{V_S} \rho_{V_L})^2 + \dots \right)}_{\text{G.P.}}$$

$$= V_{t_0} \frac{Z_L}{Z_0 + Z_L} \left(1 + \frac{R_L - Z_0}{R_L + Z_0} \right) \left(\frac{1 - (\rho_{V_L} \rho_{V_S})^n}{1 - \rho_{V_L} \rho_{V_S}} \right)$$

$$V = 1 (1 + 0.905) \left(\frac{1 - (0.6 \times 0.905)^n}{1 - 0.6 \times 0.905} \right)$$

$$4 = 4.168 (1 - 0.543^n)$$

$$0.543^n = 0.0403$$

$$n = 5.25 \Rightarrow \text{round up to } 6$$

$$\therefore \text{Total communication delay} = (2n+1)\tau = 0.325 \mu\text{s}$$

$$\text{Steady state voltage} = \lim_{n \rightarrow \infty} V = \frac{1.905}{0.457} = \underline{\underline{4.168 \text{ V}}}$$

(Physical approach — at steady-state transmission line connected load directly to source, since capacitors all 0.c. & inductor all s.c. in equivalent circuit.

$$\therefore V_{\infty} = \frac{1k}{1k + 200} \times 5 \text{ V} = \frac{5}{1.2} = \underline{\underline{4.167 \text{ V}}}$$

$V \omega R_{rad}$ given by $\frac{\hat{I}^2}{2} R_{rad} = P_{radiated}$.
 \downarrow
 radiation resistance.

It is a measure of how efficiently an antenna radiates electromagnetic waves.

b) $\underline{E} \times \underline{H} = \underline{S}$

so \underline{E} , \underline{H} and \underline{S} form a set of mutually orthogonal vectors

$\underline{e}_\theta \times \underline{e}_\psi = \underline{e}_r$ in Spherical polar

Direction of \underline{E} is \underline{e}_θ , since power is radiated in \underline{e}_r direction

Also $\frac{|\underline{E}|}{|\underline{H}|} = \eta_0$

$\underline{E} = \underline{e}_\theta \frac{\hat{I} l \beta \eta_0 \sin \theta}{4\pi r} e^{j(\omega t - \beta r)} \sin \theta$

c) $\underline{S} = \frac{1}{2} \underline{E} \times \underline{H}^* = \frac{1}{2} \frac{\hat{I} l \beta \eta_0 \sin \theta}{4\pi r} e^{j(\omega t - \beta r)} \times \frac{\hat{I} l \beta \sin \theta}{4\pi r} e^{-j(\omega t - \beta r)}$
 $= \frac{\hat{I}^2 l^2 \beta^2 \eta_0 \sin^2 \theta}{32\pi^2 r^2}$

$$d) \text{ Total power radiated} = \int_{\text{closed surface}} \underline{S} \cdot d\underline{S}$$

$$= \int_{\text{spherical surface}} S dS \quad (\text{since } \underline{S} \text{ and } d\underline{S} \text{ are parallel if the surface is a sphere centred on } r=0)$$

$$dS = r^2 \sin\theta \quad S \text{ is constant w.r.t. } r \text{ and } \psi \text{ (at const. } r)$$

$$\therefore dS = 2\pi r \sin\theta \cdot r d\theta$$

$$= 2\pi r^2 \sin\theta d\theta$$

$$P = \frac{\beta^2 \hat{I}^2 l^2 \eta_0}{32\pi^2 r^2} \cdot 2\pi r^2 \int_0^\pi \sin^3\theta d\theta$$

$$= \frac{\beta^2 \hat{I}^2 l^2 \eta_0}{16\pi} \cdot \frac{4}{3}$$


$$= \underline{\underline{\frac{\beta^2 \hat{I}^2 l^2 \eta_0}{12\pi}}}$$

$$P = \frac{\hat{I}^2}{2} R_{\text{rad}} = \frac{\beta^2 \hat{I}^2 l^2 \eta_0}{12\pi}$$

$$\therefore R_{\text{rad}} = \frac{\beta^2 l^2 \eta_0}{6\pi}$$

Using $c = \omega/\beta$ to replace β
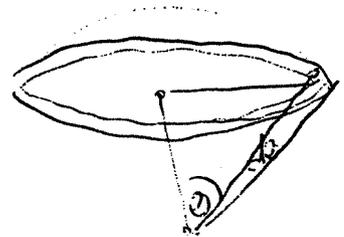
$$R_{\text{rad}} = \underline{\underline{\frac{\omega^2 l^2 \eta_0}{6\pi c^2}}}$$



e) For efficient radiation, need \hat{I} to be small i.e. want large radiation resistance $\therefore \frac{\omega l}{c}$ large \Rightarrow either large ω or large l

To keep antenna length reasonable, high frequencies are desirable.

2000 Part 1B - PAPER 5 - ANSWERS


1. a) CMRR=100 dB b) $R_C = 500 \Omega$; $R_T = 2.49 \text{ k}\Omega$ c) $V_{CC} = 19.3 \text{ V}$, $V_{EE} = 100.3 \text{ V}$
d) Use a 40 mA constant current source in place of R_T .

2. a) $R_B = 96.5 \text{ k}\Omega$; $R_L = 500 \Omega$ b) Gain = -10; $R_{in} = 5 \text{ k}\Omega$; $R_{out} = 500 \Omega$
c) $C_1 = 1.59 \mu\text{F}$ d) $f_{3dB} = 390 \text{ kHz}$

3. b) $I_{line} = 306.2 \text{ A}$; $P_{lines} = 56.2 \text{ kW}$; $V_S = 3.72 \text{ kV}$ c) $C = 109 \mu\text{F}$; $I_{line} = 272.2 \text{ A}$
d) $\cos\phi = 0.999$ leading; $I_{line} = 245 \text{ A}$. Even better power factor, but capacitors may not be adequately rated.


4. a) $E = 14.87 \text{ kV}$; $I = 3.94 \text{ kA}$ b) For 11 kV generator, $E = 16.39 \text{ kV} \angle 20.5^\circ$;
For 33 kV generator, $E = 49.17 \text{ kV} \angle 20.5^\circ$ c) Prime-mover input power controls generator output real power, rotor field current controls generator output reactive power.

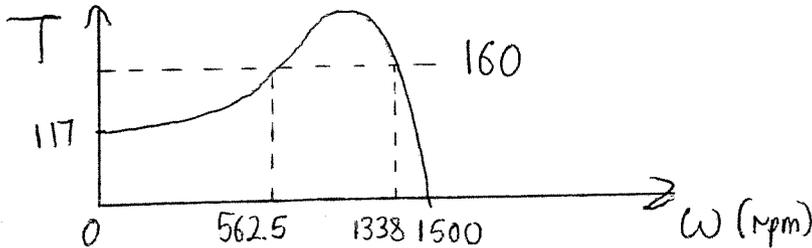5. b) i) Torque = 117 Nm ii) Speed = 562.5 rpm or 1338 rpm



c) $\eta = 77.5 \%$ at 1338 rpm, 20 % at 562.5 rpm. Therefore, operating at 1338 rpm is preferable. d) Connect additional rotor resistance via slip-rings.

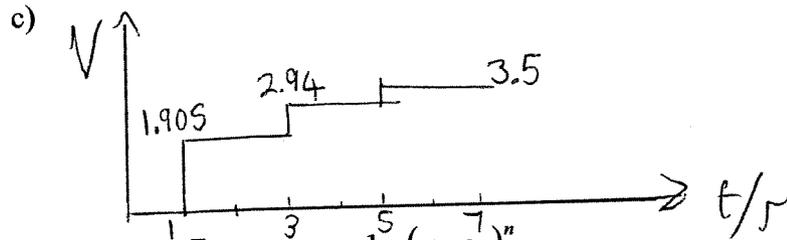6. a) $Z_0 = 50 \Omega$; $\tau = 25 \text{ ns}$ b) $\rho_S = 0.6$; $\rho_L = 0.905$



d) $V = V_{dc} \frac{Z_0}{Z_0 + R_0} (1 + \rho_L) \frac{1 - (\rho_L \rho_S)^n}{1 - \rho_L \rho_S}$; No. of reflections = 6; Total delay = 325 ns;

$$V_\infty = 4.17 \text{ V}$$

7. b) \mathbf{E} , \mathbf{H} and Poynting vector $(\mathbf{E} \times \mathbf{H}^*/2)$ are mutually orthogonal, $\eta_0 = \frac{|\mathbf{E}|}{|\mathbf{H}|} = \sqrt{\frac{\mu_0}{\epsilon_0}}$;

$\mathbf{E} = \mathbf{e}_\theta \frac{\hat{l}\beta\eta_0}{4\pi r} \sin\theta \exp(\omega t - \beta r)$ d) $P = \frac{\beta^2 \hat{l}^2 I^2 \eta_0}{12\pi}$ e) Need large R_a for efficient radiation

otherwise current is large for given radiated power \Rightarrow large ω for small l .

