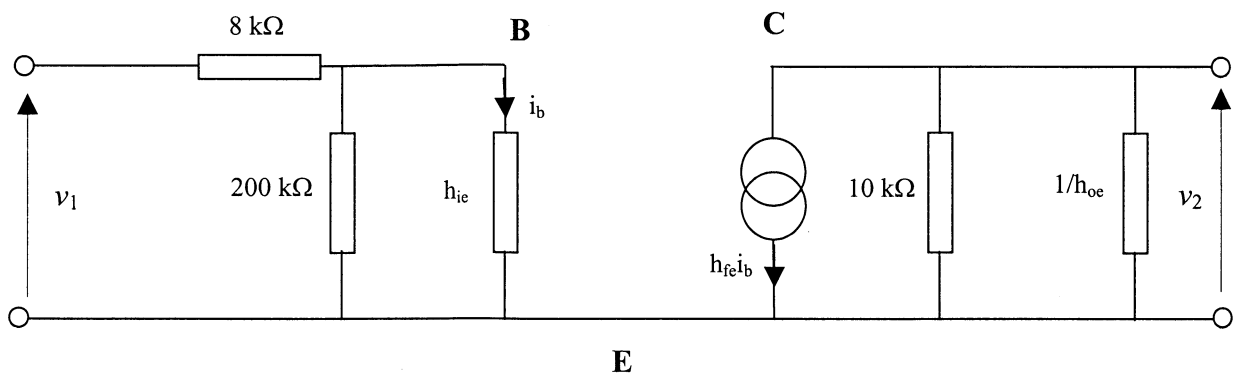


ENGINEERING TRIPOS, Part 1B 2002  
 Paper 5 – ELECTRICAL ENGINEERING  
 Solutions

1.

(a) This is called “common emitter” because the emitter is connected to ground or “common”, and is the ground common to both the input and the output.


(b) Small-signal equivalent circuit:



Now, gain =  $v_2/v_1$                        $v_2 = - h_{fe}i_b \times (10 \text{ k}\Omega // 1/h_{oe}) = -7143 h_{fe}i_b$

What is  $v_1$ ?

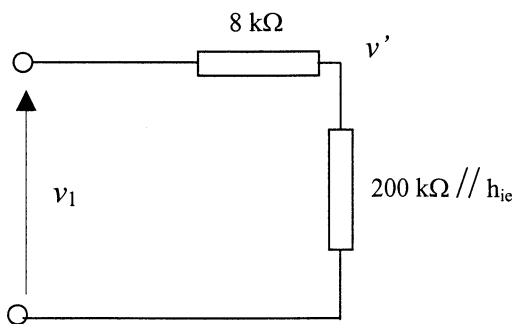Well, as seen from the input side, equivalent circuit is:



The voltage across  $h_{ie}$  is  $i_b h_{ie}$ , which we will call  $v'$ . By potential divider formula,

$$v' = \frac{v_1 \times (200 \text{ k}\Omega // h_{ie})}{8 \text{ k}\Omega + (200 \text{ k}\Omega // h_{ie})}$$


i.e.,  $v' = v_1/5.04$

Therefore,  $v_1 = 5.04i_b h_{ie}$

Gain =  $v_2/v_1 = -7143h_{fe}i_b/(5.04h_{ie}i_b) = -49.6$

Gain in dB =  $20\log_{10}(v_2/v_1) = 33.9$

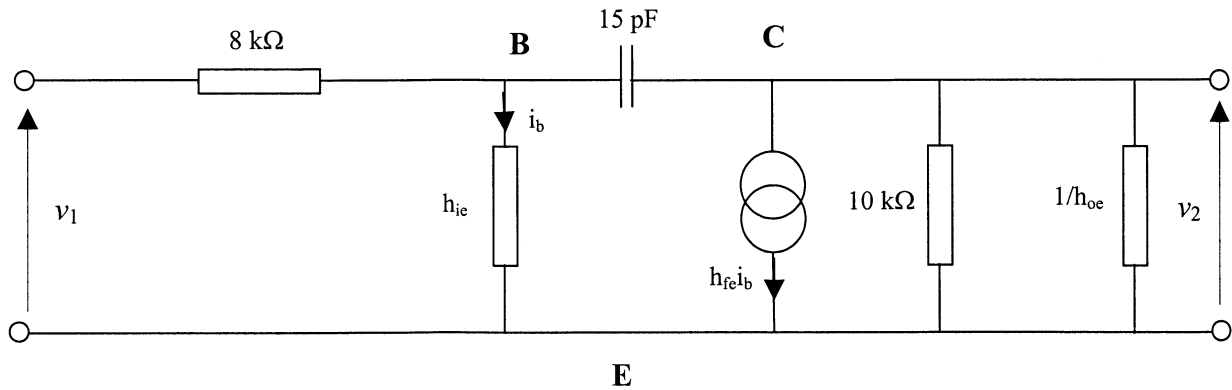(c) At high frequencies, the equivalent circuit becomes:



The output side is equivalent to:



Therefore, summing currents at the base, we get:

$$\frac{v_1 - 2000i_b}{8000} - j\omega \times 15 \times 10^{-12} \times \left( 2000i_b + \frac{70i_b}{G} \right) - i_b = 0$$

$$\Rightarrow \frac{v_1 - 2000i_b - 8000i_b - j\omega \times 0.06i_b}{8000} = 0$$

$$\Rightarrow i_b = -\frac{v_1}{10000 + 0.06j\omega}$$

i.e., when the frequency increases, the base current decreases, as current leaks across the base-collector capacitance. This reduces the current on the output side, and hence the gain.

Now, the 3dB point is when the gain is 0.707 times its mid-band value. This happens when the real part of the denominator in the expression above equals the imaginary part.

i.e.  $\omega = 166.68 \text{ kRad.s}^{-1} \Rightarrow f_{3\text{dB}} = 26.53 \text{ kHz}$ .

## 2.


(a) Using negative feedback:

- (i) Gain is stabilised, although it is reduced.
- (ii) Bandwidth is increased.
- (iii) Input impedance is increased for voltage amplifiers and reduced for current amplifiers.
- (iv) Output impedance is reduced for voltage amplifiers and increased for current amplifiers.

All of the above quantities are changed from their values in the absence of feedback by the factor  $(1 + AB)$ , where  $A$  is the open-loop gain,  $B$  is the feedback factor and  $AB$  is the loop gain.

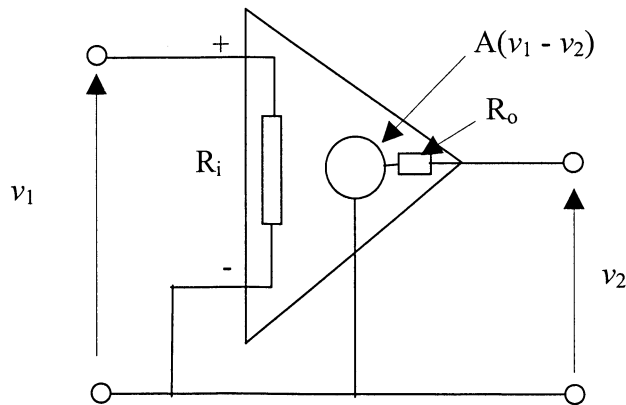(b) This is a unity-gain buffer – used as a buffer between a high impedance source and a low impedance load (eg loudspeaker).

The small-signal equivalent circuit of this amplifier is:



Summing currents at the output, we can find the gain,  $v_2/v_1$

$$\frac{v_1 - v_2}{R_i} + \frac{A(v_1 - v_2)}{R_o} - v_2 = 0$$

$$\Rightarrow \frac{v_1 R_o - v_2 R_o + AR_i v_1 - AR_i v_2 - R_i v_2}{R_i R_o} = 0$$

$$\Rightarrow v_1(R_o + AR_i) - v_2(R_o + AR_i + R_i) = 0$$

$$\Rightarrow \frac{v_2}{v_1} = \frac{R_o + AR_i}{R_o + AR_i + R_i} = \frac{1}{1 + \frac{R_i}{R_o + AR_i}}$$

i.e., Gain  $\sim 1$ , and loop gain  $\sim A$ .

**Input impedance** = input voltage/input current


$$= \frac{v_1}{(v_1 - v_2)/R_i} = \frac{R_i}{1 - \frac{v_2}{v_1}}$$

Using expression above for  $v_2/v_1$ , we obtain for the input impedance:

$$R_{in} = R_o + R_i(A+1)$$

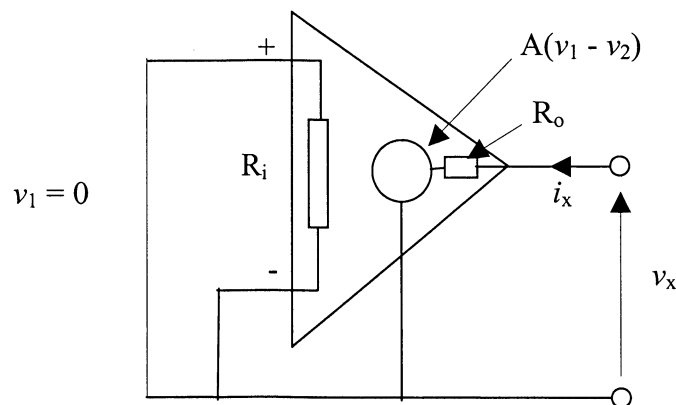**Output impedance?**

Well, the standard routine here is to apply a test voltage  $v_x$ , to the output while shorting the input, and find the resultant current,  $i_x$ .



Summing currents at the output, we find that:


$$\frac{A(0 - v_x) - v_x}{R_o} + \frac{(0 - v_x)}{R_i} + i_x = 0$$

$$\Rightarrow i_x = v_x \left[ \frac{A+1}{R_o} + \frac{1}{R_i} \right]$$

$$\Rightarrow R_{out} = \frac{R_o}{1 + A + \frac{R_o}{R_i}}$$

(c)

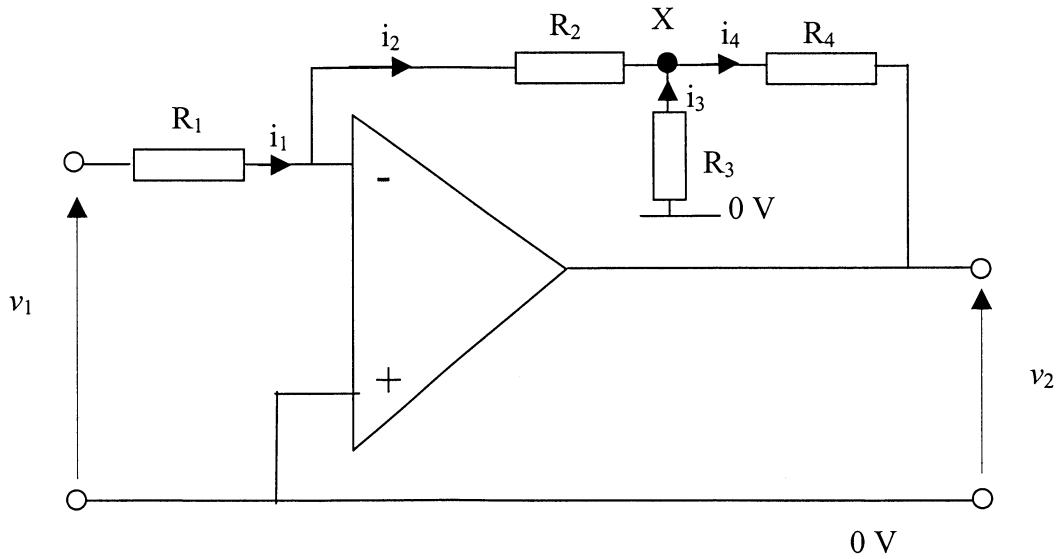Assume that Op-Amp is ideal: makes analysis much simpler.



Now, (i) Current  $i_1 = v_1/R_1 = i_2$  (Op-Amp is ideal, so draws no current)

(ii) Inverting terminal is at virtual earth

Voltage at node "X",  $v_x = 0 - i_2 R_2 = -v_1 R_2 / R_1$

Current  $i_3 = (0 - v_x) / R_3 = R_2 v_1 / R_1 R_3$

Now,  $i_4 = i_2 + i_3 = v_1 / R_1 + v_1 R_2 / R_1 R_3$ , and  $v_2 = v_x - i_4 R_4$

$$v_2 = -v_1 \frac{R_2}{R_1} - v_1 \frac{R_4}{R_1} \left( 1 + \frac{R_2}{R_3} \right)$$

Therefore,

$$\Rightarrow \frac{v_2}{v_1} = -\frac{R_2}{R_1} \left[ 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right]$$

(d) Gain for  $R_1 = R_2 = R_4 = 1 \text{ M}\Omega$ ,  $R_3 = 10.2 \text{ k}\Omega$  is **-100**.

### 3.

(a) ac is used because then voltages can be altered arbitrarily up or down by means of transformers. This is important, as many appliances operate at different voltages.


Three-phase ac is the most efficient – more phases only represent a nominal improvement in power generation, which is overshadowed by more (expensive) cabling.

The phase difference between the phase voltages is  $120^\circ$ , or  $2\pi/3$  rads.

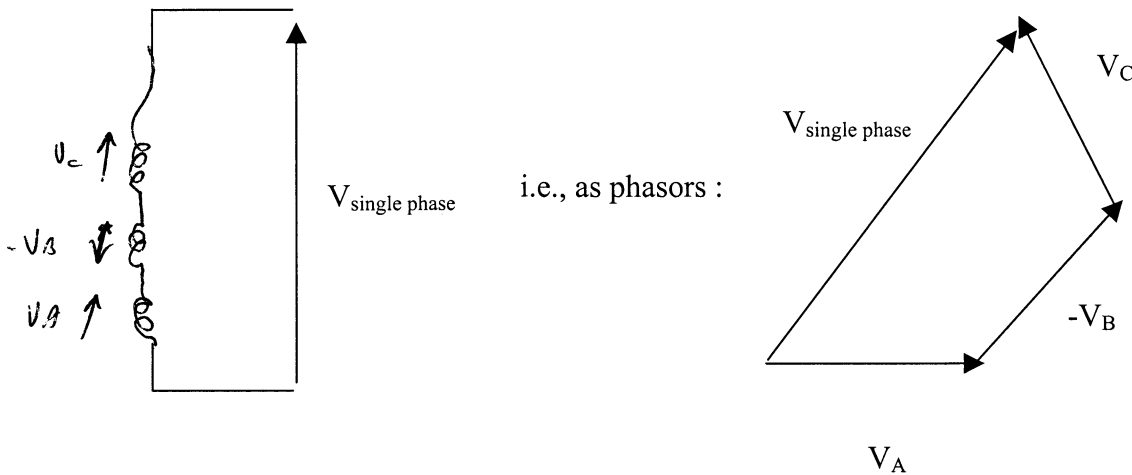(b) Well, power per phase is  $V_{ph}I_{max}$ , where  $V_{ph}$  is the phase voltage.

Therefore, for three phases, the total maximum power output is  $3V_{ph}I_{max}$ .

If we combine the phases as  $V_A - V_B + V_C$ , we get the following:



Geometrically,  $V_{single\ phase} = 2V_A$

Alternatively, if we write  $V_A = V$ ,  $V_B = Ve^{-j2\pi/3}$ ,  $V_C = Ve^{j2\pi/3}$

We can combine these to find  $V_A - V_B + V_C = V(1 + j\sqrt{3}) = 2V$

Therefore, the power is reduced from  $3V_{ph}I_{max}$  to  $2V_{ph}I_{max}$ , which is a factor of 1/3.

(c) Procedure: find P & Q for each load separately, and therefore find S.

Convert Delta load (load 1) to a Star :  $Z_1 = j\omega L/3 + R/3 = 33.3 + j104.7$

Therefore,  $|Z_1| = 109.86 \Omega$

$I_1 = V_1/Z_1 = 11 \text{ kV}/\sqrt{3} \times 109.86 = 57.8 \text{ A} \dots \dots V_{ph} = V_{line}/\sqrt{3}$

Thus,  $P_1 = 3 \times I_1^2 \times \text{Re}[Z_1]$

$= 3 \times 57.8^2 \times 100 = 333.75 \text{ kW}$

$$Q_1 = I_1^2 \times \text{Re}[Z_1]$$

$$= 57.8^2 \times 104.7 = 1049.36 \text{ kVAR}$$

Now, for star load (load 2)

$Z_2 = 10 \mu\text{F} \parallel 100 \Omega$ . Resistor & capacitor in parallel  $\Rightarrow$  both have  $V_{\text{ph}}$  across them.

$$P_2 = 3 \times V_{\text{ph}}^2 / R = 1210 \text{ kW}$$

$$Q_2 = -3 \times V_{\text{ph}}^2 \omega C = -380.121 \text{ kVAR}$$

For whole load, total  $P = P_1 + P_2 = 1543.75 \text{ kW}$

Likewise, total  $Q = Q_1 + Q_2 = 669.24 \text{ kVAR}$

(i) Therefore, to find overall power factor,  $= \cos(\tan^{-1}(Q/P)) = \mathbf{0.917, \text{ lagging}}$

(ii) Line current,  $I_1$ : Well, Total apparent power,  $S = \sqrt{(P^2 + Q^2)} = \sqrt{3} V_1 I_1$

$$\Rightarrow I_1 = \sqrt{(1543750^2 + 669240^2)} / \sqrt{3} V_1$$

$$= \mathbf{88.3 \text{ A}}$$

(iii) Capacitors to correct power factor to 0.95 lagging.

For power factor 0.95,  $\Rightarrow Q/P$  must be 0.329. As  $P$  will not change (no additional resistive components), that means net  $Q$  must be 507.89 kVAR. Therefore, Capacitors must generate  $(669.24 - 507.89) \text{ kVAR} = 161.35 \text{ kVAR}$ .

Now, how many VARS generated?

$$\text{Well, } = 3 V_{\text{ph}}^2 / X_c$$

$$= 3 \times (11000)^2 \times \omega C$$

$$\Rightarrow \mathbf{C = 1.42 \mu\text{F}}$$

#### 4.


(a) Stator is stationary, whereas rotor is on bearings and is free to rotate. Dc current is fed into the rotor coils by slip-rings and brushes. This produces a magnetic field which interacts with the rotating magnetic field produced by the three-phase windings of the stator. When the prime-mover is rotated, the rotor magnetic field will also rotate, and an emf is induced in the stator windings. For steady torque to be produced, the basic principle is that the rotor and stator fields must rotate at the same speed, and there must be a phase lag (load angle not equal to zero) between these two fields. The two conditions which allow this are (i) The rotor and stator-driven fields must have the same number of poles, and (ii) the rotor speed must be equal to the stator-field speed.

(b) Now, Power,  $P = 3V_{ph}I_{ph}\cos\phi$

$$\text{Power} = 300 \text{ MW} \Rightarrow I_{ph} = 300 \times 10^6 / (3 \times 22000 / (\sqrt{3} \cos\phi))$$

$$= \mathbf{8287 \text{ A}}$$

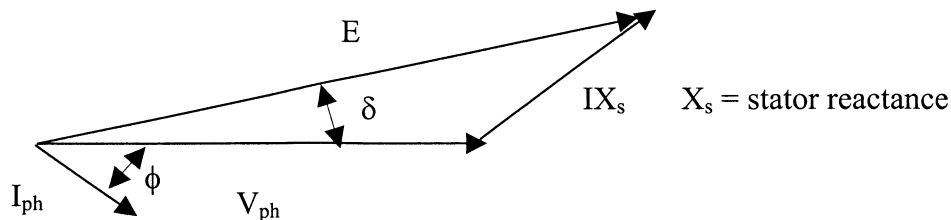To calculate load angle,  $\delta$  and line-line excitation EMF,  $E$ , consider phasor diagram:



By cosine rule,  $E = \sqrt{(V + IX_s \sin\phi)^2 + (IX_s \cos\phi)^2}$


$$\Rightarrow \mathbf{E = 20.3 \text{ kV}} \Rightarrow \mathbf{E_{line} = \sqrt{3}E = 35.16 \text{ kV}}$$

Load angle, by sine rule,  $\sin\delta = IX_s \cos\phi / E \Rightarrow \mathbf{\delta = 35.5^\circ}$

(c) Well, excitation remains constant, as will terminal voltage and stator reactance. Therefore,  $E$  moves in an arc. Power is proportional to the vertical height of the triangle shown above.



i.e.:

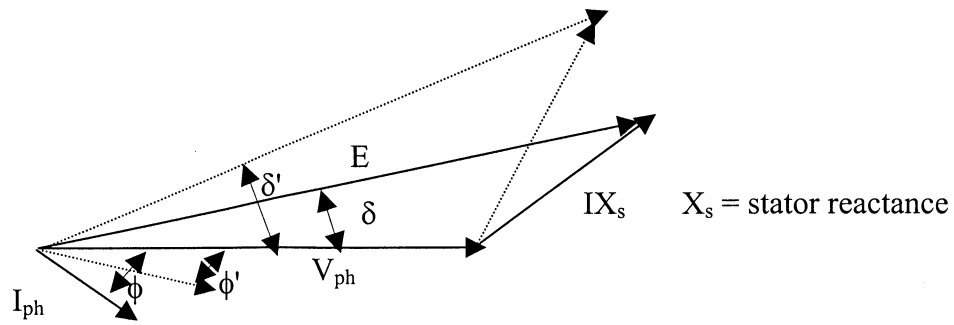

Now, Power,  $P = 3VI\cos\phi$

By sine rule,  $P = 3VE\sin\delta/X_s$

All are constants apart from  $\delta$  &  $\delta'$ .

Therefore, (New Power)/(Old Power) =  $\sin\delta'/\sin\delta$

$$\Rightarrow \sin\delta' = 4\sin\delta/3 = 0.774$$

$$\Rightarrow \delta' = 50.74^\circ$$

New stator current?

Well, by cosine rule,  $(I'X_s)^2 = E^2 + V^2 - 2EV\cos\delta'$

$$\Rightarrow I' = 10488 \text{ A}$$


Power factor?

$$P = 3VI'\cos\phi' \Rightarrow \cos\phi' \sim 1$$

(d)

Operating chart: scale sides of phasor diagrams above by factor  $3V/X_s$

i.e.

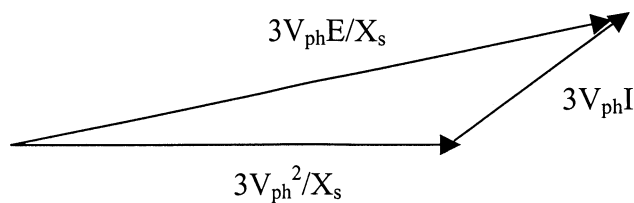


Side lengths:  $3V_{ph}^2/X_s = 322.7 \text{ MVAR}$

$3V_{ph}I = \text{stator heating limit (SHL)} = \text{VA rated} = 500 \text{ MVA}$

$3V_{ph}E/X_s = \text{rotor heating limit (RHL)} = 490 \text{ MVAR}$

i.e.

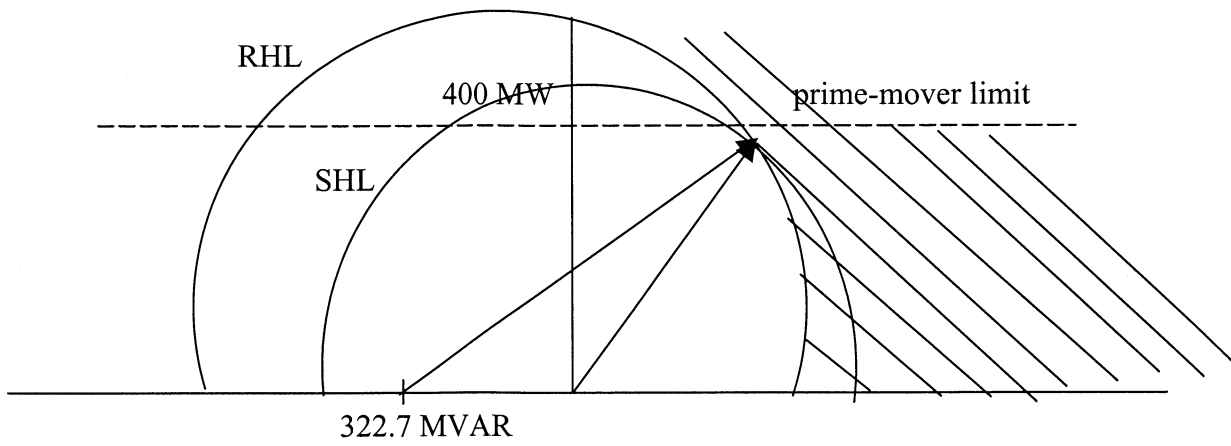

## 5.

(a) (i) Armature EMF equation

Well, conductor of length  $l$  in a magnetic field of strength  $B$ , and moving with velocity  $v$ , has an induced EMF =  $Blv$  (from Faraday's law and Lorentz Force).

Average B field per pole is (flux per pole)/(pole area)

$$= \phi / (2\pi r l / 2p) \dots \dots \dots p = \text{number of pole pairs}$$

$$\Rightarrow \text{EMF} = Blv = p\phi v / \pi r$$

But, velocity,  $v = r\omega$  (spinning about an axis at angular velocity  $\omega$ , at a distance  $r$  from the axis, where  $r$  is the coil's radius).

$$\Rightarrow \text{EMF} = p\phi\omega / \pi$$

If there are  $n$  conductors,  $\text{EMF} = np\phi\omega / \pi = e_a = K\phi\omega \dots \dots \dots K = np/\pi$ , a constant

(ii) Torque equation

Force on a current,  $i_a$  in a wire of length  $l$ , in a magnetic field  $B$  is  $F = Bi_a l$  (Lorentz force).

But, from before, average  $B = p\phi / \pi r l \Rightarrow \text{Force} = p\phi i_a / \pi r$

$$\text{Torque for } n \text{ conductors is } Fnr = pni_a\phi / \pi = T = K\phi i_a$$

(b) Power,  $P = T\omega$ , where  $T$  is torque and  $\omega$  is angular velocity. If machine delivers 30 kW, and 1.5 kW are lost, then must generate 31.5 kW

Convert rpm to rads/s.  $1000 \text{ rpm} = 2\pi \times 1000 \text{ rad/min} = 2\pi \times 1000 / 60 \text{ rad/s} = 104.72 \text{ rad.s}^{-1}$ .

$$\Rightarrow T = P/\omega = 31500 / 104.72 = 300.8 \text{ Nm}$$

To find values of field current, use databook equations for dc motors.

i.e.

$$V_a = e_a + i_a r_a$$

$$\Rightarrow V_a i_a = e_a i_a + i_a^2 r_a$$

$$\text{but, } T\omega = K\phi i_a e_a / K\phi = e_a i_a$$

$$\Rightarrow V_a i_a = T\omega + i_a^2 r_a$$

$$\Rightarrow 500 i_a = 31500 + 0.8 i_a^2$$

$$\Rightarrow i_a^2 - 625i_a + 39375 = 0$$

$$\Rightarrow i_a = 553.9 \text{ A or } 71.1 \text{ A}$$

Now, open circuit test  $\Rightarrow i_a = 0$ , so  $V_a$  as measured is actually  $e_a$ . We need to find values of  $i_f$  corresponding to the above values for  $i_a$ .

$$e_a = V_a - i_a r_a$$

$$\Rightarrow \text{for } i_a = 553.9 \text{ A, } e_a = 56.9 \text{ V, and for } i_a = 71.1 \text{ A, } e_a = 443.12 \text{ V.}$$

$$\text{Now, } 56.9 \text{ V @ } 1000 \text{ rpm} = 569 \times 0.8 \text{ V @ } 800 \text{ rpm (remember, } e_a \text{ scales linearly with speed)}$$

$$= 45.52 \text{ V}$$

$$\text{And, } 443.12 \text{ V @ } 1000 \text{ rpm} = 354.5 \text{ V @ } 800 \text{ rpm.}$$

From data in table 1, graphical estimate is that at  $V_{oc} = 354.5 \text{ V}$ ,  $i_f = 3.3 \text{ A}$ , and  $45.52 \text{ V}$  corresponds to  $i_f = 0.4 \text{ A}$ .

Choose value of  $i_f$  corresponding to lowest value of  $i_a$  (71.1 A), i.e.  $i_f = 3.3 \text{ A}$ . Other value of  $i_f$  means using  $i_a$  of 553.9 A, as compared to 71.1 A, so is 61 times less efficient!

(c) Remember,  $T = K\phi i_a = K' i_f i_a$

$\Rightarrow$  if  $i_f$  is decreased from 3.3 A to 1.75 A while  $T$  remains constant, then  $i_a$  is increased by factor of  $3.3/1.75 = 1.89$ .

$$\Rightarrow e_{a2} = V_a - i_{a2} r_a$$

$$= 500 - 142.2 \times 0.8$$


$$= 386.24 \text{ V}$$

$$\text{But, } e_{a2}/e_{a1} = (K_2' i_{f2} \omega_2)/(K_1' i_{f1} \omega_1) = (K_2'/K_1) \times (\omega_2/1.89\omega_1)$$

$$\Rightarrow \omega_2 = 1.89\omega_1 \times 386.24/443.12 \times (K_1/K_2')$$


Now, graphically,  $K_1/K_2' \sim 1.09$

$$= 1790 \text{ rpm}$$

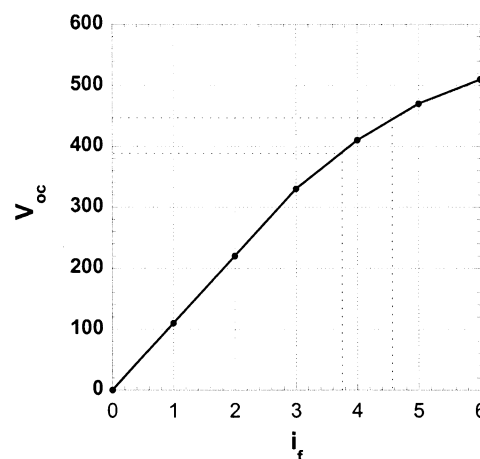

6.

(a)

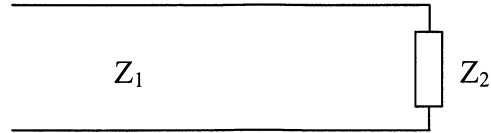

(i) In the case of a matched transmission line where  $Z_1 = Z_2$ , then the reflection coefficient is zero at the end of the line. All the signal power is therefore transmitted to the load.

(ii) For  $Z_1 \neq Z_2$ , some power is reflected, and the voltage reflection coefficient is  $\rho = (Z_2 - Z_1)/(Z_2 + Z_1)$ .


(b) Reflected voltage,  $V_- = \rho V_+$

$$V_- = \left( \frac{Z_2 - Z_1}{Z_2 + Z_1} \right) V_+$$

$$= \left( \frac{j150 - 70}{j150 + 70} \right) V_+$$

$$= (0.642 + j0.766) V_+$$

(c)

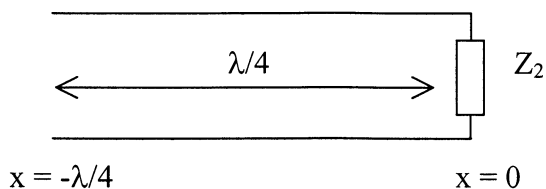

Total voltage at  $x = -\lambda/4$  is the sum of the forward and reflected voltages:

$$V\left(x = -\frac{\lambda}{4}\right) = V_+ e^{-j\frac{2\pi}{\lambda}\left(\frac{-\lambda}{4}\right)} + V_- e^{+j\frac{2\pi}{\lambda}\left(\frac{-\lambda}{4}\right)}$$

i.e.

$$= j(V_+ - V_-)$$

We can use a similar argument for the current to find  $I(x = -\lambda/4) = j(I_+ - I_-)$

But,  $I_+ = V_+/Z_1$ , and  $I_- = -V_-/Z_1 = -\rho V_+/Z_1$

The input impedance as observed at  $x = -\lambda/4$  is

$$Z_{in}\left(\frac{\lambda}{4}\right) = \frac{V(x = -\lambda/4)}{I(x = -\lambda/4)}$$

$$= \frac{j(V_+ - V_-)}{j(I_+ - I_-)}$$

$$= \frac{(V_+ - \rho V_+)}{\frac{V_+}{Z_1} + \rho \frac{V_+}{Z_1}}$$

$$= Z_1 \left( \frac{1 - \rho}{1 + \rho} \right)$$

$$= 0.023 - j32.7 \text{ Ohm}$$

$$\sim j32.7 \text{ Ohm}$$

(d) Case where  $x = \lambda/2$ , use a similar argument

$$V\left(x = -\frac{\lambda}{2}\right) = V_+ e^{-j\frac{2\pi}{\lambda}\left(\frac{-\lambda}{2}\right)} + V_- e^{+j\frac{2\pi}{\lambda}\left(\frac{-\lambda}{2}\right)}$$

$$= -(V_+ + V_-)$$

$$Z_{in}\left(\frac{\lambda}{2}\right) = \frac{V(x = -\lambda/2)}{I(x = -\lambda/2)}$$

$$= \frac{-(V_+ + \rho V_+)}{-\frac{V_+}{Z_1} + \rho \frac{V_+}{Z_1}}$$

$$= Z_1 \left( \frac{1 + \rho}{1 - \rho} \right)$$

$$= 4.3 + j148$$

$$\sim j150 \text{ Ohm}$$

The input impedance is an oscillatory function of the transmission line length, and for  $l = 5\lambda/4$ , it is the same as for  $\lambda/4$ , i.e. it is  $-j32.7 \text{ Ohm}$

7.

(a) Wave equation

$$\frac{\partial^2 E}{\partial x^2} + \frac{\partial^2 E}{\partial y^2} + \frac{\partial^2 E}{\partial z^2} = \epsilon_0 \mu_0 \frac{\partial^2 E}{\partial t^2}$$

$$\text{Test, } E_y = E_0 e^{j(\omega t - \beta z)}$$

i.e.

$$\frac{\partial^2 (E_0 e^{j(\omega t - \beta z)})}{\partial z^2} = \epsilon_0 \mu_0 \frac{\partial^2 (E_0 e^{j(\omega t - \beta z)})}{\partial t^2}$$

$$\text{i.e. } \beta^2 = \epsilon_0 \mu_0 \omega^2$$

This is a solution for a plane wave propagating in the Z direction provided that  $\beta/\omega = \sqrt{\epsilon_0 \mu_0}$

$$(b) E_x = E_0 e^{j(\omega t - \beta z)}$$

also propagates in the positive Z direction, the only difference being the direction of polarisation.

(c) The signal is broadcast isotropically, hence power per unit area, P at a distance r from the source is

$$P = 5000/(4\pi r^2) \quad \text{Watt.m}^{-2}$$

But, the receiver area is only  $0.02 \text{ m}^2$ , hence the power received at the antenna,  $P_{\text{rec}}$  is:

$$P_{\text{rec}} = P \times 0.02 \text{ Watt} = 100/(4\pi r^2) \text{ Watt}$$

For the maximum distance  $r_{\text{max}}$ , the power received is only  $2 \times 10^{-9} \text{ Watt}$ , hence

$$2 \times 10^{-9} = 100/(4\pi r_{\text{max}}^2)$$

$$\Rightarrow r_{\text{max}} = 63 \text{ km}$$

(d)

If the receiver is placed at 90%  $r_{\max}$ , then the power received is 20% above the minimum required level. If the receiver is inclined at an angle  $\theta$  to the optimum angle for picking up the signal, then the effective area is reduced by a factor  $\cos \theta$ .

Hence, the antenna can be mis-oriented by  $\theta_{\max}$  and still pick up the minimum required signal where

$$\cos(\theta_{\max}) = 0.8$$

$$\Rightarrow \theta_{\max} = 37^\circ$$