

ENGINEERING TRIPOS PART IB

---

Wednesday 2 June 2010 2 to 4

---

Paper 5

ELECTRICAL ENGINEERING

*Answer not more than **four** questions.*

*Answer at least **one** question from each section.*

*All questions carry the same number of marks.*

*The **approximate** number of marks allocated to each part of a question is indicated in the right margin.*

*Answers to questions in each section should be tied together and handed in separately.*

*There are no attachments.*

STATIONERY REQUIREMENTS

Single-sided script paper

SPECIAL REQUIREMENTS

Engineering Data Book

CUED approved calculator allowed

**You may not start to read the questions printed on the subsequent pages of this question paper until instructed that you may do so by the Invigilator**

## SECTION A

*Answer at least one question from this section*

- 1 (a) State what is meant by the terms *Class A*, *Class B* and *Class AB* amplifiers. What Class of amplifier is the emitter-follower amplifier shown in Fig. 1? [4]
- (b) Calculate the base current that flows into the bipolar junction transistor in Fig. 1 if the d.c. current gain  $h_{FE}$  is 50 and the base-emitter voltage  $V_{BE}$  is 0.7 V when the transistor is active and no input signal is applied. [4]
- (c) The same transistor has small-signal parameters of  $h_{ie} = 1 \text{ k}\Omega$ ,  $h_{fe} = 50$  and  $h_{oe} = 0.5 \text{ mS}$ . Derive expressions for the small-signal voltage gain and the output resistance of the circuit and calculate their numerical values. You may assume that the capacitors  $C_1$  and  $C_2$  have negligible reactance at the signal frequencies being used and that  $h_{re}$  is negligible. [8]
- (d) What value of load resistor  $R_L$  should be connected across the output terminals of the circuit to maximize the output power? Estimate the resulting maximum ac power that can be delivered into this load for a sinusoidal signal. [4]

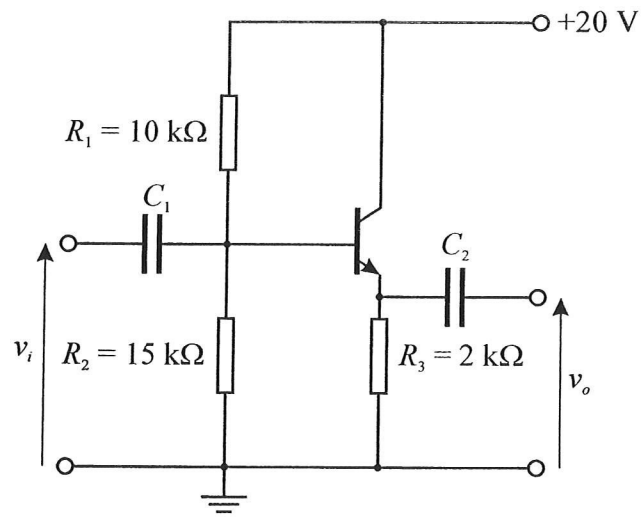


Fig. 1

2 (a) Fig. 2 shows a simple differential amplifier circuit for amplifying a high frequency ( $\sim 10$  kHz) signal from a light meter. Interference from the a.c. mains means that there is an unwanted additional signal at 50 Hz. Explain, with the aid of a diagram, the meaning of the terms *difference signal* and *common-mode signal*. Why is the differential amplifier in Fig. 2 suitable for this application? [5]

(b) The operational amplifier in the circuit shown in Fig. 2 is considered to be ideal. If  $R_1 = R_2$  and  $R_3 = R_4$ , derive an expression for the differential gain of the circuit. [4]

(c) If the operational amplifier in the circuit shown in Fig. 2 actually has a finite gain  $A$  and finite input resistance  $R_i$ , but is otherwise ideal, show that, for  $R_1 = R_2$  and  $R_3 = R_4$ , the differential gain of the circuit,  $G$ , is now given by

$$G = \frac{1}{\frac{R_1}{A} \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{2}{R_i} \right) + \frac{R_1}{R_3}} . \quad [7]$$

(d) The gain of the operational amplifier is  $A = 10^7$  and the input resistance  $R_i = 10$  M $\Omega$ . Using the equation given in part (c), suggest suitable values for  $R_1$  and  $R_3$  if the difference signal ( $v_2 - v_1$ ) is to be amplified by a factor of 100 and the operational amplifier also has a small output resistance of 10  $\Omega$ . [4]

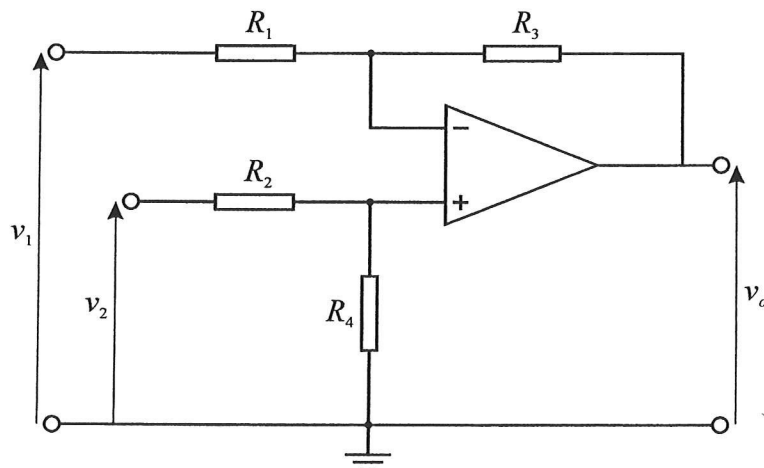


Fig. 2

**SECTION B**

*Answer at least one question from this section*

- 3 (a) Explain why power is commonly transmitted from a power station to a town using *high voltage three-phase a.c. electric power* rather than using *d.c. power*. Why is it necessary to consider a town as being a balanced load on the transmission line? [3]
- (b) A set of three-phase a.c. transmission lines are connected to a town which acts as a balanced load consuming 100 MW of power at a power factor of 0.85 lagging. If the line voltage at the town is 33 kV, what is the line current per phase? [4]
- (c) Each feeder line to the town has an impedance of  $(0.02 + j0.05) \Omega$  per kilometer and is 100 km long. Calculate the power dissipated in the transmission lines and the line voltage at the sending end of the feeder. [8]
- (d) By how much would power dissipation be reduced if the power factor of the town could be improved to 0.9 lagging? Describe one method by which this improvement could be achieved. [5]

4 (a) a.c. synchronous generators that are connected to a grid normally consist of a rotor and stator separated by an air gap. Sketch a graph showing how torque varies as a function of load angle. Identify the regions in which the system is *generating* and *motoring*. Also identify the points at which synchronicity is lost. [4]

(b) A star-connected, 4-pole synchronous generator which is rated at 750 MVA delivers 400 MW of power to a 50 Hz infinite bus with a line voltage of 22 kV and a power factor of 0.85 lagging. The synchronous reactance is  $1.2 \Omega$  per phase and the stator resistance is negligible. Calculate:

(i) the prime mover torque; [3]

(ii) the generator excitation voltage; [6]

(iii) the load angle. [2]

(c) Explain how the amount of reactive power delivered to the infinite bus can be controlled by the synchronous generator whilst maintaining a constant real power output. What is the maximum reactive power that can be delivered by the generator if it is limited by stator heating? [5]

5 An 8-pole, three-phase, star-connected induction motor is connected to a balanced 50 Hz supply with a line voltage of 415 V. The following tests are performed on the induction motor:

| Line voltage, $V_l$ | Line current, $I_l$ | Input power, $P_{in}$ | Speed   |
|---------------------|---------------------|-----------------------|---------|
| 415 V               | 4.2 A               | 1100 W                | 750 rpm |
| 90 V                | 65 A                | 4500 W                | 0 rpm   |

The stator winding resistance,  $R_1$ , is  $0.2 \Omega$ . The stator leakage reactance,  $X_1$ , is half that of the rotor leakage reactance referred to the stator,  $X'_2$ .

- (a) Find the values of the following in the equivalent circuit of the induction motor:
- (i) the iron loss resistance,  $R_i$ ; [3]
  - (ii) the magnetizing reactance,  $X_m$ ; [2]
  - (iii) the rotor winding resistance referred to the stator,  $R'_2$ ; [3]
  - (iv) the stator leakage reactance,  $X_1$ . [2]
- (b) Calculate the maximum torque and the slip and speed at which it occurs. [6]
- (c) What resistance should be added to the rotor circuit via the slip rings to maximize the starting torque if the ratio of stator turns to rotor turns is 2? [4]

## SECTION C

*Answer at least one question from this section*

6 (a) Fig. 3 shows the equivalent circuit for a small section  $\delta x$  of a lossless transmission line where  $C$  and  $L$  are the capacitance per unit length and inductance per unit length of the transmission line respectively. Using this circuit element, derive the Telegrapher's Equations:

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2} \quad \text{and} \quad \frac{\partial^2 I}{\partial x^2} = LC \frac{\partial^2 I}{\partial t^2} \quad [4]$$

(b) The capacitance per unit length and inductance per unit length of a lossless coaxial cable are given by

$$C = \frac{2\pi\epsilon_0\epsilon_r}{\ln(r_2/r_1)} \quad \text{and} \quad L = \frac{\mu_0\mu_r \ln(r_2/r_1)}{2\pi}$$

where  $r_1$  is the outer radius of the inner conductor,  $r_2$  is the inner radius of the outer conductor, and  $\epsilon_r$  and  $\mu_r$  are the relative permittivity and relative permeability of the filling dielectric respectively. Derive an expression for the velocity of a wave on this coaxial transmission line in the absence of reflections. Comment on the physical significance of your answer. [4]

(c) Calculate the ratio of the radii of the conductors,  $r_2 / r_1$ , if the coaxial cable is to have a characteristic impedance of  $75 \Omega$ , and PTFE is used as the dielectric filling which has a relative permittivity of 2.1 and a relative permeability of 1. [4]



(d) This coaxial cable is to be connected to a second coaxial cable with a characteristic impedance of  $50\ \Omega$  which is itself terminated with a  $50\ \Omega$  load. To eliminate reflections, a short section of a third coaxial cable is connected between the other two, which also uses PTFE as the filler dielectric. The system is to carry signals at a frequency of 10 MHz. Starting from the information in Section 3.10.1 of the Electrical and Information Data Book, calculate the characteristic impedance and length of this third (connecting) coaxial cable.

[5]

(e) What practical problems will be encountered if this system is being used to transmit a frequency modulated (FM) communications signal where the carrier frequency is 10 MHz?

[3]

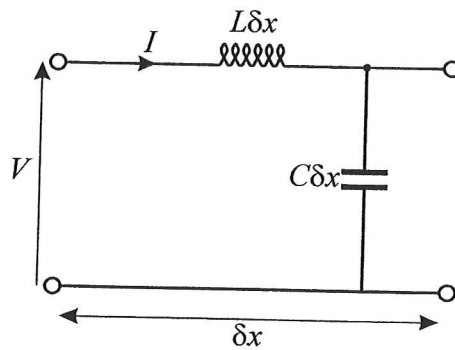


Fig. 3

7 (a) A plane electromagnetic wave propagates through free space along the  $z$ -axis in Cartesian coordinate space. The components of the electric field intensity along each Cartesian axis are given by:

$$\begin{aligned} E_x &= E_{x0} \exp[j(\omega t - \beta z)] \\ E_y &= E_z = 0 \end{aligned}$$

Given that in this simple case, the Maxwell equation  $\nabla \times \mathbf{E} = -\dot{\mathbf{B}}$  reduces to

$$\frac{\partial E_x}{\partial z} = -\frac{\partial B_y}{\partial t},$$

derive an expression for the  $y$ -component of the magnetic field intensity,  $H_y$ .

[5]

(b) Wireless data (Wi-Fi) networks operating at a frequency of 2.4 GHz may be contained within a building by coating glass windows in a thin film of a transparent conductive material, such as indium tin oxide (ITO). ITO has a conductivity of  $10^5 \Omega^{-1} \text{m}^{-1}$ , a relative permittivity of 3.8 and a relative permeability of 1. Using the information in Section 3.10.4 of the Electrical and Information Data Book, calculate the propagation constant,  $\gamma$ , and intrinsic impedance,  $\eta$ , of the ITO seen by the Wi-Fi electromagnetic wave.

[5]

(c) An electromagnetic wave passes from a medium with an intrinsic impedance  $\eta_1$  into a medium with an intrinsic impedance  $\eta_2$  where the direction of propagation is perpendicular to the plane of the surface. If the components  $\mathbf{E}$  and  $\mathbf{H}$  parallel to the boundary surface are continuous across the boundary, show that the transmission coefficient is given by

$$\rho_T = \frac{E_t}{E_i} = \frac{2\eta_2}{\eta_2 + \eta_1},$$

where  $E_t$  and  $E_i$  are the amplitudes of the transmitted and incident electromagnetic waves respectively.

[5]

(d) If the incident Wi-Fi electromagnetic wave has a power density of  $10^{-2} \text{ W m}^{-2}$  in free space at the surface of the ITO, calculate the minimum thickness of ITO required to attenuate the power of the wave to less than  $10^{-7} \text{ W m}^{-2}$ . The power density decays with depth into the conductor,  $d$ , as  $\exp(-2\alpha d)$  where  $\alpha$  is the real component of the propagation constant.

[5]

**END OF PAPER**