

ENGINEERING TRIPOS PART IB

---

Wednesday 8 June 2011

2 to 4

---

## Paper 5 – NUMERICAL SOLUTIONS

## ELECTRICAL ENGINEERING

- 1 (b) Gain = -55.9  
(c) (i) Gain = -222  
(ii)  $Z_{in} = 188 \Omega$
- 2 (c)  $R_1 = 10 \text{ k}\Omega$   
(d)  $C = 1.06 \text{ nF}$
- 3 (b)  $E = 15.3 \text{ kV}$  and  $\delta = 33.9^\circ$   
(c)  $\delta = 29.2^\circ$ ,  $I = 13271 \text{ A}$  and the power factor is 0.99
- 4 (a) (ii) The power is reduced by a factor of one third  
(b) (i) The power factor is 0.84 lagging and the line current is 2650 A  
(ii)  $C = 345 \mu\text{F}$   
(iii) The change in power is 2.3 MW
- 5 (b) (i)  $T_{max} = 180.3 \text{ Nm}$  and  $N_r = 716 \text{ rpm}$   
(ii) Efficiency is 57%
- 6 (b) (i)  $\lambda = 0.467 \text{ m}$   
(ii) The electric field strength is  $0.17 \text{ V m}^{-1}$  and the magnetic field strength is  $459 \mu\text{A m}^{-1}$   
(iii)  $I_{rms} = 0.46 \text{ mA}$   
(iv)  $I_{rms} = 0.39 \text{ mA}$
- 7 (c) (i) Reflected power is 0.275 W  
(ii) Time is  $3.33 \mu\text{s}$