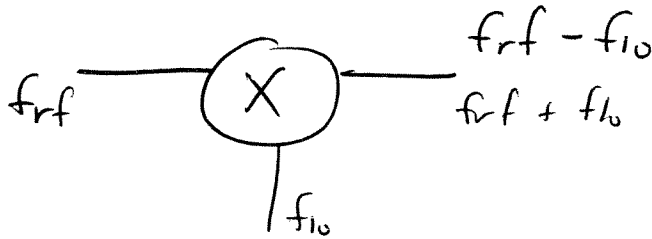



PART IIA MODULE 3B1 2003 SOLUTIONS

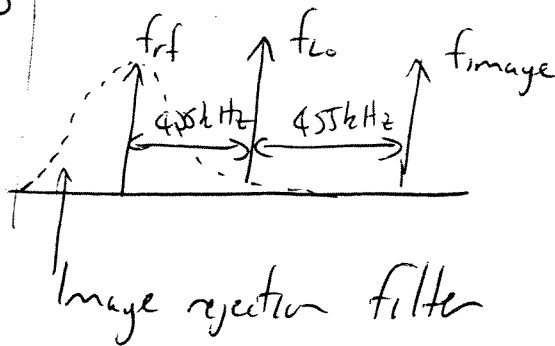Q1 a) Image rejection is an important part of a Superhet Am radio. The mixer produces two possible combinations of the input frequencies: the sum & the difference.



The sum frequency  $f_{rf} + f_{lo}$  is removed by the IF filter stage, however there is still a second RF frequency  $455 \text{ kHz}$  above the  $f_{lo}$  which will be mixed down to  $f_{lo} - f_{rf} = 455 \text{ kHz}$  which is the image frequency.


The image frequency is removed by tuning the input RF signal through a filter ganged to the LO.



$$f_{lo} = 1.6 \text{ MHz}$$

$$\Rightarrow \text{radio station} = f_{lo} - 455 = 1.145 \text{ MHz}$$
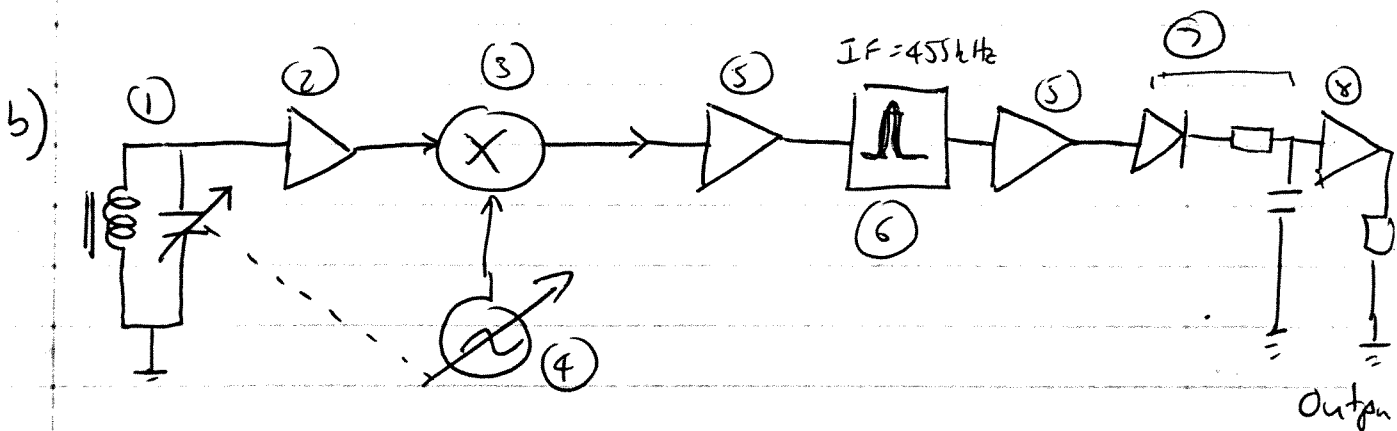
$$\text{Image frequency} = f_{lo} + 455 \text{ kHz} = 2.055 \text{ MHz}$$




① Aerial (inductor) + tuned capacitor ganged to LO. This forms the image rejection filter

- ② RF amp to boost the RF signal & to match impedances (buffer)
- ③ Mixer (analogue multiplier) forms the analogue product of the ~~two~~ two inputs (sum & difference)
- ④ Local oscillator (LO) provides a strong oscillation geared to the RF filter.
- ⑤ IF amps to boost IF ~~frequency~~ signal, narrow band at 455 kHz.
- ⑥ IF filter. Removes sum frequency & other harmonics generated in the LO & mixer ~~plus~~ also removes residual LO signal.
- ⑦ AM demodulator. Performs envelope detection on the IF signal & filters out the sum frequency, leaving the base band signal.
- ⑧ Base band amplifier. (audio amp).


Advantages

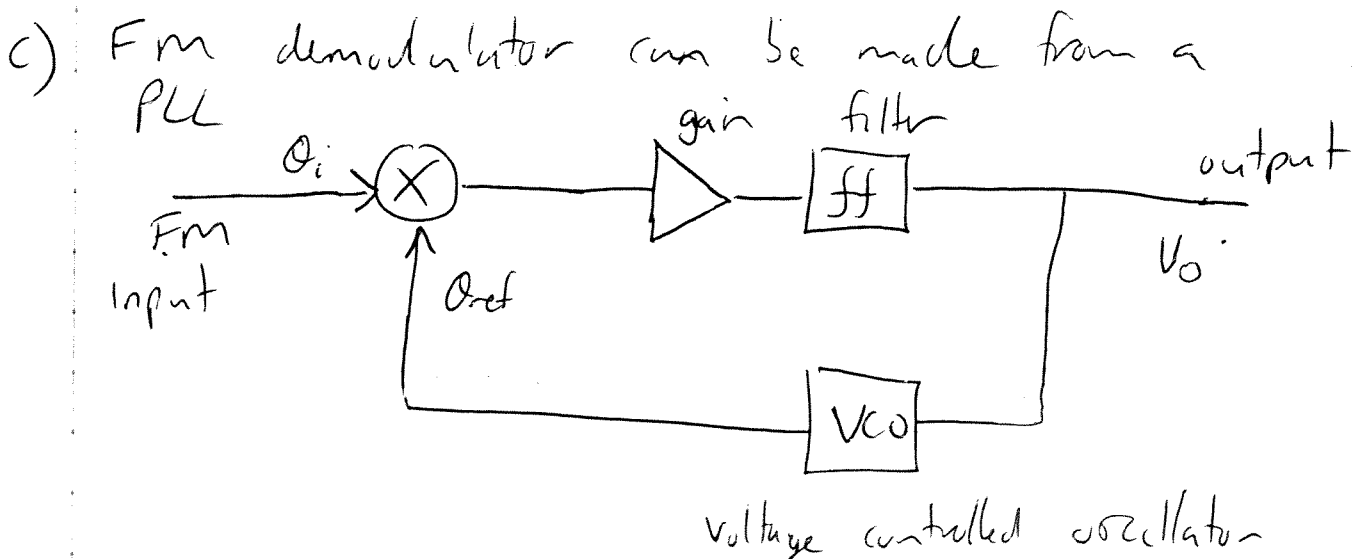- \* More selective than the RF radio
- \* IF amplifier & filter work at fixed frequency  $\Rightarrow$  are simple to design and narrow band
- \* Easier to produce large signal ~~IF~~ (IF) for the AM demodulator  $\Rightarrow$  more linear.
- \* More resistant to noise.




PLL changes the frequency of  $\omega_{ref}$  so that the difference  $\omega_i - \omega_{ref}$  will be zero. Hence the voltage into the VCO is proportional to the frequency of the input signal. If the response time of the PLL is fast enough, then  $V_o$  will be the FM demodulated version of the input signal.

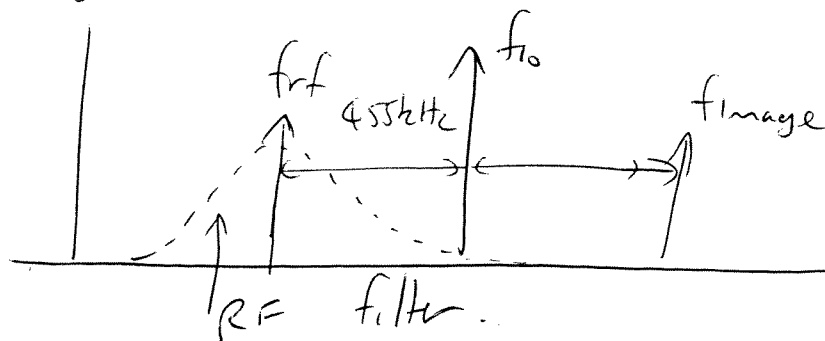d) The LC & RF filter must track in a superhet radio so that the image frequency corresponding to the LC frequency will be rejected. If a static RF filter is used, then the radio response will follow the filter, giving a narrow tuning range for the radio.



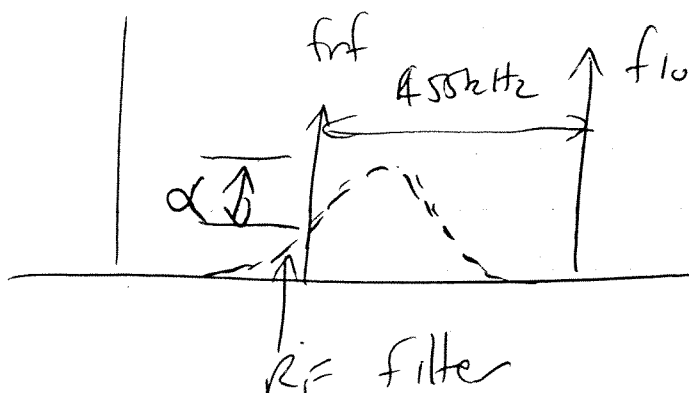
We always want the frequency  $f_{rf}$  which is 455 kHz less than  $f_c$  to be at the peak of the RF filter. Hence it must be ganged to  $f_c$ .



$\alpha$  represents the amount of attenuation due to the RF filter if not properly ganged.

Q2

SSM.

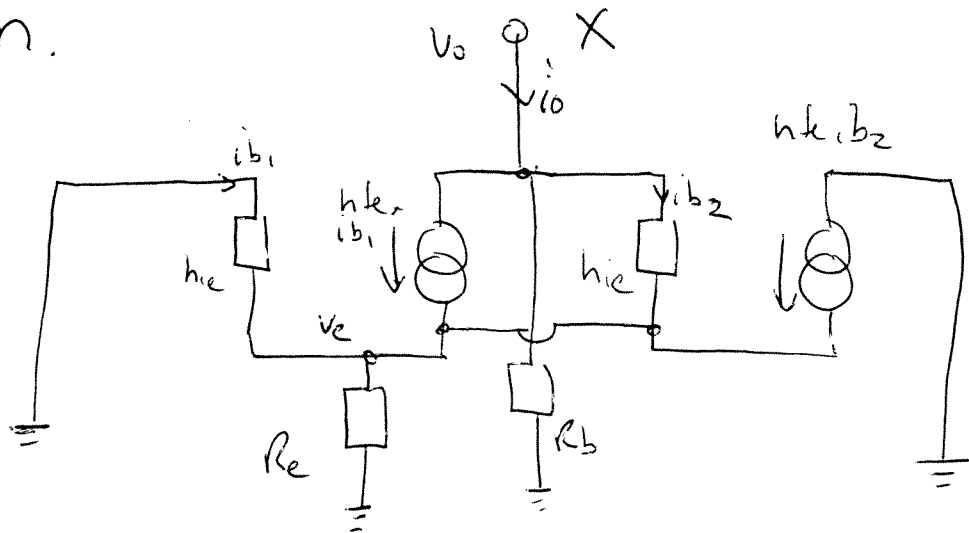

Assume that  $h_{ie}$  is the same for both transistors and that  $C$  is low impedance.

$$\Rightarrow i_{b1} = \frac{0 - v_e}{h_{ie}} = -\frac{v_e}{h_{ie}} \quad i_{b2} = \frac{v_o - v_e}{h_{ie}}$$

$$v_e = (\cancel{1+h_{fe}})(i_{b1} + i_{b2})R_e$$

$$i_o = h_{fe} i_{b1} + i_{b2} + \frac{v_o}{R_b} \quad \text{sub for } i_{b1} + i_{b2}$$

$$= -\frac{h_{fe} v_e}{h_{ie}} + \frac{v_o - v_e}{h_{ie}} + \frac{v_o}{R_b} \quad (1)$$

$$v_e = \left[ -\frac{h_{fe} v_e}{h_{ie}} + \frac{h_{fe} v_o}{h_{ie}} - \frac{h_{fe} v_e}{h_{ie}} \right] R_e = \frac{h_{fe} R_e v_o}{h_{ie}} - \frac{2h_{fe} v_e}{h_{ie}}$$

$$\Rightarrow v_e = \frac{v_o}{2 + \frac{h_{ie}}{h_{fe} R_e}} \quad (2) \quad \text{sub (2) into (1)}$$

$$\Rightarrow i_o = -\frac{h_{fe}}{h_{ie}} \frac{v_o}{2 + \frac{h_{ie}}{h_{fe} R_e}} + \frac{v_o}{h_{ie}} - \frac{1}{h_{ie}} \frac{v_o}{2 + \frac{h_{ie}}{h_{fe} R_e}} + \frac{v_o}{R_b}$$

$$= \frac{v_o}{h_{ie}} + \frac{v_o}{R_b} - \frac{v_o (\cancel{1+h_{fe}})}{h_{ie} \left( 2 + \frac{h_{ie}}{h_{fe} R_e} \right)}$$

if  $h_{fe} R_e \gg h_{ie}$  then  $h_{ie}/h_{fe} R_e \rightarrow 0$

$$\Rightarrow i_o \approx \frac{V_o}{h_{ie}} + \frac{V_o}{R_b} - \frac{V_o h_{fe}}{2 h_{ie}}$$

$$\Rightarrow Z_o = \frac{V_o}{i_o} = \left[ \frac{1}{h_{ie}} + \frac{1}{R_b} - \frac{h_{fe}}{2 h_{ie}} \right]^{-1} = R_b // h_{ie} // \left( -\frac{2 h_{ie}}{h_{fe}} \right) \\ = (-2 r_e)$$

Hence with the correct choice of  $R_b$  &  $R_e$ ,  $Z_o$  will be negative

Check  $V_{SS} = -5V \Rightarrow V_E = -0.75V$

$$\Rightarrow 2 I_E = \frac{-0.75 - (-5)}{22k} = 0.193 mA \quad I_E = 0.1 mA$$

$$\Rightarrow I_C = h_{fe} I_B = \frac{h_{fe} I_E}{1 + h_{fe}} \approx I_E \Rightarrow r_e = \frac{25}{I_C} = \frac{25}{0.1} \text{ mV}$$

$$= 250 \Omega$$





$$h_{ie} = h_{fe} r_e = 50 k\Omega$$

$$\Rightarrow h_{fe} \times R_e = 200 \times 22k = 4.4 M\Omega (\gg h_{ie})$$

$\Rightarrow$  approximation is OK

$$Z_o = 10k // 50k // (-2 \times 250) = -532 \Omega$$

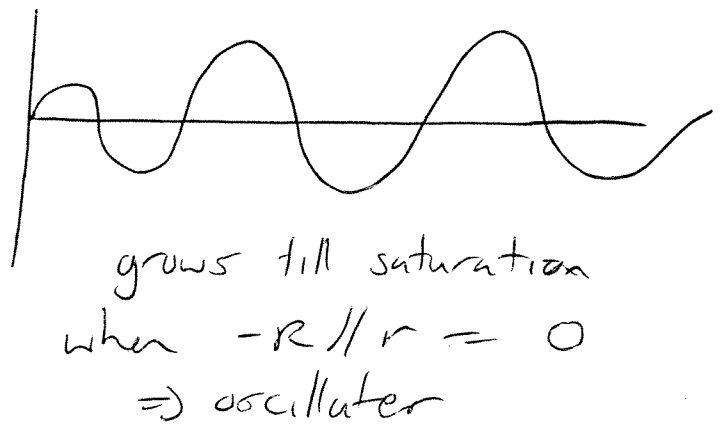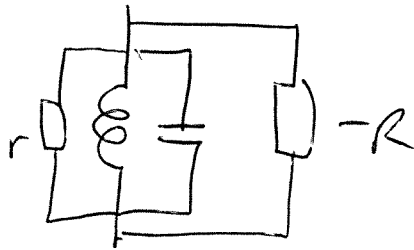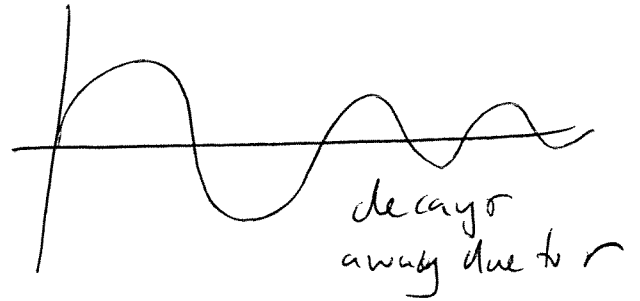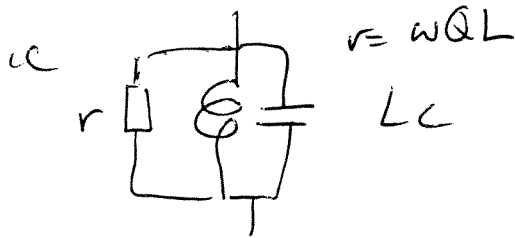b) if a -ve R is combined with an LC resonant tank, then the result will be unstable as long as the -ve R // r at resonance is still negative




1 MHz oscillation  $\Rightarrow \omega^2 = \frac{1}{LC} = (2\pi f)^2$

$\Rightarrow$  choose  $C \approx 50 \text{ pF}$  typical for a tunable capacitor

$\Rightarrow L = \frac{1}{C(2\pi f)^2} = 507 \mu\text{H}$   
 $r = \omega Q L = 2\pi \times 1 \times 10^6 \times 50 \times 507 \times 10^{-6} = 160 \text{ k} (> |r|)$

c) Approx  $f_T = \frac{1}{2\pi C_{ie} r_e} \Rightarrow C_{ie} = \frac{1}{2\pi \times 250 \times 250 \times 10^6}$



$= 2.5 \text{ pF}$

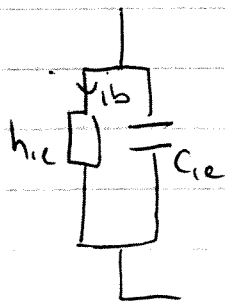

$\Rightarrow \frac{1}{\sqrt{2}}$  point for  $i_b = \frac{1}{2\pi C_{ie} h_{ie}}$

$= 1.27 \text{ MHz} \Rightarrow \text{OK (just)}$

Q3 a)

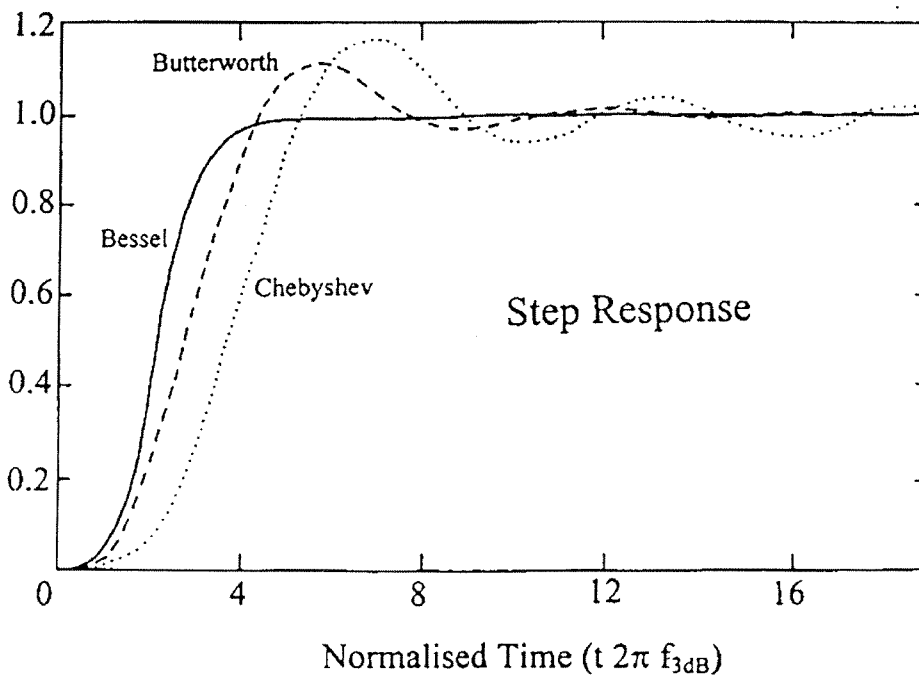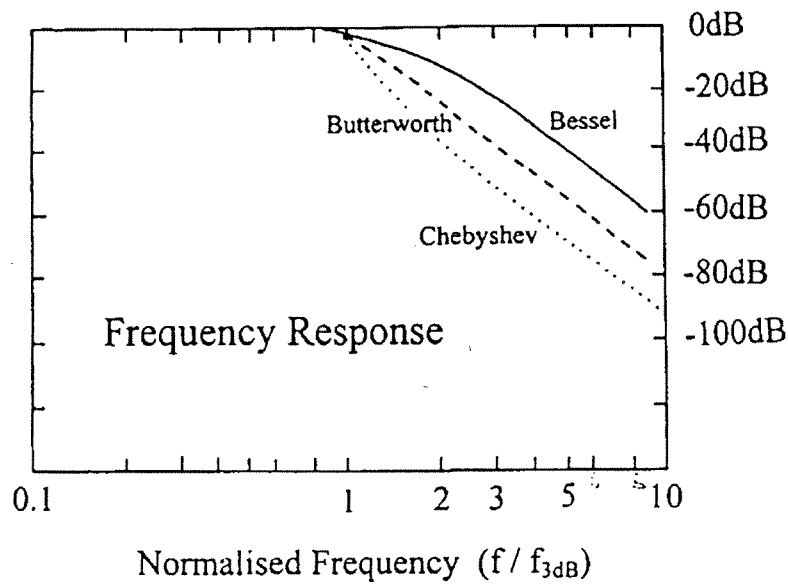


The optimum choice of filter for any particular application will depend on the relative importance of frequency and time performance. The **Bessel** filter is best for **passing transients undistorted**, the **Chebyshev** is best for **sharp frequency cut-off** and the **Butterworth** offers a fair compromise between the two as a **general all-rounder**.

Bessel filter is best when no overshoot is required such as a filter for a chart recorder pen


Chebyshev is best when sharp response is desired such as in an IF amp.

Butterworth is a good compromise between the two  
ie audio filter in a CD player.

Q3 b) Band stop Filter

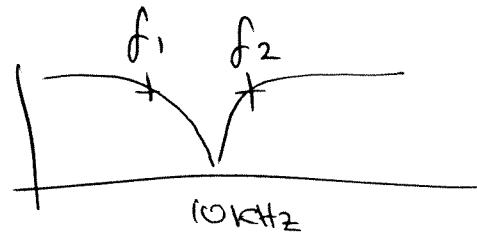

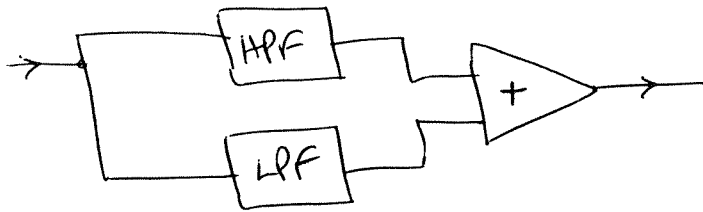Can be made with a LPF and HPF in parallel and adding outputs (assume phase shifts ok for this)



$\Rightarrow$  5 op-amps  $\therefore$  2 op-amps per filter available = 4 poles

$$\text{Butterworth filter atten.} = \left[ 1 + \left( \frac{f}{f_c} \right)^{2n} \right]^{-1/2} \quad (n=4)$$

$$\Rightarrow \frac{1}{100} = \left[ 1 + \left( \frac{f}{f_c} \right)^{2 \times 4} \right]^{-1/2}$$

$$\Rightarrow \frac{1}{10^4} = \frac{1}{1 + \left( \frac{f}{f_c} \right)^8} \Rightarrow \frac{1}{10} = \left( \frac{f}{f_c} \right)^2$$

$$\therefore \left( \frac{f}{f_c} \right)^2 = 10 \quad \therefore \frac{f}{f_c} = \sqrt{10} = 3.16$$


$$\Rightarrow \text{LPF } f_1 = \frac{10\text{K}}{3.16} = 3.16 \text{ kHz}$$

$$\text{HPF } f_2 = 3.16 \times 10\text{K} = 31.6 \text{ kHz}$$

$$\therefore \text{band stop width} = 31.6 - 3.16 = \underline{\underline{28.4 \text{ kHz}}}$$



$\Rightarrow$  VCUS 4pole (2 op-amps)

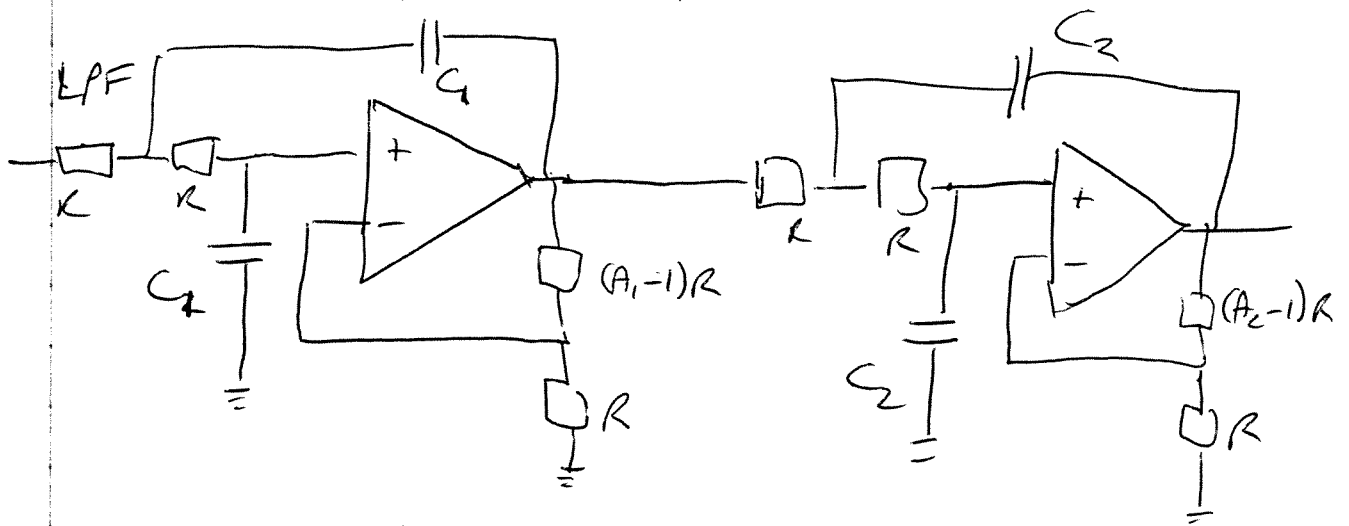

Choose  $R = 10k$

$$\Rightarrow A_1 = 1.586 \quad (A_1 - 1)R = 5.86k\Omega \quad (5.6k\Omega)$$

$$f_{n=1} \Rightarrow f_1 = \frac{1}{2\pi RC_1} = 5.5kHz$$

$$\Rightarrow C_1 = 2.9nF \quad (2.7nF)$$

$$A_2 = 2.235 \quad (A_2 - 1)R = 12.35k\Omega \quad (12k\Omega)$$

$$f_{n=1} \text{ for all } n \Rightarrow C_2 = C_1 = 2.9nF$$

For HPF swap around  $R$  &  $C$ 's in ckt above and use  $1/f_n = 1$

$$\Rightarrow A_1 = 1.586 \quad (A_1 - 1)R = 5.86k\Omega \quad (5.6k\Omega)$$

$$1/f_n = 1 \quad f_2 = \frac{1}{2\pi RC_2} = 18kHz$$

$$\Rightarrow C_3 = 0.88nF \quad (820pF)$$



$$(A_2 - 1)R = 12.35 \text{ k}\Omega \quad (12 \text{ k}\Omega)$$

$$C_4 = C_3 = 820 \text{ pF}$$



Final Op/amp can be used to add together the two filters to give the final band-stop.

c) Design such that at  $10 \text{ kHz}$ , the attenuation will be  $100$ .


LPF

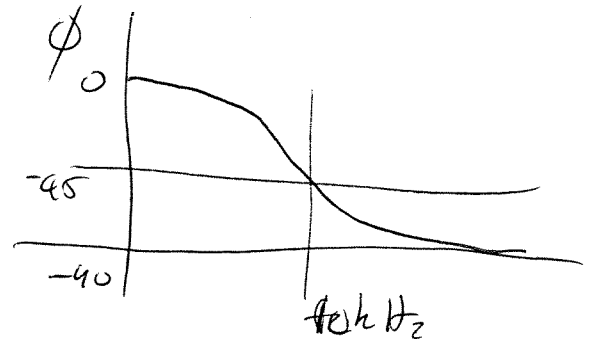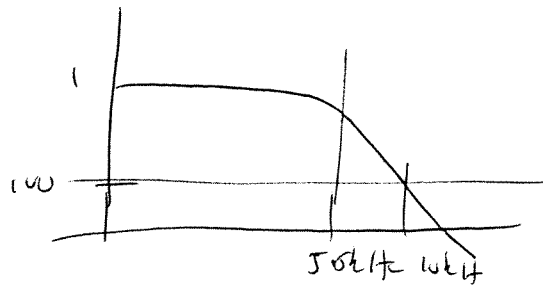



HFP

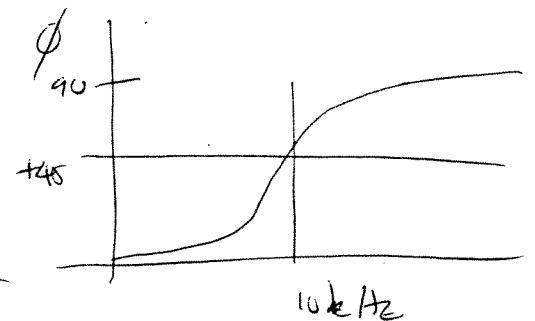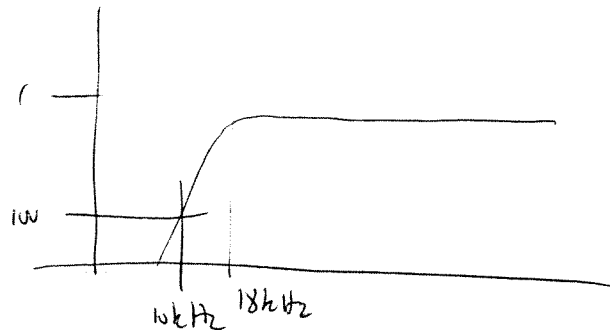

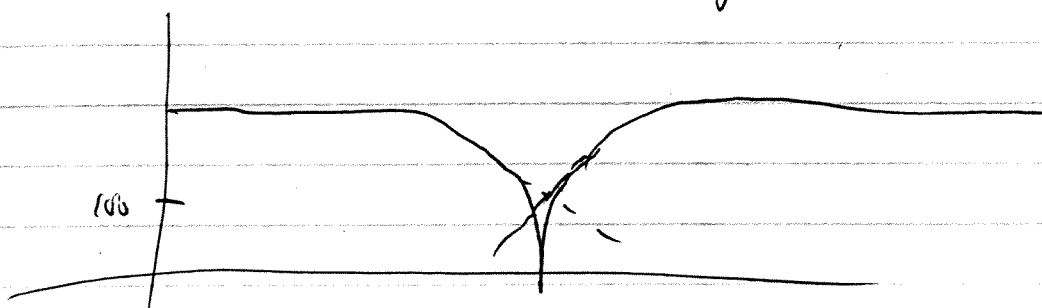LPF & HPF are out of phase at  $f_c = 10 \text{ kHz}$ . Hence there will be strong destructive interference at the  $f_c$  frequency when the two filters are added together. This gives a much stronger attenuation than the  $100$  designed for at  $10 \text{ kHz}$ .




Q4 a) Quarter wave match

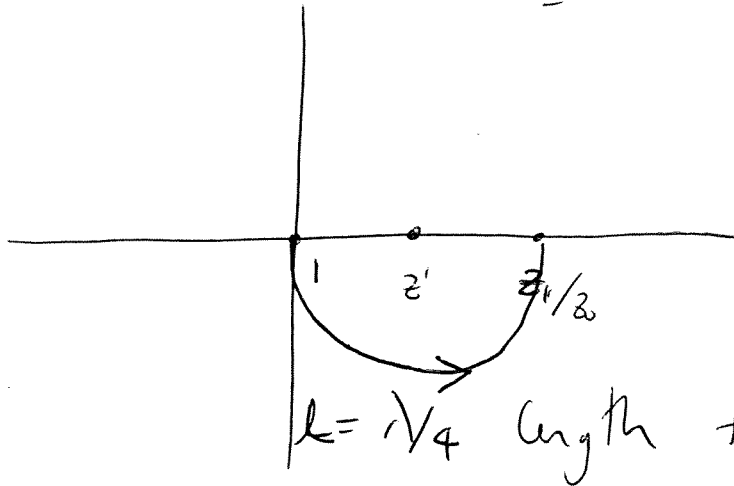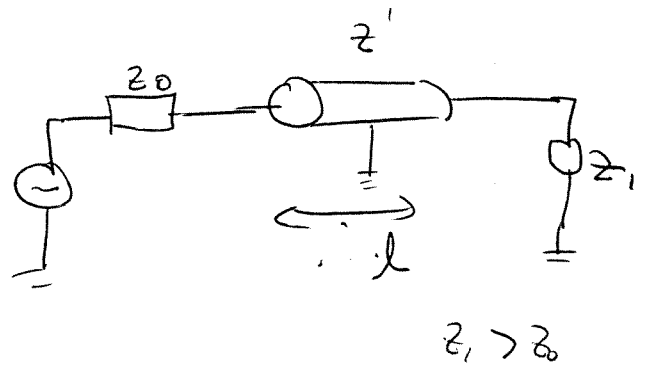

$$Z' = \sqrt{Z_0 Z_L}$$

ii) Series Inductor/capacitor

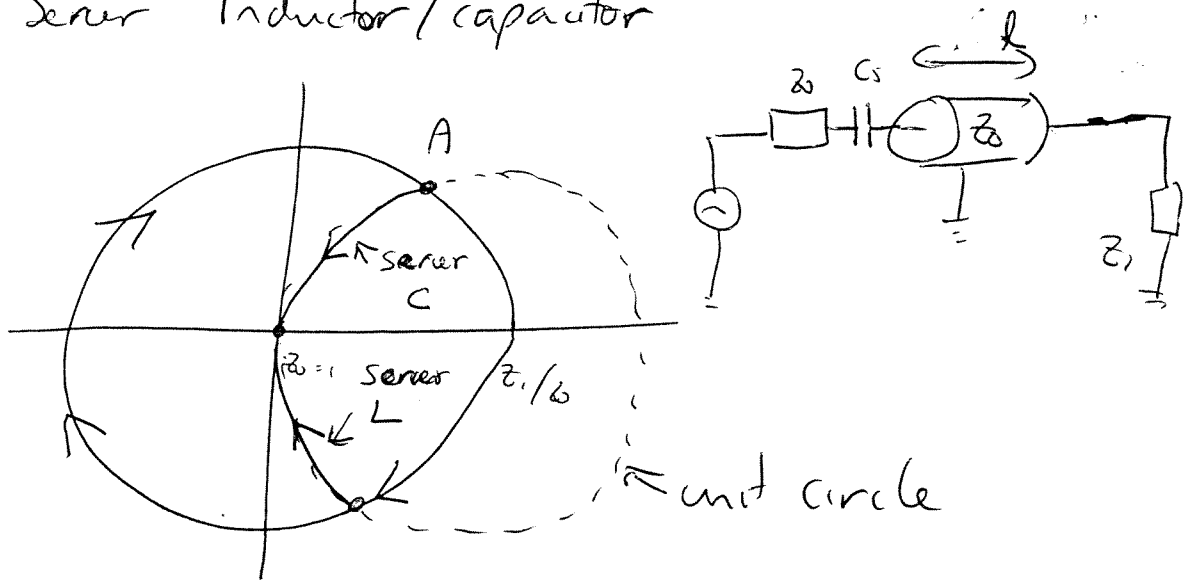

Point A gives the intersection of the transmission line path with the unit circle. This defines the series capacitance needed to match the line

Point B gives the intersection of which defines the series inductance

b) Capacitance  $C = \frac{A\epsilon}{d} = \frac{(w+2d)\epsilon_0\epsilon_r}{d}$  per m


The  $2d$  component allows for fringing field effects

$$Z_0 = \sqrt{\frac{L}{C}} \quad v = \frac{1}{\sqrt{LC}} \quad C_0 = \frac{1}{\sqrt{\mu_0\epsilon_0}}$$

Speed  $v = \frac{1}{\sqrt{\epsilon_r\epsilon_0\mu_0}} = \frac{C_0}{\sqrt{\epsilon_r}}$

$$Z_0 = \sqrt{\frac{L}{C}} = \frac{1}{vC} = \frac{d}{\epsilon_0\epsilon_r(w+2d)} \times \frac{\sqrt{\epsilon_r}}{C_0}$$
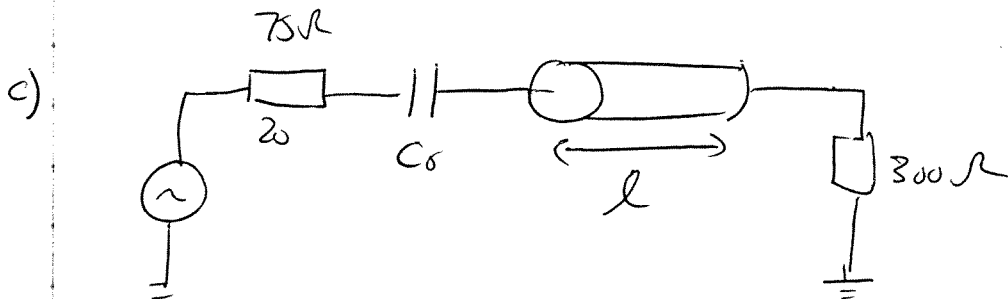
$$= \frac{d}{(w+2d)C_0\epsilon_0\sqrt{\epsilon_r}}$$



choose  $Z_0 = 75\Omega$

$$75 = \frac{0.15 \times 10^{-3}}{(w + 1 \times 10^{-3})^2 \times 3 \times 10^8 \times 8.85 \times 10^{-12} \times \sqrt{3.13}}$$

$\Rightarrow w = 0.38 \text{ mm}$  (ib/300 $\Omega$  cannot be made in this system)

$$Z_0 = 75\Omega \quad \text{and} \quad Z_L = \frac{300}{75} = 4$$

\* See Smith Chart  
12

# The Complete Smith Chart


## Black Magic Design

SERIES  $C_s$   
= 1.15

$$Z_0 = 75 \Omega$$

$$l_c = 0.25 + 0.1765 = 0.4265 \lambda$$

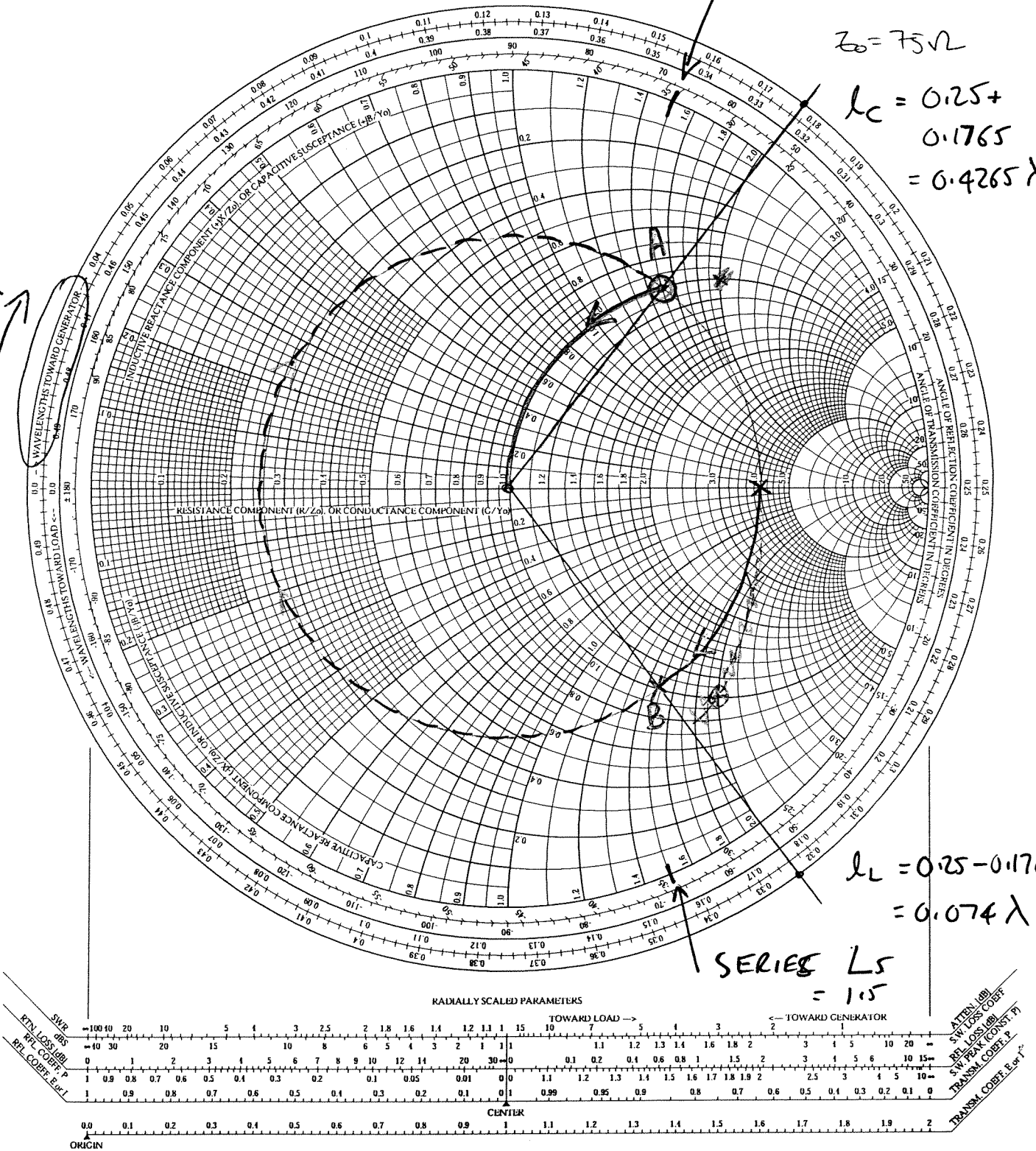WAVELENGTHS TOWARD GENERATOR  
WAVELENGTHS TOWARD LOAD



c) For Series Capacitor

$$X_C = 115 \times 75 = 112.5 \Omega = \frac{1}{\omega C_S}$$

$$\Rightarrow C_S = \frac{1}{\omega X_C} = \frac{1}{2\pi \times 10^9 \times 112.5} = 1.4 \text{ pF}$$

$$\text{length } l_c = 0.4265 \lambda \quad \lambda = \frac{v}{f} = \frac{c_0}{f \sqrt{\epsilon_r}} = \frac{3 \times 10^8}{1 \times 10^9 \sqrt{3.3}} = 0.165 \text{ m}$$

$$\Rightarrow l_c = 0.4265 \times 0.165 = 0.07 \text{ m (70 mm)}$$

For dc path you must have a series inductor.

$$\Rightarrow X_L = 115 \times 75 = 112.5 \Omega = \omega L_S$$

$$\Rightarrow L_S = \frac{112.5}{2\pi \times 10^9} = 18 \text{ nH}$$

$$l_c = 0.074 \lambda = 0.074 \times 0.165 = 0.012 \text{ m (12 mm)}$$

If  $\lambda/4$  matching were to be used, then ~~the~~

$$Z_0 = \sqrt{75 \times 300} = 150 \Omega$$

$\Rightarrow w = -0.3 \text{ mm}$  which means that this characteristic impedance is not possible.

$\Rightarrow \lambda/4$  matching will not work.