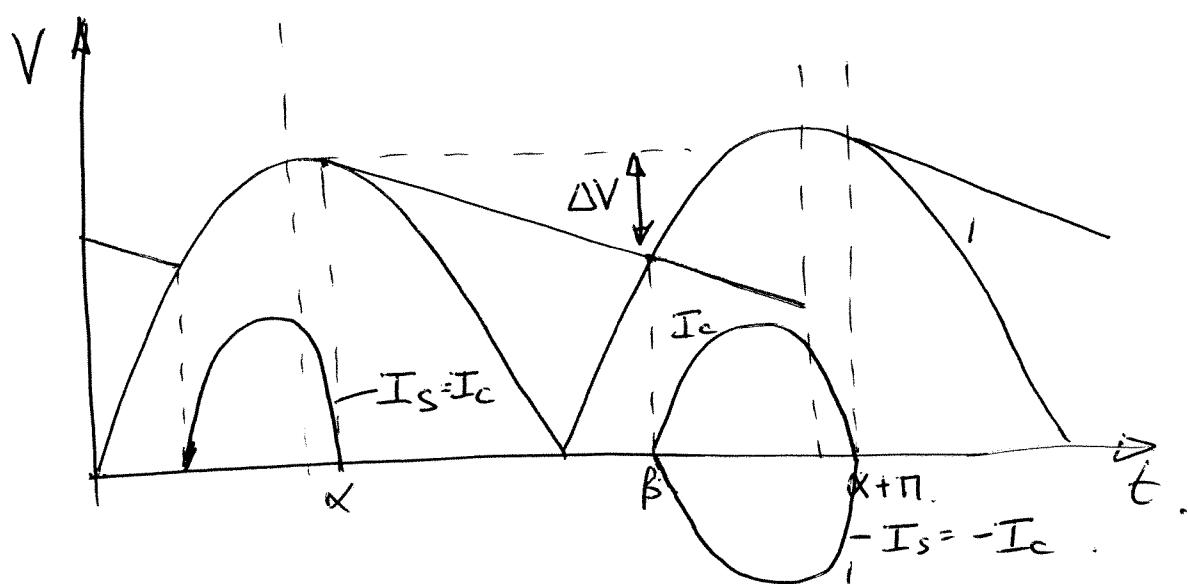


(a)



Charging from β to $\alpha + \pi$ each half cycle.
Discharging from α to β , with ripple of ΔV

For simple equation assume

1, Charging time is negligible.

2, Linear decay in voltage.

$$\text{so } I = C \frac{dV}{dt} = C \frac{\Delta V}{\Delta T}$$

$$\text{Ripple } \Delta V = \frac{I \Delta T}{C} = \frac{I}{2FC} \cdot 4$$

Taking large currents at the top of the supply voltage waveform causes problems due to the impedance of the supply. The voltage peak gets flattened - $\frac{1}{3}$ harmonic.²


1(b).

$$\begin{aligned}
 I &= C \frac{d}{dt} 415\sqrt{2} \sin \omega t \\
 &\quad \text{80%} \rightarrow \frac{\sin^{-1} 0.95}{72^\circ} \\
 &= C \cdot 415\sqrt{2} \cdot 2\pi \cdot 50 \cos 80^\circ 72^\circ \\
 &= 11.36 \text{ m} \cdot 415\sqrt{2} \cdot 100\pi \cdot 0.174 \\
 &= \underline{363A} \cdot \underline{653A^2}
 \end{aligned}$$

$$I = C \frac{dV}{dt}$$

$$\Delta V = \frac{I}{C} \cdot \Delta T$$

60° each pulse.

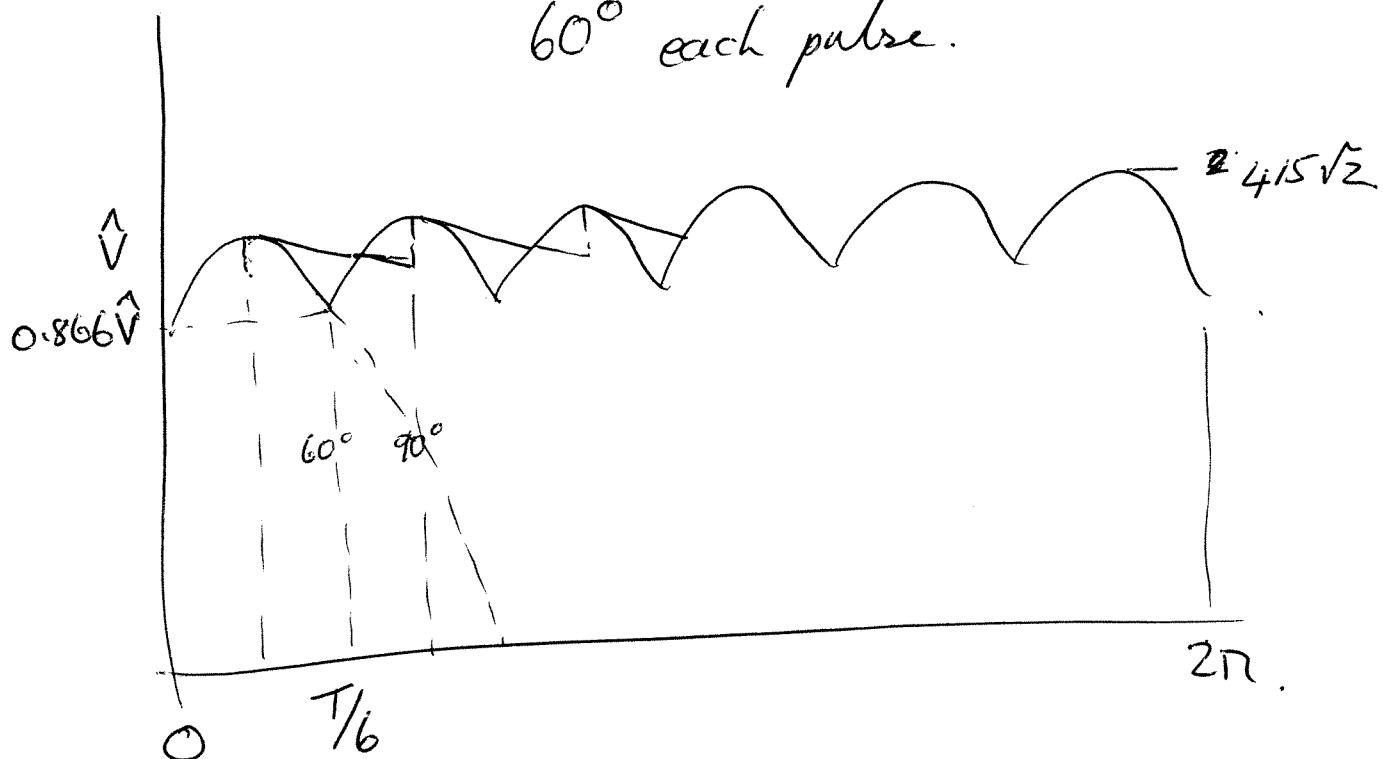


5% ripple. $\Delta V = I \frac{\Delta T}{C}$

$$C = 100A \cdot \frac{1}{6f} \cdot \frac{1}{415\sqrt{2} \times 0.05}$$

$$= 11.36 \text{ mF}$$

For 1% ripple

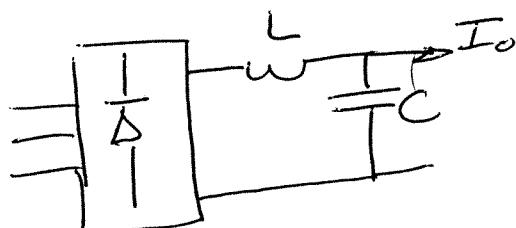

Treat it as a filter to the 3wo frequency.

$$\frac{1}{1 + -9\omega^2 LC} = 0.01$$

1(b) cont

$$\frac{1/j\omega C}{1/j\omega C + 1/j\omega L} = \frac{1}{1 + j\omega^2 LC} = 0.01 \times 10^{-14}$$

$$1 - j\omega^2 LC = 100^{-14}$$

$$3rd \approx 0.14 \times 415\sqrt{2} \text{ ph-ph.}$$

Reduced to $0.01 \times 415\sqrt{2}$.

Ratio of 14

$$|j\omega^2 LC| = \frac{13}{99}$$


$$\omega^2 LC = \frac{13}{99} \cdot \frac{1}{q}$$

$$L = \frac{13}{99} \cdot \frac{1}{9C\omega^2}$$

$$= \frac{13}{99 \cdot 11.36 \text{ m} \times (314)^2 \cdot 9}$$


$$= 1.29 \text{ mH}$$

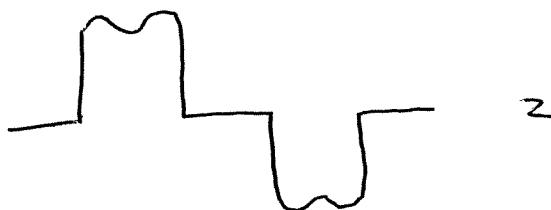The inductor keeps the current I_0 flowing, even when the supply voltage is dropping, so the supply current become quasi square with the ripple on top.



2 a) IGBTs are good devices for voltages between 600V and 3.3kV (or above). They are available in current ratings from about 25A to 2500A. IGBTs have a MOS-gate so the drive requirements are pretty easy compared to Bipolars, GTOs. IGBTs may also be operated at high frequencies, depending on the rating — inaudible, reduced harmonics.

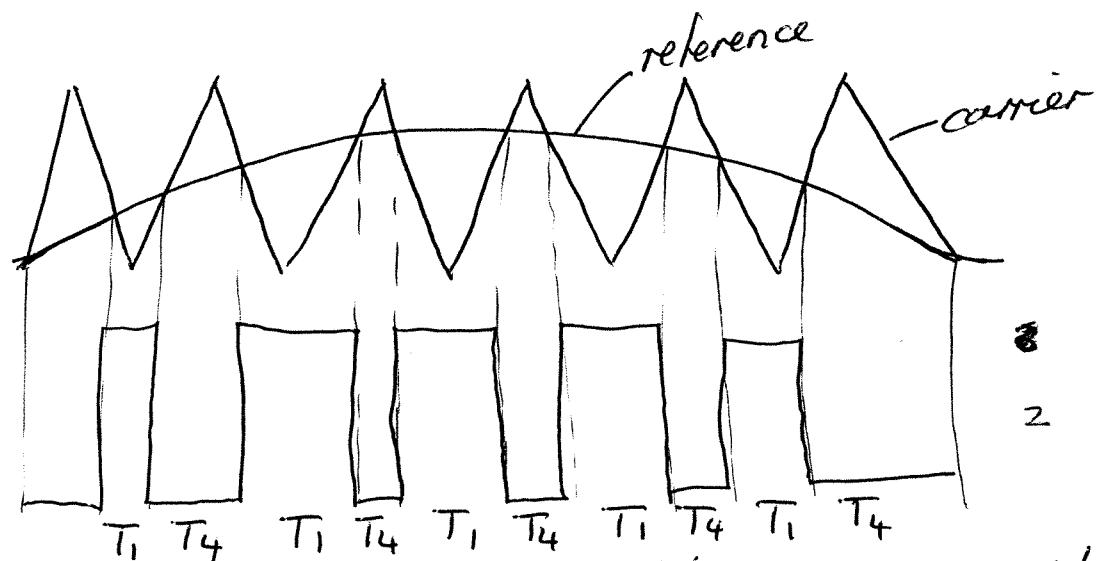Sinusoidal pwm control signals are created using a carrier frequency waveform and a sinusoidal modulating waveform (reference).



Not a great sketch!

In the inverter:

switches: top	1	3	5
lower	4	6	2
	V _A	V _B	V _C

2a cont

The three legs are controlled in a similar fashion, with there being 3 reference waveforms, which are 120° apart ($0^\circ, 120^\circ, 240^\circ$), to give the correct phasing of the outputs V_A, V_B, V_C . Clearly analog circuits may be used, but these are unattractive for such complexity. A $\frac{1}{4}$ cycle of pwm may stored and duty ratio modulation added to it*. Then three pointers are clocked through it at a variable rate.

* for variable voltage.

Or a large ROM lookup table used. Proprietary chipsets seem to have disappeared with the advent of DSPs and chip microprocessors.²

Gear changing is required to keep the switching frequency in a small range, while the reference frequency changes ~ losses are stable, delays accommodated and integral, odd integer ratio of carrier to reference maintained (no subharmonics)²

2 (b)



States.

	A	B	C	State
1	0	0	0	V_1
1	1	0	0	V_2
0	1	0	0	V_3
0	1	1	0	V_4
0	0	1	0	V_5
1	0	1	0	V_6
1	1	1	0	V_7
0	0	0	0	V_8

4

The voltages produced by the bridge can be considered as summing as a vector, where V_A , V_B and V_C are 120° apart.
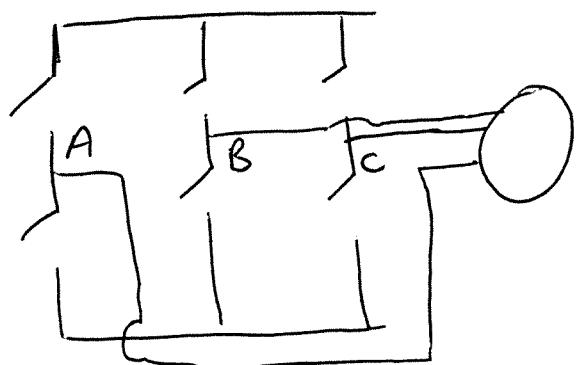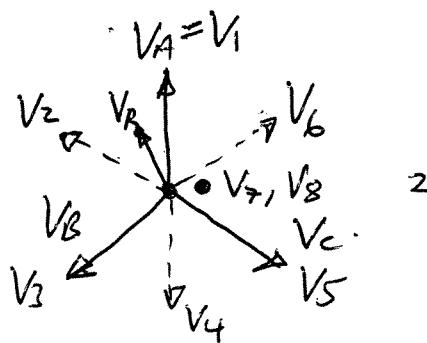
$$\text{eg. } V_1 \Rightarrow V_{AB} = V_{dc}, V_{AC} = V_{dc}.$$



For V_R as drawn.


$$V_R = m_A V_{A1} + m_B V_{B2} \text{ for SVM.}$$

$$V_R = m_A V_A + m_B V_B + m_C V_C \text{ for PWM}$$

So C is not switching if V_8 is the PNM=SVM for massive overmodulation, zero state used. 4

3. (a) 2 advantages:
1. Efficiency of SMPS is greater.
 2. Energy storage elements are smaller due to higher operating frequencies (these include isolation transformer).

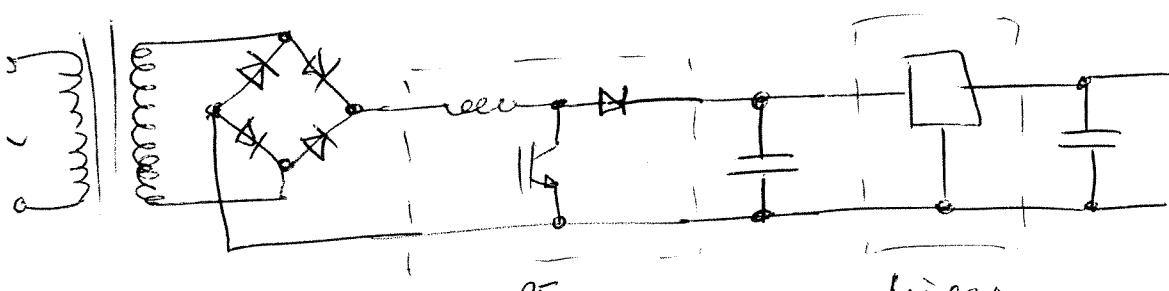Example circuit: SMPS (boost converter) provides power factor correction for linear regulator circuit.





(Produces sinusoidal current in diodes and transformer
⇒ low distortion, good power factor)

linear regulator.

(Provides better ripple rejection than PFC regulator for low-noise applications).

3 (b).

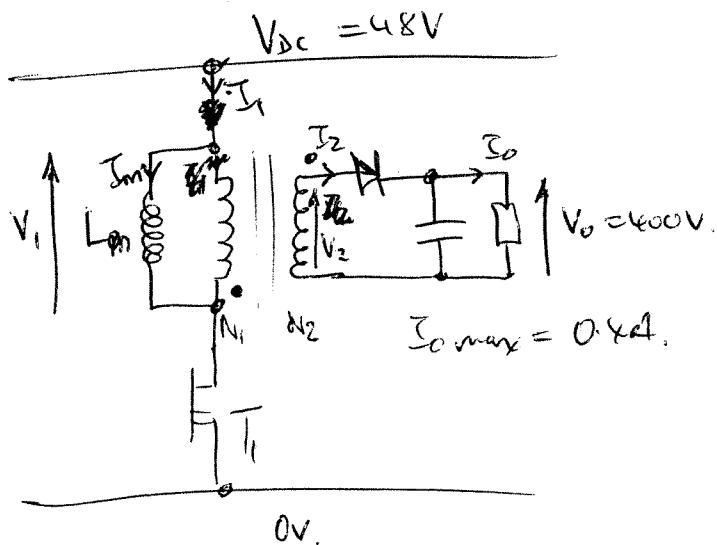

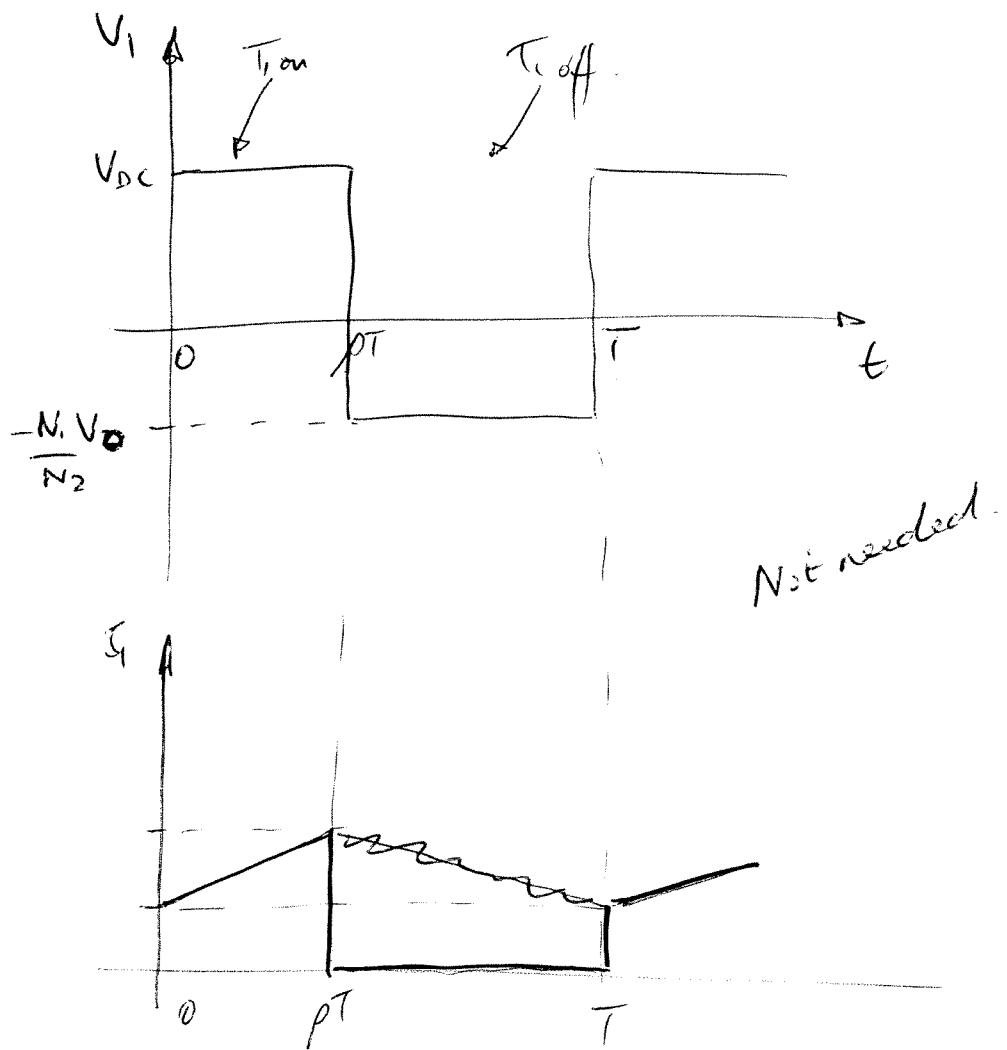

~~Other cases~~


$$\Rightarrow N_2 I_2 = \alpha (I_m - I_1) N_1$$

$$\Rightarrow I_2 = \frac{N_1}{N_2} (I_m - I_1)$$

~~Now~~ Now $I_2 = 0$ for $0 \leq t < pT$

$I_1 = 0$ for $pT \leq t < T$.

$\Rightarrow I_m$ is:

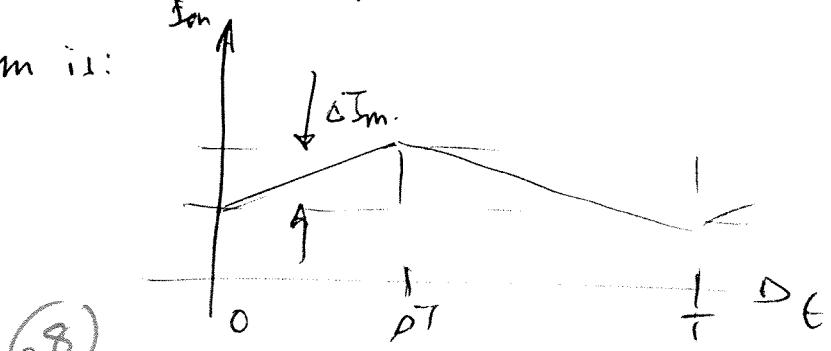

Considering & $V_i = \text{Im} \frac{\Delta I_m}{dt}$

$$\Rightarrow T_{\text{m}}: V_{dc} = \frac{\text{Im} \Delta I_m}{PT} \quad (1)$$


$$T_{\text{eff}}: -\frac{N_1 V_o}{N_2} = -\frac{\text{Im} \Delta I_m}{(1-p)T} \quad (2)$$

$$\Rightarrow (2) \div (1) \text{ is: } \frac{V_o N_1}{N_2 V_{dc}} = \frac{p}{1-p}$$

$$\Rightarrow V_o = V_{dc} \frac{N_2}{N_1} \frac{p}{1-p}$$

Average $I_o = 0.4A$.

Waveforms: I_2

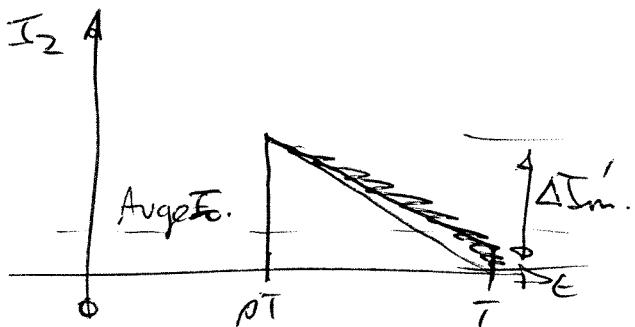

$$\text{Avg. } I_o = (1-p) \frac{\Delta I_m'}{2} = 0.4$$

$$p = 0.3 \Rightarrow \Delta I_m' = \frac{0.4 \times 2}{0.7} = \frac{0.8}{0.7} A.$$

$$V_o = V_{dc} \frac{N_2}{N_1} \frac{p}{1-p}$$

$$\Rightarrow 400 = 48 \left(\frac{N_2}{N_1} \right) \left(\frac{0.3}{0.7} \right) \Rightarrow \frac{N_2}{N_1} = \frac{400 \times 0.7}{48 \times 0.3} = 19.444, \text{ say}$$

20.

$$\Rightarrow \Delta I_m \text{ on primary side} = \frac{0.8 \times 20}{0.7} = 22.9 A$$

$$T = 10e-6 \text{ sec} \\ (\text{perm} f = 100 \text{ Hz}) \Rightarrow V_{dc} = \frac{\text{Im} 22.9}{n = 100, 100} \Rightarrow \text{Im} = \frac{48 \times 0.3 \times 10e-6}{22.9} = \underline{\underline{6.3 \mu H}}$$


3 cont

assume capacitor C is ~~ideal~~ provides ideal smooth current under all conditions.

Energy in during $V = \frac{Ldi}{dt}$.

$\frac{1}{2} I_0$ means $\frac{1}{2}$ power $\Rightarrow \frac{1}{2}$ energy.
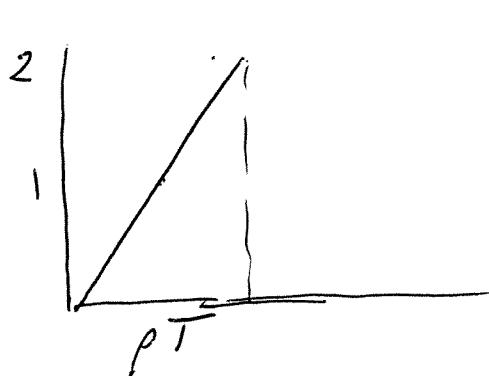
$$\text{Energy} = \int VI dt = V \int Idt \text{ here.}$$



$$= V_{DC} \cancel{\frac{1}{2}} 2PT$$

$$\text{The } V = \frac{Ldi}{dt}$$

$$I = \frac{1}{L} \int V dt$$

$$= \cancel{\frac{1}{2} \int \frac{V^2}{L} dt}$$

$$\Delta I_0 = \frac{1}{L} V_{DC} PT$$

$$\text{Energy} = \frac{1}{2} V_{DC} \cdot PT \times \frac{1}{L} V_{DC} PT = \frac{1}{2} V_{DC}^2 \cdot \frac{1}{L} P^2 T^2$$

V_{DC}, L, T are fixed


$$\frac{1}{2} \text{ Energy } P_2^2 = \frac{P_1^2}{2} = \frac{0.3^2}{2}$$

$$P_2 = \frac{0.3}{\sqrt{2}} = \underline{\underline{0.212}} \quad 4$$

What is the conduction time of the diode
~~under these conditions~~


Comment on the requirements for C under these conditions.

4

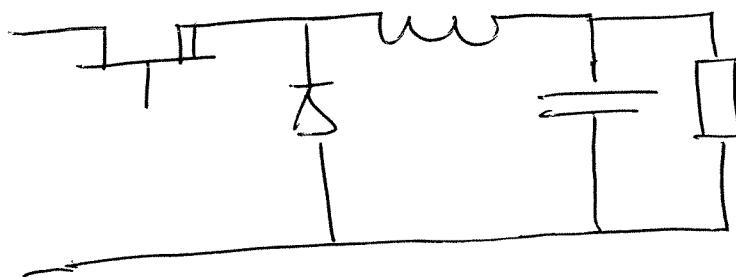


T	D
I	I
T	O
O	I
O	O

diode recovery.

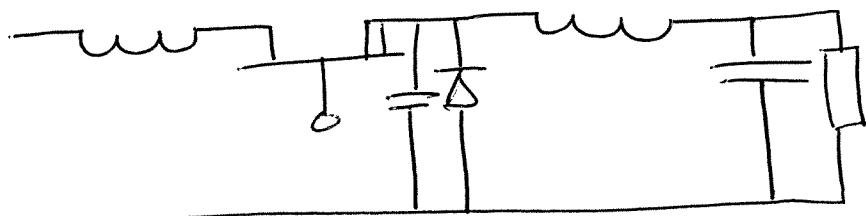

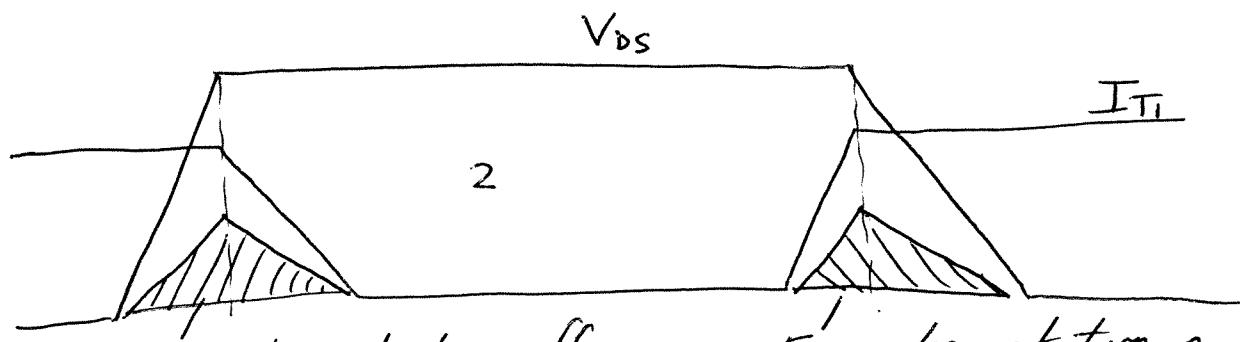
a) L and C are small for effective filtering
and a fast response due to a high 'sampling'
rate.²




Energy loss at turn off.

Energy loss at turn on

$$\text{Power losses} = \text{Energy loss} \times \text{freq.} + \text{on-state losses}^2$$

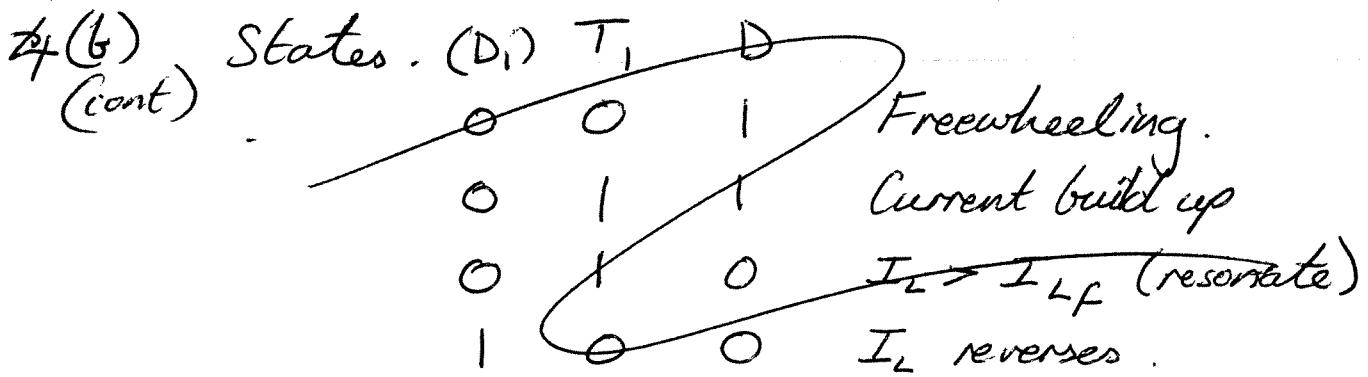States.

	(D_1)	T_1	D	
(1)	0	1	0	Mosfet on L_f
(2)	0	0	0	" off / current is in C (charge)
(3)	0	0	1	$C \& L$ resonate (voltage on C grows)
	1	1	1	/
	1	1	1	and comes back again!
	1	0	1	$V_c = 0$ Diode in T_1 conducts
	1	1	1	and T_1 turned on!
	1	1	1	Constant $\frac{dI_L}{dt}$ bringing I_L
(4)	0	1	0	up from -ve value.

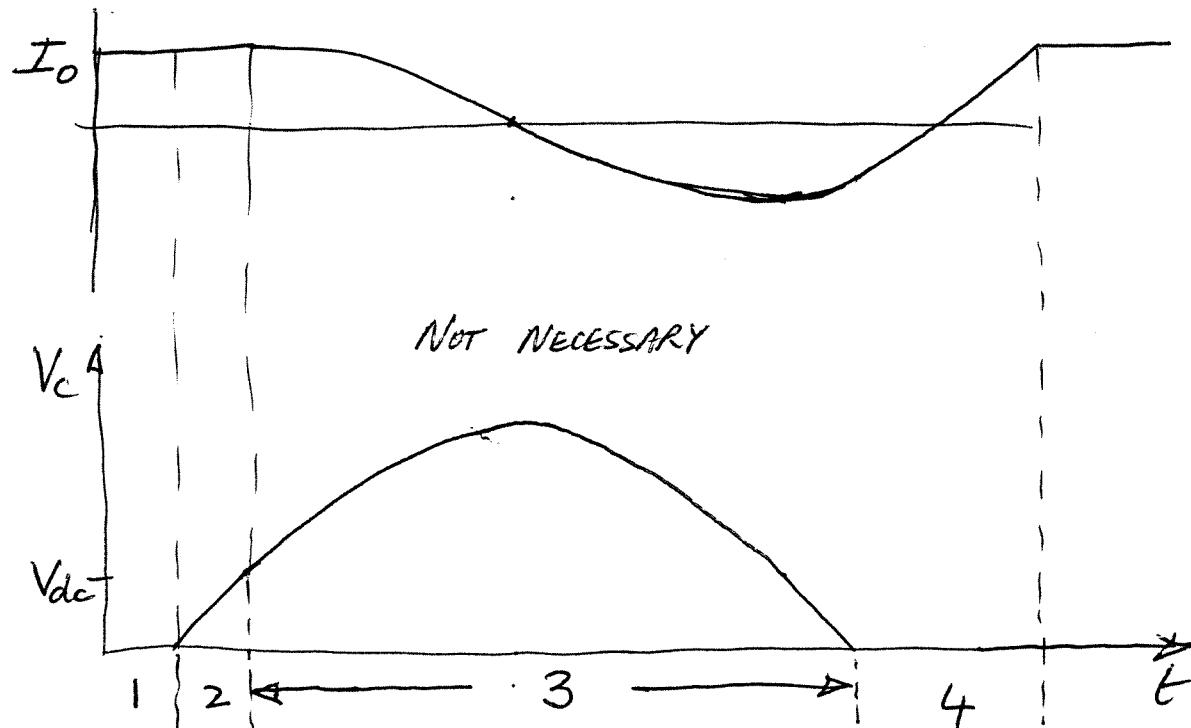


4(b) MOSFET ON, DIODE OFF \rightarrow ^{Usual} Output pulse.

\rightarrow MOSFET OFF, DIODE OFF \rightarrow C charges.
 Not usually possible
 MOSFET OFF, DIODE ON \rightarrow ^{Usual} freewheeling
 MOSFET ON, DIODE ON \rightarrow Usual Diode recovery*

* except the inductance is higher than usual, which is good for diode recovery.

For each state in turn, see attached table and waveforms.

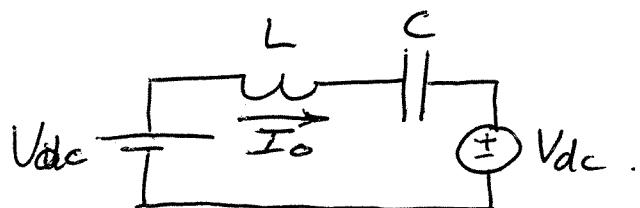The initial voltage on C can be ignored as the Laplace version is



$$\text{So } \max \hat{V}_c = I_o Z_0 + V_{dc} \quad (\text{max switch voltage too})$$

Last Bit

Notice it is resonating the whole time the diode Df is conducting. This is the (1-PT) time for the (SMPS) step down converter. So this time is fixed by the resonance. So the range of P must be set (by the requirements), the basic frequency set and then 1-PT is known.