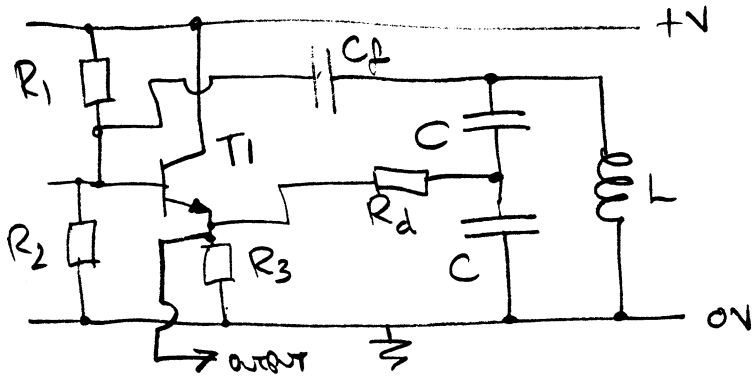


**ENGINEERING TRIPOS PART IIA 2004**

Solutions to Module 3B1  
Radio Frequency Electronics  
Principal Assessor: Dr P A Robertson  
Second Assessor: Dr F Udrea

1 a)



$R_1$  &  $R_2$  base bias resistors

$R_3$  emitter load resistor

$L$  &  $C$ 's resonant tank circuit

$R_d$  tank drive resistor

$C_f$  feedback path

$$f_{osc} = \frac{1}{2\pi\sqrt{LC/2}}$$

$L$  &  $C$ 's provide a resonant parallel LC circuit - with voltage gain, from  $C$  mid-point to top of tank, of  $\times 2$  at resonance. The transistor  $T_1$  is connected as an emitter follower of voltage gain  $\approx 1$   $\therefore$  loop gain  $\approx 2$  and oscillation starts up. Amplitude is limited by the falling gain of  $T_1$  and non-linearity as the emitter swing approaches the voltage supply rails.

b)  $3\text{dBm} \equiv 10 \log_{10} \left( \frac{P}{10^{-3}} \right)$

$\therefore P = 2 \times 10^{-3} \text{ W} = \frac{V^2}{R}$

across  $11\Omega \therefore V = \sqrt{2} \text{ rms}$

$\therefore V_{\text{pk-pk}} = 4\text{V}$  ✓ fine for 10V supply

$f_{osc} = 3 \times 10^6 = \frac{1}{2\pi\sqrt{LC/2}}$

choose  $L = 10 \mu\text{H}$  (arb.)

$\therefore C = 560 \text{ pF}$

$\therefore LC = 5.63 \times 10^{-5}$

b) cont. To bias emitter at +5V, set base at 5.7V.

$$\therefore \frac{R_2}{R_1 + R_2} \cdot 10 = 5.7 \quad \text{Choose } R_2 = 100 \text{ k}\Omega$$

$$\therefore R_1 = 75 \text{ k}\Omega$$

$$R_3 \approx 1.5 \text{ k}\Omega \quad (1.5 \times \text{load impedance})$$

$$R_d \approx (R_1 \parallel R_2 \parallel h_{fe} R_3 \parallel h_{fe} R_{load}) / 5$$


$$= 6.3 \text{ k}\Omega$$

(say 5.6 kΩ standard value) assume  $h_{fe} = 200$

$C_f = 10 \text{ nF}$  say - large value (only  $r_{be}$  impedance @ 3MHz).

Output is likely to be 6V<sub>pp</sub>. (60% of supply) so may need attenuator for 4V<sub>pp</sub>.

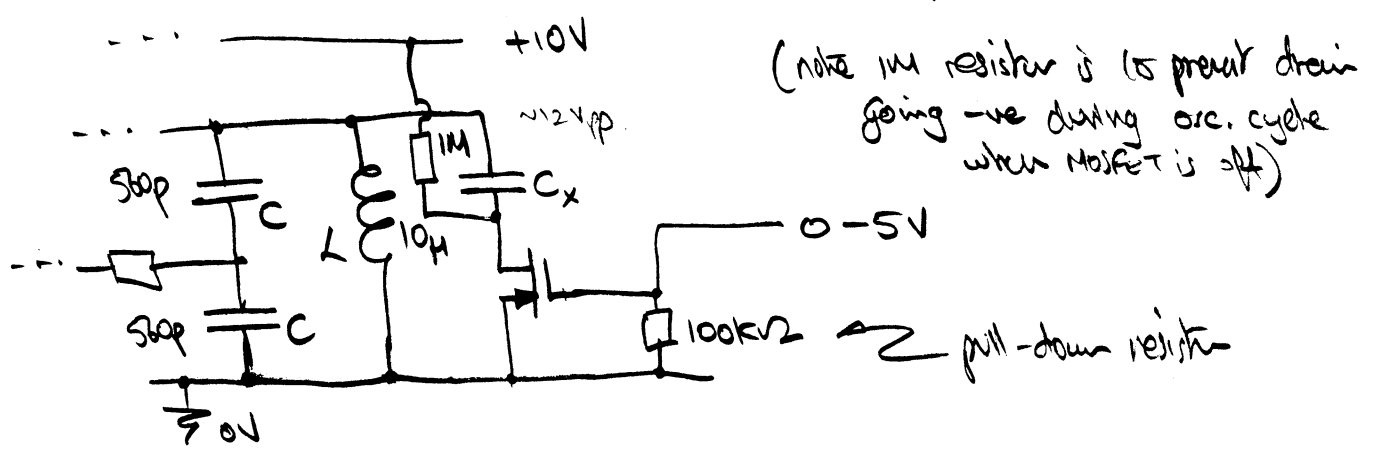c). Tank circuit includes switchable capacitor to drop frequency to 2.5 MHz. - use a MOSFET, check




$$f_{osc} = 2.5 \times 10^6 = \frac{1}{2\pi \sqrt{10^{-5} \cdot (280 \times 10^{-12} + C_x)}}$$

$$\therefore C_x = 125 \text{ pF} \quad (\text{say } 120 \text{ pF standard value})$$

(note: a varactor diode could be used instead, but the large voltage swings would cause non-linear distortion in the signal.)

2a)

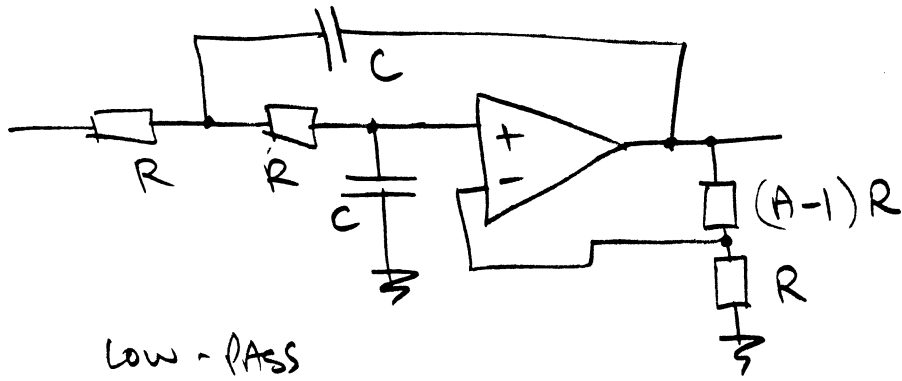


Low-PASS

$$f_{LP} = \frac{1}{2\pi R C}$$

For high pass change over R's and C's at inputs

$$f_{HP} = \frac{f_m}{2\pi R C}$$

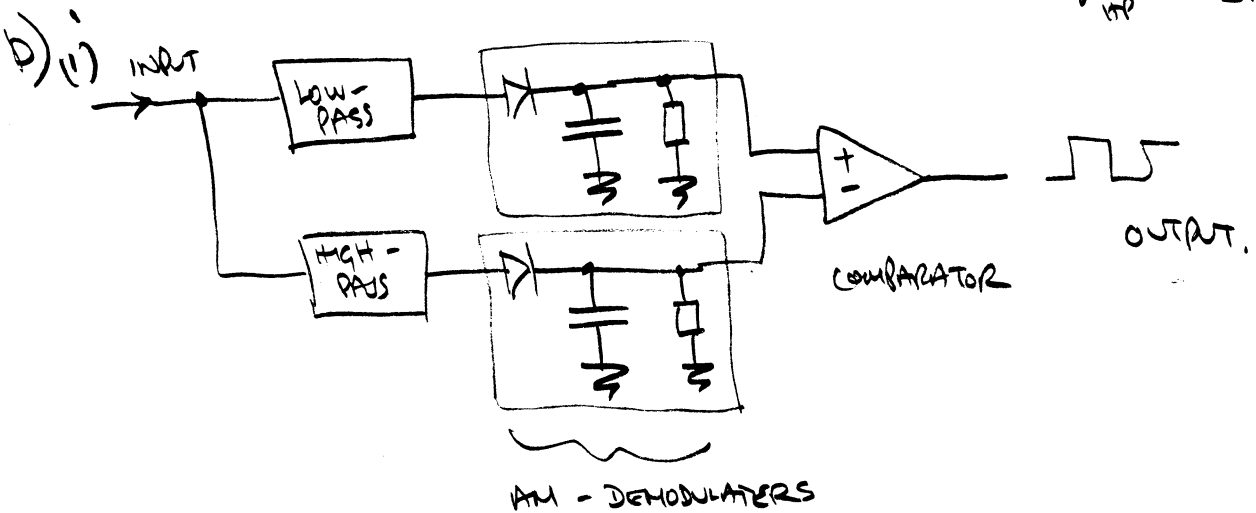

(ii) Choose Chebyshev filter for steeper response in freq. domain and set cut-off frequency at mid-point of 2 FSK frequencies i.e. 2.75 MHz.

For low pass,  $f_m = 1.231$ ,  $A = 1.842$

$$\text{set } R = 1k\Omega \quad \therefore 2.75 \times 10^6 = \frac{1}{2\pi \cdot 1.231 \cdot 10^3 \cdot C}$$

$$\therefore C = 47 \text{ nF}$$

$$(A-1)R = 842 \Omega$$

(820  $\Omega$  std.)

$$\text{For high pass, } 2.75 \times 10^6 = \frac{1.231}{2\pi \cdot 10^3 \cdot C}$$

$$\text{set } R = 1k\Omega$$

$$\therefore C = 31 \text{ nF (say } 33 \text{ nF std.)}$$

$$(A-1)R = 842 \Omega$$

(820  $\Omega$  std.)

2b) ii) cont.

DEMODULATORS :-


(4)

Choose Schottky diodes in demodulators for min drop.

$$\text{(Peak amplitude} = 0.5V \times \frac{1.842}{\sqrt{2}} = 0.65V) \\ \text{@ } -3dB \text{ freq.}$$

$R = 1k\Omega$  - set  $C$  for say 5 cycles equivalent time constant.
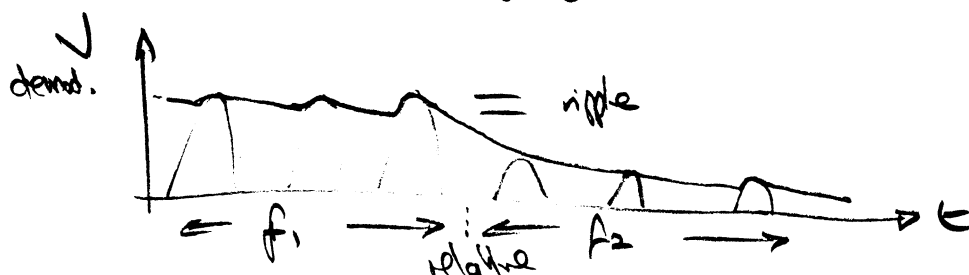
$$\therefore CR = \frac{5}{2.75 \times 10^6} = 1.8 \mu s \quad \therefore C = 1.8 nF$$



We need to check the attenuation gives greater amplitude difference than the ripple. For Chebyshev, we don't know the exact ripple but it is better than a plain CR. So for 20% freq. difference, 2-pole filter the amplitudes of HP and LP outputs will differ by ~40%, or ~0.3V.

Voltage drop with CR diode demodulator given by

$$\approx (1 - e^{-t/CR}) 0.65V \quad \text{where } t \approx \frac{1}{2.75 \times 10^6}$$


$$= (1 - e^{-0.2}) 0.65V$$

$$= 0.12V. \quad \text{OR } \approx \underline{\underline{0.3V}}$$

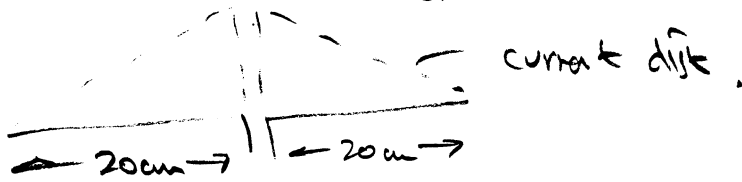b) (iii). Data rate limits are imposed by CR demodulator and depend on time-constant selected (which must be longer than carrier period). Looking at the above, the best we could do is say make the CR time constant  $\approx 2.5 \times$  carrier period.

Then data rate max  $\approx 1MHz$ , (with  $CR \approx 1\mu s$ ).

- 3(a) Skin depth: see part (d)  
 Radiation Resistance,  $R_r$ : power radiated  $P_r = \frac{1}{2} I^2 R_r$  ( $I$  is amplitude not rms)  
 Radiation efficiency,  $e$ :  $= P_r / P_{in}$  where  $P_{in} = \frac{1}{2} I^2 (R_r + R_{ohmic})$  (5)  
 Gain,  $G$ :  $=$  (Max power density radiated in peak direction)  
 Effective Aperture;  $A_e$ : Power received  $= A_e$  Power density (Power density in isotropic antenna)
- (b) 40 MHz,  $\lambda = \frac{3 \times 10^8}{40 \times 10^6} = 7.5 \text{ m}$ .




For ideal dipole (with rectangular current disk)

$$R_r = 80 \pi^2 \left( \frac{\Delta z}{\lambda} \right)^2$$

So for the linear loop case  $\Delta z$  is effectively halved.

$$\therefore R_r' = 20 \pi^2 \left( \frac{\Delta z}{\lambda} \right)^2$$
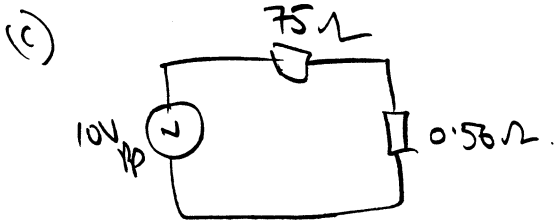
$$R_r' = 20 \pi^2 \left( \frac{0.4}{7.5} \right)^2 = 0.56 \Omega$$



$$P_r = I_{rms}^2 R_r'$$

$$10V_{pp} = 3.54V_{rms}, \quad I_{rms} = 0.047 \text{ A} \quad \therefore P_r = 1.23 \text{ mW}$$

$$\text{Power density on axis} = \frac{P_r}{4\pi r^2} \cdot G = \frac{1.23 \times 10^{-3}}{4\pi \cdot 10^6} \times 1.5 = 1.47 \times 10^{-10} \text{ W/m}^2$$

(Gain = 1.5)

$$\text{Now, } G = \frac{4\pi A_e}{\lambda^2} \quad \text{antenna eqn.}$$


$$\therefore A_e = \frac{G \lambda^2}{4\pi} = \frac{1.5 \times 7.5^2}{4\pi} = 6.71 \text{ m}^2$$

$$\therefore P_{recd} = 1.47 \times 10^{-10} \times 6.71 = \underline{\underline{0.986 \text{ nW}}}$$

(assuming lossless antennas)

$$3(d) \text{ skin depth, } \delta = \sqrt{\frac{2}{\omega \mu \sigma}} = 7.26 \times 10^{-5} \text{ m} \quad (6)$$

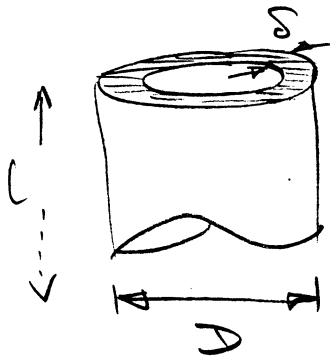(current may be considered to be carried in outer skin of depth,  $\delta$ )  
Assume equal current over 1 arm :-



$$R_{\text{ohmic}} = \frac{l}{\pi D \delta \sigma} = \frac{0.2}{\pi \cdot 10^3 \cdot 7.26 \times 10^{-5} \cdot 1.2 \times 10^6}$$

$$= 0.731 \Omega$$


$$\therefore \text{Radiation Efficiency} = \frac{R_r}{(R_r + R_{\text{ohmic}})} = 0.43$$

$= 0.56 \Omega \text{ from (b)}$

OR     43%

(This is strictly for a rectangular current distribution over half the full length)

4 a)

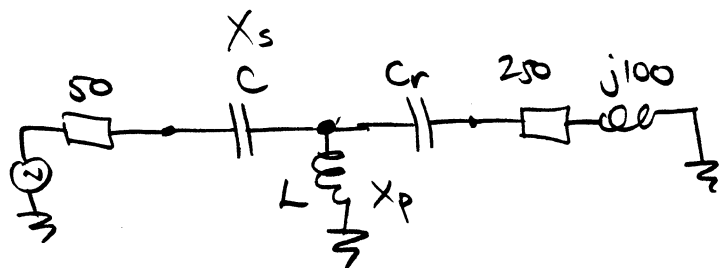

⊙ 200MHz

- Select  $C_r$  to resonate with  $j100$  to cancel reactive part at 200MHz

$$\therefore -j100 = \frac{-j}{2\pi f C_r} \rightarrow \therefore C_r = 7.96 \times 10^{-12} \text{ F}$$

$\uparrow$   
200 × 10<sup>6</sup>

(or 82 pF std. value)


- Then match 250Ω to 50Ω using LC

$$Q = \sqrt{\frac{250}{50} - 1} = 2 = \frac{250}{X_p} = \frac{X_s}{50}$$

$$\therefore X_p = 125 = 2\pi f L \Rightarrow L = 99.5 \text{ nH (100 nH std.)}$$

$$X_s = 100 = \frac{1}{2\pi f C} \Rightarrow C = 7.96 \text{ pF (8 pF std.)}$$

b)

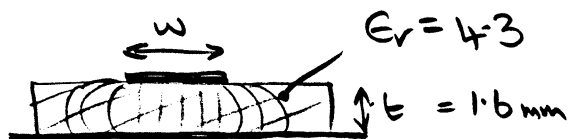

$$C \text{ per unit length} \approx \frac{(w + 2t) \cdot \epsilon_0 \epsilon_r}{t}$$

(allowing width of  $t$  each side of  $w$  for fringing fields)

$$v = \text{speed of light in dielectric} = \sqrt{\frac{1}{\mu \epsilon}} = \frac{c_0}{\sqrt{\epsilon_r}}$$

speed of light

$$Z_0 = \sqrt{\frac{L}{C}}, \text{ characteristic impedance}$$

$$\therefore 50 = \sqrt{\frac{L}{C}} \Rightarrow 2500 C = L$$

$$\therefore \sqrt{\frac{1}{2500 C^2}} = \frac{3 \times 10^8}{\sqrt{4.3}} \quad \therefore C = 1.38 \times 10^{-10} \text{ F/m}$$

$$\therefore 1.38 \times 10^{-10} = \frac{(w + 3.2 \times 10^{-3}) \cdot 8.854 \times 10^{-12} \cdot 4.3}{1.6 \times 10^{-3}} \Rightarrow w = 2.61 \text{ mm}$$

$\therefore w = 2.61 \times 10^{-3} \text{ m}$



Q4a)

SMITH CHART  
ALTERNATIVE  
SOLN.



•  $250 + j100 \Omega$  normalise to  $50 \Omega$   
 $\Rightarrow 5 + 2j$  Point A

• work with admittances  $\rightarrow B$   
• move  $B \rightarrow C$  with parallel inductor (conductance component unchanged)

$\therefore \frac{1}{\omega L} = (0.38 - 0.07) / 50$


$\omega = 2\pi \times 200 \times 10^6$

$\Rightarrow L = 128 \text{ nH}$

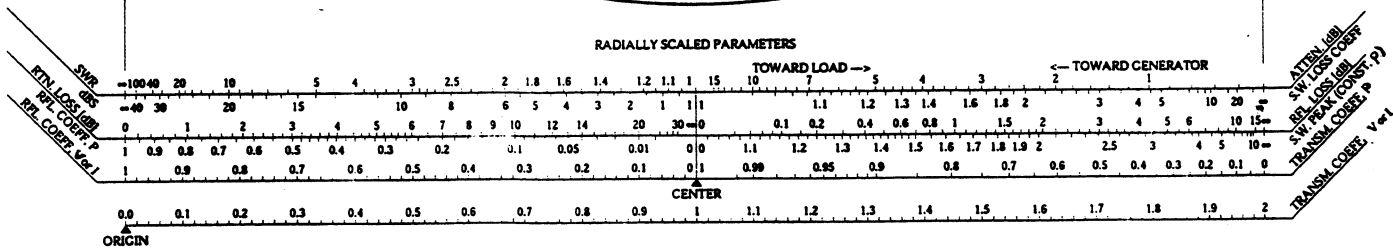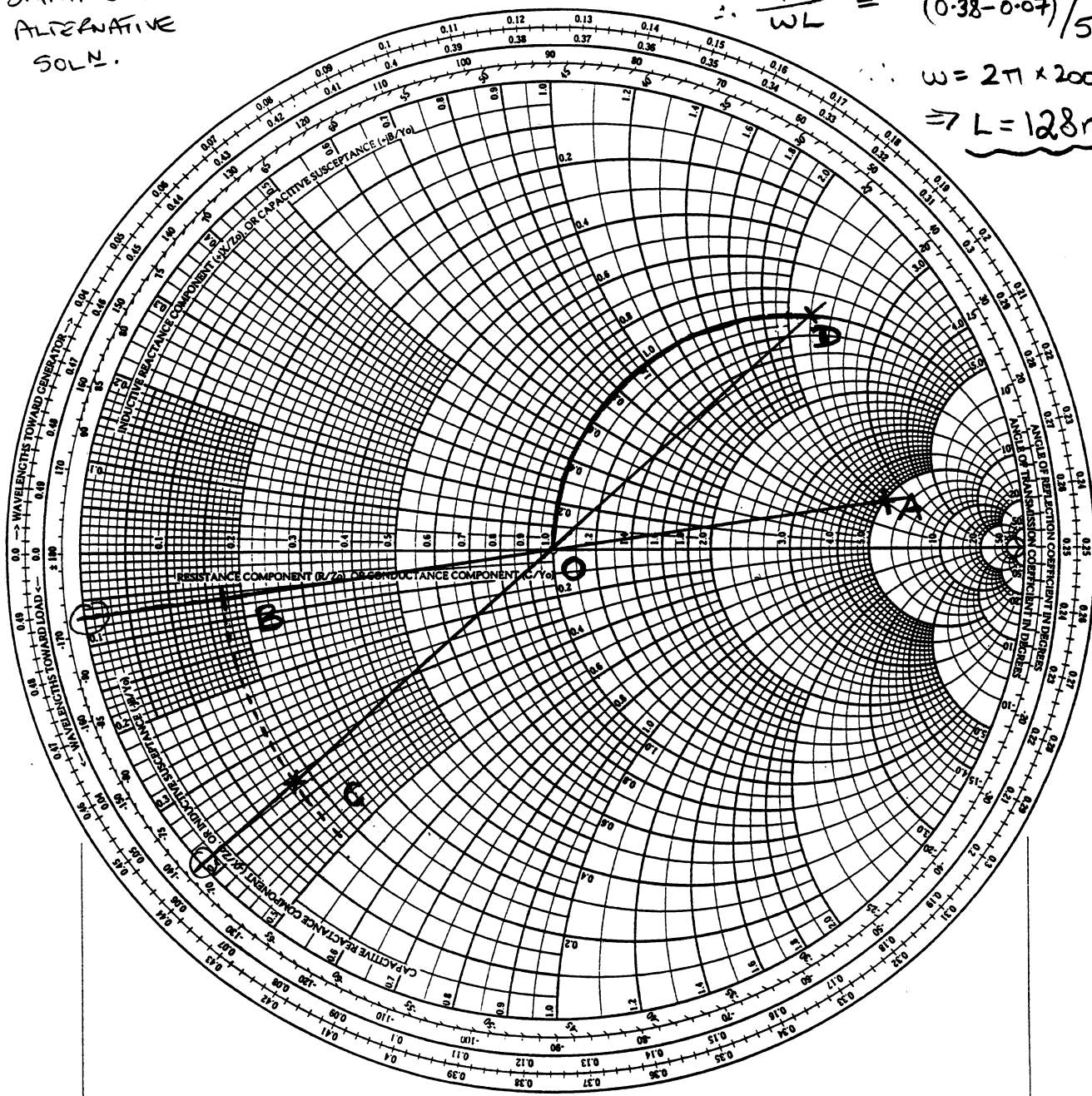



• series capacitor  $D \rightarrow 0$

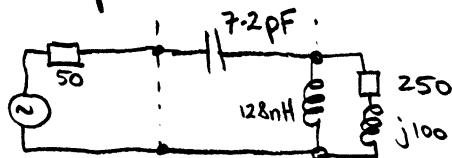$50 \times 2.2 = \frac{1}{\omega C} \therefore C = 7.2 \text{ pF}$



(parallel capacitor and series inductor solns. also possible)

Q.4c)

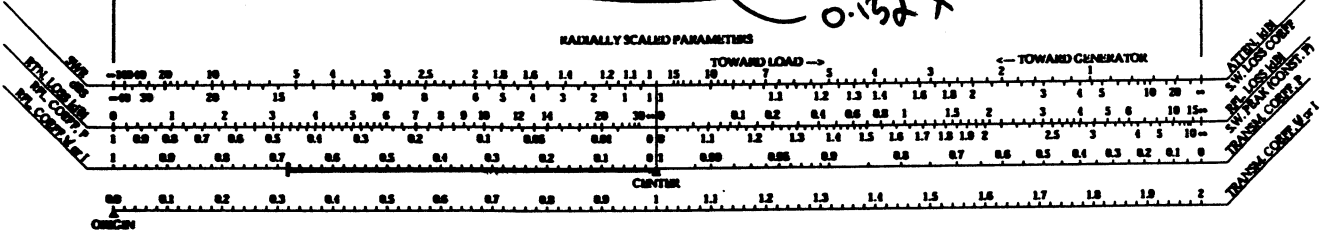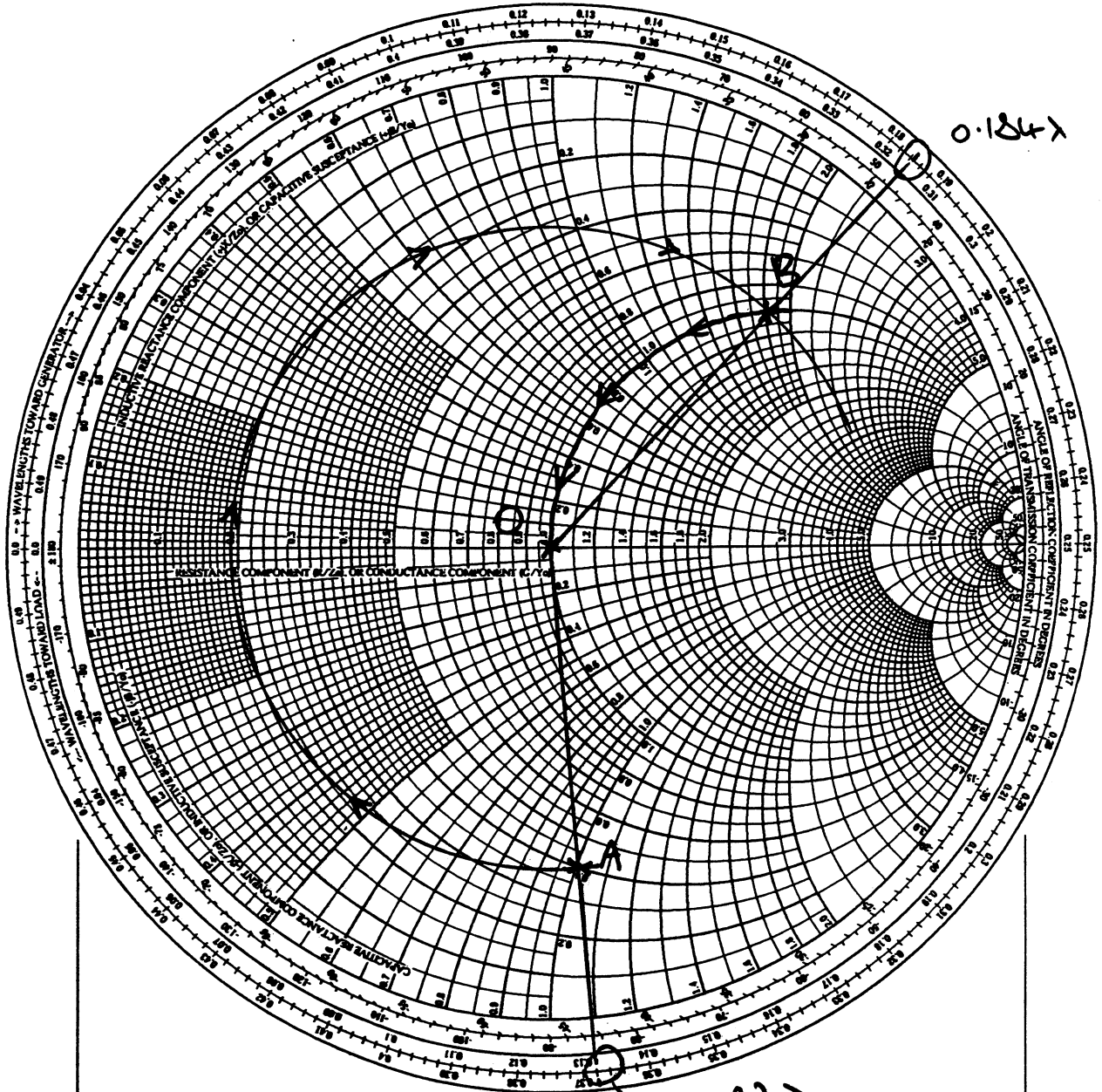

4c).  $0.68 \angle -85^\circ$   $S_{11}$  plots as  $(0.4 - j)$  on the Smith Chart. (10)  
 point A.

- To track round to point B  $\rightarrow$  @  $1 + j1.82$ , where the circular path centred, 0, at  $(1 + j0)$  cuts the  $\text{Re} = 1$  line, we need an electrical length of  $(0.132\lambda + 0.184\lambda) = 0.316\lambda$ .
- To track from B to 0, we need  $-j1.82$  in the series capacitor.

So,  $v = \frac{3 \times 10^8}{\sqrt{4.3}} = f\lambda$  with  $f = 200 \times 10^6$  Hz

$\therefore \lambda = 0.723$  m

$\therefore 0.316\lambda \equiv \underline{\underline{228 \text{ mm of microstrip}}}$

And,  $-j1.82 \times 50 = \frac{-j}{2\pi f C_s}$

(Normalising impedance for Smith chart)  $\therefore \underline{\underline{C_s = 8.7 \text{ pF}}}$   
 series capacitor

(see, 39 pF // 47 pF. std. values)