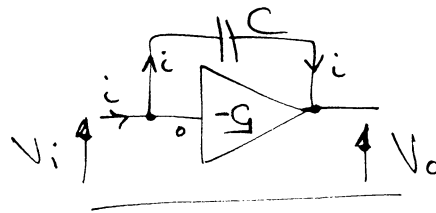


1(a) Consider a general amplifier with capacitance between input and output




$$V_o = -G V_i$$

Sum currents at input node:-

$$i = \frac{V_i - V_o}{\frac{1}{j\omega C}} \quad \text{where } V_o = -G V_i$$

$$\therefore i = j\omega C (1+G) V_i = \frac{V_i}{\frac{1}{j\omega(1+G)C}}$$

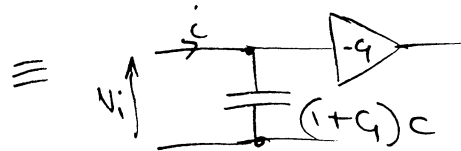$\therefore$  equivalent input capacitance to ground =  $(1+G) \times C$




i.e. much increased input capacitance

Hence, if the input source has significant impedance, the system acts as a low pass filter. So the

$$f_{-3dB} = \frac{1}{2\pi (1+G)C \cdot R}$$

Miller effect can limit the frequency response of a circuit.
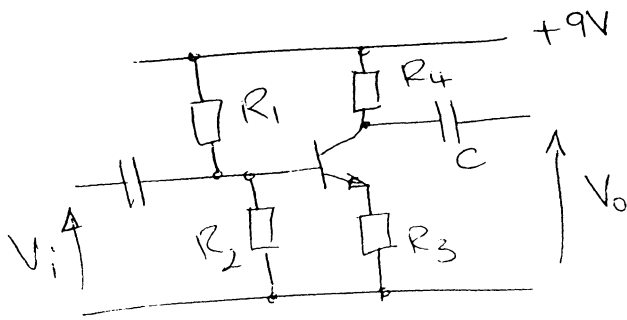
## 1b). Basic single transistor amplifier



$$R_{out} = R_4$$

$$G_{ain} = \frac{-R_4}{R_3 + r_e}$$

$$r_e = V_T / I_c$$

$$V_T = kT/q \approx 0.025V$$

$R_4 = 100\Omega$  for reqd. output impedance

For power gain = 6dB = x4 power  $\approx$  x2 voltage  
(i/p and o/p impedances similar)

So select  $R_3 = 39\Omega$  say to give  $>2 \times$  gain.

If  $V_{d.c.}$  is +4.5V, then  $I_c = 45mA$  and  $r_e = 0.56\Omega$

$$\therefore \text{net gain} = \frac{100}{39.6} = 2.51 \quad (\approx 8dB)$$

$$V_E = 45 \times 10^{-3} \times 39 = 1.76V, \quad V_{BE} = 0.65V \text{ assumed.}$$

$$\therefore V_B = 2.4V \quad (\text{base current} \approx \frac{45 \times 10^{-3}}{200} = 0.2mA)$$

$$\text{Input impedance} = R_1 \parallel R_2 \parallel h_{fe}(R_3 + r_e) = 75\Omega \text{ target}$$


$$\text{and } 2.4 = 9 \cdot \frac{R_2}{R_1 + R_2} \text{ to set } V_B \quad \sim 2k\Omega \therefore \text{ignore}$$

So choosing  $R_2 = 120\Omega$ ,  $R_1 = 330\Omega$   $\therefore R_{in} = 88\Omega$   
or buy  $= 100\Omega$   $= 270\Omega$   $= 73\Omega \checkmark$  ok.

C's must be small impedance @ 600MHz, say  $\leq 1\Omega \Rightarrow C \rightarrow \frac{1}{2\pi \cdot 600 \times 10^6}$

$$\therefore \underline{1nF \text{ OK.}} \quad = 265pF.$$

1(c) Small signal model of input :-

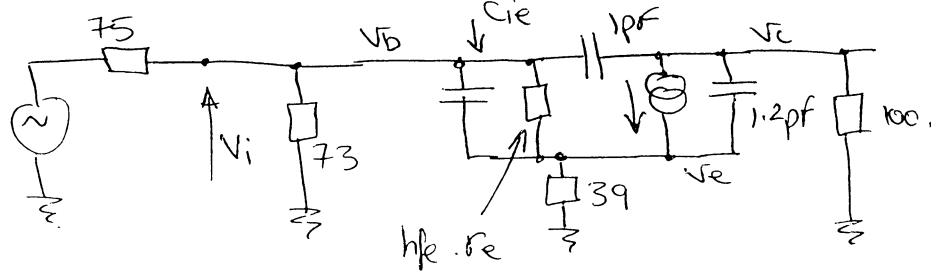

$$C_{ie} = \frac{1}{2\pi f r_e h_{fe}} = 56.8 \text{ pf}$$


$\swarrow$   $0.56$        $\nwarrow$   $5 \times 10^9$

To refer there to grid.  
 $C_1 = -2.5$ , so the Miller effect on  $C_{cb} = \times 3.5$

Also, as  $V_e = \frac{R_3}{(r_e + R_3)} \cdot V_i = 0.986 V$ . then b-e impedances

are multiplied by  $\frac{1}{(1 - 0.986)} = \times 71$

So, input circuit becomes :-

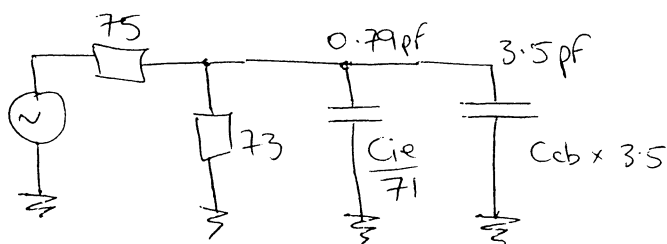


$$C' = 43 \text{ pf}$$

$$R' = 37 \Omega$$

$$\text{So } f_{-3dB} = \frac{1}{2\pi R' C'} = \underline{\underline{1.0 \text{ GHz}}} \quad \checkmark \text{ O.K. for } 600 \text{ MHz.}$$

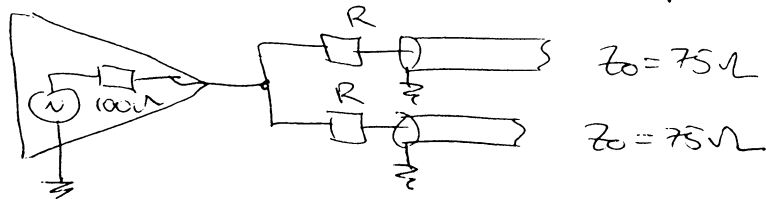
d) Amplifier has  $100 \Omega$  output impedance. To provide 2 identical matched outputs, use a pair of resistors :-



$$\text{For each line to see } 75 \Omega \quad \left[ (75 + R) \parallel 100 \right] + R = 75$$


$$\therefore \underline{\underline{R = 25 \Omega}}$$

2(a).

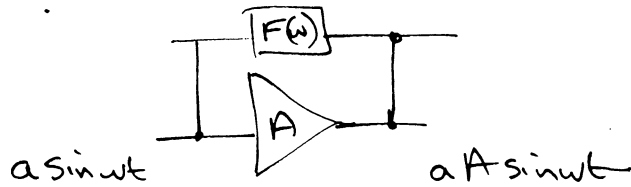

- Phase shift around loop = 0
- Loop gain = 1

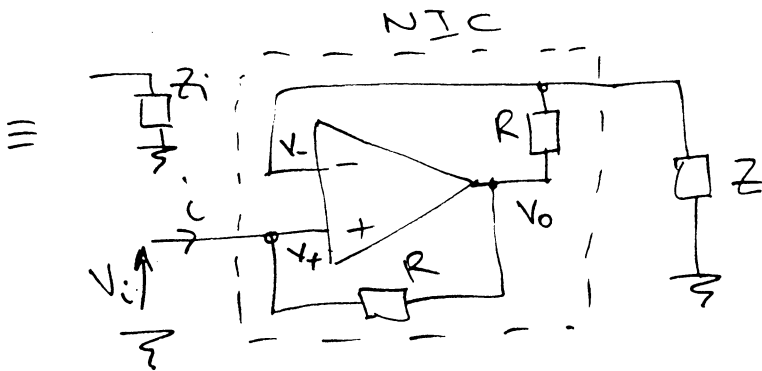(b). Consider a negative impedance converter. (NIC):



$$i = \frac{V_i - V_o}{R} \quad (1)$$

$$\frac{V_o - V_-}{R} = \frac{V_-}{Z} \quad (2)$$

$V_+ = V_i = V_-$  for ideal op-amp

$$\therefore V_o = V_i (1 + R/Z) \quad \text{from (2)}$$


$$\text{and } \therefore i = \frac{V_i - V_i - V_i R/Z}{R} \quad \text{sub into (1)}$$

$$\therefore i = -\frac{V_i}{Z}$$

$$\therefore Z_i = -Z$$

Checking these together:
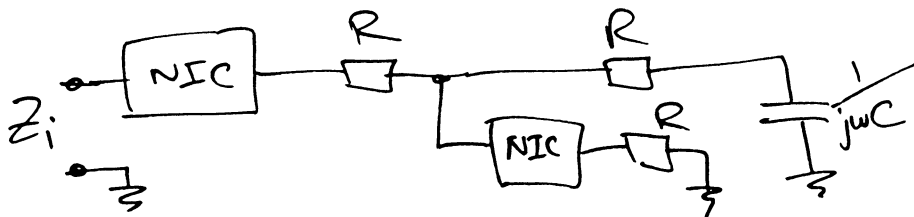
$$Z_i = - \left[ \frac{-R(R + 1/j\omega C)}{1/j\omega C} + R \right]$$




$$\therefore Z_i = j\omega C R (R + 1/j\omega C) - R = \underline{j\omega C R^2} \equiv \text{inductor } L = CR^2$$

2 (b) cont'd.

- o Synthesised inductors only work where the op-amp behaves as such so, there are <sup>current</sup> /, frequency, voltage and slew-rate limits above which the device model fails.
- o synthesised inductors can be more compact, low cost and less prone to interference and can be easily varied (change R or C) and do not suffer non-linearity of magnetic core material.

(c)

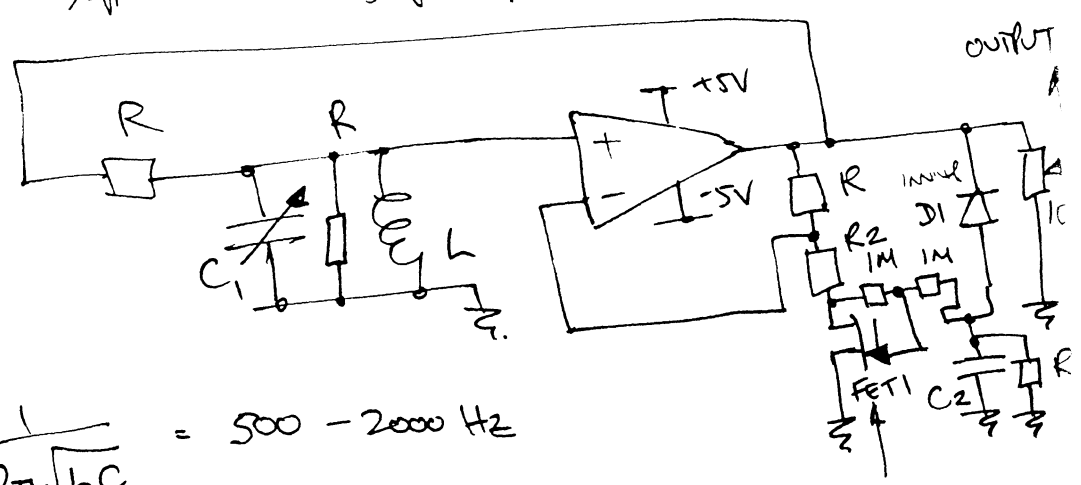

$$f_{res} = \frac{1}{2\pi\sqrt{LC}} = 500 - 2000 \text{ Hz}$$

choose R's = 10kΩ nominal

Inductor synthesised as in part (b) with

$$C = 10 \text{ nF} \quad \text{and} \quad R = 10 \text{ k}\Omega \Rightarrow L = 1 \text{ H}$$

$$\therefore C_1 = 101 \text{ nF to } 6.3 \text{ nF}$$

max.                      min.

depth in mode FET: -ve voltage turns off.

At resonance, C1 and L impedances cancel, therefore a gain of 2 is required in the op-amp for an overall loop gain of unity. Hence choose R2 = 6.8kΩ say. then for start-up the loop gain > 1 (as FET has low resistance channel).

Amplitude control is set by the demodulator D1, C2, R controlling the FET gate. Larger oscillations increase the FET impedance


(c) Contd.

and the op-amp gain falls. It will settle at several V amplitude. The output potentiometer sets the final output amplitude. The  $C_2R$  time constant must be long for low sine-wave distortion eg:  $1s \therefore C_2 = 100\mu F$ .


The  $2 \times 1M\Omega$  gate resistors reduce the FET distortion (by adding  $v_{gs2}$  to the gate voltage to cancel the non-linear term).


d) To accurately lock the oscillator frequency to  $1.5kHz$ , with reference to a  $10MHz$  crystal oscillator - we need to divide both down to the <sup>same</sup> frequency eg: oscillator  $\div 15 = 100kHz$   
reference  $\div 10^5 = 100kHz$ .

Use a phase-locked-loop (PLL) :-

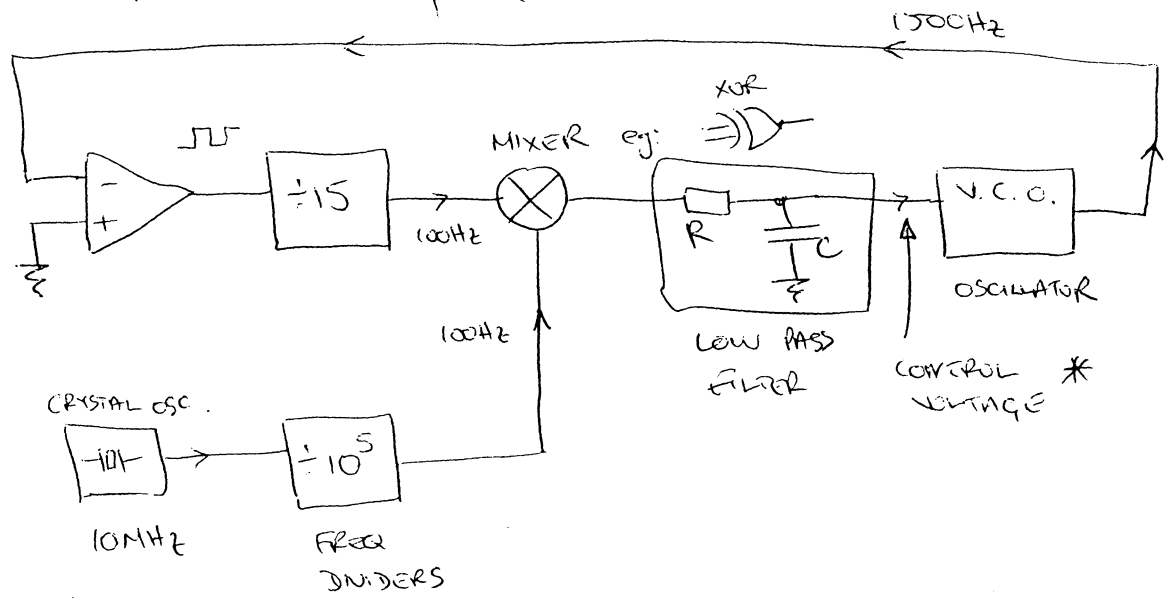

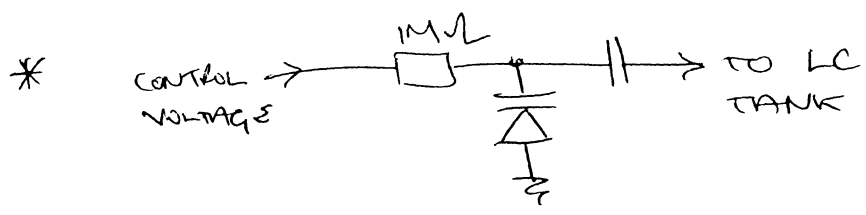To make oscillator tuneable, put varactor across the LC tank :-



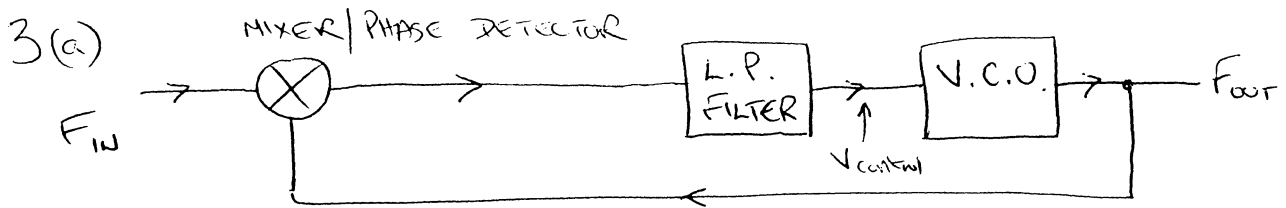


- A phase detector compares the phase/frequency of the input with the voltage controlled oscillator output
- If the freq's are different, the phase detector outputs the sum & difference frequencies. The (lower) diff. freq. passes through the low pass filter and this modulates the V.C.O. output - putting sidebands onto its spectrum
- one of the sidebands is equal in freq. to the input,  $F_{in}$ .
- Hence the phase detector produces a d.c. component pushing the V.C.O. to match  $F_{in}$  i.e. the loop locks.
- Once locked, the V.C.O. follows  $F_{in}$ , but has a 'flywheel' effect - not following fast changes or drop-outs in  $F_{in}$ . The loop 'inertia' and stability are set by the loop gain and L.P. filter bandwidth.

(b)

In order to extract the phase-keyed data from the radio carrier, we shall use a PLL to create a stable version of the carrier and look for the phase shifts with respect to this. We can work with square wave signals  $\therefore$  use an XOR gate as the phase detector.


3 b) control.

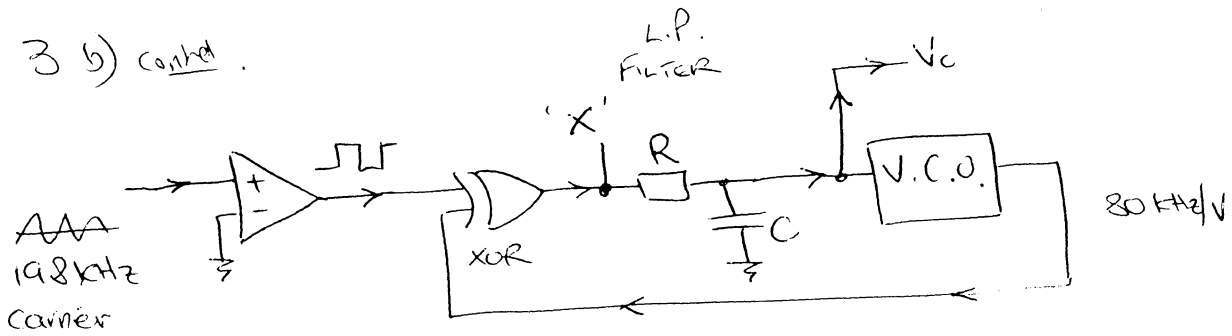

- In the steady state,  $V_c = \frac{19.8}{80} = 2.475 \text{ V d.c.}$
- For an XOR with 5V supply, the phase sensitivity =  $5/120 \text{ }^\circ/\text{deg}$   
hence  $\pm 22.5^\circ$  gives  $\pm 0.63 \text{ V}$  swing in the d.c. component at 'X'.
- Choose R & C such that there is very little change in  $V_c$  as the phase shift keying (PSK) occurs i.e. we want a steady signal at the XOR to compare the carrier to.
- The frequency of the PSK data is approx.  $\frac{1}{2 \times 20 \text{ ms}} = 25 \text{ Hz}$ , so if we choose RC to give a cut-off at say 1 Hz, then the PLL 'flywheel' effect will be significant.


$$\therefore \frac{1}{2\pi RC} = 1 \quad \text{with } R = 100 \text{ k}\Omega, C = 1.5 \mu\text{F}$$

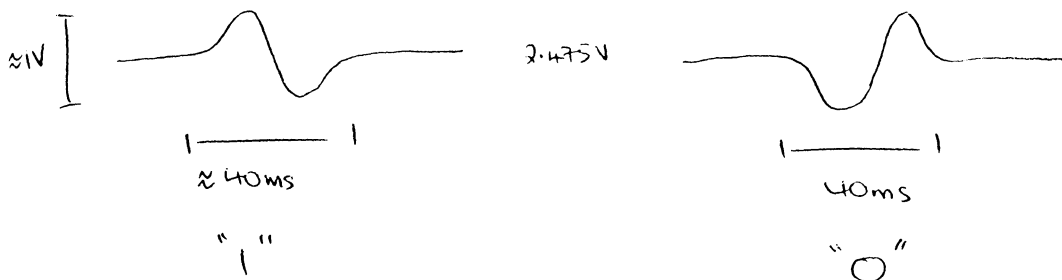- To extract the PSK data, we need to look at the signal at 'X'. If we filter this with a low pass filter at  $\sim f_{\text{data}}$  then, we shall see the d.c. component of the XOR output carrying the data :-






3 (b) contd.

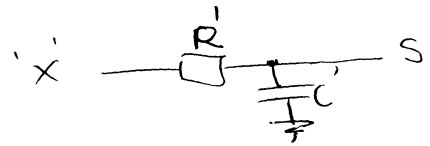

$S_0 = \frac{1}{2\pi R' C}$   $\therefore R' = 10k\Omega$   
 $C' = 330nF$

- To reconstruct the original 'i's and 'o's from the L.P. filtered signal at 'x', this can be done in a number of ways using comparators, logic and/or analogue circuits.

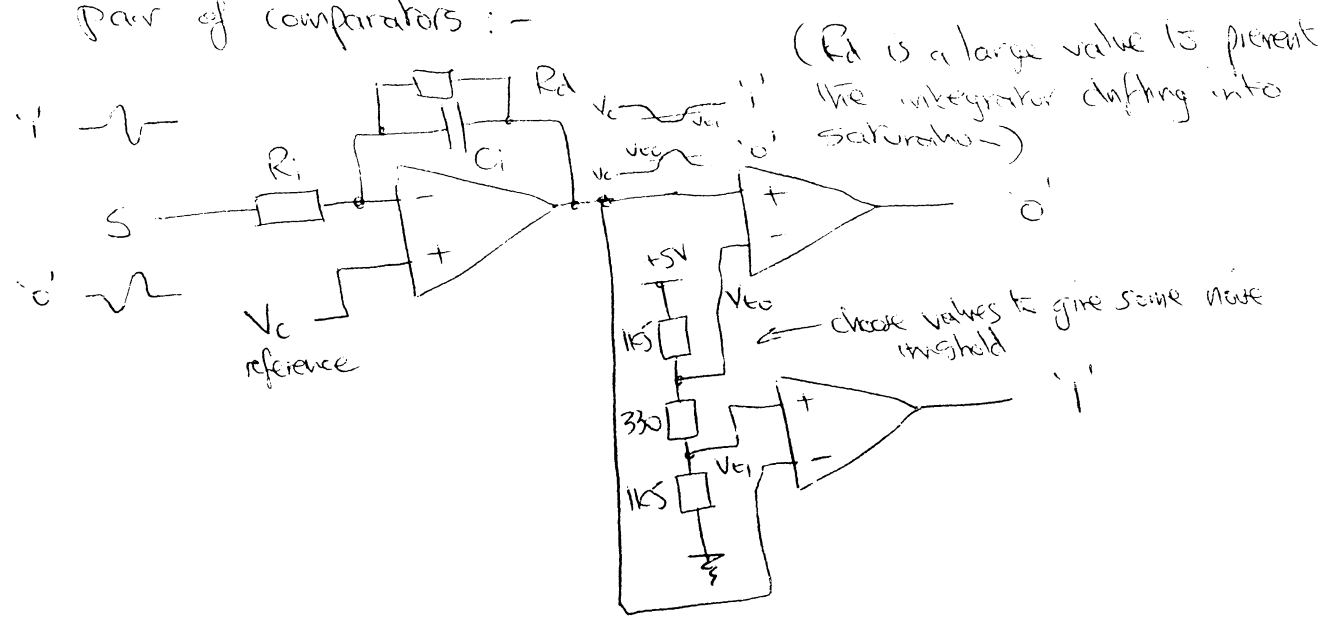For example, we can use an integrator followed by a pair of comparators :-



( $R_d$  is a large value to prevent the integrator drifting into saturation)

choose values to give some noise margin

- Set integrator gain to give reasonable output signals, so if the input  $S$ , swings by  $0.5V$  for  $20ms$  and  $R_i = 10k\Omega$  say, then to get  $0.5V$  at the integrator output:

$$i_{xt} = \frac{20 \times 0.5 \times 10^{-3}}{10^4} = C_i \times \Delta V = 0.5 \times C_i \quad \therefore C_i = 2\mu F$$
  
 (and set  $R_d = 1M\Omega$  say)

- The comparator thresholds are set so that only a PST signal causes the integrator output to cross the thresholds.
- Note, because an integrator is a L.P. filter, we could omit  $R'$  and  $C'$  in this implementation.

4(c) contd.

$$\therefore \text{at } 60\text{kHz}, \delta = \sqrt{\left(\frac{2}{2\pi \cdot 60 \times 10^3 \cdot 4\pi \times 10^{-7} \cdot 3.33 \times 10^7}\right)}$$

$$= 3.56 \times 10^{-4} \text{ m } (0.36 \text{ mm})$$

Since, the wire is only 0.25 mm dia., we shall assume the full section carries the current and ignore the skin effect.

$$\therefore \text{Resistance of 1m Cu wire, } R_c = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2}$$


$$\therefore R_c = 0.611 \Omega$$

$$\text{Radiation efficiency} = \left(\frac{R_e}{R_c + R_e}\right) \times 100\%$$

$$= \underline{\underline{0.005\%}}$$

(or less for triang. current distrib. by factor of 4)

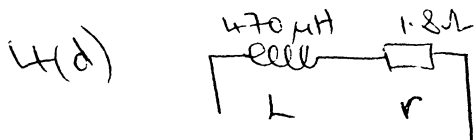This is a low efficiency, so might need more amplifier gain - hence cost saving may not be worth it!




$$\text{at } 60\text{kHz}, \omega L = 177 \Omega$$

$$\therefore Q = \frac{\omega L}{r} = \frac{177}{1.8} = \underline{\underline{98.4}}$$

$$\text{Bandwidth} = f_0 / Q = \frac{60 \times 10^3}{98.4} \approx \underline{\underline{610 \text{ Hz}}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 60 \times 10^3 \quad \therefore \text{with } L = 470 \mu\text{H}$$
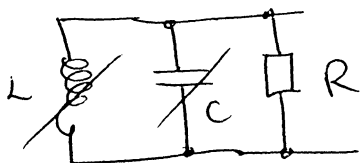
$$\Rightarrow \underline{\underline{C = 15 \text{ nF}}}$$



$$\text{For parallel resonance, with same } Q$$

$$98.4 = \frac{R}{\omega L} \quad \therefore \underline{\underline{R = 17.4 \text{ k}\Omega}}$$

$$4(a) \quad 15 \times 10^3 \text{ W @ } 60 \text{ kHz}$$

$$c = f\lambda = 3 \times 10^8 \text{ m/s} \quad \therefore \quad \underline{\lambda = 5000 \text{ m}}$$

$$\text{Power density, } P = \frac{G \times 15 \times 10^3}{4\pi R^2}$$

$$\begin{aligned} \text{Gain, } G &= 1.5 \\ \text{Range, } R &= 102 \times 10^3 \text{ m} \end{aligned}$$

$$\therefore \quad \underline{P = 1.72 \times 10^{-7} \text{ W/m}^2}$$

$$P = \frac{1}{2} \underline{E} \times \underline{H}^*, \quad |P| = \frac{1}{2} H^2 \eta \quad \text{where } \eta = \sqrt{\mu_0 / \epsilon_0} = 120\pi$$

$$\therefore \quad \underline{H = 3 \times 10^{-5} \text{ A/m}} \quad (E = 11 \text{ mV/m})$$

$$(b) \quad \text{Antenna eqn.} \quad \underline{G} = \frac{4\pi A_e}{\lambda^2}$$

$$-76 \text{ dB} \equiv 2.5 \times 10^{-2} \text{ linear} \quad \therefore \quad A_e = 0.05 \text{ m}^2$$

$$\begin{aligned} \therefore \text{ power into } 250 \Omega \text{ matched load} &= 8.6 \text{ nW} \\ &= V^2/R \end{aligned}$$

$$\therefore \quad \underline{V = 1.5 \text{ mV}_{\text{rms}} \text{ amplitude}}$$

$$(c) \quad \text{Radiation resistance, } R_e \approx 80\pi^2 \left(\frac{l}{5000}\right)^2 \Omega$$

$$R_e = 3.16 \times 10^5 \Omega$$

v. short  
 $\therefore$  assume ideal dipole

(or could  $\div 4$  for triangular current dist'n)

$$\text{Skin depth } \delta = \sqrt{\frac{2}{\omega \mu \sigma}}$$

$$\text{Taking resistivity of copper wire } \rho = 3 \times 10^{-8} \Omega\text{m}$$

$$\therefore \quad \delta = 3.33 \times 10^{-7} \text{ s/m}$$