

1. (a) The Quine-McClusky tabular method is based on building lists with adjacent blocks containing the same number of 'High' variables. By comparing, and if appropriate, combining each term from one block with the block below we build subsequent lists. The terms that did not combine in each list (including the last) are termed 'Prime Implicants' (PIs). The 'Prime Implicant table' is formed of the PIs and the original terms of the logic function. The idea is to select the minimal and the simplest PIs which cover all the original terms. This can be done by visual inspection or by a formalised method.

If the logic function is not in a canonical form (or not brought to a canonical form) it is difficult to deal with terms that have fewer variables. Such terms may be introduced in the second or subsequent lists but this results in missing the chance to combine parts of them (canonical components of such terms) with other terms from the first list (or previous lists) and thus the method does not always deliver an optimal solution. [30%]

(b) By using the reverse engineering method from Fig 1 we can obtain:

$$J_0 = Q_2Q_1 + \overline{Q_2}\overline{Q_1}$$

$$K_0 = Q_2\overline{Q_1} + \overline{Q_2}Q_1$$

$$J_1 = \overline{Q_2}Q_0$$

$$K_1 = Q_2Q_0$$

$$J_2 = Q_1\overline{Q_0}$$

$$K_2 = \overline{Q_1}\overline{Q_0}$$

In a J-K bistable the next state Q^+ function of the present state Q is given by :

$$Q^+ = J\overline{Q} + \overline{K}Q$$


Thus we can calculate the next states Q_0^+ , Q_1^+ , Q_2^+

$$Q_0^+ = Q_2Q_1 + \overline{Q_2}\overline{Q_1}$$

$$Q_1^+ = \overline{Q_2}\overline{Q_1}Q_0 + \overline{Q_2}Q_1 + \overline{Q_0}Q_1$$


$$Q_2^+ = Q_1\overline{Q_0}\overline{Q_2} + Q_1Q_2 + Q_0Q_2$$

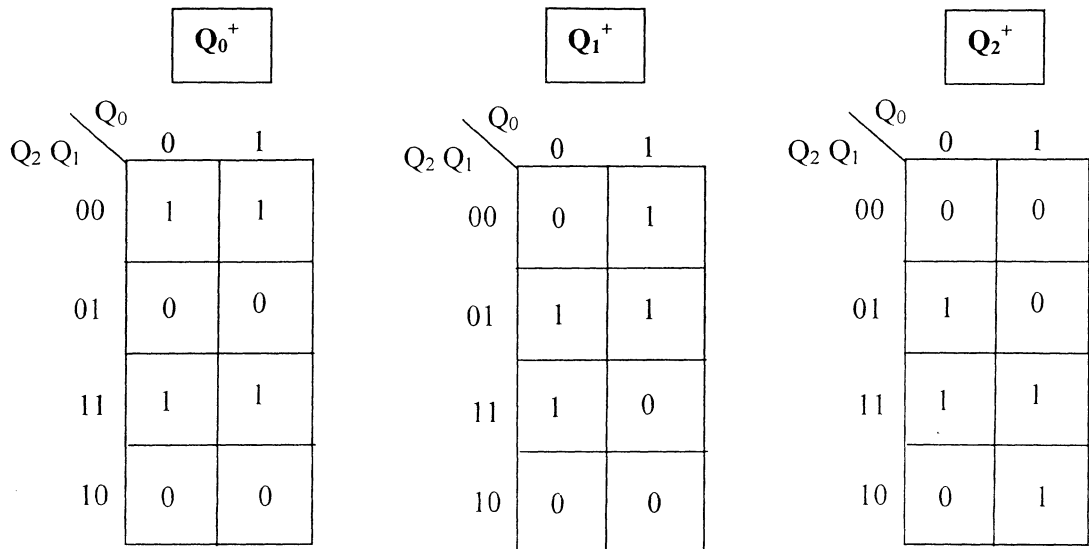The k-maps obtained from the expressions above will help to build the state table:



From these K-maps we can build the state table and the state diagram. Since this is a counter (there are no inputs) it makes sense to write the states in the counting sequence:

Present state	Next state
000	001
001	011
011	010
010	110
110	111
111	101
101	100
100	000
000	000

 

[50%]

One can see that from the one state to another only one bit changes at a time. This is therefore a 3-bit Gray code counter !


[20%]

2. (a) The design rules to implement a combinational circuit free of static or dynamic hazards using only NOR gates are:

- (i) All the adjacent terms in the K-map of the complement of the function should be covered by a common 0-term
- (ii) There should be no 0-terms that contain both a variable and its complement.

[20%]

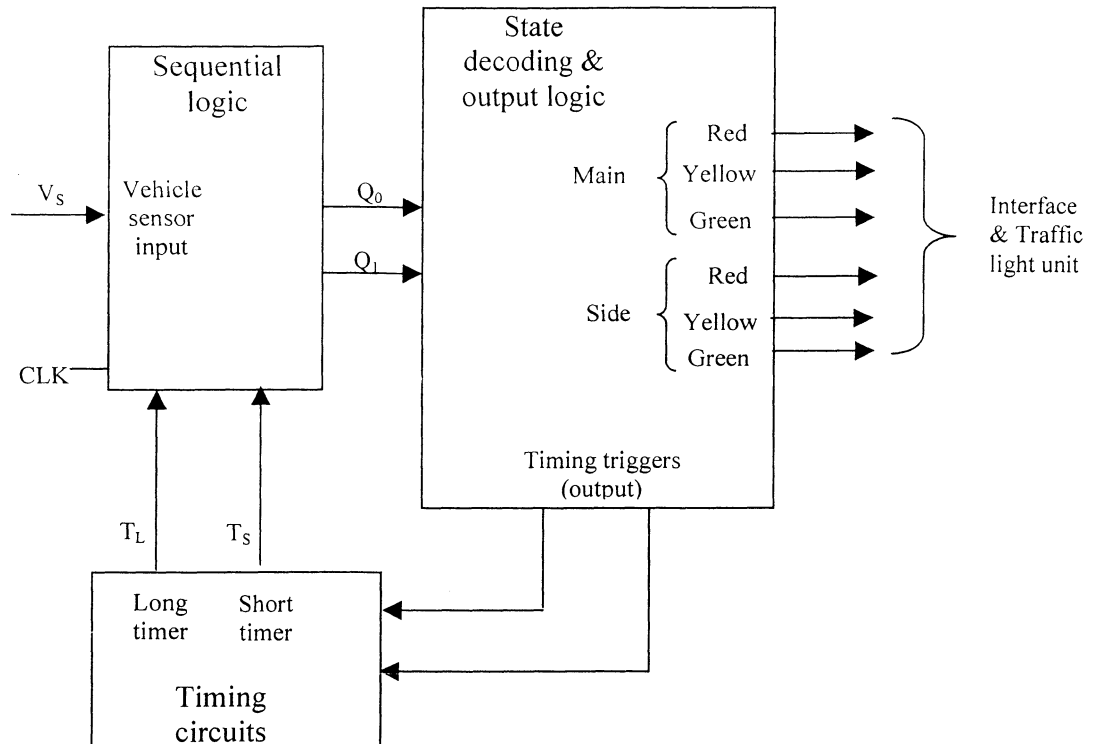(b) The block diagram is shown below (other schematic variants can also be correct):




[20%]

First state. The Gray code for this state is 00. The main street light is green and the side street light is red. The system remains in this state for at least 25 seconds when T_L is 1 or as long as there is no vehicle on the side road, $V_s=0$. The system goes to the next state when the 25 s timer is off (T_L becomes 0) and there is a vehicle on the side street ($V_s=1$).

Second state: Gray code is 01. The main street light is yellow and the side street is red. The system remains in this state for 4 seconds when the short timer is on (T_s is 1) and goes to the next state when T_s becomes 0 (after 4seconds – counted by the timing circuit).

Third state: Gray code is 11. The main street light is red and the side street light is green. The system remains in this state when T_L is 1 and there is a vehicle on the side road, $V_s=1$. The system goes to the next state when the 25 s timer is off (T_L becomes 0) or there is no vehicle on the side street ($V_s=0$), whichever comes first.

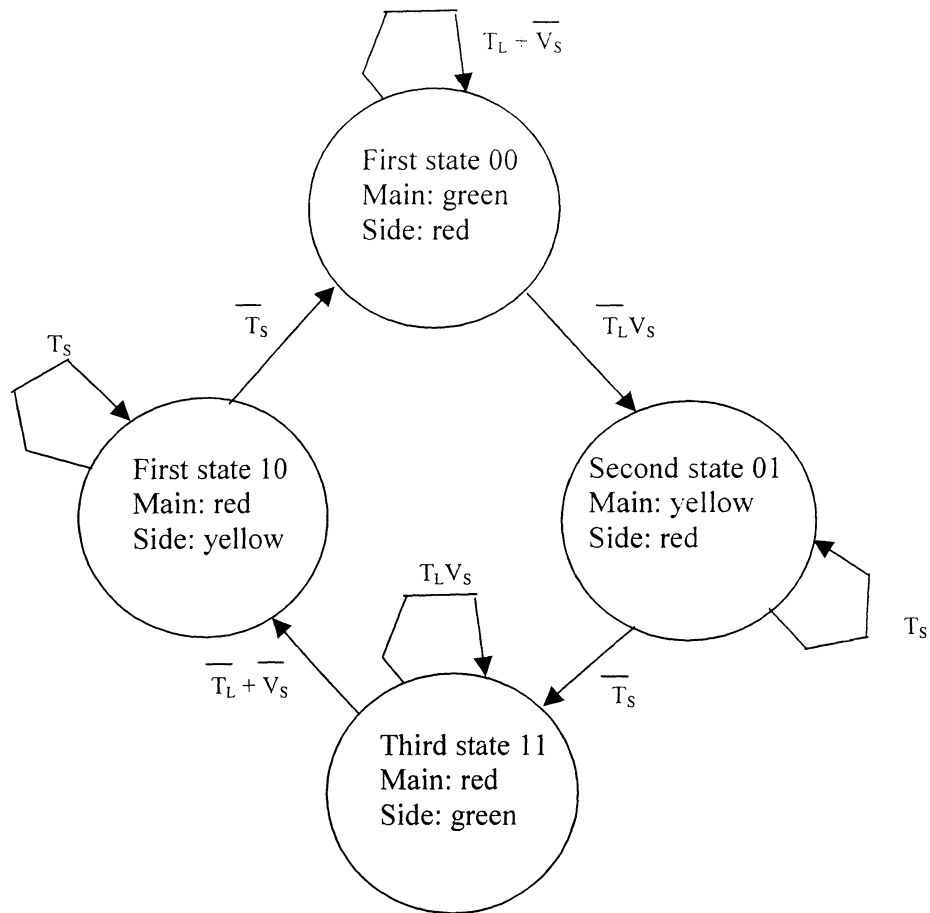Fourth state: Gray code is 10. The main street light is red and the side street is yellow. The system remains in this state for 4 seconds when the short timer is on (T_s is 1) and goes to the first state when T_s becomes 0 (after 4seconds – counted by the timing circuit).



[30%]

Present state	Light outputs						Trigger outputs	
	MR	MY	MG	SR	SY	SG	Long	Short
00	0	0	1	1	0	0	1	0
01	0	1	0	1	0	0	0	1
10	1	0	0	0	0	1	1	0
11	1	0	0	0	1	0	0	1

[30%]


3B2 2005 Qn B

- a) (i) For MOS transistors saturation describes the region of operation where the channel is pinched off near the drain. This typically corresponds to high values of V_{DS} . The necessary condition is (for n-channel)

$$V_{DS} > V_{GS} - V_T$$

If $V_{DS} = V_{GS} - V_T$, pinch-off happens right at the drain. As V_{DS} increases, the pinch-off region advances progressively towards the source. To a first approximation I_D remains unchanged as V_{DS} increases, and the device acts as a constant current source/sink. A MOSFET biased so its gate is marginally above V_T and with high V_{DS} will therefore be in the saturation region.

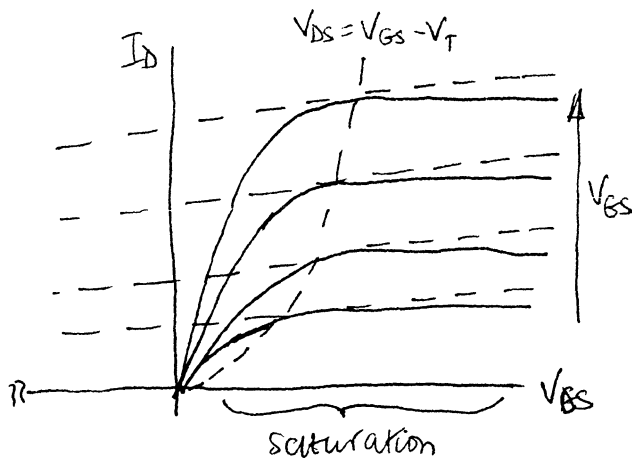In fact, as V_{DS} increases the resultant shortening of the channel (channel length modulation) slightly enhances the conductance and there is a gradual increase in I_D .



The near-constant current is a useful characteristic in linear circuits.

Also, a FET connected with D & G shorted is by definition in saturation, and may be used as a load in place of a resistor - it also occupies less space

- (ii) For bipolar devices saturation is observed when the base potential V_{BE} causes a large collector current to flow. Assuming a load is connected between collector & supply V_{CE} falls to a low limiting value V_{CEsat} (typically $\sim 0.2V$) and is less than V_{BE} (typically about $0.8V$).

In this situation $V_{CB} < 0$ (NPN), and the C-B junction becomes forward biased, and the collector injects electron charge into the base, accounting for some excess base current.

In bipolar, saturation gives a clearly defined low V_{CE} with a typically high V_{BE} and I_B , and a large I_E . The low V_{CE} can be used to define a logic level (as in saturated mode logic). The excess charge stored in the base has to be removed before the device can leave saturation & stop conducting. This takes $\sim 0.50ns$ & limits switching speed available with saturated mode logic.

3B2 2005 Qn3 (cont)

- b) In this ckt, for T_2 $V_{DS} \equiv V_{GS}$ since D shorted to G.
 Hence $V_{DS} > V_{GS} - V_T$ so T_2 is in saturation by definition.
 We cannot know for certain the state of T_1 since V_{out} is unknown, but we will assume that, because V_{GS} is high, V_{DS} will likely be low with the device in its non-saturation region.
 We must verify this at the end.
 Hence use 1st equation for T_1 , 2nd eqn for T_2 .
 Assuming no current drawn from output, equate I_D for $T_1 + T_2$.

$$I_D = \frac{K_1}{2} (2(V_{GS1} - V_T) V_{out} - V_{out}^2) = I_{D2} = \frac{K_2}{2} (V_{GS2} - V_T)^2$$

For T_1 , $V_{GS1} = 5V$. For T_2 $V_{GS2} = V_{DD} - V_{out} = 10 - V_{out}$

$$\frac{80}{2} (2(5-1) V_{out} - V_{out}^2) = \frac{15}{2} (10 - V_{out} - 1)^2$$

$$128 V_{out} - 16 V_{out}^2 = 243 - 54 V_{out} + 3 V_{out}^2$$

$$19 V_{out}^2 - 182 V_{out} + 243 = 0 \quad \text{Solving,}$$

$$V_{out} = \frac{182 \pm \sqrt{182^2 - 4 \times 19 \times 243}}{38} \quad \text{Hence } V_{out} = 4.79 \pm 3.18$$

$$= 1.61 \text{ or } 7.97 \text{ V} \quad \text{The second root is not consistent with } T_1 \text{ in non-saturation}$$

$$\Rightarrow \underline{V_{out} = 1.61 \text{ V}} \quad (V_{out} < 4V). \text{ Hence first root applies}$$

- c) σ describes the degree of saturation of the bipolar circuit.
 $\sigma = 1$ means the circuit is not saturated; $\sigma = 0.1 \equiv$ heavily sat.

σ is defined as $I_C / h_{FE} I_B$. If $\sigma = 0.2$, the base current drive is $5 \times$ that required to sustain collector current I_C , and the circuit is well into saturation so V_{CE} may be taken as V_{CEsat}

$$\text{Hence } I_C = \frac{V_{CC} - 0.1}{R_L} = \frac{4.9}{3000} = 1.63 \text{ mA}$$

$$\text{And } I_B = I_C / \sigma h_{FE} = 1.63 \times 10^{-3} / 0.2 \times 50 = 163 \mu\text{A}$$

If $V_{BEsat} = 0.7 \text{ V}$, apply KVL to get V_B , which is given by

$$V_B = I_B R_B + V_{BEsat} = 163 \times 10^{-6} \times 5000 + 0.7 = \underline{1.52 \text{ V}}$$

3B2 2005 Qn 4

a) Logic swing is 1.2V, symmetric about $V_R = -1.5$

$$V_{OH} = V_R + \frac{1}{2} \times 1.2 = -1.5 + 0.6 = -0.9V$$

$$V_{OL} = V_R - \frac{1}{2} \times 1.2 = -1.5 - 0.6 = -2.1V$$

and $V_{OH} - V_{OL} = 1.2$
as required.

The max. available I_E should be used to maximise switching speed so take $I_E = 5mA$. When input A is high ($-0.9V$),

$$V_{E1} = V_{OH} - V_{BE1} - V_{EE} \text{ and}$$

$$R_E = (V_{OH} - V_{BE1} - V_{EE}) / I_{E1} = (-0.9 - 0.8 + 6) / 5 \times 10^{-3} = 860 \Omega$$

We must choose R_1 so the NOR o/p is at $V_{OL} = -2.1V$ when T_3 on and

$$R_1 = V_{CC} - (V_{CC} + V_{BE3}) / I_{E1} = (0 + 2.1 - 0.8) / 5 \times 10^{-3} = 260 \Omega$$


R_2 is not just the same as R_1 , since V_R is held fixed at $-1.5V$. Choose it so the OR output is at $V_{OL} = -2.1$ when A is low.

$$I_{E2} = (V_R - V_{BE2} - V_{EE}) / R_E = (-1.5 - 0.8 + 6) / 860 = 3.7 / 0.86 = 4.2mA$$

(which is 5mA as required)

$$\text{Hence } R_2 = (V_{CC} - (V_{OL} + V_{BE4})) / I_{E2} = (0 + 2.1 - 0.8) / 4.2 \times 10^{-3} = 309 \Omega$$

b) Typical circuit

 


R_7, R_8, D_1, D_2 are a potential divider to set V_{B5} to $(-1.5 + 0.8)V$

D_1, D_2 enhance temperature stability

T_5 is an emitter follower: choose R_6 for acceptable reference current, few mA
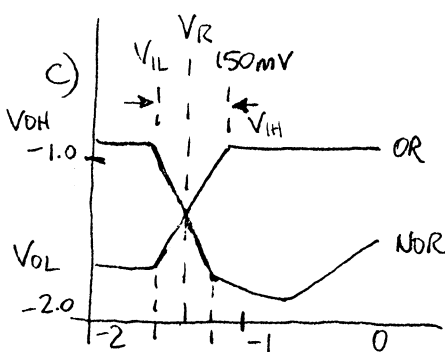
$$V_{B5} \sim V_{CC} - (V_{CC} - 2V_{diode} - V_{EE}) R_7 / (R_7 + R_8)$$



$$V_{IH} = -1.5V + 150/2mV = -1.425V$$

$$V_{IL} = -1.5 - 150/2mV = -1.575V$$

$$N_{MH} = V_{OH} - V_{IH} = -0.9 + 1.425 = 0.525V$$

$$N_{ML} = V_{IL} - V_{OL} = -1.575 + 2.1 = 0.525V$$

3B2 2005 Qn 4 (cont)

- d) If $\beta_{T_4} = 50$ then $I_{B_4} = I_{E_4}/51$. I_{B_4} flows thru R_2 and slightly reduces V_{B_4} and hence V_{OH} , so eroding the NM. If the gate does not drive other gates:

$$I_{E_4} = (V_{OH} - V_{EE})/R_4 = (-0.9 + 6)/50 \times 10^3 \sim 102 \mu A$$

$$\text{Hence } I_{B_4} = 102/51 = 2 \mu A.$$

This extra current which flows thru R_2 , will increase the voltage drop across this component by $2 \times 10^{-6} \times 309 \sim 600 \mu V$ hence reducing V_{OH} to $-0.90006 V$. The difference is quite negligible.

- e) Each driven stage consumes a small amount of current from the output of the driving stage. The greater the current, the greater the fall in drive voltage, until the noise margin drops to an unacceptable level.

The noise margin can drop by $525/10 mV$ owing to loading. We do not know how much current each subsequent gate requires at its input, so estimate. If the gates are of the same family with $I_E \sim 5 mA$ and $\beta \sim 50$, then the required base current is $\sim 100 \mu A$.

Owing to the emitter follower T_4 (and T_3) the increase in base current I_{B_4} due to each additional driven input is about $100 \times 10^{-6} \times R_2/51$. Taking worst case, $R_2 = 309 \Omega$, $\Delta V_{OH} \approx 620 \mu V$.

If a reduction of $52 mV$ is allowable, this corresponds to > 80 driven gates

In practice the capacitance of driven gate inputs will limit the switching times achievable, and the fanout should probably not be allowed to exceed 10.

Draft Examiner's report for ques 3 & 4

Does not include info from script 5244B

Question 3, on saturation in MOS and bipolar transistor circuits, was attempted by 59 candidates. Most were able to solve the ~~two~~ problems involving MOS and bipolar devices, but some appeared to be unaware of the different meanings of saturation in the two families. ~~The mean is~~ There was some evidence of candidates treating this as their final question and committing insufficient time to it. The mean mark was ~~47.8%~~ 54.4%.

Question 4, on emitter-coupled logic, was attempted by 24 candidates. Most were able to calculate plausible resistance values, but ~~many~~ not all were able to describe a voltage reference or ^{estimate} calculate the fanout. ~~There was some~~ Some candidates clearly treated this as their final question and had insufficient time. The mean mark was ~~44.1%~~ 51.0%.