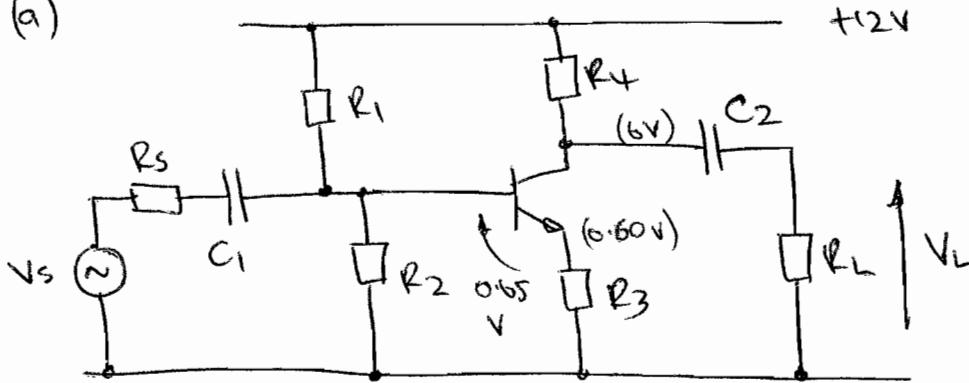


3B1 Datasheet: None

1) (a)



Bias resistors  $R_1, R_2$   
 Load  $R_L$   
 collector load  $R_4$

$$\text{Gain} \approx -R_4/R_3$$

$$\text{B/widht @ input (high-pass)} = \frac{1}{2\pi C_1 (R_s + R_1 \parallel R_2 \parallel h_{fe} \cdot R_3)}$$

$$\text{B/widht @ output (high-pass)} = \frac{1}{2\pi C_2 (R_4 + R_L)}$$

(b)  $V_s = 75 \text{ mV}_{pp}$  ,  $R_s = 100 \text{ k}\Omega$   
 $V_L = 1 \text{ V}_{pp}$  ,  $R_L = 10 \text{ k}\Omega$

Assume  $h_{fe} = 200$

$$\therefore \frac{P_{in}}{P_{out}} = \frac{\left(\frac{75}{2} \times 10^{-3}\right)^2 / 10^5}{1^2 / 10^4} = 1.46 \times 10^{-4} = -38.5 \text{ dB}$$

$\therefore$  allowing 20dB gain/stage, we need 2 stages (40dB)

linear gain (voltage) per stage =  $\sqrt{\frac{1}{75 \times 10^{-3}} / \frac{1}{23}} = 10.3$   $\therefore$  10 say as 3 couplings  
 and input/output impedance ratio =  $\sqrt{\frac{100}{10}} \approx 3.3$

(b) cont.

Setting base bias @ 1.4Vdc.  $\therefore \frac{R_2}{R_1 + R_2} \times 12 = 1.4 \text{ V}$   
 $\sim (0.6 + 0.65) \text{ V} + 10\%$

[and choose  $R_2 \sim 1.5 \times \text{reqd } R_{in}$ ]  $\therefore R_1 \approx 8R_2$


(100k source)	$R_1$	$R_2$	$R_3$	$R_4$	$[R_4 = \text{reqd. } R_{out}]$
stage 1:	1M $\Omega$	150K	3K $\Omega$	33K	} near standard values.
stage 2:	390K	47K	1K	10K	
(10K load)					

For 50Hz :  $\frac{1}{2\pi \cdot 214 \times 10^3 \cdot C_1} = 50 \therefore C_{11} = 15 \text{ nF}$


$C_{21} \equiv C_{12} > 47 \text{ nF} \therefore \text{say } 100 \text{ nF}$  and  $C_{22} > 150 \text{ nF}$

And for 2kHz high-freq roll-off, we shall need to shunt the load resistance with a capacitor :-  $\therefore \text{say } 330 \text{ nF}$

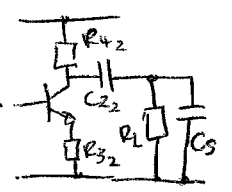$2000 = \frac{1}{2\pi \left(\frac{10 \times 10^3}{2}\right) C_s} \therefore C_s = 15 \text{ nF}$



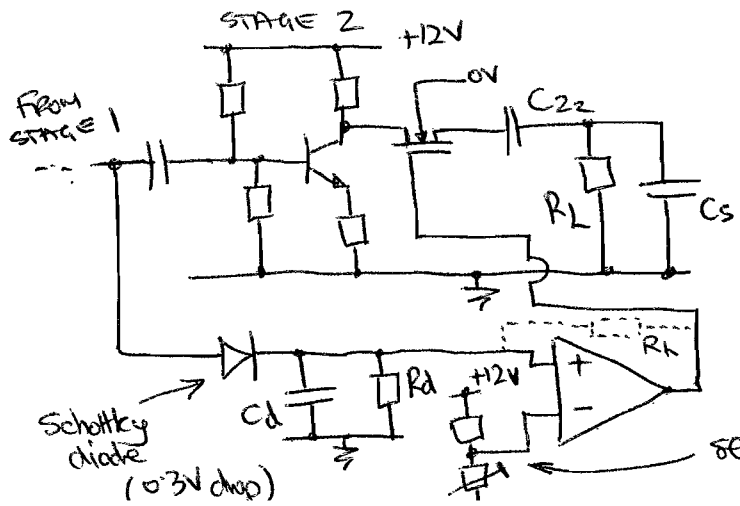
(c) We need to monitor the audio signal amplitude  $\therefore$  use a diode demodulator on the output of stage 1 and use this to control a MOSFET analogue switch to control the signal path to  $R_L$  (note we need stage 2 as a buffer or switching  $R_L$  will alter the output level being monitored)



- Choose  $C_d \times R_d \sim \text{seconds}$   
 eg:  $R_d = 1 \text{ M}\Omega$   
 $C_d = 3.3 \mu\text{F}$
- Can also add hysteresis with  $R_h$  eg: 22 M $\Omega$

set for  $\left(8 \times \frac{75 \times 10^{-3}}{2}\right) + 6 - 0.3 \text{ V} \approx 6.0 \text{ V}$  threshold.

2(a)

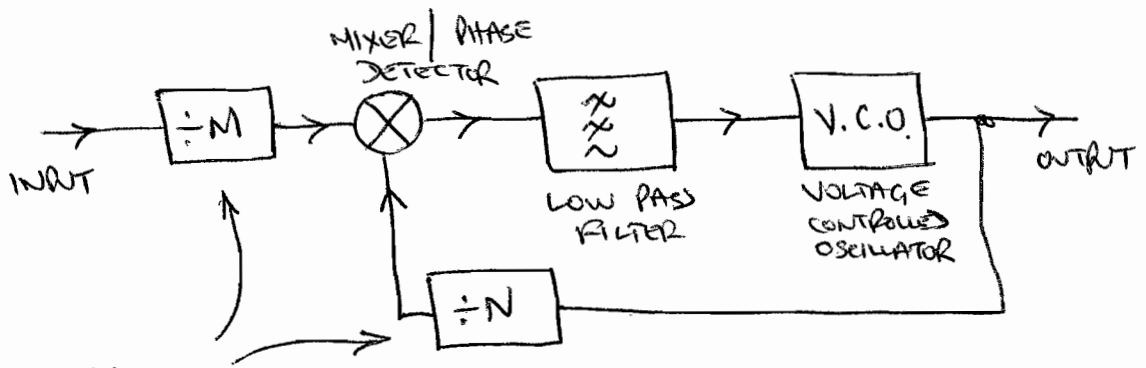


DIGITAL  
COUNTER / DIVIDERS  
FOR FREQ. SYNTHESIS

P.L.L. SCHEMATIC

The output from a VCO (perhaps divided down in freq.) is compared to the input signal (perhaps also divided down by a different factor) by a phase detector. The output of the phase detector controls the V.C.O. through a low-pass filter such that it pushes the V.C.O. output to match the input in frequency and phase. The low-pass filter gives a 'flywheel' effect to the V.C.O. output freq. and with dividers M and N, it is possible to create an output freq.,  $f_{out}$ , such that  $\frac{f_{out}}{N} = \frac{f_{in}}{M}$  - hence

a fixed reference freq.,  $f_{in}$ , may be scaled to a digitally selectable output frequency from the V.C.O.

(b)

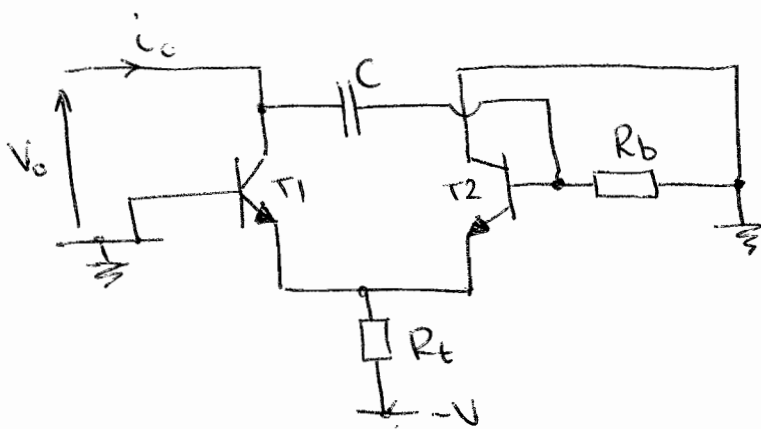


Consider the transistor pair connected above.

Small signal model :-

(using  $r_e$  transistor model; or could use  $h_{ie}$  as in lecture notes)

2b)

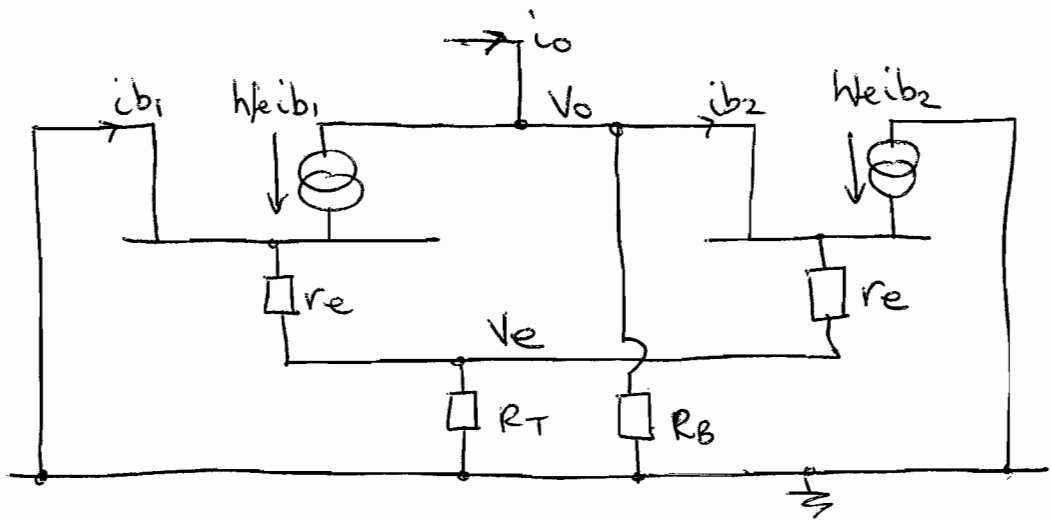

(4)

① —  $V_e = hfe (ib_1 + ib_2) R_T$  ,  $V_e = -hfe ib_1 re$  — ②

③ —  $i_o = hfe ib_1 + \frac{V_o}{R_B} + ib_2$

④ —  $V_o - V_e = re hfe ib_2$

Sub. for  $ib_1$  from ② in ③ }  $i_o = -\frac{V_e}{re} + \frac{V_o}{R_B} + \frac{V_o - V_e}{hfe re}$   
 and for  $ib_2$  from ④ in ③ }

⑤ —  $\therefore i_o = -\frac{V_e}{re} + \frac{V_o}{R_B} + \frac{V_o}{hfe re} - \frac{V_e}{hfe re}$  Small compared to 1st term as  $hfe \gg 1$

Sub. for  $ib_1$  from ② in ① }  $V_e = -\frac{V_e R_T}{re} + (V_o - V_e) \frac{R_T}{re}$   
 and for  $ib_2$  from ④ in ① }

⑥ —  $\therefore V_e = \frac{V_o R_T}{re(1 + 2R_T/re)} = V_o \cdot \frac{R_T}{(re + 2R_T)} \approx V_o/2$  as  $re \ll R_T$

Sub. ⑥ into ⑤ to eliminate  $V_e$  :  $i_o = V_o \left[ \frac{-1}{2re} + \frac{1}{R_B} + \frac{1}{hfe re} \right]$


Hence the input impedance =  $\left[ \frac{-1}{2re} + \frac{1}{R_B} + \frac{1}{hfe re} \right]^{-1}$  which is  $\therefore$

equivalent to  $-2re \parallel R_B \parallel hfe re$   
 $\underbrace{\hspace{10em}}_{h_{is} = h_{ie}}$

So, we have a negative resistance ( $re$  is small)

2(b) If  $L = 10nH$  @  $1GHz$   $j\omega L = j63\Omega$

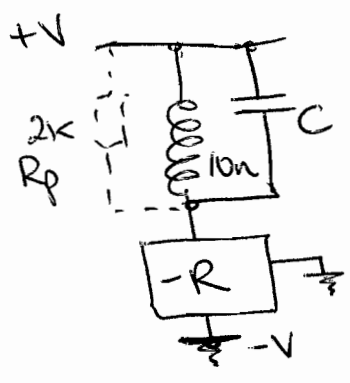so a Q factor of 30 gives an effective parallel loss resistance of  $30 \times 63 \approx 2k\Omega$  - hence the -ve resistance must be less than this



$$\frac{1}{2\pi\sqrt{LC}} = 10^9 \text{ Hz}$$

$$10 \times 10^{-9} \therefore C = 2.53 \text{ pF}$$

For the -ve resistance circuit, we need  $r_e \approx 100's \Omega$  at most.  $\therefore$  choose  $R_b = 10k\Omega$  say ( $\gg R_p$ )


$r_e = \frac{0.025}{I_c}$  where  $I_c$  is the collector bias current in mA

$\therefore$  set  $I_c = 1mA$  say  $\therefore r_e = 25\Omega$   
giving a negative resistance  $\sim -50\Omega$


eg: for a supply of  $\pm 5V$ ,  $R_T = 2k\Omega$  will bias each transistor with approx.  $1mA$ .

2(d)

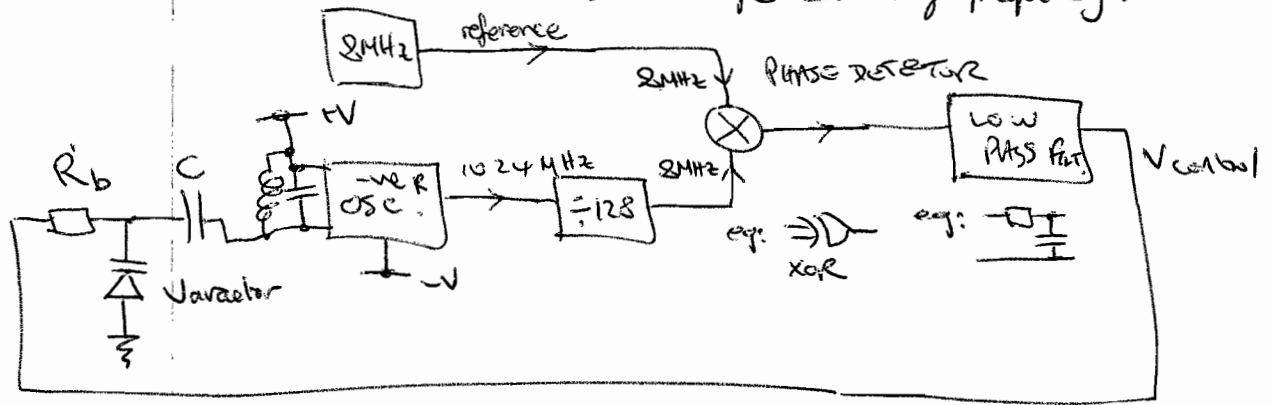Putting a varactor in parallel with the inductor L allows voltage control of frequency.




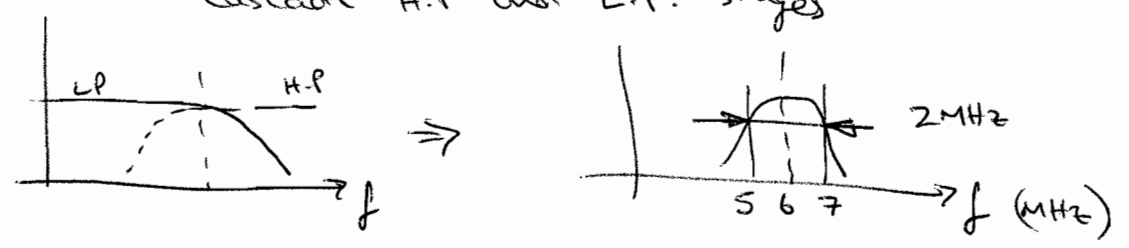3(a). VCVS - choose Chebyshev for sharpest band edges  
 - cascade H.P. and L.P. stages




H.P. :  $f_c = 5 \text{ MHz}$   
 L.P. :  $f_c = 7 \text{ MHz}$

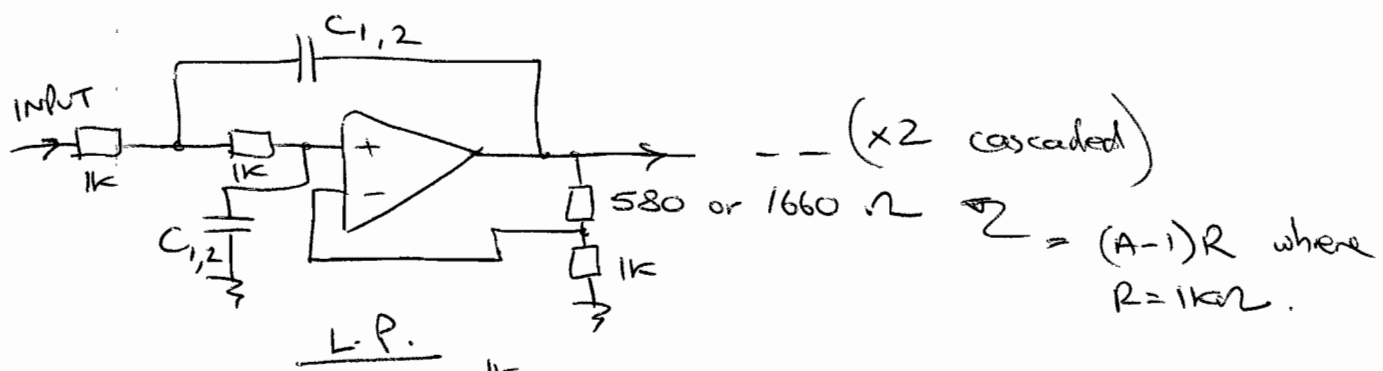$f_m = 0.597$      $A = 1.582$   
 $1.031$              $= 2.660$



$Z = (A-1)R$  where  $R = 1k\Omega$ .

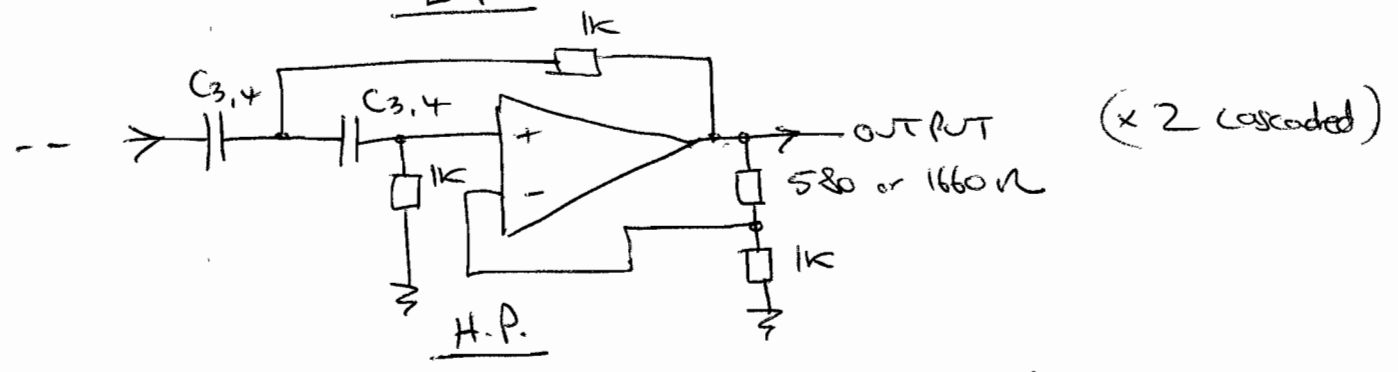


For L.P.  $f_c = \frac{1}{2\pi f_n R C_{1,2}} = 7 \times 10^6$ ,  $R = 1k\Omega$  throughout

H.P.  $f_c = \frac{1}{2\pi f_n R C_{3,4}} = 5 \times 10^6$


$\therefore C_1 = 38 \text{ pF}$   
 $C_2 = 22 \text{ pF}$

$C_3 = 19 \text{ pF}$   
 $C_4 = 33 \text{ pF}$

(b)

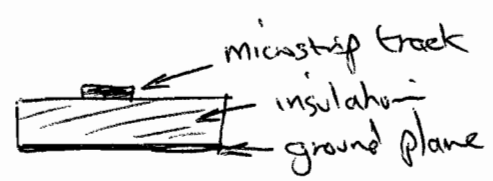

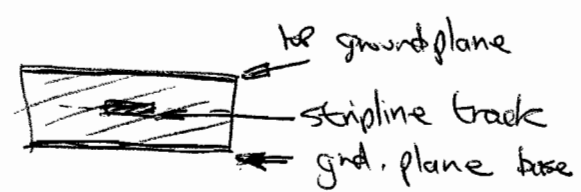- Easy to attach components & make connections
- $Z_0$  can be higher for given board thickness




- Lower losses + radiation
- Lower cross-coupling to other lines
- $Z_0$  can be lower for given board thickness.

3(b) cont.


$$Z_0 = \sqrt{\frac{L}{C}} \quad v = \frac{1}{\sqrt{LC}} = \frac{c_0}{\sqrt{\epsilon_r}}$$

For microstrip:

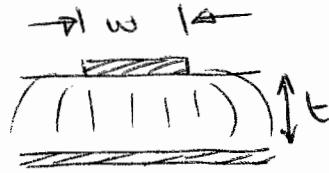

$$C \approx \frac{(w + 2t) \epsilon_0 \epsilon_r}{t}$$

For stripline:

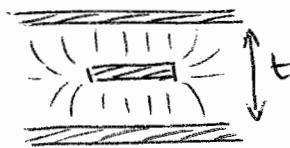

$$C \approx \frac{2(w + t) \epsilon_0 \epsilon_r}{t/2}$$

For  $\epsilon_r = 3.8 \Rightarrow v = 154 \times 10^6 \text{ m/s} = \frac{1}{\sqrt{LC}}$

with  $Z_0 = 33 = \sqrt{\frac{L}{C}} \quad \therefore L = 1089 C$

$$(154 \times 10^6)^2 = \frac{1}{LC} = \frac{1}{1089 C^2} \quad \therefore C = 197 \times 10^{-12} \text{ F/m}$$

For microstrip:  $197 \times 10^{-12} = \frac{(w + 2 \times 10^{-3}) \cdot 3.8 \cdot 8.854 \times 10^{-12}}{10^{-3}}$

$$\therefore w = 3.35 \times 10^{-3} \text{ m} = \underline{3.35 \text{ mm}}$$


For stripline:  $197 \times 10^{-12} = \frac{4(w + 10^{-3}) \cdot 3.8 \cdot 8.854 \times 10^{-12}}{10^{-3}}$

$$\therefore w = 4.6 \times 10^{-4} \text{ m} = \underline{0.46 \text{ mm}}$$

3(c)  $f = 1030 \times 10^6 \text{ Hz} \quad \therefore \frac{154 \times 10^6}{v} = 1030 \times 10^6 \cdot \lambda$


Hence  $\lambda = 0.15 \text{ m} \text{ (15 cm)}$

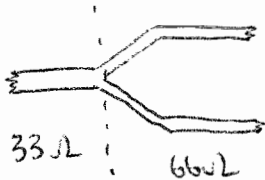For  $90^\circ$  phase shift  $\equiv \lambda/4 = \underline{3.7 \text{ cm back difference}}$



For matching  $Z_0 = 66 \Omega \quad \therefore w = 0.92 \text{ mm}$   
in microstrip

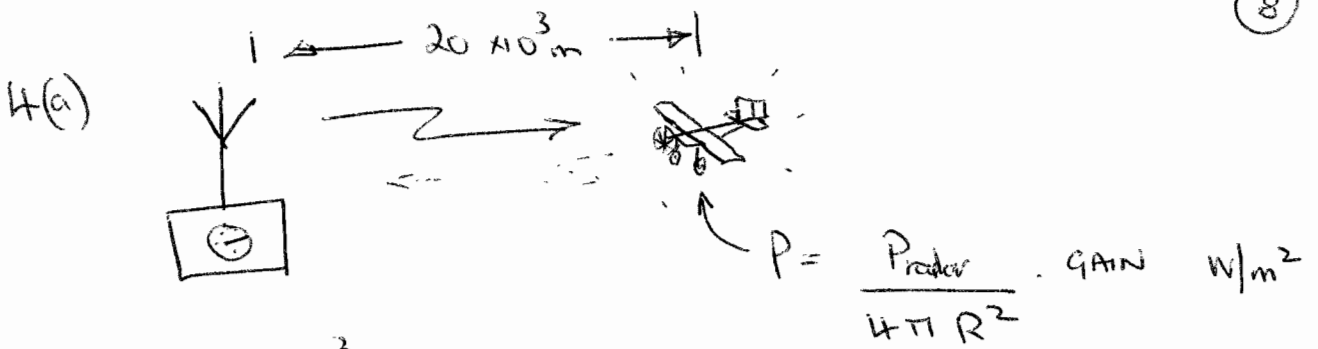But for  $Z_0 = 66 \Omega$  in stripline,  $w = \underline{0.26 \text{ mm!}}$   
 $\therefore$  not possible



$$P = \frac{25 \times 10^3}{4\pi (20 \times 10^3)^2} \cdot 500 = 2.5 \times 10^3 \text{ W/m}^2$$

$$P = \frac{1}{2} \eta H^2 = \frac{1}{2} E^2 / \eta \quad \text{with } \eta = 120\pi$$

$$\therefore H = 3.6 \times 10^{-3} \text{ A/m}, \quad E = 1.37 \text{ V/m}$$

(b)  $P_{\text{rad}} = 2.5 \times 10^{-3} \times 20 = 0.05 \text{ W}$  isotropic

$$G = \frac{4\pi A_e}{\lambda^2} = 500 \quad \text{and} \quad \lambda = \frac{c}{f} = 0.291 \text{ m}$$

$$\therefore A_e = \frac{500 \cdot 0.291^2}{4\pi} = 3.35 \text{ m}^2$$


$$\therefore P_{\text{rec}} = \frac{50 \times 10^3}{4\pi (20 \times 10^3)^2} \cdot 3.35 = 33 \text{ pW}$$

$$\therefore 33 \times 10^{-12} = \frac{1}{2} \frac{V^2}{R} = \frac{V^2}{100} \Rightarrow \underline{V = 58 \mu\text{V}}$$

with  $R = 50 \Omega$

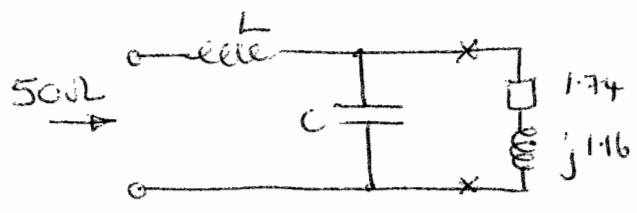(c)  $87 + j58 \Omega / 50 \Omega \rightarrow 1.74 + j1.16$

From Smith chart, volt. ref. coef. = 0.46






# 4(c) SMITH CHART

•  $A = 1.74 + j1.16$   
 ↓  
 admittance  $B = 0.4 - j0.26$

•  $C = 0.4 + j0.49$   
 hence parallel capacitor gives  
 susceptance of  $j(0.49 - 0.26)$   
 =  $j0.75$

• Draw line CD such  
 that  $CO = OD$   
 with  $Re C = 0.4$   
 and  $Re D = 1$

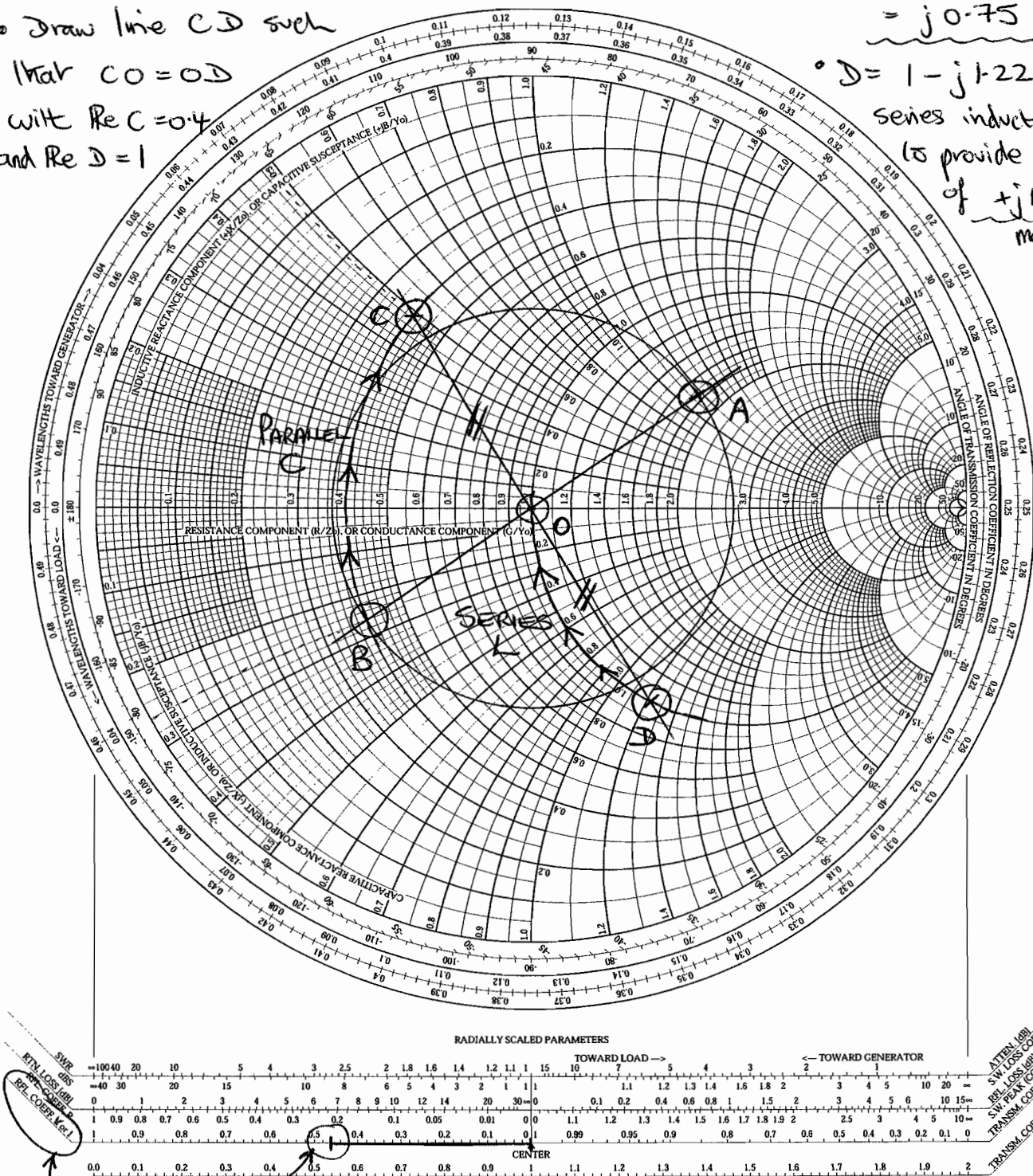•  $D = 1 - j1.22$ , so  
 series inductor needs  
 to provide reactance  
 of  $+j1.22$  to  
 match at  
 O.



Hence:  
 $j\omega C = j0.75/50$   
 $j\omega L = j1.22 \times 50$   
 with  $\omega = 2\pi \times 1030 \times 10^6$   
 $\Rightarrow C = 2.3 \text{ pF}, L = 9.4 \text{ nH}$

•  $0.46$   
 impedance  
 admittance  
 $D, C$

## **ENGINEERING TRIPOS PART IIA 2006**

### **Module 3B1, Radio Frequency Electronics - Assessors' Report**

#### **Q1. Transistor amplifier**

This was a fairly popular question and generally well attempted. All candidates knew the basic circuit layout for an amplifier and many made good attempts at the design, although some chose impractical component values. The final part, on a signal switching circuit, was not answered very well in many cases; with few attempts including the required demodulator circuit.

#### **Q2. Phase locked loop & oscillator**

Most candidates could draw the PLL schematic and knew how it worked. Also, many candidates correctly derived the negative impedance part (which was standard book-work) although some had remembered the final result and contrived to get there with an incorrect circuit. Several candidates made a good attempt at the final PLL design, locking the 1.024 GHz signal to an 8 MHz quartz crystal reference.

#### **Q3. VCVS filter & microstrip design**

The most popular question and well answered in most cases. Only a few candidates did not recall the VCVS circuits accurately and almost all selected the most appropriate filter type. The second half on microstrip design was also generally well answered, although only a few worked out the impedance of a stripline geometry and realised that the final part, needing a 66 ohm characteristic impedance, could only be realised in microstrip.

#### **Q4. Antenna theory & Smith chart**

This was also a fairly popular question attracting a wide range of attempts. The first part was quite straightforward and most candidates managed to work out the radar signal levels quite well. The section on impedance matching was well answered in most cases, although a number of attempts used a different design method to the graphical method elicited in the question and some candidates used an extra series capacitor to simplify the Smith chart plot.

Dr P.A. Robertson, May 2006

### 3B1 – Radio Frequency Electronics 2006

(some numerical answers etc.)

- 1(b) 

<u>R1</u>	<u>R2</u>	<u>R3</u>	<u>R4</u>	
1M2	150k	3k3	33k	stage 1
390k	47k	1k	10k	stage 2

 100nF coupling caps, 15nF shunt cap.
- 1(c) Use diode demodulator and comparator to monitor signal level and MOSFET analogue switch to mute the signal when at low levels.
- 2(b) With  $L = 10 \text{ nH}$  @  $1 \text{ GHz} = j63 \Omega$ , so Q factor = 30 gives shunt resistance of  $\sim 2 \text{ k} \Omega$ , hence choose transistor bias to give  $-R$  of LESS than this eg.  $-50 \Omega$  to guarantee oscillation.  $C = 2.53 \text{ pF}$  for LC resonance at  $1 \text{ GHz}$ .
- 3(a) Choose Chebyshev for sharp frequency cut-off. Low pass up to  $7 \text{ MHz}$ , high pass from  $5 \text{ MHz}$  gives cascaded bandpass  $5\text{-}7 \text{ MHz}$ .  
 $C1 = 38 \text{ pF}$ ,  $C2 = 22 \text{ pF}$  (low pass stages),  $(A-1)R = 580$  or  $1660 \Omega$   
 $C3 = 19 \text{ pF}$ ,  $C4 = 33 \text{ pF}$  (high pass stages), ditto
- 3(b)  $w = 3.85 \text{ mm}$  microstrip,  $0.46 \text{ mm}$  stripline for  $33 \Omega$ .
- 3(c)  $37 \text{ mm}$  track length difference =  $90$  degrees.  
For  $66 \Omega$  track, use microstrip  $0.92 \text{ mm}$  wide; not possible in stripline ( $-0.26 \text{ mm}$ ).
- 4(a)  $P = 2.5 \text{ mW/m}^2$ ,  $H = 3.6 \times 10^{-3} \text{ A/m}$ ,  $E = 1.37 \text{ V/m}$ .
- 4(b)  $P_{\text{rec.}} = 33 \text{ pW}$ ,  $V_{\text{rec.}} = 58 \mu\text{V}$  into  $R = 50 \Omega$ .
- 4(c) Normalise to  $1.74 + j1.16$ . Voltage refl. coeff. =  $0.46$   
Match with  $C = 2.3 \text{ pF}$  and  $L = 9.4 \text{ nH}$ .