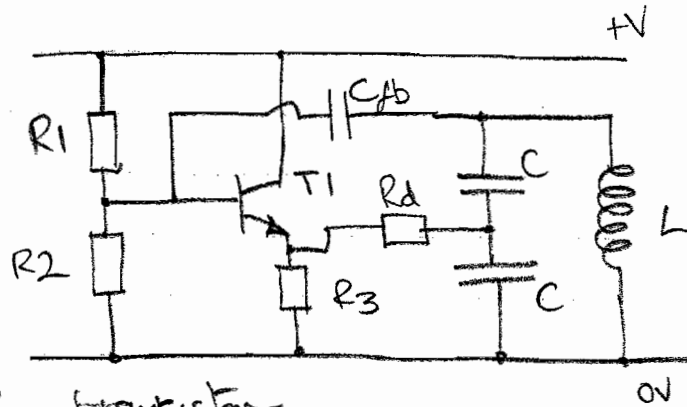


1. a)



- T1 : transistor
- R1 + R2 : base bias resistors
- R3 : emitter load resistor
- L + C : resonant circuit
- Cfb : feedback capacitor
- Rd : diode resistor

$$f_{res} = \frac{1}{2\pi\sqrt{LC/2}}$$

LC circuit is maintained in oscillation by transistor buffer. The capacitor's mid-point voltage is doubled at resonance and fed back to the transistor base. The buffer has a gain ≈ 1 , hence loop gain is ≈ 2 (unloaded) - so oscillation starts up. The amplitude is limited by the transistor non-linearity at voltage swings approaching the supply rails. The output can be taken from the emitter (low impedance but distorted esp. even harmonics) or the top of L (high impedance loads only - or oscillation will be damped or pulled in frequency).

b) $f_{res} = 434 \text{ MHz} = \frac{1}{2\pi\sqrt{L \frac{220 \times 10^{-12}}{2}}} \quad \therefore L = 1.22 \text{ nH}$

Power level: 2mW into 100Ω, low impedance \therefore take output from the emitter.

$$2 \times 10^{-3} = \frac{V^2}{100}$$

$$P = \frac{V^2}{R}$$

$$\therefore V = 0.45 \text{ V rms}$$

$$\approx 1.26 \text{ V pp} \quad \checkmark \text{ ok.}$$

as less than 2/3 of supply

1b) cont.

choose $R_3 = 220 \Omega$ (twice load resistance) $C_{fb} = 10 \text{ nF}$ (large compared to C) $C = 220 \text{ pF}$

$\omega L = 3.3 \Omega \Rightarrow$ assuming Q factor of 50, gives a parasitic load of $\approx 170 \Omega$. Hence $R_d \approx \frac{170}{4} = 33 \Omega$ say


choose R_1 & R_2 to bias the emitter at $\frac{3.3 \text{ V}}{2}$, taking $V_{BE} = 0.65 \text{ V} \Rightarrow V_B = 2.3 \text{ V}$.

So choose $R_1 = 1 \text{ k}\Omega$ & $2.3 = 3.3 \cdot \frac{R_2}{1000 + R_2} \therefore R_2 = 2.3 \text{ k}\Omega$

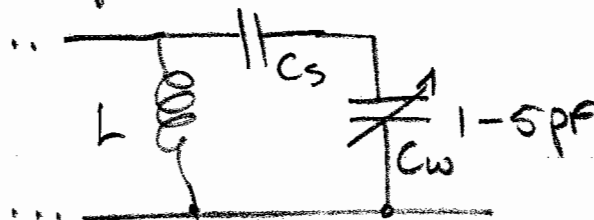c) wind speed signal = 1 V_{pp} @ $10 - 100 \text{ Hz}$: AM
wind dirn signal = $1 - 5 \text{ pF} = C_w$: FM

Taking FM case first, we must connect C_w across the LC tank ckt. But for 2 MHz FM on a carrier of 434 MHz , $\frac{\Delta f}{f} \approx 0.5\%$ $\therefore \frac{\Delta C}{C} \approx 1\%$

for correct modulation swing. So, the LC tank must see a capacitance swing of $\sim 1 \text{ pF}$. we achieve this with a series capacitor ...



with a little thought, we can see C_s should be approx. 2 pF

2 pF in series $1 \text{ pF} = 0.6 \text{ pF}$

2 pF in series $5 \text{ pF} = 1.43 \text{ pF}$

$\rightarrow 0.77 \text{ pF}$ by guessing or we can solve by eqn.

$$AC = 1 = \left(\frac{1}{C_s + 5} \right)^{-1} - \left(\frac{1}{C_s + 1} \right)^{-1}$$

1 d) cont.

$$1 = \frac{5C_s}{5+C_s} - \frac{C_s}{1+C_s}$$

$$(5+C_s)(1+C_s) = 5C_s(1+C_s) - C_s(5+C_s)$$


$$5 + 6C_s + C_s^2 = 5C_s + 5C_s^2 - 5C_s - C_s^2$$

$$\therefore 3C_s^2 - 6C_s - 5 = 0$$

$$\therefore C_s = \frac{6 \pm \sqrt{36 + 60}}{6} \quad \Rightarrow C_s = 2.63 \text{ pf}$$

$$\Delta C = 1.72 \text{ pf} \rightarrow 0.72 \text{ pf} \quad (\text{1 pf})$$

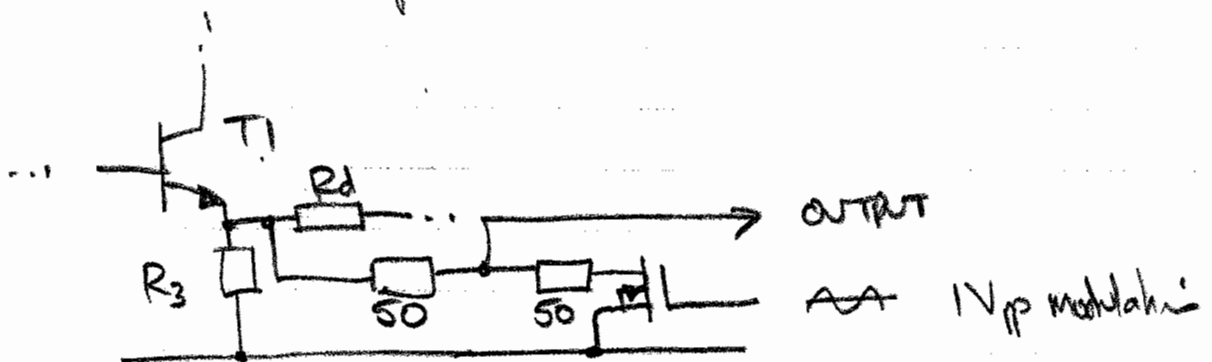
For the amplitude modulation, we need V_{pp} to modulate the output by $\sim 50\%$. \therefore use a (MOS) FET potential divider or bipolar transistor



(or, more elegantly, the main oscillator transistor base bias could be modulated through $\sim 1k\Omega$ resistor).

3B1

2 a)

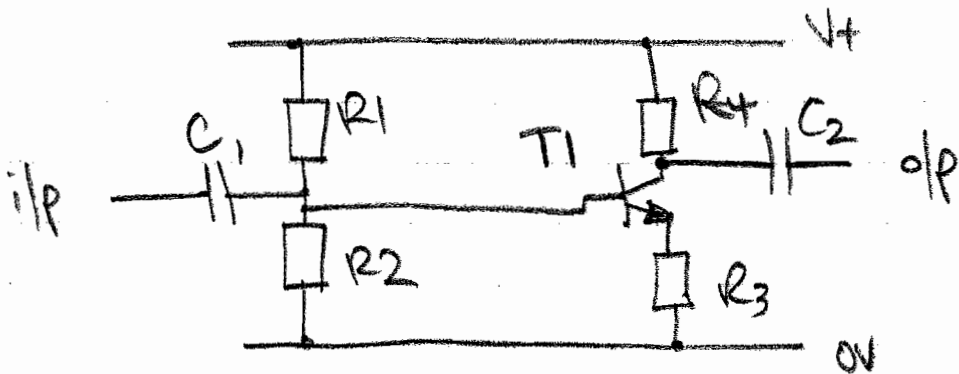

R_1, R_2 base bias resistors: define input impedance and aim to set $V_c \approx V_{supply}/2$

R_3 emitter resistor: to define gain $-R_4/R_3$ and provide $-ve$ feedback for bias stability

R_4 collector load resistor: defines output impedance and gain

C_1, C_2 coupling capacitors: block dc loads from source and/or load for transistor bias point

b) $R_{in} = R_{out} = 100\Omega$
 $2mW$ input \Rightarrow $200mW$ output for $20dB$ ($\times 10$) gain

$R_4 = 100\Omega$ for output impedance = 100Ω
 $R_3 = 2.5\Omega$ for gain of $\times 40$ unloaded = $\times 10$ loaded
 dc output & input

$0.2W = P = \frac{V^2}{100}$ $\therefore V_{rms} = 4.5V \approx 13V_{pp}$
 \checkmark OK for $20V$ supply

\therefore set $V_c = 10V$ $\therefore V_B = 10.7V$ for $V_{BE} = 0.7V$

$\therefore \frac{R_2}{R_1 + R_2} \times 20V \approx 12V$ (allowing for base loading)

2b) contd.

\therefore choose $R_1 = 220\Omega$ ($\approx 2\times$ input impedance reqd.)


$$0.6 = \frac{R_2}{220 + R_2} \Rightarrow R_2 = 330\Omega$$

note: - $220 \parallel 330 \parallel h_{ie} R_3 = 120\Omega \checkmark 0.1k$.
 (could reduce $R_1 + R_2$, or shunt with 620Ω for better match is 100Ω).

choose C_1 & C_2 to be small impedance at $400\text{MHz} +$
 eq: $\frac{1}{2\pi f C} \approx 50\Omega \therefore C_{1,2} \approx 1\text{nF}$

note: $I_C = 100\text{mA} \therefore r_e = 0.25\Omega$, so could reduce R_3 to compensate.

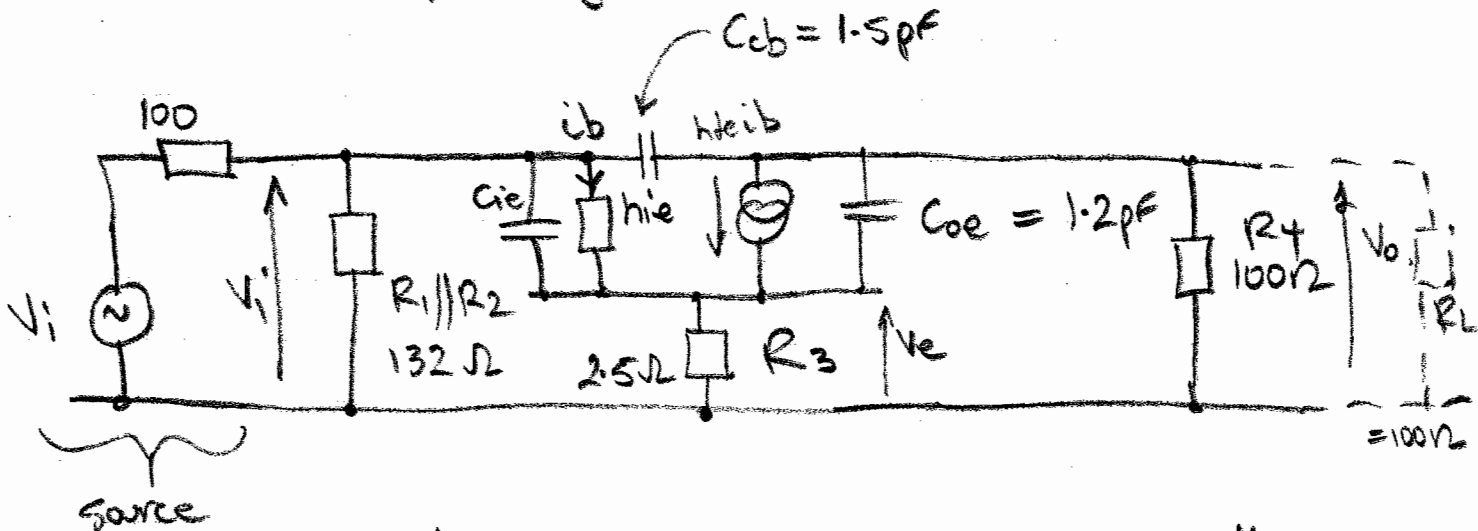c) Now consider small signal model of input to see roll-off frequency:



Net amplifier gain $\frac{V_i}{V_o} = -20 \therefore$ Miller effect on

$$C_{cb} = 0.25\text{pF} \times 21 \approx 3.2\text{pF}$$


From $f_c = 18\text{GHz} = \frac{1}{2\pi C_{ie} r_e}$ $\leftarrow 0.25\Omega$

$\therefore C_{ie} = 35\text{pF}$ and $h_{ie} = h_{fe} \cdot r_e = 63\Omega$

3B1.

2c) contd.

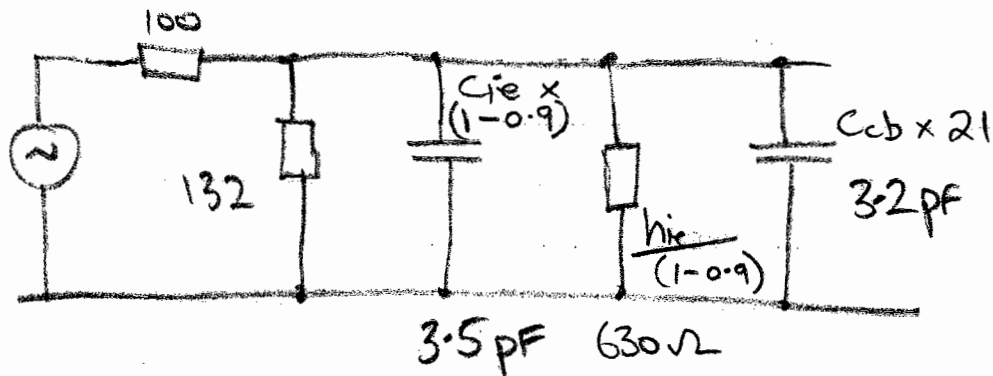$V_e \approx \frac{R_3}{R_3 + r_e} V_i = 0.9 V_i$ here small signal model, with components referred to ground \Rightarrow




Combining R 's & C 's we get: $R' = 52 \Omega$ $C' = 6.7 \text{ pF}$

$$f = \frac{1}{2\pi R C} = 457 \text{ MHz}$$

Hence, the circuit is only just fast enough for 434 MHz operation and will have $< 50\%$ of the required gain at 868 MHz.


(Even if loaded gain is assumed as $\times 10$, then the roll-off is still less than 600 MHz).

3 (a)

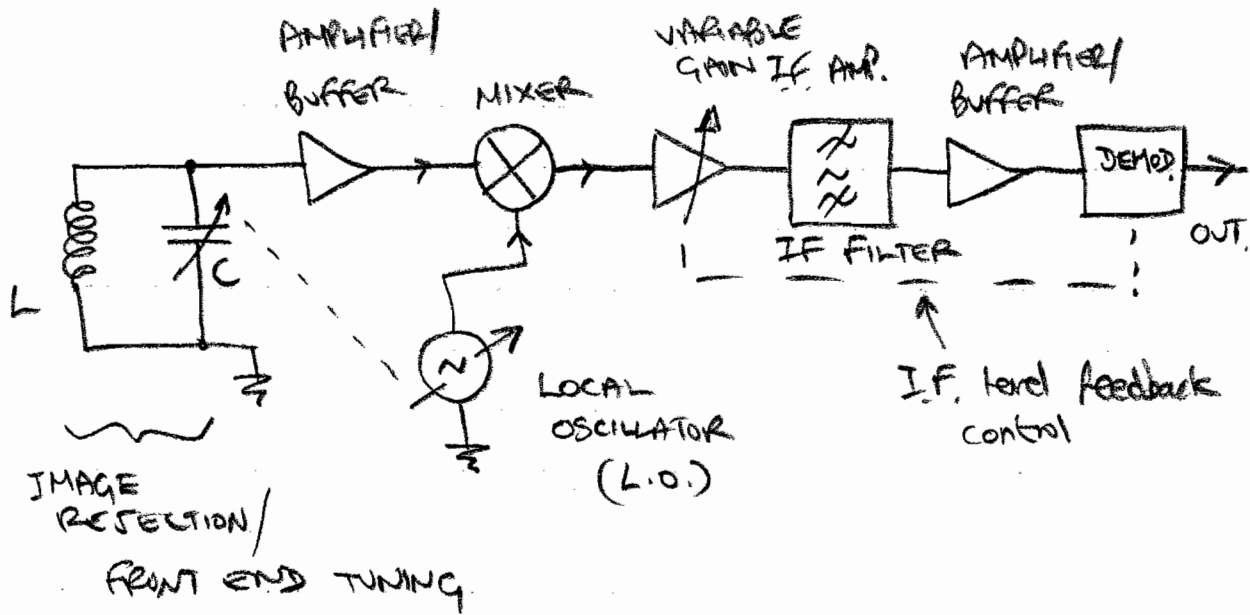

- The front-end LC tank selects which of $f_{LO} \pm f_{IF}$ is selected for reception
- Controlling the I.F. signal level with an electrically variable gain amplifier gives all received stations similar volumes / audio levels.
- Other details in course notes.

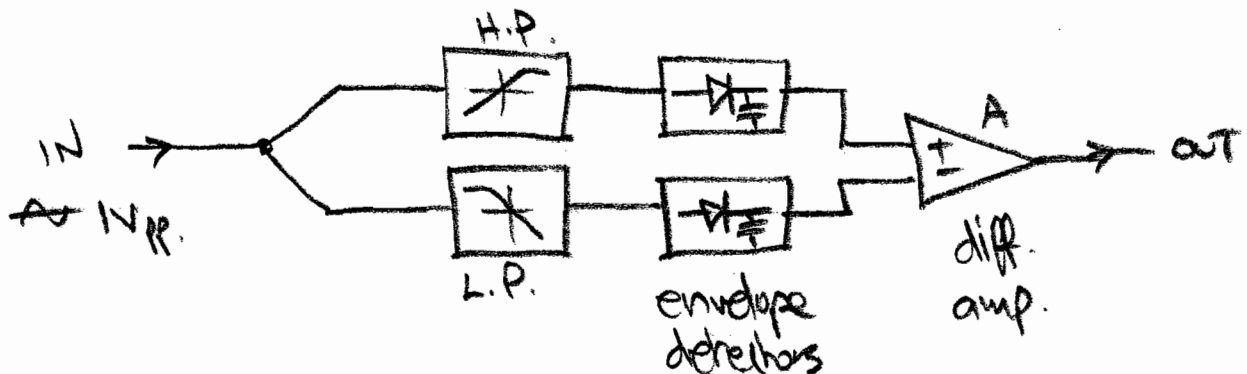
(b) To demodulate an FM signal on the I.F. of 20MHz, we shall use a high-pass and low-pass filter pair and a differential amplifier using the envelopes from the 2 filters. The 2MHz modulation depth gives 10% modulation on the I.F. i.e. 19-21 MHz



For the filters, we need to be on the roll-off slopes. Choose eg. Butterworth response as good compromise in f and t domains.

3c)

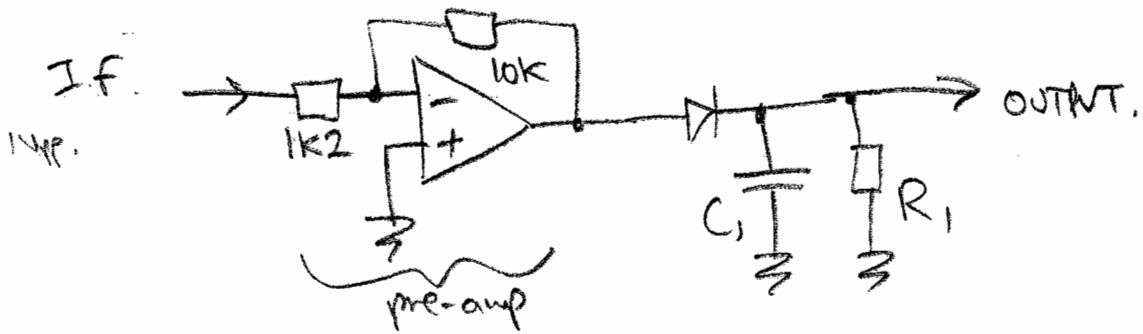AM demodulation can use diode envelope detector




50% of a $1V_{pp}$ signal = $0.5V_{pp} = 0.25V_{pk}$ change
 \therefore gain of $\frac{2}{0.25} = 8$ required for $2V_{pp}$ output -
 also pre-amp. ensures a large signal for the envelope detector diode.

Choose output time constant = $1ms$
 (for $< 100Hz$ signal)

$$R_1 = 10k\Omega$$

$$C_1 = 100\mu F$$

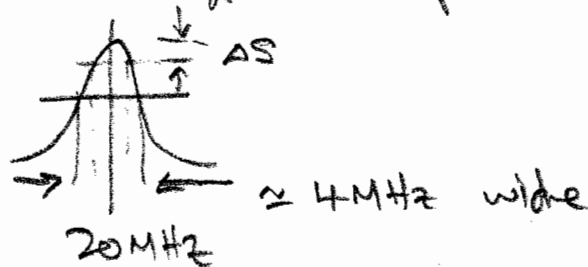d) If the I.F. ^{filter} has a peaked response, then as the





frequency is modulated around $20MHz$ (I.F.), so the amplitude will drop each side - hence the FM signal will be mixed into the AM signal.

For $Q=5$, the signal drops by 30% ($-3dB$) for $\pm 2MHz$ deviation - or perhaps around 10% for $\pm 1MHz$, which would be typ. 20% of the AM signal. This could be compensated by combining the $20\mu V_{pk}$ signal to produce a corrected AM signal. Also though, the non-steep band edges of a low Q filter can give poor channel selectivity in a crowded waveband - where the 'stations' are close in frequency.

381

3 b) contd.

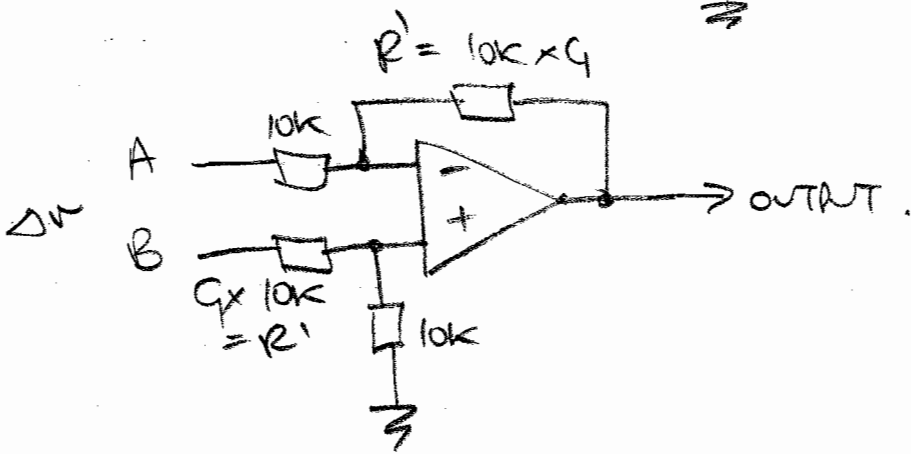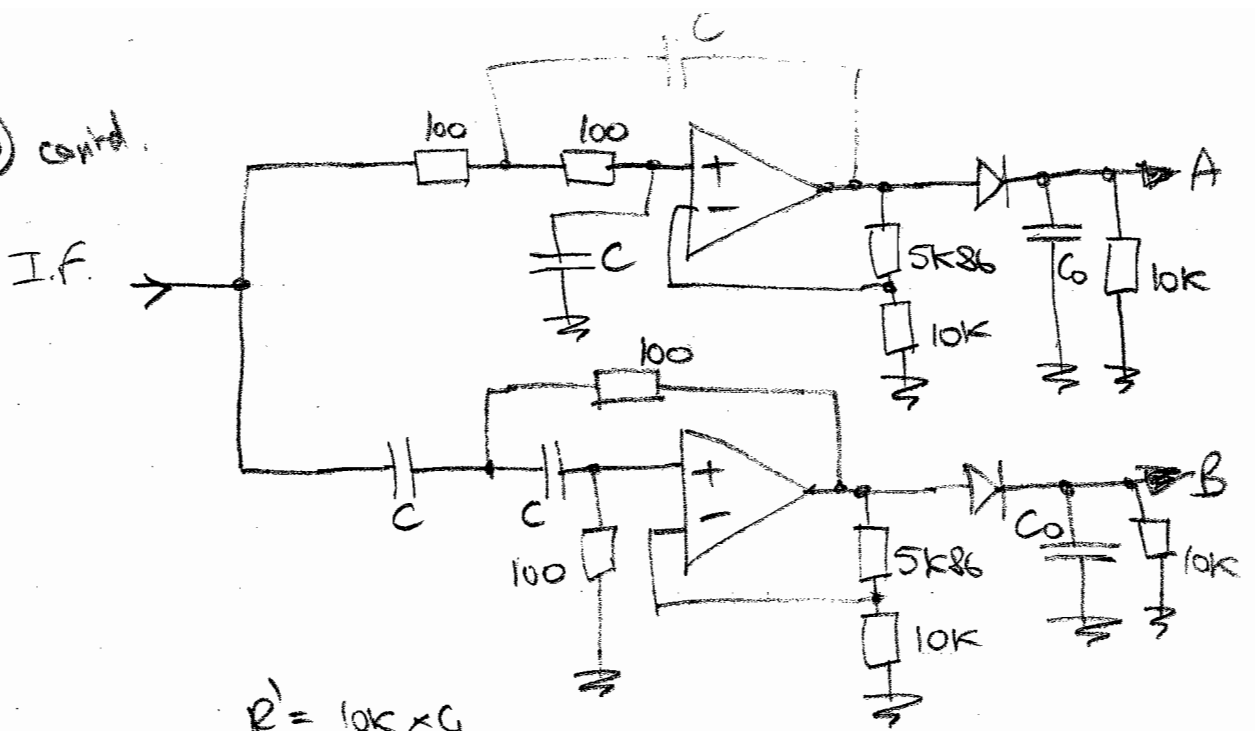

Set high-pass $f_0 = 30\text{MHz}$ and for low-pass, $f_0 = 15\text{MHz}$
 (so that 20MHz is on roll-off slopes).

Then $\frac{1}{2\pi f C R} = 30\text{MHz}$ or 15MHz ; $m=1$, $R=100\Omega$


\downarrow $C = 53\text{pF}$ \downarrow $C = 106\text{pF}$

Set demodulator time constant $150\mu\text{s} = 10^4 \cdot C_0 \therefore C_0 = 10\text{nF}$

Both filter attenuations are approx. $\div 2$ of I.F. and a 10% frequency change will result in 20% amplitude change with a 2-pole filter. $\therefore \Delta V \approx \frac{1}{2} \cdot 0.2 = 0.1\text{V}$
 \therefore diff. amp gain $G = \times 10$. $\therefore R' = 100\text{k}\Omega$.

381

4(a)

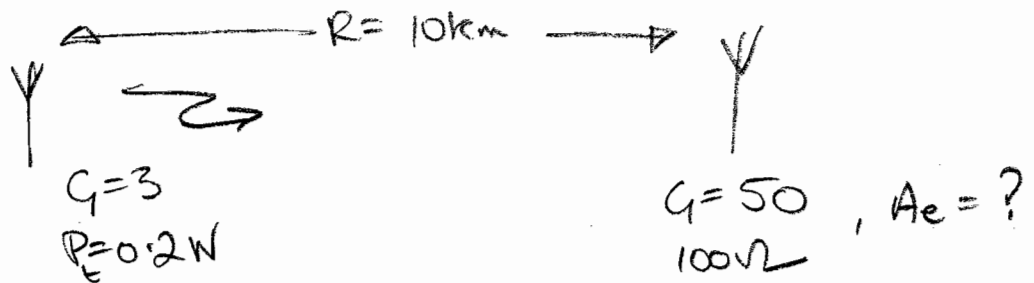

$$f = 434 \text{ MHz}$$

$$\therefore \lambda = \frac{3 \times 10^8}{434 \times 10^6} = 0.691 \text{ m}$$


From $G = \frac{4\pi A_e}{\lambda^2} = 50$

$$\therefore A_e = 1.90 \text{ m}^2$$

So, $P_r = \frac{P_t \cdot G \cdot A_e}{4\pi R^2} = \frac{0.2 \times 3 \times 1.90}{4\pi \cdot (10^4)^2} = 0.91 \mu\text{W}$

Into a 100Ω matched load, $P_r = \frac{V_r^2}{R} = 0.91 \times 10^{-9} = \frac{V_r^2}{100}$
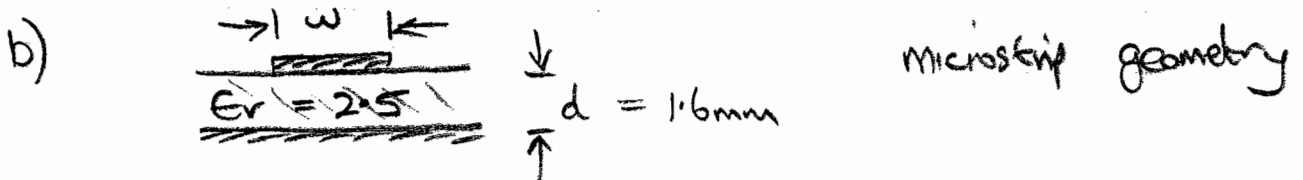
$$\therefore V_r = 0.30 \text{ mV}_{\text{rms}} = 0.85 \text{ mV}_{\text{pp}}$$



Capacitance/m = $C = \frac{(w + 2d) \cdot \epsilon_0 \epsilon_r}{d}$ and $Z_0 = \sqrt{\frac{L}{C}}$

also, velocity of elm wave, $v = \frac{1}{\sqrt{LC}} = \frac{3 \times 10^8}{\sqrt{\epsilon_r}}$


$$\therefore \frac{1}{LC} = \frac{(3 \times 10^8)^2}{\epsilon_r} \Rightarrow L = \frac{\epsilon_r}{C \cdot (3 \times 10^8)^2}$$

$$\therefore Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\left(\frac{\epsilon_r}{C^2 \cdot (3 \times 10^8)^2}\right)} = \frac{\sqrt{\epsilon_r}}{C \cdot 3 \times 10^8} = 100 \Omega$$

$$\therefore 100 = \frac{\sqrt{2.5} \times 1.6}{(w + 3.2) \cdot 8.854 \times 10^{-12} \cdot 2.5 \cdot 3 \times 10^8} \Rightarrow w = 0.61 \text{ mm}$$

381


4b) contd.

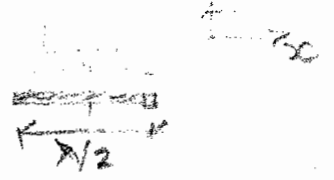

For the patch to be resonant, it should be $\frac{1}{2}$ wavelength long (for the guided wave).

$$\lambda_g = v/f = \frac{3 \times 10^8}{\sqrt{2.5} \cdot 434 \times 10^6} = 0.437 \text{ m}$$

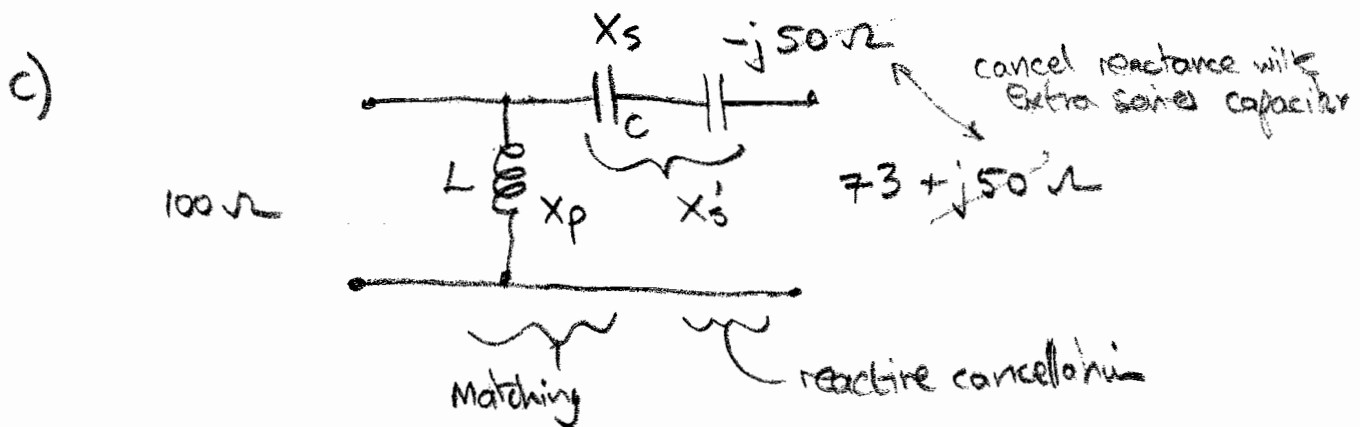\therefore the patch should be 21.9 cm long.



$$Q = \sqrt{\frac{100}{73} - 1} = \frac{100}{X_p} = \frac{X_s}{73} = 0.608$$

$$\therefore X_p = 164 = \omega L \quad \text{and} \quad X_s = 44 = \frac{1}{\omega C}$$

$$\text{with } \omega = 2\pi \times 434 \times 10^6 = 2.73 \times 10^9 \text{ rad/s}$$

$$\therefore L = 60 \text{ nH} \quad ; \text{ for } C', \text{ combine into single } C' \text{ with}$$

$$X_s' = 44 + 50 = 94 = \frac{1}{\omega C'}$$

$$\therefore C' = 3.9 \text{ pF}$$

The resonant standing wave along the patch gives max. voltage swing at the ends and max. current in the centre, hence the feed point impedance, V/I , will increase moving from centre to end.