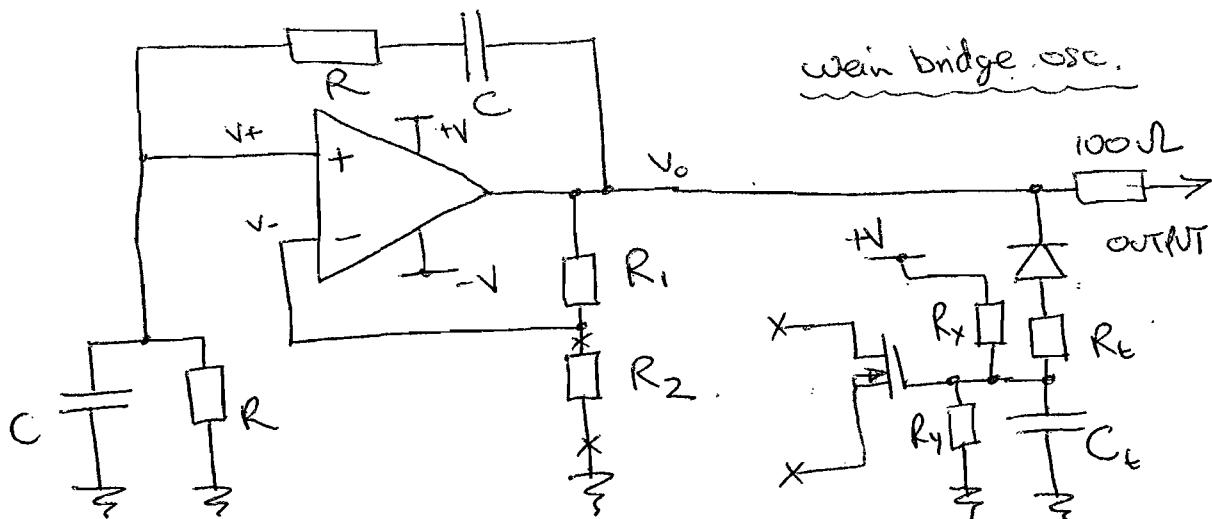


1 (a)



$$V_+ = V_o \cdot \frac{\frac{R}{1+j\omega CR}}{\frac{R}{1+j\omega CR} + R + \frac{1}{j\omega C}} = \frac{1}{1 + \frac{R + \frac{1}{j\omega C}}{\frac{R}{1+j\omega CR}}}$$


$$\therefore V_+ = \frac{V_o}{3 + j\omega CR + \frac{1}{j\omega CR}}, \text{ hence with } \omega = \frac{1}{CR} : V_+ = \frac{V_o}{3}$$

Hence $1 + \frac{R_1}{R_2} = 3$ for stable oscillation and $f = \frac{1}{2\pi RC}$

We can stabilise the output using a nF thermistor as R_1 , or by using a FET or MOSFET as a variable resistance to control the gain of the op-amp in response to the output amplitude. R_x and R_y are chosen to bias the FET to give a gain > 3 for start-up. R_t and C_t are chosen to give a long time constant compared to the oscillations e.g. $R_t = 100k\Omega$, $C_t = 100nF$ ($\tau = CR = 0.01s$). For 100kHz, let $R = 1k\Omega$ then $C = 1.59 nF$. Supply rails $\pm V$ can be $\pm 5V$ for 5Vpp output.


[35%]

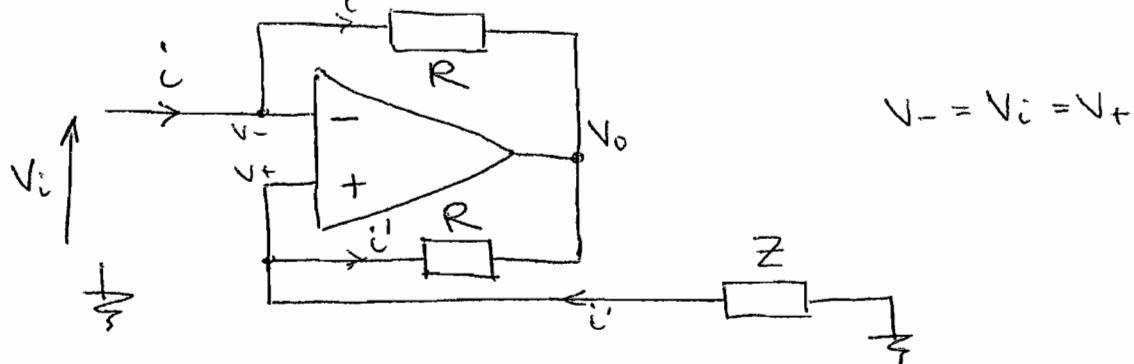1b) Firstly we need a Negative Impedance Converter (NIC). -



As $V_+ = V_-$ then the voltage across the impedance $Z = V_i$ and since $(V_o - V_i)$ appears across both + and - feedback resistors then $i' = i \Rightarrow V_+ = -iZ \therefore V_i = -iZ$, hence the input impedance $\frac{V_i}{i} = -Z$.

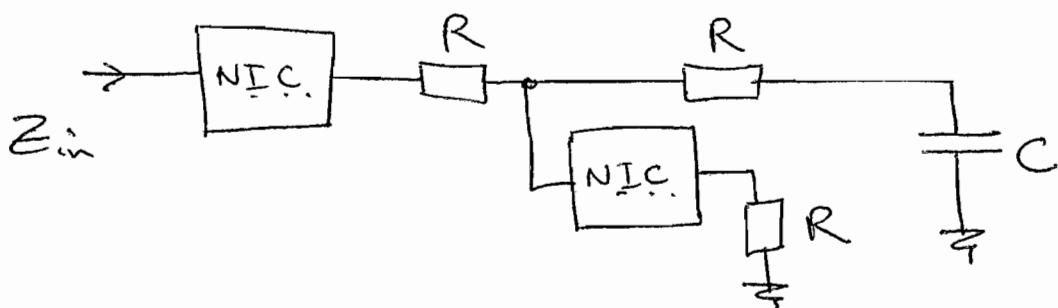
To synthesize an inductor, we cascade two NIC's with other passive components :-



$$\begin{aligned} Z_{in} &= - \left[R + -R \parallel \left(R + \frac{1}{j\omega C} \right) \right] \\ &= - \left[R + \frac{-R \left(R + \frac{1}{j\omega C} \right)}{-R + R + \frac{1}{j\omega C}} \right] \\ &= - \left[R - \frac{R^2 j\omega C - R}{R^2 j\omega C} \right] = j\omega C R^2 = j\omega L \end{aligned}$$

Hence, synthesized inductor $L = CR^2$. To vary L electrically, we shunt C with a varactor diode.

i) b) contd.

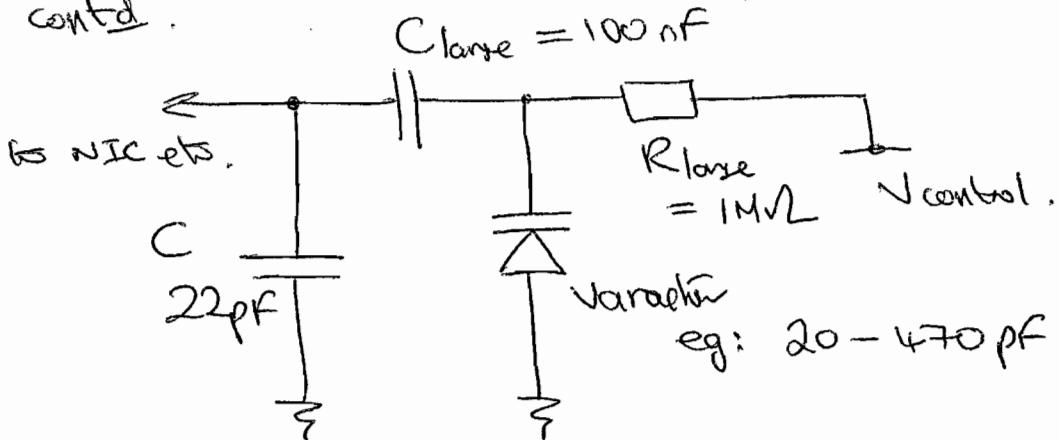

Let's assume the varactor can vary $20 - 470\text{ pF}$, hence with $C = 22\text{ pF}$, the total capacitance varies $42 - 492\text{ pF}$ (i.e. just over 10:1 range).

So select $47\text{ pF} \Rightarrow 1\text{ mH}$ ($470\text{ pF} \approx 10\text{ mH}$)

$$L = CR^2 = 10^{-3} = 47 \times 10^{-12} R^2 \therefore R = 4.6\text{ k}\Omega$$


[30%]

c) Plot impedance point A, then susceptance B. A parallel inductor moves B \rightarrow C $-j(0.315 - 0.182) = -j0.133$

Point C is such that $C_D = 0\text{ D}$, where D lies on the unit Re circle. A series capacitor $-j2.85$ matches point D to 0. For 100 kHz, $\omega = 2\pi \times 10^5 \text{ rad/s}$

$$\therefore \text{Inductor impedance (shunt)} = \frac{10}{-j0.133} = j75.2 = j\omega L \quad \therefore L = 120\mu\text{H}$$
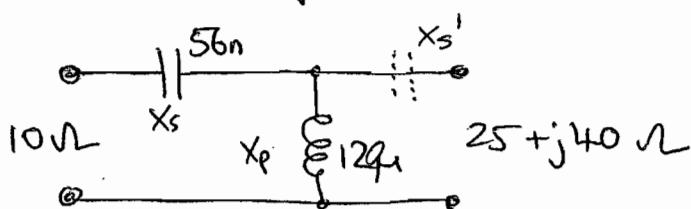
$$\text{Series capacitor} = -j2.85 = \frac{1}{j\omega C} \quad \therefore C = 56\text{ nF}$$




This can also be solved by calculation using $\frac{X_s}{10} = \frac{25}{10} = \sqrt{\frac{25}{10} - 1}$
but needs an additional X_s' ($-j40\Omega$) to cancel the inductor load term

Chart for question 4; to be detached and handed in with script.

1 c)


Normalise to 10Ω .

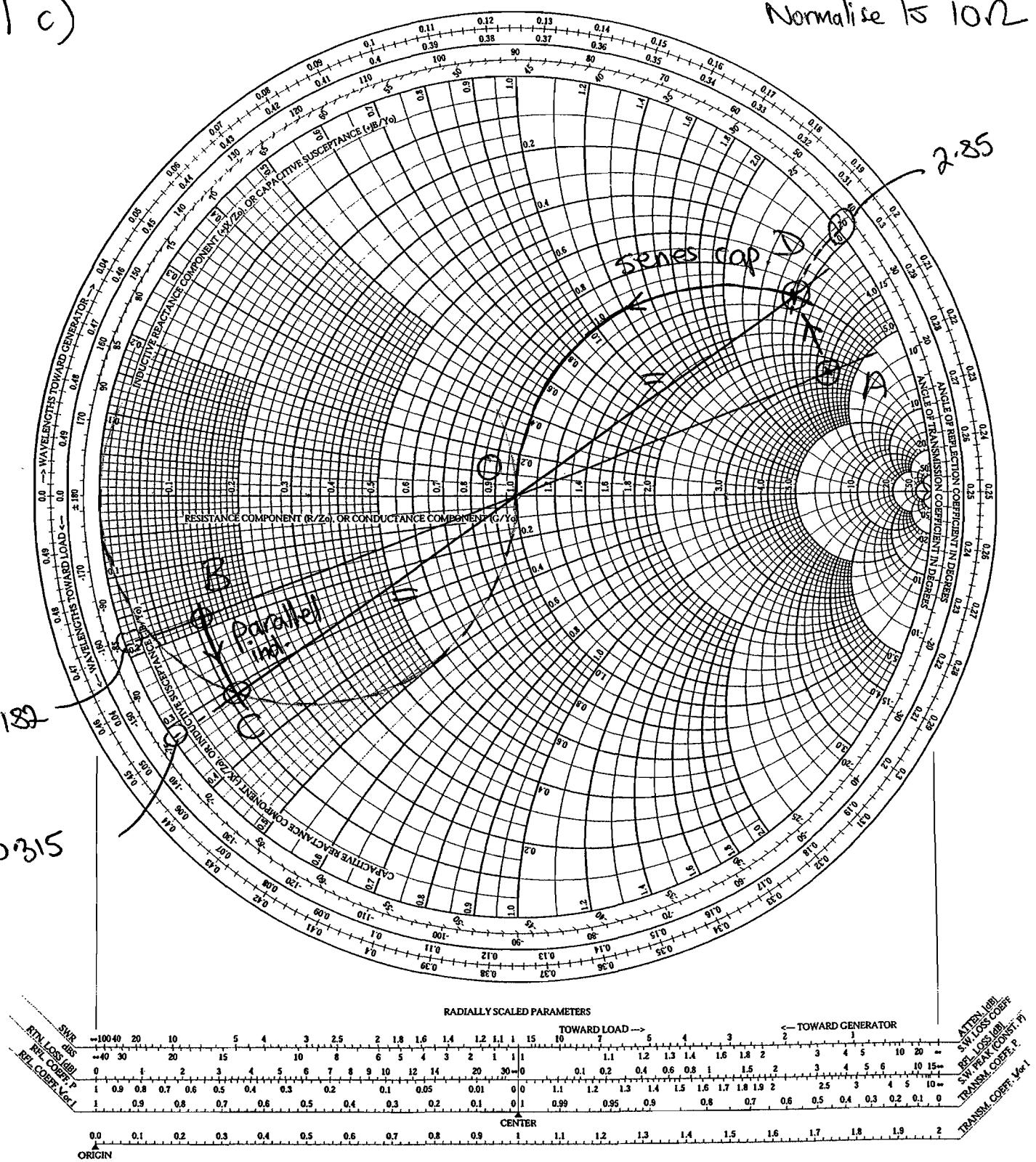

at 100 kHz, $\omega = 2\pi \times 10^5$ rad/s.

[35%]

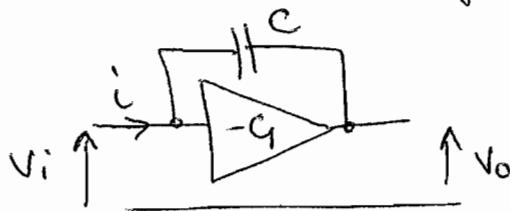2 a) The Miller Effect is apparent in electronic circuits which have gain and capacitance between input and output.



For example, summing the currents at the input :-


$$i = \frac{V_i - V_o}{\frac{1}{j\omega C}} \quad \text{where } V_o = -G V_i$$

$$\therefore i = \frac{V_i + G V_i}{\frac{1}{j\omega C}} = \frac{V_i (1+G)}{\frac{1}{j\omega C}} = \frac{V_i}{\frac{1}{j\omega (1+G)} C}$$

Hence, the equivalent value of capacitance seen at the input node is $(1+G)C$ and so the source impedance R will combine with this to give a -3dB roll-off at a frequency which decreases as the gain increases : $f_{-3\text{dB}} = \frac{1}{2\pi R(1+G)C}$

b) Cascade circuit

[10%]

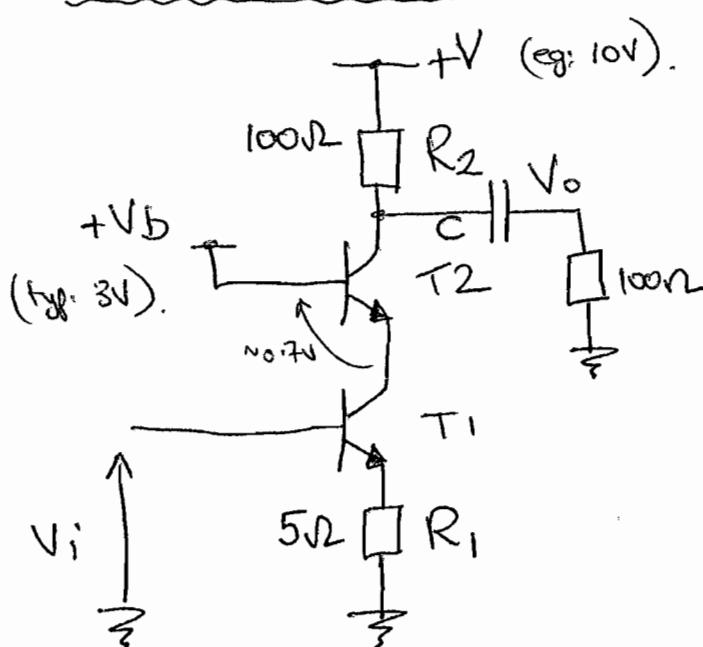


$$\frac{V_o}{V_i} = -\frac{100/2}{5} = -10.$$

T_1 is the input transistor, it has current gain but not voltage gain - hence the Miller effect is small, i.e. the collector voltage is kept

nearly constant by the B-E diode of T_2 . T_2 provides the voltage gain but since the base is connected to a low impedance source, the CR time constant remains small - so maintaining the bandwidth. $\Gamma_1 < 7$

2c)

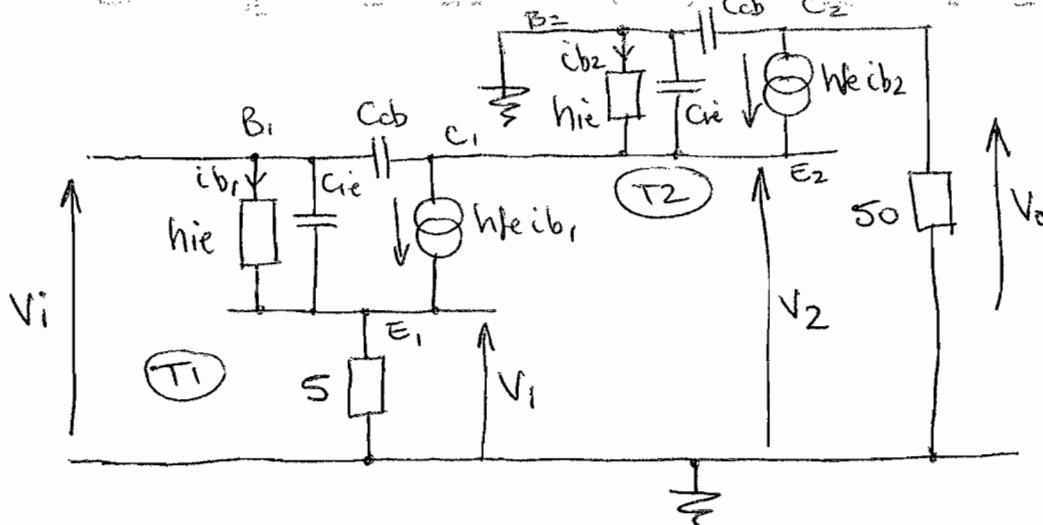

$$h_f = 500$$

$$f_c = 250 \text{ MHz}$$

$$C_{cb} = 5 \text{ pF}$$

$$r_e = \frac{V_t}{I_C}$$

$$h_{ie} = h_{fe} r_e$$

$$f_c = \frac{1}{2\pi r_e C_{ie}}$$

With DC bias current of $50 \mu\text{A}$, $r_e = \frac{0.025}{0.05} = 0.5 \Omega$

$\therefore h_{ie} = 250 \Omega$ and $C_{ie} = 1275 \text{ pF}$


$$V_1 = \frac{5}{5+r_e} V_i = \frac{10}{11} V_i, \quad V_2 = -i_{b2} h_{ie} \quad \text{where } i_b \approx i_{b2}$$

(from summing current at V_2 node) and $i_{b1} = \frac{V_i - V_1}{h_{ie}} = \frac{V_i}{2750} = \frac{V_i}{11 h_{ie}}$

$$\therefore V_2 = -\frac{V_i \cdot h_{ie}}{11 h_{ie}} = -\frac{V_i}{11}$$

for T1

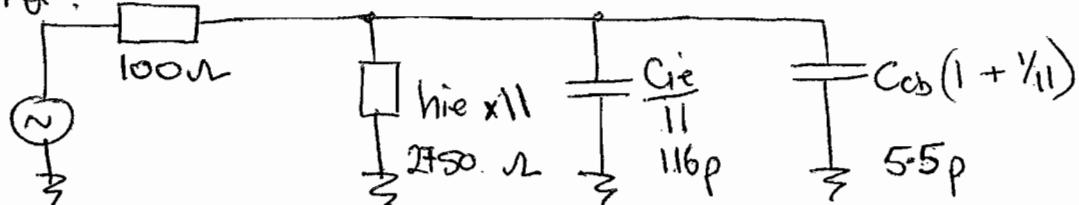Hence, looking at the input circuit and referring R_s and C_s to ground:



$$\therefore R = 100 // 2750 \Omega \quad C = 116 + 6 \text{ pF}$$

$$\therefore f_{-3dB} = \frac{1}{2\pi \cdot 96.12 \times 10^{-2}} = \underline{13.6 \text{ MHz}}$$

Without the Cascode's second transistor, C_{cb} would be multiplied by 11 = 55 pF and the roll-off would be $\approx 9.7 \text{ MHz}$.

Note: for T2 input cat. the grounded base gives a very small time constant with f_c roll-off.

[65%]

$$3 a) \text{ Power density from ideal dipole} = \frac{1.5 P_r}{2\pi R^2}$$

$$\therefore \text{at } 100\text{ km}, P_r = \frac{1.5 \times 15 \times 10^3}{2\pi (10^5)^2} = 3.58 \times 10^{-7} \text{ W/m}^2$$

$$\text{at } 350\text{ km}, P_r = \frac{1}{3.5^2} \cdot 3.58 \times 10^{-7} = 2.92 \times 10^{-8} \text{ W/m}^2$$

(8.2% of higher value)

$$P = \frac{1}{2} \eta H^2 = \frac{1}{2} \frac{E^2}{Z} \quad \text{where } Z = 120\pi = \text{impedance of free space}$$

$$\therefore \underline{H = 1.2 \times 10^{-5} \text{ A/m}} \quad \underline{E = 4.7 \text{ mV/m}} \quad [20\%]$$

$$b) A_e = \frac{\pi L^2}{4} = 78.5 \text{ m}^2 \text{ with } L = 10 \text{ m}$$

$$\therefore \text{Received power} = 78.5 \times 2.92 \times 10^{-8} \text{ W} = 2.29 \mu\text{W}$$

into a matched load = $4\text{k}\Omega$ gives

$$2.29 \times 10^{-6} = \frac{V_r^2}{4000} \quad \therefore V_r = 96 \text{ mV rms or } 0.27 \text{ Vpp}$$

$$G = \frac{4\pi A_e}{\lambda^2} \quad \text{with } \lambda = 5000 \text{ m @ 60 kHz}$$

$$\therefore G = 3.94 \times 10^{-5} \equiv -44 \text{ dB}$$

$$R_r = 20\pi^2 \left(\frac{L}{\lambda}\right)^2 \quad \text{assuming a linear current distribution}$$

$$= \underline{2.51 \times 10^4 \Omega}$$


7.89

[35%]

$$3c) \quad \delta = \sqrt{\frac{2}{\omega \mu_0}} = \sqrt{\frac{1}{\pi f \mu_0}} = 0.325 \text{ mm} @ 60\text{kHz}$$

\therefore assuming 500 turns of $0.325 \text{ mm} \phi$ wire around 5cm diameter,
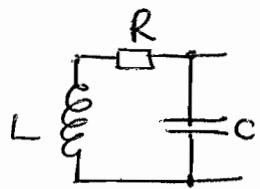
$$\text{the resistance } R, = \frac{\rho L}{A} = \frac{N \pi D}{\sigma \frac{\pi d^2}{4}} = \frac{4ND}{\sigma d^2}$$



$$\therefore R = \frac{4 \cdot 500 \cdot 0.05}{4 \times 10^7 \cdot (0.325 \times 10^{-3})^2} = 23.7 \Omega.$$

If the coil is resonant at 60kHz with $C = 660 \text{ pF}$, then

$$60 \times 10^3 = \frac{1}{2\pi \sqrt{LC}} \quad \text{and } L = 10.6 \text{ mH}$$

and at 60kHz, $\omega L = 4.0 \text{ k}\Omega$ hence the Q-factor is given by :-

$$Q = \frac{4000}{23.7} = \underline{169}$$

[assuming the capacitor is ideal - lossless]

[25%]


$$?d) \quad B = \mu_0 H \quad \therefore \quad B = 4\pi \times 10^{-7} \times 1.2 \times 10^{-5} = 16 \text{ pT}$$

$$V_{induced} = N B A \frac{2\pi f}{2\pi} \quad \leftarrow (\text{from } V = N \frac{d\phi}{dt})$$

$$A = \pi r^2 = \frac{\pi}{4} 0.05^2 = 1.96 \times 10^{-3} \text{ m}^2 \quad \phi = BA$$

$$\therefore V_i = 500 \cdot 16 \times 10^{-12} \cdot 1.96 \times 10^{-3} \cdot 2\pi \cdot 60 \times 10^3 = 5.91 \mu\text{V} \quad [\text{not resonant}]$$
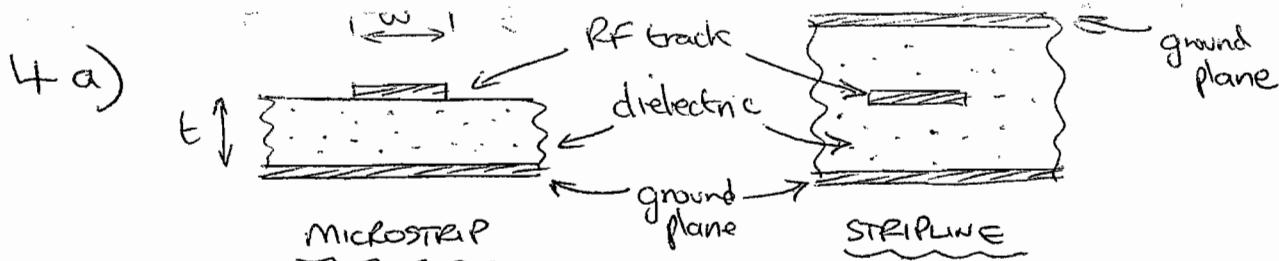
$$\therefore V_i' = 169 \times 5.91 = 1.0mV \quad [\text{resonant}] \quad [20\%]$$



- easy to fabricate
- easy for surface mount components /connections
- higher radiation losses
- more complex fabrication
- vias required for connections
- low loss

[10%]

b) Taking $\epsilon_r = 3$ $t = 0.25 \text{ mm}$ $Z_0 = 50 \Omega$

$$C \text{ per unit length} = \frac{A \epsilon_0 \epsilon_r}{t} = \frac{(w+2t) \epsilon_0 \epsilon_r}{t}, \text{ assuming}$$

The effective track width is to be $w + 2t$ each side of w .

$$\text{Speed of light in polymer, } V = \frac{1}{\sqrt{\epsilon_0 \epsilon_r}} = \frac{1}{\sqrt{LC}} = \sqrt{3 \times 10^8 \text{ m/s}}$$

$$\text{Characteristic impedance, } Z_0 = \sqrt{\frac{L}{C}} = \frac{1}{\sqrt{C}}$$

$$\therefore Z_0 = \frac{t}{(w+2t) \epsilon_0 \epsilon_r V} = 50 \Omega = \frac{0.25 \times 10^{-3}}{\sqrt{3 \times 10^8} \cdot (w + 0.5 \times 10^{-3}) \cdot 8.854 \times 10^{-12} \cdot 3}$$

$$\therefore w = 0.587 \text{ mm}$$

$$Z_0 \text{ range} = \sqrt{\frac{3}{3 \pm 0.5}} \cdot 50 \Omega = \underbrace{46}_{\text{ie. } \pm 8\% \text{ off}} \rightarrow 55 \Omega \quad \begin{matrix} 9\% \text{ pp} \\ \text{ie. } \pm 8\% \text{ off} \end{matrix}$$

[40%]

c) Max. speed of light = $\frac{3 \times 10^8}{\sqrt{2.5}} : \text{Min.} = \frac{3 \times 10^8}{\sqrt{3.5}}$
 $= 1.90 \times 10^8 \text{ m/s} : = 1.60 \times 10^8 \text{ m/s}$

$$\therefore \text{wavelength} @ 6 \text{ GHz} = 31.7 \text{ mm} : = 26.7 \text{ mm}$$

4c) contd. relative

$$\begin{aligned}
 \text{Hence phase shift over } 50\text{ mm} &= 360^\circ \times \left(\overbrace{\frac{50}{26.7} - \frac{50}{31.7}}^{\Delta N \lambda \text{ in } 50\text{ mm}} \right) \\
 &= 360^\circ \times 0.295 \\
 &= \underline{106^\circ} \quad [30\%]
 \end{aligned}$$

- d) To resonate, the patches should be $\lambda/2$ across. With $\epsilon_r = 3$
 $v = \sqrt{\epsilon_r} \times 3 \times 10^8 \text{ m/s}$ and $\lambda = 28.9 \text{ mm}$ @ 6.5 GHz
Hence the patches will be 14.4 mm square . (v.small)

To control polarisation, the 2 edges of the square can be driven with different phases : $\pm 90^\circ$ gives right or left hand circular polarisation

