

1(b)

(i) LS-TTL drives CMOS

$$N_{MH} = V_{OHls-ttl} - V_{IHcmos} = 2.5 - 3.5 = -1.0 \text{ V}$$

$$N_{ML} = V_{ILcmos} - V_{OLls-ttl} = 1.0 - 0.4 = 0.6 \text{ V}$$

(ii) CMOS drives LS-TTL

$$N_{MH} = V_{OHcmos} - V_{IHls-ttl} = 4.9 - 2.0 = 2.9 \text{ V}$$

$$N_{ML} = V_{ILls-ttl} - V_{OLcmos} = 0.7 - 0.1 = 0.6 \text{ V}$$

(c) CMOS → BiCMOS would give the following margins:

$$N_{MH} = V_{OHcmos} - V_{IHBiCMOS} = 4.9 - 3.5 = 2.9 \text{ V}$$

$$N_{ML} = V_{ILBiCMOS} - V_{OLcmos} = 1.0 - 0.1 = 0.6 \text{ V}$$

BiCMOS → CMOS

$$N_{MH} = V_{OHbicos} - V_{IHcmos} = 4.3 - 3.5 = 0.8 \text{ V}$$

$$N_{ML} = V_{ILcmos} - V_{OLbicos} = 1.0 - 0.7 = 0.3 \text{ V}$$

3.

$$\text{If } G_1 = 1, O_1 = \bar{X} + \bar{Y}$$

$$\left\{ \begin{array}{l} \text{If } G_1 = 0 \text{ and } G_2 = 1 \\ O_1 = \bar{X} + \bar{Y} \\ O_2 = XY \end{array} \right.$$

$$\text{If } G_1 = 0 \text{ and } G_2 = 0$$

$$\left\{ \begin{array}{l} T = \bar{Q}XY \\ Q^+ = QT + \bar{Q}T = Q(Q + \bar{X}\bar{Y}) + \bar{Q}XY = Q + \bar{Q}XY = Q + XY \\ O_1 = \bar{X} + \bar{Y} \\ O_2 = Q \end{array} \right.$$

4

$$J = AB$$

$$K = \bar{A}\bar{B}$$

$$Q^+ = \bar{Q}J + Q\bar{K} = \bar{Q}AB + Q(\bar{A} + \bar{B})$$

$$Z_i = A \oplus B \oplus Q$$