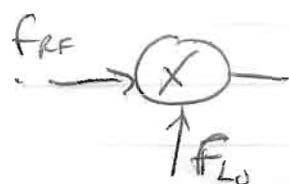


Q1 a) In the superhet there is no way of discriminating between one +ve freq, hence there are multiple combinations of freqs that mix to the one IF



$$\begin{aligned} f_{RF} \\ f_{RF} - f_{LO} \\ f_{RF} + f_{LO} \end{aligned}$$


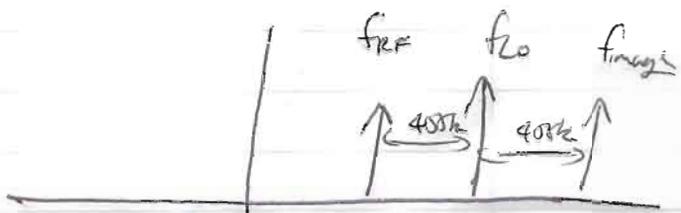


Image rejection or any technique that prevents these unwanted freqs from getting into the IF filter.

$$\text{eg } f_{LO} = 1.5 \text{ MHz } f_{IF} = 458 \text{ kHz } f_{RF} = f_{LO} - 458 \text{ kHz} \\ = 1.045 \text{ MHz} \\ \text{Assume we take } f_{IF} = f_{LO} - f_{RF} \quad f_{image} = f_{LO} + 458 \text{ kHz} \\ = 1.955 \text{ MHz}$$

b) Superhet Am

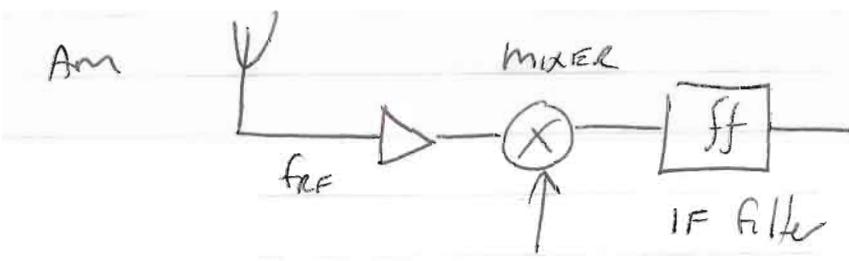



Tuning is formed by the combination of the LO frequency + the mixer. Mixer forms the product of the RF input freq

$$\text{ie } \frac{A}{B} \underset{\text{A}}{\cancel{(X)}} - A.B. = A \sin(\omega_1 t) * B \sin(\omega_2 t) \\ = \frac{1}{2} AB (\sin(\omega_1 + \omega_2)t + \sin(\omega_1 - \omega_2)t)$$

we take $\omega_1 = \omega_2 = \omega_R = \text{RF} \Rightarrow$ tune by filtering out the $\omega_1 - \omega_2$ freq with the IF filter. IF filter is very narrow band to allow only the desired RF band to pass thru.

458 kHz

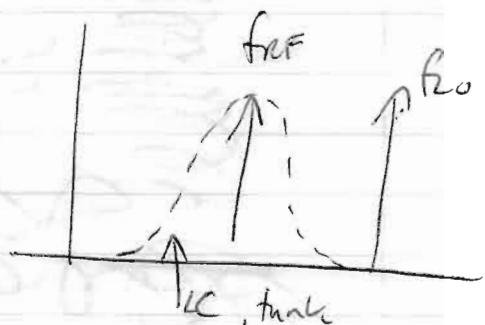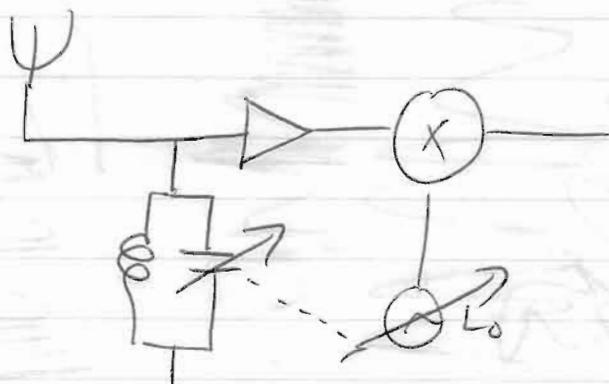
Through Tuning can be modified to include image rejection by adding a tunable LC tank at the input to the mixer.




LC tank pre-filter the RF + removes image freq.
It requires a good Q tank filter and must track with the tuning of the LO. (tracking)

Tracking depends on LC Q.

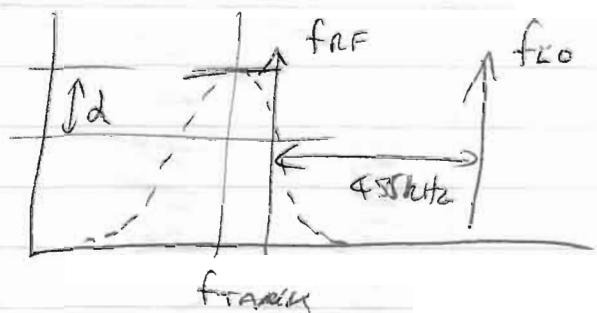
If tracking is not set to 455kHz then there will be a loss of signal (α).





c) FM demodulator can be made from PLL

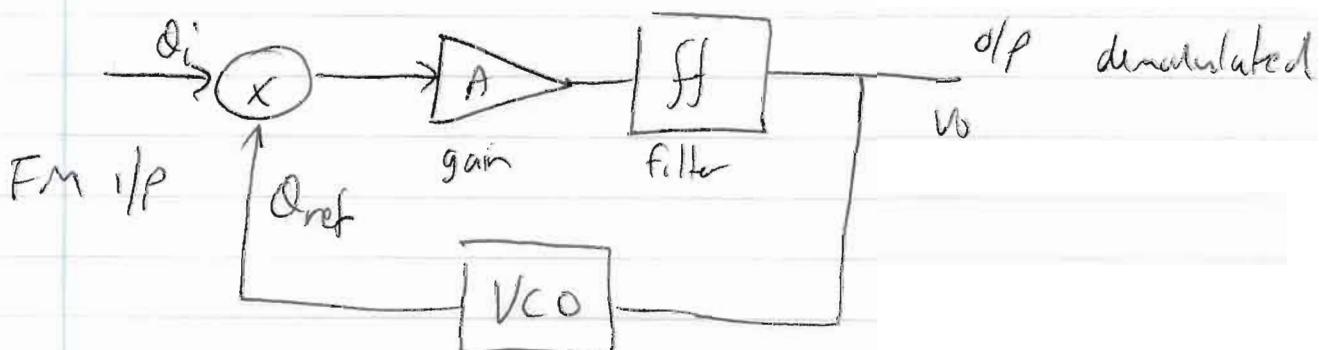

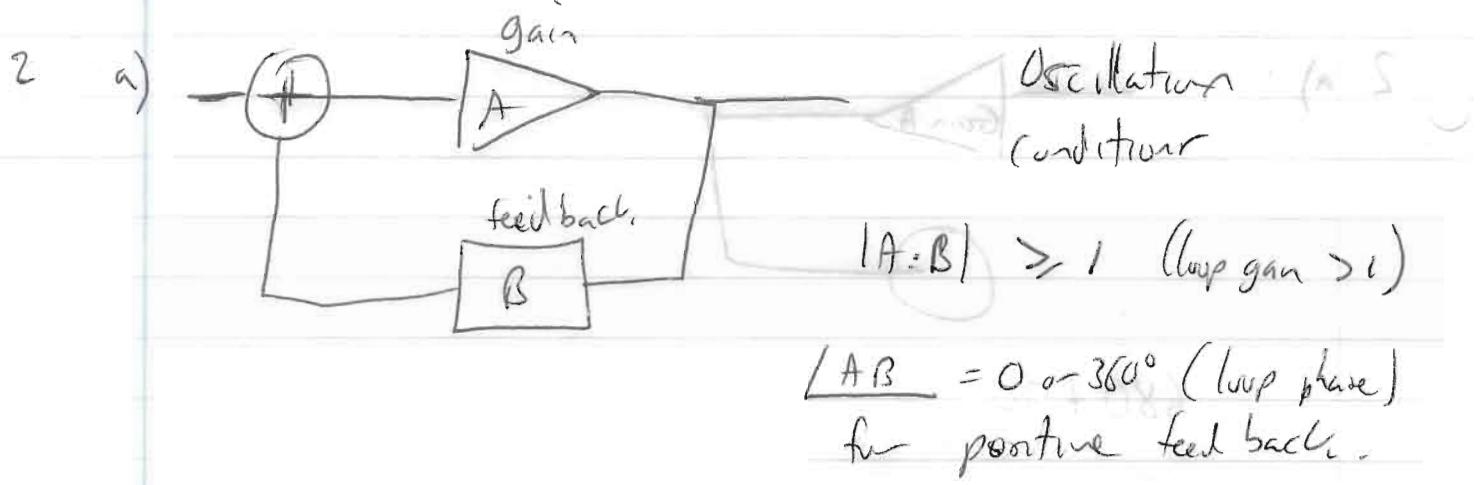PLL sets VCO so that $\phi_i - \phi_{ref} = 0$. Hence the control voltage to the VCO is proportional to the freq of the input signal.
If the PLL response time is fast enough, then Vb will track the freq difference & give a demodulated output.



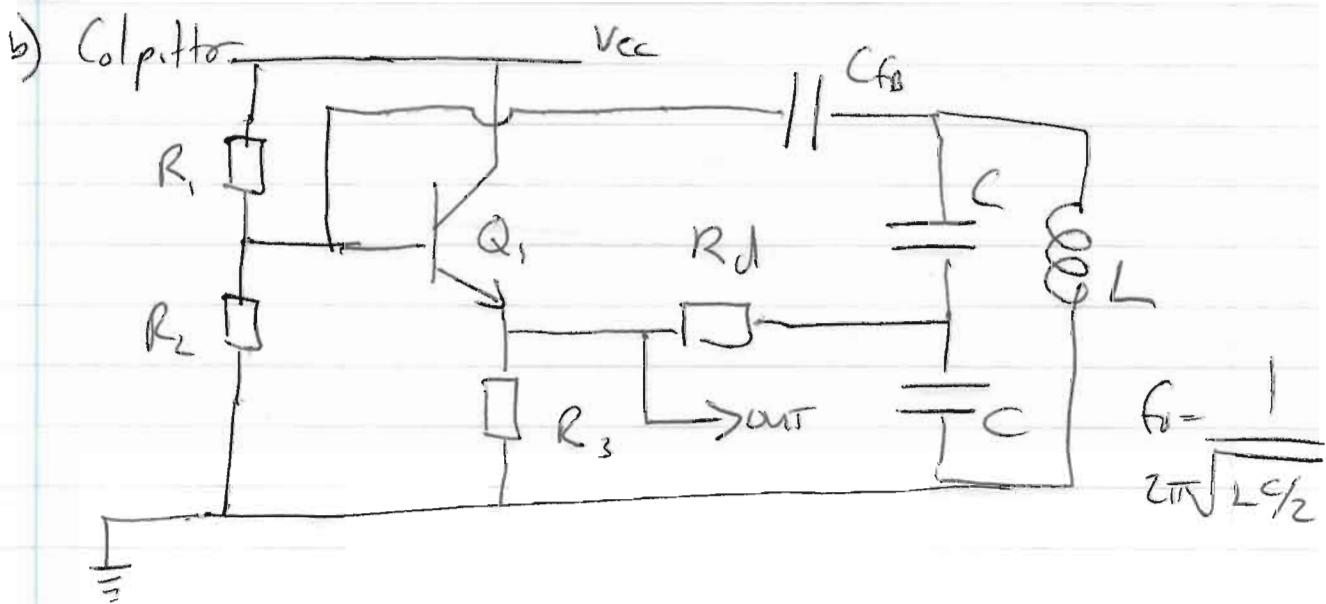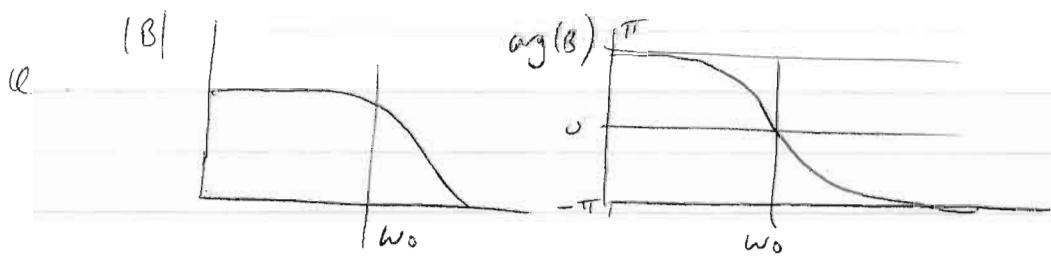Oscillator is designed by making B a freq dependent network which only satisfies the above conditions at a single freq -



$R_1 + R_2$ - base bias R_b
 R_3 - emitter load

C_{fb} - feed back decoupling capacitor

LC - resonant tank ckt (gain of 2)
 R_d - tank drive resistance

LC s provide resonant feedback ckt. Split C gives effective gain of $\times 2$. Q or emitter follower amplifier.

$$b) \text{ 3 } \text{dBm} = 10 \log_{10} \left(\frac{P}{P_{\text{ref}}} \right) \Rightarrow P = 2 \text{mW}$$

$$= V^2/R$$

with 400Ω load $\Rightarrow V = 0.8 \text{V}_{\text{rms}}$

$$V_{p-p} = 2.25V \Rightarrow 5V \text{ Vcc or dc.}$$

$$f_{osc} = 1.5 \text{MHz} = \frac{1}{2\pi\sqrt{LC/2}} \quad f_f = 200 \text{MHz} \gg f_{osc} \checkmark$$

$$L = 15 \mu\text{H} \Rightarrow C = \frac{1}{\left(\frac{1.5 \times 10^{-6}}{2\pi} \times 2\pi \right)^2 \times 15 \times 10^{-6}} \Rightarrow \frac{C}{2} = 7.5 \times 10^{-10} \text{ F}$$

Converting to pF, $C = 1.5 \text{nF}$

b) bias emitter at $V_{ce}/2 = 2.5 \text{V}$ set base at 3.25V

$$\Rightarrow \frac{R_2 \times 5}{R_1 + R_2} = 3.25 \text{V} \quad (\text{choose } R_2 = 100 \text{k}\Omega)$$


$$\Rightarrow R_1 = 54 \text{k}\Omega \quad (56 \text{k}\Omega)$$

n/b or could use $R_1/R_2 \approx h_{fe}(R_3/R_L)$ to give similar value
 $\text{NOT} \Rightarrow R_3 \approx 1.5 \times R_{\text{load}} = 1.5 \times 400 = 600 \Omega \quad (580 \Omega)$


$$R_d \approx (R_1 \parallel R_2 \parallel h_{fe} R_3 \parallel h_{fe} R_{\text{load}})/5 = 4.1 \times 10^3 \approx 4.1 \text{k}\Omega$$

$$C_{fb} = 10 \text{nF} \quad (\text{large value or low impedance at 105MHz})$$

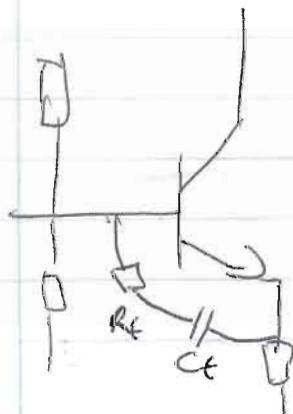c) If o/p has harmonic distortion, then the emitter follows with a small amount of negative feedback to help remove the unwanted harmonics in the o/p.



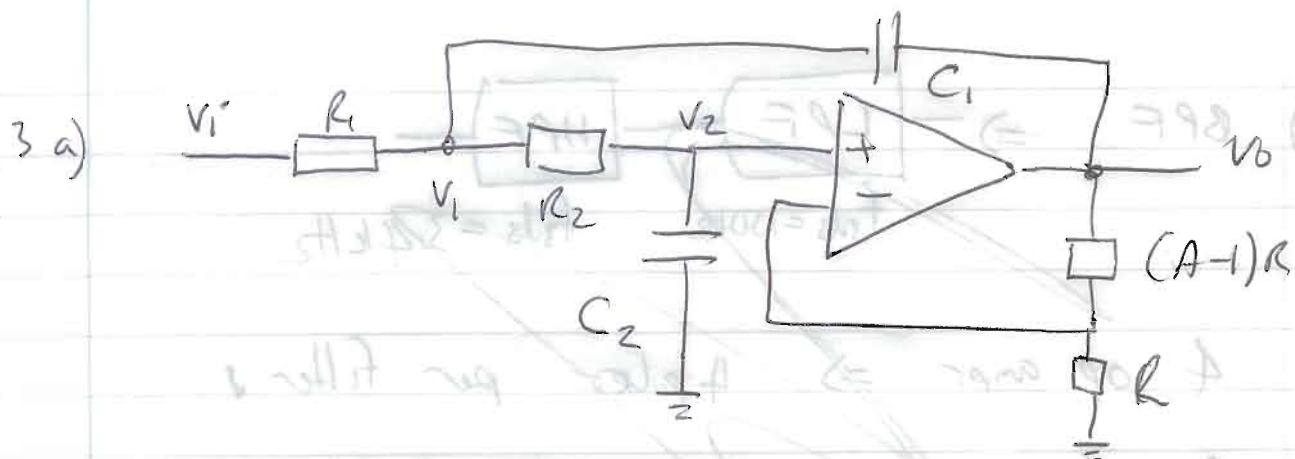$R_f + C_f$ form a simple f/b network. The exact values of $R_f + C_f$ can't be calculated based on the value of R_d & the 3rd harmonic freq, but a simpler method is to try different values to see what improves the o/p quality.



Assume $R_1 = R_2 + C_1 = C_2 \Rightarrow$ op-amp is ideal.

$$\Rightarrow V_o = \cancel{A} V_i \quad \text{Pdivider} \Rightarrow V_2 = \frac{V_o C_1}{R_2 + j\omega C_1} = \frac{V_i}{1 + j\omega CR} \quad (2)$$

Summing currents at the V_1 node we have:

$$\frac{V_i - V_1}{R} = \frac{V_1 - V_o}{j\omega C} + \frac{V_1 - V_2}{R} \Rightarrow V_i = V_1(2 + j\omega CR) - V_o j\omega CR - V_2$$

Sub for $V_1 \propto V_2$ from (1) & (2)

$$\Rightarrow V_i = \left(\frac{1 + j\omega CR}{A} \right) V_o (2 + j\omega CR) - V_o j\omega CR - V_o / A$$


$$= \frac{V_o}{A} \left[1 - (\omega CR)^2 + j\omega CR(3 - A) \right]$$

$$\Rightarrow \left| \frac{V_o}{V_i} \right| = A \left[(1 - (\omega CR)^2)^2 + (\omega CR)^2 (3 - A)^2 \right]^{-1/2}$$


$$= A \left[1 + (\omega CR)^2 [(3 - A)^2 - 2] + (\omega CR)^4 \right]^{-1/2}$$

$$= A \left[1 + \left(\frac{\omega}{\omega_n} \right)^2 \beta + \left(\frac{\omega}{\omega_n} \right)^4 \right]^{-1/2}$$

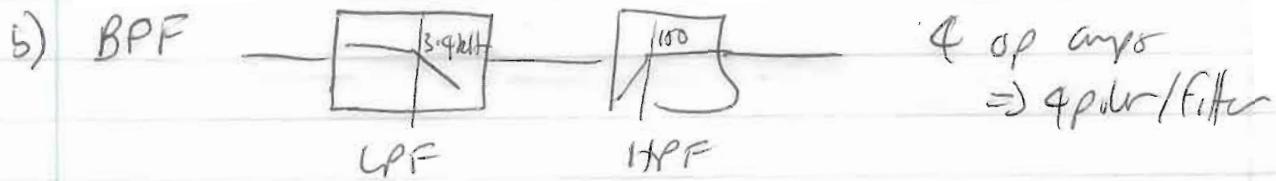where $\omega_n = \frac{1}{RC}$ & $\beta = (3 - A)^2 - 2$



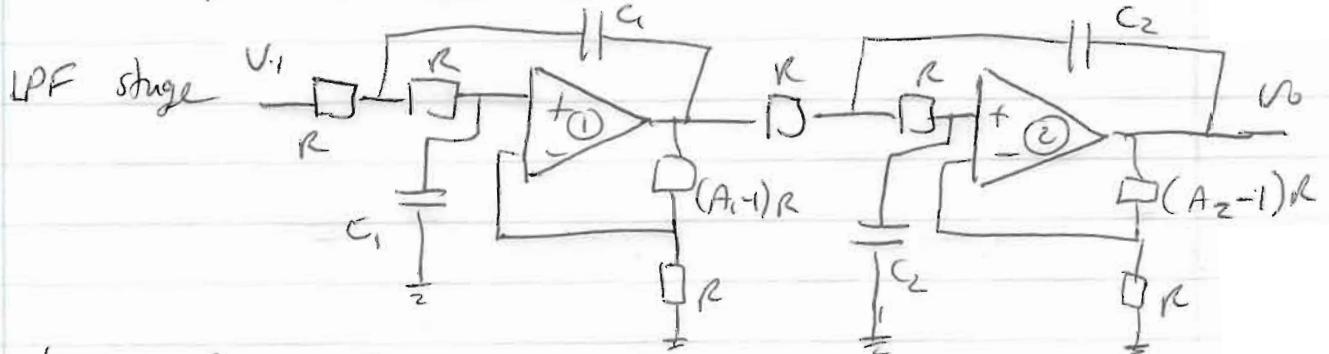No ripples in passband \Rightarrow Bessel filter q polar.



choose $R = 10 \text{ k}\Omega$


$$\textcircled{1} A_1 = 1.084 \Rightarrow (A_1-1)R = 840\Omega \quad (820\Omega)$$

$$f_n = 1.432 \quad f_c = \frac{1}{2\pi R C_1 f_n} \quad f_c = 3.4 \text{ kHz} \Rightarrow C_1 = 3.27 \times 10^{-9} \text{ F} \quad (3.27 \text{ nF})$$

$$\textcircled{2} A_2 = 1.759 \Rightarrow (A_2-1)R = 76 \times 10^3 \Omega \quad (8.2 \text{ k}\Omega)$$

$$f_n = 1.606 \Rightarrow f_n' = \frac{1}{f_n} \quad C_2 = 2.91 \times 10^{-9} \text{ F} \quad (2.7 \text{ nF})$$

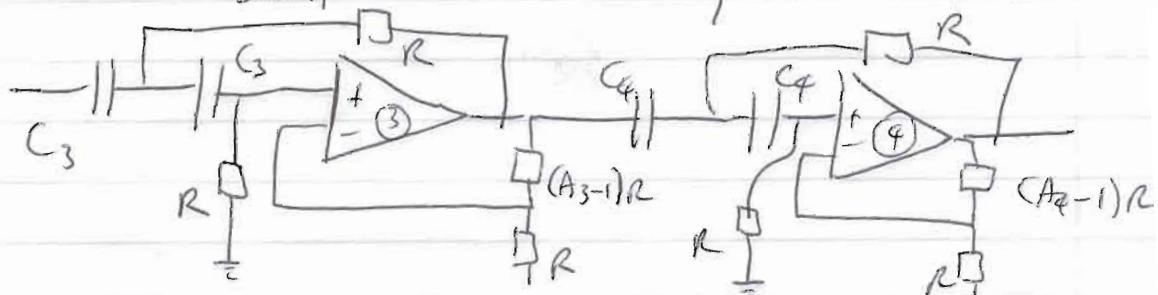For HPF swap $R_L + C_2$, $f_n' = 1/f_n$ $f_c = 150 \text{ Hz}$




$$\textcircled{3} A_3 = 1.084 \Rightarrow (A_3-1)R = 840\Omega \quad (820\Omega)$$

$$f_n' = \frac{1}{1.432} = 0.698 \Rightarrow C_3 = 1.5 \times 10^{-7} \text{ F} \quad (150 \text{ nF})$$

$$A_4 = 1.759 \quad (A_4-1)R = 7.6 \text{ k}\Omega \quad (8.2 \text{ k}\Omega)$$

$$f_n' = \frac{1}{1.606} = 0.622 \quad C_4 = 1.7 \times 10^{-7} \text{ F} \quad (180 \text{ nF})$$

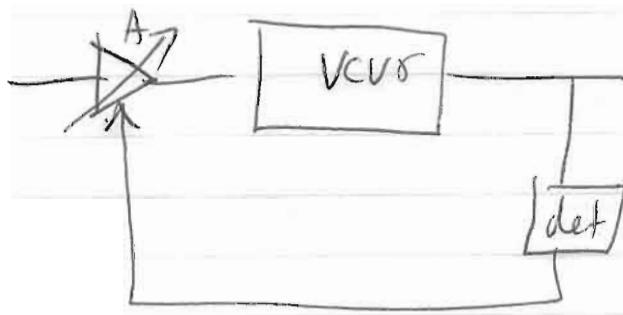c) The poor band could be flattened further by adding one out of AGC system to the filter. The simplest method would be to add a variable gain element before the VCO & then control the gain via a MOSFET or a varactor diode.





The detection circuit must be very sensitive (possibly a differential system) to control the gain very accurately.

It is also possible to tweak the gains of the VCO itself by a small amount.


Q + a) Quarter-wave match

$$Z' = \sqrt{Z_0 Z_1}$$

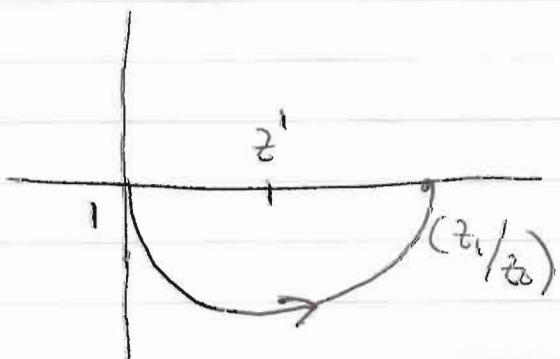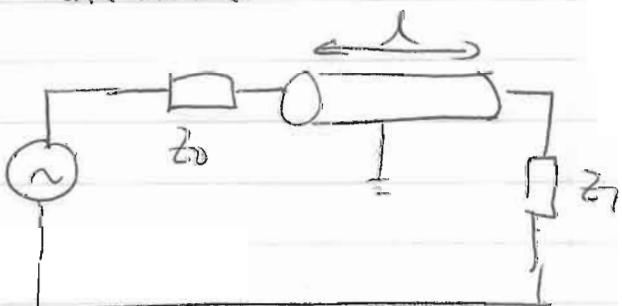

Extrinsic line length plots a circle on the Smith chart from Z_0 (1) to Z_1/Z_0 . This will be $\lambda/4$ of extrinsic line ~~$\lambda/2$~~ with char impedance of Z' .

i) Series inductor/capacitor

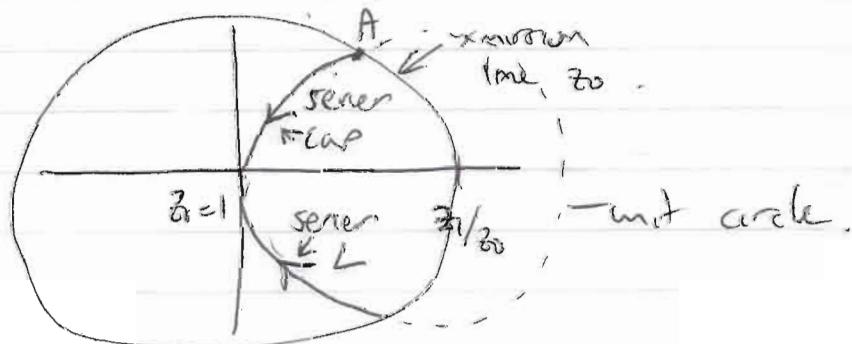

Point A is the intersection of the z_0 known line with the unit circle. This defines a series ~~inductor~~^{Cap} or capacitor to get to the unity point. Lower intersection point defines a series inductor. Clockwise given both of known line required.

b) Capacitance $C = \frac{A \epsilon_0}{d} = \frac{(w+2d)\epsilon_0 \epsilon_r}{d}$


The $2d$ component allows for the effect of fringing fields.

$$Z_0 = \sqrt{\frac{L}{C}} \quad r = \frac{1}{\sqrt{LC}} \quad C_0 = \frac{1}{\sqrt{\mu_0 \epsilon_0}}$$

$$\Rightarrow \text{velocity } v = \frac{1}{\sqrt{\epsilon_0 \epsilon_r \mu_0}} = \frac{C_0}{\sqrt{\epsilon_r}} \quad (\mu_r = 1)$$

$$Z_0 = \sqrt{\frac{L}{C}} = \frac{1}{rC} = \frac{d}{\epsilon_0 \epsilon_r (w+2d)} \propto \frac{\sqrt{\epsilon_r}}{C_0}$$
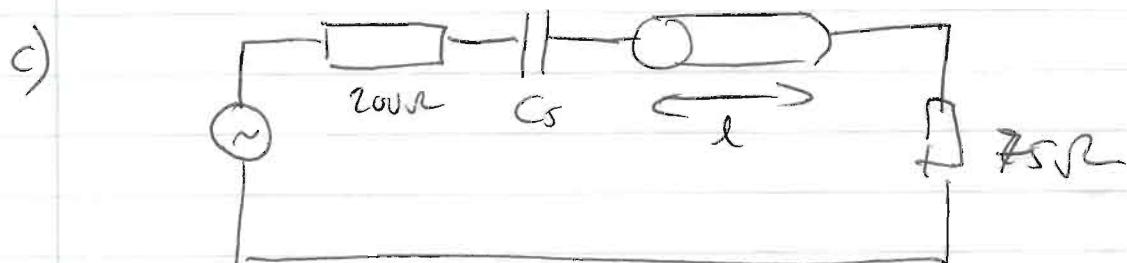
$$= \frac{d}{(w+2d)C_0 \epsilon_0 \sqrt{\epsilon_r}}$$



Choose $Z_0 = 75\Omega \Rightarrow$ ~~approximate~~
~~maximum~~

$$75 \Omega = \frac{d}{(2d + 0.5 \times 10^{-3}) 3 \times 10^8 \times 8.85 \times 10^{-12} \times \sqrt{3.7}} \quad \text{Thickness of PCB} \\ \Rightarrow d = 0.182 \text{ mm}$$

Choose $Z_0 = 200 \Omega$ * $\Rightarrow Z_L = 75 \Omega$
 *See Smith chart. normalized = 0.375

For series cap $X_S = 1.58 \times 200 = 316 = \frac{1}{\omega C_S}$
 $\Rightarrow C_S = \frac{1}{\omega X_S} = \frac{1}{2\pi f \times 1.58 \times 200} = 0.28 \mu F$

length of meander $l_C = 0.178 \lambda$ $\lambda = \frac{V}{f} = \frac{C_0}{f \sqrt{\epsilon_r}} = \frac{3 \times 10^8}{118 \times 10^9 \sqrt{3.7}}$
~~= 118.6 mm~~
 $l_C = 0.178 \lambda = 15.4 \text{ mm}$ $= 86.6 \text{ mm}$

length is ok, but series cap is very small & difficult to fabricate

c) DC Power \Rightarrow need series inductance (point B)

$$\Rightarrow X_L = 1.58 \times 200 = 316 \Omega = \omega L_S$$

$$\Rightarrow L_S = \frac{316}{\omega} = \frac{316}{2\pi \times 1.58 \times 10^9} = 28 \text{ nH.}$$

$$l_C = 0.315 \lambda = 0.315 \times 86.6 = \cancel{27.3} \text{ mm}$$

* NB also could choose $Z_0 = 75 \Omega \Rightarrow$ normalized to give 2.67. This gives a similar plot on the Smith chart, but be careful of the direction to source / generator

From chart get cap path $1.05j$
 $\Rightarrow C = 1.12 \mu F$

$$\text{length} = 0.913 \lambda \Rightarrow l = 35.8 \text{ mm}$$

The Complete Smith Chart

Black Magic Design

Series Cap ≈ 2.2
 $= -1.58j$

$L_C = 0.178\lambda$

$L_L = 0.345\lambda$

Series inductor $= j1.58$

