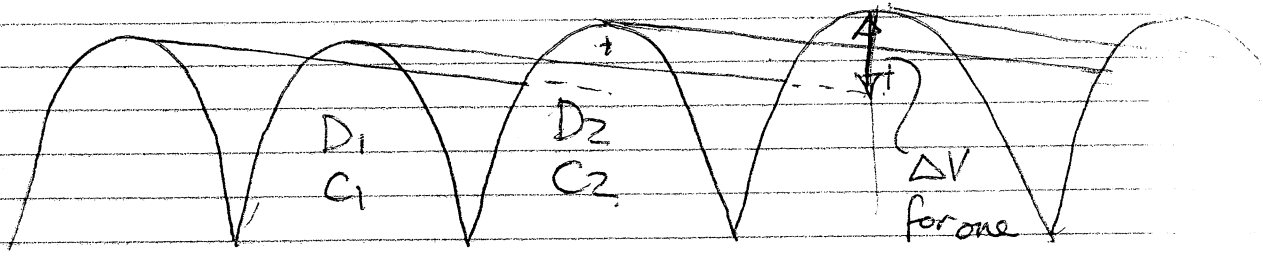


1 a) Charging. D_1, C_1




$$I = C \frac{dV}{dt} \quad \Delta V = \frac{I}{fC} \text{ for 1 half}$$

Symmetrical but displaced ^{total}

In $\frac{1}{2}$ cycle drops $2 \times \frac{\Delta V}{2} = \Delta V$

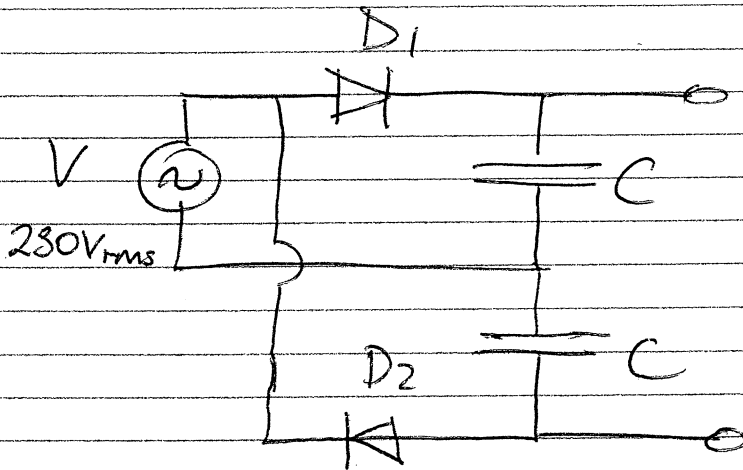So $\Delta V = \frac{I}{fC}$ is the ripple ²




Values: $\frac{650 \times 0.05 \times 50}{6} = \frac{1}{C} \quad C = 3.7 \text{ mF}$

1b

3 phase 1400A \Rightarrow 2000A at low freq.
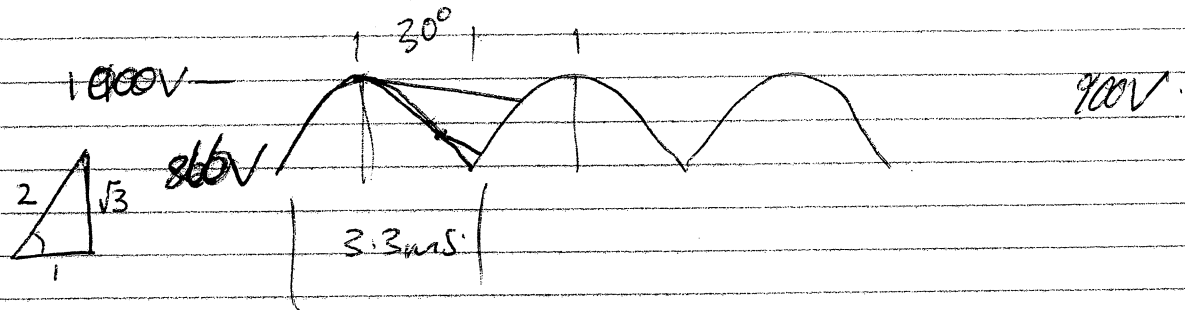
$$900\mu\text{F} \times 6 \times 3 = 16.2\text{ mF}$$



$$I = \frac{CdV}{dt} \quad dV = \frac{2000 \times 3.3\text{m}}{16.2\text{mF}} = 407.$$

$$\frac{dV}{dt} = \frac{2000}{16.2\text{m}} = 123\text{ V/ms} \approx$$

$$v = V \sin 2\pi ft = 1000 \sin 2\pi \cdot 50 t.$$

$$\frac{dV}{dt} = 1000 \cdot 100\pi \cos 100\pi t = -123,000.$$

$$\cos \theta = \frac{123}{100\pi} = 0.39.$$


$$\theta = \frac{7100}{67}, 113 \Rightarrow \frac{920}{2}.$$

$$\frac{7}{30} \times \frac{3.33\text{m}}{2}$$

$$\frac{dV}{dt} = \frac{2000}{16.2\text{m}} \times \frac{7}{30} \times \frac{3.33\text{m}}{2} = 48\text{ V} \approx$$

$$920 - 48 = 872\text{ V}.$$

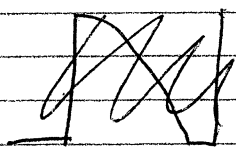
Estimate conduction angle $\approx 60^\circ - 113^\circ$
 ie $\approx 7^\circ$ missing.



Sketch waveform.

$$2000\text{A} + \frac{CdV}{dt}$$


$$I \approx 2000$$

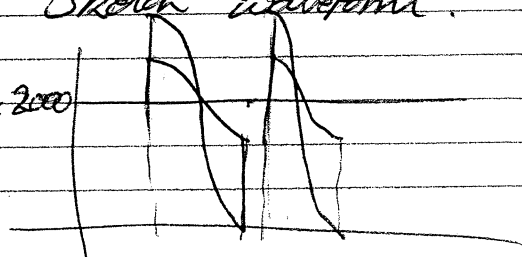

nice

ab ac bc ba ca cb

↑ ↑ ↓ ↓

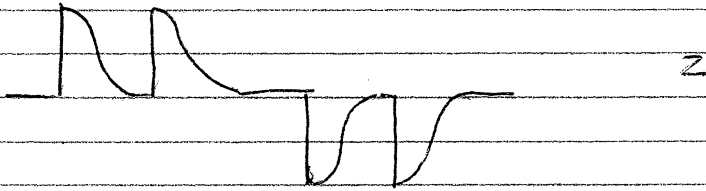

Detailed calculations are needed as the ripple is small, but so is that of unsmoothed three-phase (rectified).

2(a) ^{Easy} (Capable of 160A, & 10kHz) easy to drive and can be used in a rect 3 ϕ dc system.



- 1) Fast switching
- 2) Diode recovery (check)
- 3) Switching losses.

5


00 01 11 10

Equal periods of 01 & 10 give AC.

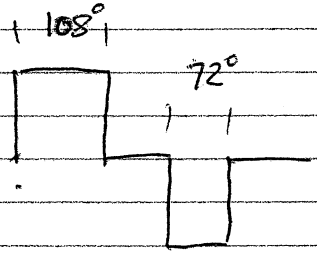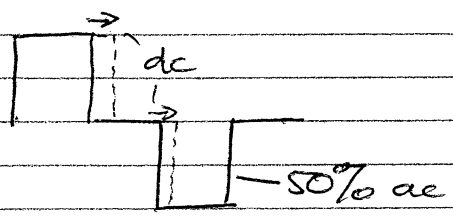Unequal periods give dc, magnitudes set by 00, 10



4

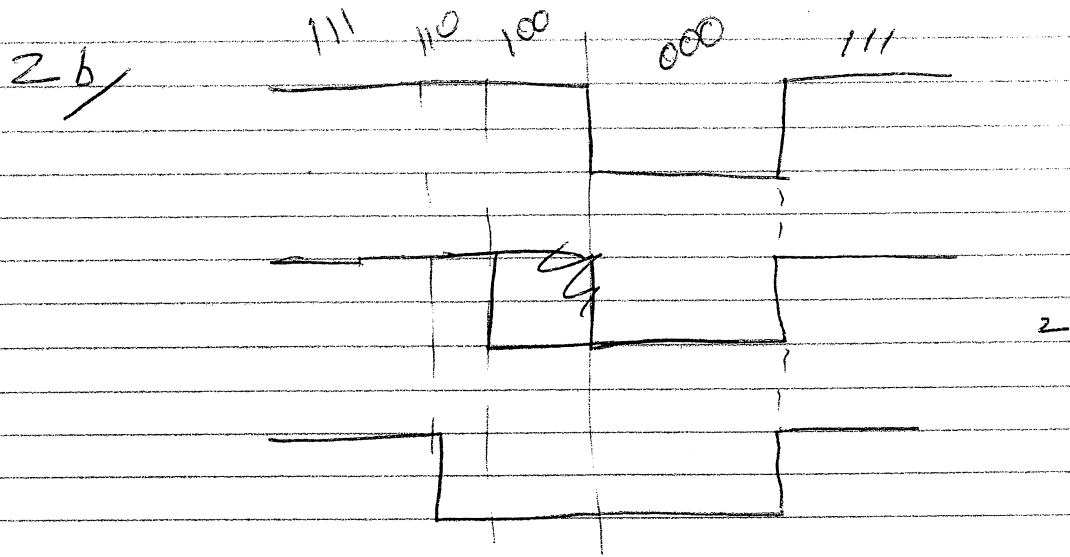


But this lacks the effective doubling of the switching frequency.

Also there are wasted switching instants such as 000 to 111 causing more losses.

Splitting the 000 & 111 states evenly within the cycle of T_s as shown in the Fig 2c reduces

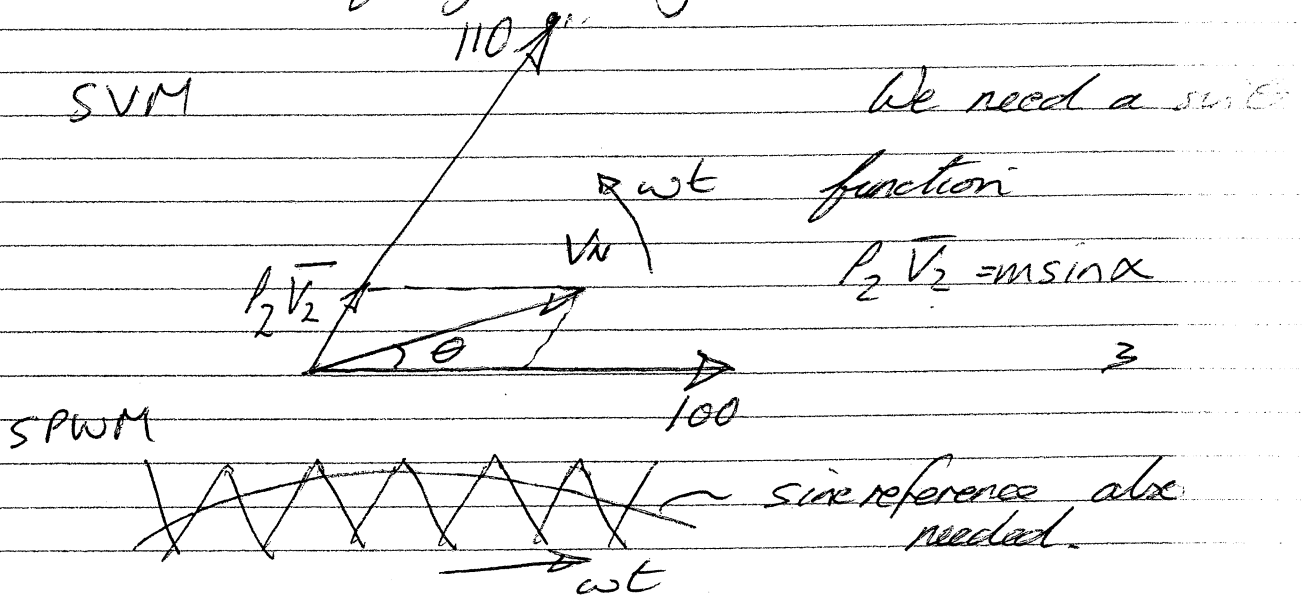the harmonic content of the output by means of symmetry.




3 a) Mosfets can be integrated easily by "parallelising" actually making wide devices which can carry large currents. However the need to be a channel and that requires a bootstrap circuit for the upper device. D_3 & D_4 are the freewheel diodes for T_2 & T_1 respectively. T_4 charges the bootstrap for T_1 .

T_3 sinks overvoltage at the output.

1 for each sentence.

3b/

Step down.

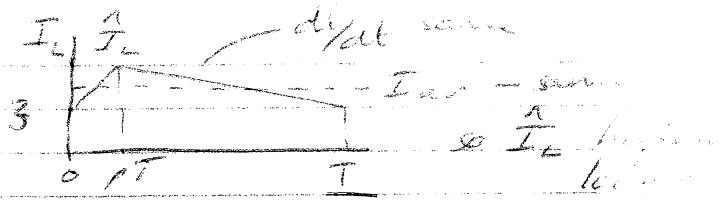

$$\Delta I = \frac{V_0}{L} \left(1 - \frac{12}{32}\right) T \quad \bar{I} = 5A$$

$$\Delta I = 1.5A$$

$$L = \frac{12 \left(1 - \frac{12}{32}\right)}{1.5 \times 4000 \text{ kHz}} = \frac{12 \times 5/8}{7/4 \times 4000} = \frac{5}{0.4} \mu$$

$$\hat{I} = \frac{5 + 1.5}{2} = 5.75 = 12.15 \mu$$

Step up.

$$\Delta I = \frac{1}{L} V_{oc} p T = \frac{V_0 (1-p) p T}{L} \quad \text{--- (2)}$$

try $V_{oc} = 8 \quad V_0 = 12 \quad \frac{8}{(1-p)} = 12 \Rightarrow p = \frac{1}{3}$

$V_{oc} = 10 \quad V_0 = 12 \quad \frac{10}{(1-p)} = 12 \Rightarrow p = \frac{1}{6}$

put into (2) $\frac{2}{9} > \frac{5}{36}$ 8 is lowest V_{oc} goes

$$\Delta I = \frac{12 \cdot \frac{2}{3} \cdot \frac{1}{3} T}{12.15 \mu} = \frac{12 \times 2 \times 0.4}{12.15 \times 9} = 0.533$$

ΔI is smaller (here than for step down)

$$\hat{I} = \frac{\bar{I} + \Delta I}{2}$$

$$(1-p)\bar{I} \times V_0 = P \quad \bar{I} = \frac{60}{12 \times 2/3} = 7.5A$$


$$\hat{I} = \frac{7.5 + 0.533}{2} = \underline{\underline{7.75A}}$$

~~Efficiency of step up is much worse than that of step down. Inductor design should be optimized for efficiency.~~

4 a) Trace control of the basic oven means trying to phase control a transformer with a big magnetising inductance, so the coil is burst mode only - cycles on & cycles off. It lacks precision, as one finds heating some things in a microwave!

The 50 Hz transformer is large with fairly large losses making the oven inefficient.

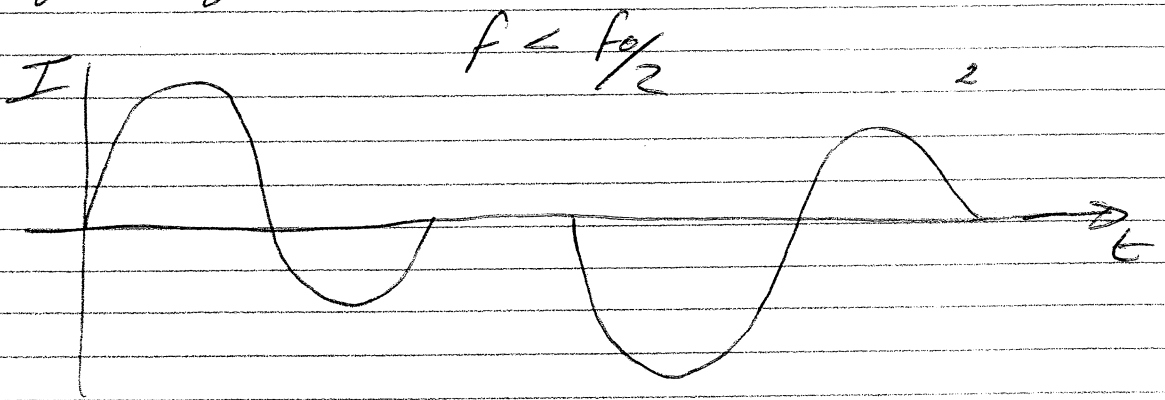At half resonant frequency the inverter completes a full cycle of current then stops and waits.




So $f_0/2 < f < f_0$ merges these waveforms.

$f > f_0$ simple "resonant" but really acts like a filter.

	$f < f_0/2$	$f_0/2 < f < f_0$	$f > f_0$
IGBT	(ZCS)	stress at turn-on	stress at turn-off
DIODE	(ZCS)	stress at recovery	-
	no stress!		

4b

2x0.124
0.45 μF on drawing

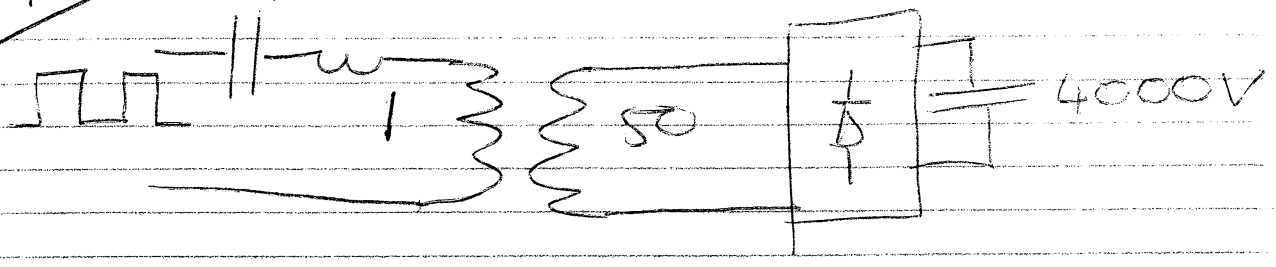

10 kHz

$$Z = \frac{1}{\sqrt{LC}}$$


$$L = \frac{1}{0.45 \times 10^{-6} \times 10^4}$$

$$= \frac{1}{0.45 \times 4 \times \pi^2 \times 10^8}$$

$$= \frac{1}{1.8 \times 10^8}$$

$$= 5.63 \times 10^{-4}$$

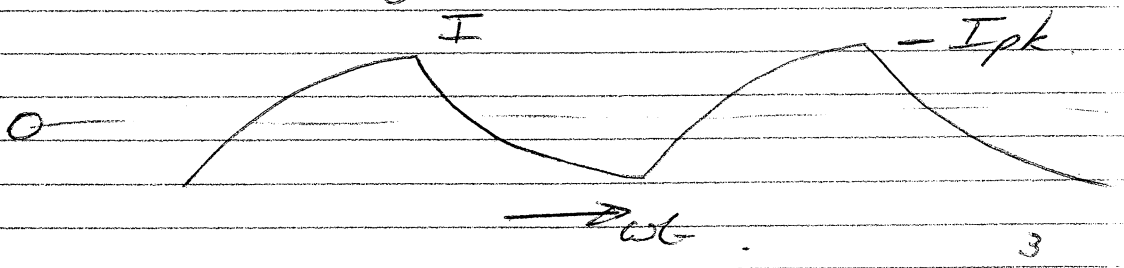20 kHz its very inductive ~ like a filter



$$I_{pk} = \frac{325/2}{162.5} \times \frac{80}{4000/50}$$

$$\frac{4 \times 82.5}{\pi} \text{ over } j\omega L + \frac{1}{j\omega C} = j \frac{1 \times 2\pi \times 20k}{1.8k} + \frac{1}{j \times 2\pi \times 20k \times 0.45 \times 10^{-6}}$$

$$= 70.75 + j17.68$$

$$= 53 j \Omega$$

$$I = \frac{4 \times 82.5}{\pi \times 53} = 1.56 A \times \frac{4}{\pi} = 1.98 A$$

Rectified through the bridge $\frac{2\sqrt{2}}{\pi} \times 1.98 = 1.78 A$

Through the transformer: $1.78 \times \frac{3000}{50} = 107 W$