

3B1 Radio Frequency Electronics 2011 – Numerical Answers

1(b) $R_1 = 920 \Omega$, $R_2 = 120 \Omega$, $R_3 = 9 \Omega$, $R_4 = 75 \Omega$, $C = 10 \text{ nF}$

1(c) $R' = 43 \Omega$, $C' = 1.6 \text{ pF}$, $f_{-3\text{dB}} = 2.31 \text{ GHz / stage}$

2(b) $w = 0.72 \text{ mm}$

2(c) $\lambda/2 = 15.6 \text{ cm}$

2(d) $P_r = 3.9 \text{ nW}$, $V_r = 0.54 \text{ mV}_{\text{rms}}$

2(e) $\eta = 90 \%$

3(b) $C = 23.1 \text{ pF}$, $R_3 = 150 \Omega$, $R_2 = 18 \text{ k}\Omega$, $R_1 = 10 \text{ k}\Omega$, $R_d = 1 \text{ k}\Omega$, $\eta = 6 \%$

3(d) $X_s = 130 \Omega$, $X_p = 173 \Omega$ so, $L = 59 \text{ nH}$ & $C = 2.6 \text{ pF}$ OR $L = 44 \text{ nH}$, $C = 2 \text{ pF}$

4(a) Bessel, $C_1 = 11 \text{ nF}$, $R_1' = 840 \Omega$, $C_2 = 9.9 \text{ nF}$, $R_2' = 7590 \Omega$ with $R = 10 \text{ k}\Omega$

4(b) $T/\text{line length} = 0.233 \text{ m}$ ($= 0.446 \lambda$), $C = 4.8 \text{ pF}$

4(c) $L = CR^2$ hence for $R = 10 \text{ k}\Omega$, $C = 100 \text{ pF}$