Numerical answers 3B2 - 2011

1.
$$I_{D} = 4.5k$$

$$t_{SAT} = 0.13 \frac{C_{L}}{k}$$

$$t_{NON-SAT} = 2.64 \frac{C_{L}}{3k}$$

$$t_{fall} = t_{SAT} + t_{NON-SAT} = \frac{C_{L}}{3k} (0.39 + 2.64)$$

$$t_{fall} = \frac{15 \times 10^{-12}}{3 \times 1.2 \times 10^{-5}} \times 3.03 = 1.26 \text{ } \mu\text{s}$$

2

$$\tau = C \times (3 - V_{SW}) / I_{LEAK} = 2.1 \text{ ms}$$

The proportion of clock cycles lost to refresh and not available for regular read/write is:

$$\frac{1/2 \times 10^{-3}}{10^8}$$
 = $\frac{500}{10^8}$ = 1 cycle in 200,000, a negligible overhead.

The total leakage current for a 1 Mbit memory would be $50 \times 10^{-12} \times 10^6$, or 50 μ A. At a supply voltage of 3 V this corresponds to a power loss of 150 μ W.