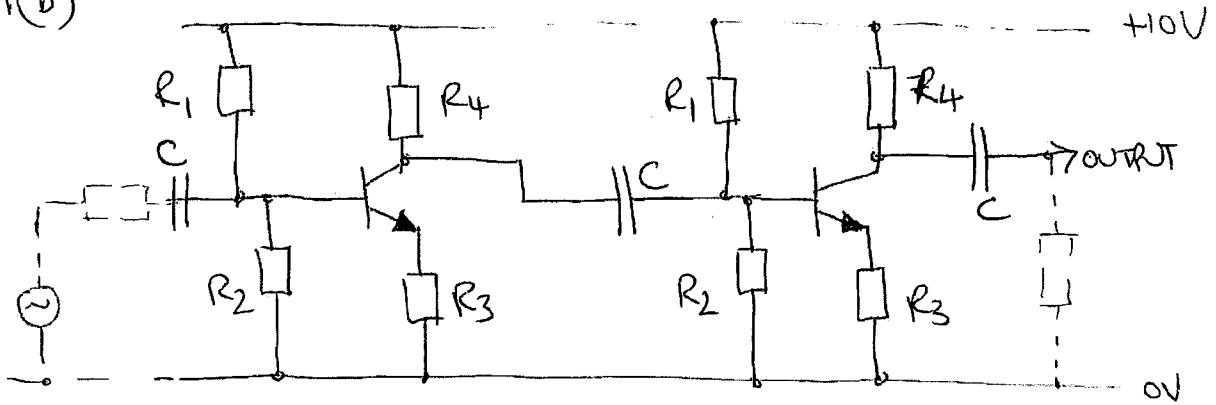


- The incoming radio signal is coupled via the antenna into a pre-tune LC resonant circuit, after which it is amplified by a low noise, RF amplifier.
- The signal (at carrier RF freq.) is mixed with that from a local oscillator to produce the Intermediate frequency (I.f.) The action of the mixer (multiplier) is to produce sum and difference frequencies of the inputs, at the output. Hence, for a given I.f., there are 2 possible RF frequencies i.e.: $f_{LO} \pm f_{I.f.}$. The choice between these is made by the pre-tune section (image rejection).
- The I.f. signal carries the same modulation as the RF carrier (AM or FM), hence demodulation of the I.f. signal, after amplification, yields the required audio signal - which is output via a loudspeaker for example.
- "Tracking" is the term given to the frequency alignment of the L.O. and R.F. tank frequencies - they should differ by a fixed frequency (I.f.) over the tuning range. [30%]

1(b)



- Same values of $R_1 - R_4$ for each circuit with 12 dB net gain per stage for 24 dB total.
- $R_4 = 75 \Omega$ matched to i/p & o/p impedance
- $R_2 = 120 \Omega$ approx. 2x i/p, o/p impedance
- Gain = 24 dB = $\times 16 \times \underbrace{2^2}_{\text{extra coupling losses over 3 stages}} = \times 64 \Rightarrow \sqrt{64}$ per stage = 8
- $R_3 = 75 / 8 = 9.4 \Omega$
- $V_{base} = 6.6 \Omega \times 0.06 A + 0.65 = 1.05 V$ + 10% for base loading
- $r_e = \left(\frac{0.06}{0.025}\right)^{-1} = \left(\frac{I_c}{N_e}\right)^{-1} = 0.42 \Omega$ \therefore say 1.15V for R_1, R_2 potential divider
- $1.15 = 10 \cdot \frac{R_2}{R_1 + R_2} \xrightarrow{120} \therefore R_1 = 920 \Omega$

check i/p impedance: $R_{in} \approx R_1 \parallel R_2 \parallel h_{fe}(R_3 + r_e) = 99 \Omega$


- $\therefore R_3 = 9 \Omega$ just abt 0.1e, close to 75 Ω
- choose C's large eg: 10 nF for RF coupling [30%]

1(c) $f_t = 24 GHz = \frac{1}{2\pi C_{ie} r_e} \xrightarrow{0.42 \Omega} \therefore C_{ie} = 15.8 pF$

Small signal model: $V_e = \frac{9}{9 + 0.42} \cdot V_b = 0.955 V_b$

1(c) contd.

Small signal model for input :-

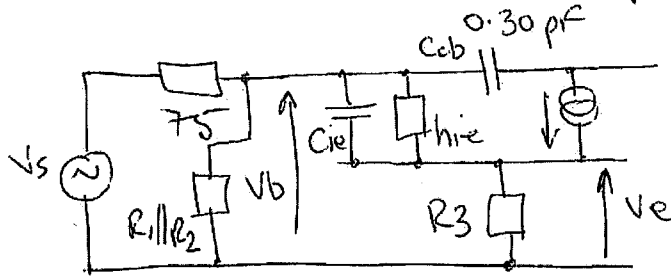


$$\begin{aligned}
 h_{ie} &= r_e \times h_{fe} \\
 &= 0.42 \times 150 \\
 &= 63 \Omega
 \end{aligned}$$

So, referring C_{ie} & h_{ie} to ground and C_{cb} to ground.

$$\begin{aligned}
 &\div 22.4 \quad \times 22.4
 \end{aligned}$$

$$\begin{aligned}
 &\times \left(1 + \frac{8}{2^2}\right) = \times 3 \\
 &(1 + \text{Gain})
 \end{aligned}$$

Revised SSM :-

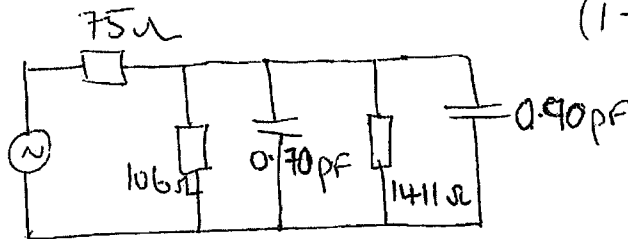

$$\begin{aligned}
 R' &= 75 \parallel 106 \parallel 1411 = 43 \Omega \\
 C' &= 1.6 \text{ pF}
 \end{aligned}$$

$$\text{So, } f_{-3dB} \approx \frac{1}{2\pi \cdot 43 \cdot 1.60 \times 10^{-12}}$$

$$\approx 2.31 \text{ GHz}$$

At 2 stages will roll-off a bit earlier i.e. -6dB @ 2.31 GHz


So, ok at ~ 500 MHz.

$$\text{(Lower end } (2\pi \cdot 10 \text{ nF} \cdot 96 \Omega)^{-1} = 1.66 \times 10^5 \text{ Hz)}$$

[40%]

- 2(a)
- Impedance mismatch will give reflections and distort the signal.
 - Maximum power matching when source & load impedances are the same \therefore better signal/noise

(b)

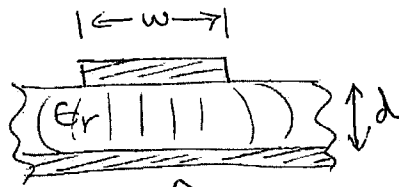

$$C \approx \frac{(w+2d) \epsilon_r \epsilon_0}{d}$$

per unit length

$$Z_0 = \sqrt{\frac{L}{C}}, \quad C = \frac{1}{\sqrt{LC}}$$

$$C = \frac{C_0}{\sqrt{\epsilon_r}}$$

velocity of light in dielectric

$$\therefore \sqrt{L} = \frac{1}{C \sqrt{C}} \quad \therefore Z_0 = \frac{1}{C C} = \frac{\sqrt{\epsilon_r}}{C_0 C}$$

where

$$Z_0 = \frac{\sqrt{\epsilon_r} \cdot d}{C_0 (w+2d) \sqrt{\epsilon_r} \epsilon_0}$$

$$\therefore d = 1.6 \text{ mm}$$

$$\epsilon_r = 4.2$$

$$C_0 = 3 \times 10^8 \text{ m/s}$$

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

$$Z_0 = 75 = \frac{1.6}{3 \times 10^8 \cdot (w+3.2) \cdot \sqrt{4.2} \cdot 8.854 \times 10^{-12}}$$

$$\therefore w = 0.72 \text{ mm}$$


[25%]

- (c) For efficient, resonant antenna the patch length should be $\lambda/2$.
- $$\lambda_0 = \frac{3 \times 10^8}{468 \times 10^6} = 0.641 \text{ m in free space}$$

$$\therefore \lambda_{\text{pds}} = \frac{0.641}{\sqrt{4.2}} = 0.313 \text{ m} \quad \therefore \lambda/2 = 15.6 \text{ cm}$$

For 'see-saw' patch resonance, the feed point has low impedance at the patch centre (low V, high I) and ~~the~~ increases towards the edge. So, feed point position is selected for 75 Ω

[15%]

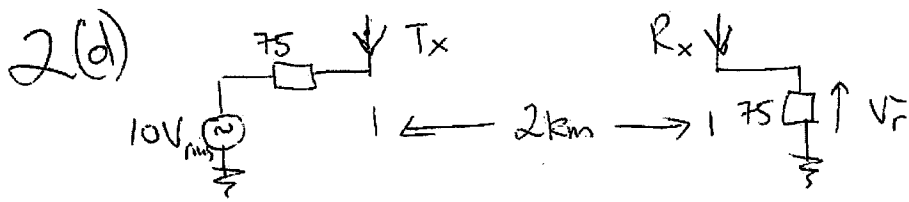

Assume patch antenna gain = 3 (same as dipole, but radiation into 1/2 hemi-sphere only - due to ground plane of patch).

$$G = \frac{4\pi A_e}{\lambda^2} = 3 \quad \text{with } \lambda = 0.641 \text{ m} \quad \therefore A_e = 0.098 \text{ m}^2$$

$$\therefore P_{\text{trans}} = \frac{10^2}{(75 \times 2)} = 0.667 \text{ W}$$

$$\therefore P_{\text{rec}} = \frac{0.667 \cdot 3 \cdot 0.098}{4\pi (2000)^2} = \frac{P_{\text{trans}} \cdot G \cdot A_e}{4\pi R^2} = 3.9 \text{ nW} = \frac{V_r^2}{75}$$

$$\therefore V_r = 0.54 \text{ mV rms}$$

(e) $\eta_{\text{radn.}} = \frac{R_{\text{radn.}}}{R_{\text{radn.}} + R_{\text{ohmic}}}$ ← radiation resistance = 75 Ω say. [25%]

$$= \frac{75}{75 + \left(\frac{\rho L}{A}\right)} \leftarrow 7.8$$

$\eta_{\text{radn.}} \approx 90\%$


$$\rho = 3 \times 10^{-5} \text{ } \Omega \text{m}$$

$$L = 0.156 \text{ m}$$

$$A = 20 \times 10^{-6} \times 30 \times 10^{-3} \text{ m}^2$$

[20%]

3(a)

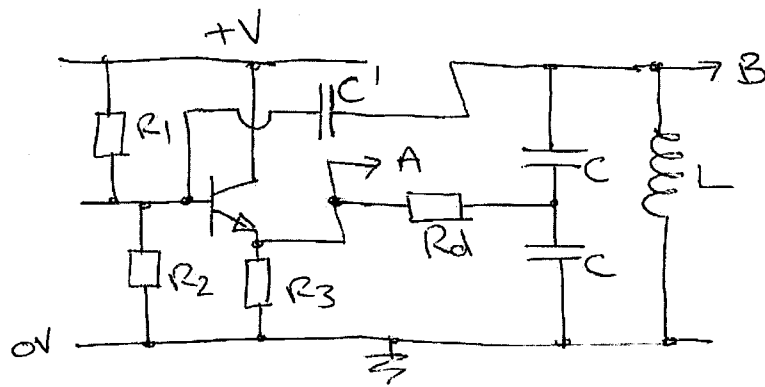

- \$R_1\$ & \$R_2\$ are base bias resistors for transistor buffer/emitter follower: gain \$\approx 1\$
- \$R_3\$ is emitter load resistor
- \$R_d\$ is drive resistor for LC's tank circuit
- LC's provide resonant at $f_{res} = \frac{1}{2\pi\sqrt{LC}}$
- \$C'\$ is feedback d.e. block capacitor
- LC's tank gives \$\times 2\$ voltage gain @ resonance from centre top \$\therefore\$ with \$\times 1\$ buffer gives \$\times 2\$ loop gain - so oscillation start up, limited by transistor voltage
- take o/p from A for low impedance + small load effect
B for better harmonic purity by loads will pull freq./amplitude.

(b) $46\text{d} \times 10^6 = \frac{1}{2\pi\sqrt{10 \times 10^{-9} \cdot C/2}} \therefore C = 23.1 \text{ pF} \quad [25\%]$
for \$L = 10 \text{ nH}\$

75 \$\Omega\$ load - take from point A as low impedance

F.dBm = 5mW into 75 \$\Omega\$ $0.005 = \frac{V^2}{75} \therefore V = 0.61 \text{ V}_{rms}$

choose \$R_3 = 75 + 2 = 150 \Omega\$ (1.73V_{pk})
OK.

bias is 2.5Vdc. \$\therefore\$ base voltage \$\approx 3.2 \text{ V d.c.}\$

and \$R_d = 1 \text{ k}\Omega\$ \$\therefore R_2 = 18 \text{ k}\Omega\$ and \$R_1 = 10 \text{ k}\Omega\$
ie: resistor \$(R_1 || R_2) / 4\$ (with \$R_1, R_2 \sim h_{fe} \times R_3 \approx 10 \text{ k}\Omega\$)

3(b) contd.

with $R_3 = 150 \Omega$ and $V_E = 2.5V$

$$I_C = 16.7 \text{ mA}$$


and base bias $\approx 0.2 \text{ mA}$

$$\text{DC } P_{in} = 5 \times 16.9 \text{ mW} \approx 85 \text{ mW}$$

$$\text{RF } P_{out} = 5 \text{ mW}$$


$$\therefore \eta \approx \frac{5}{85} \times 100\% \approx 6\%$$

(c)

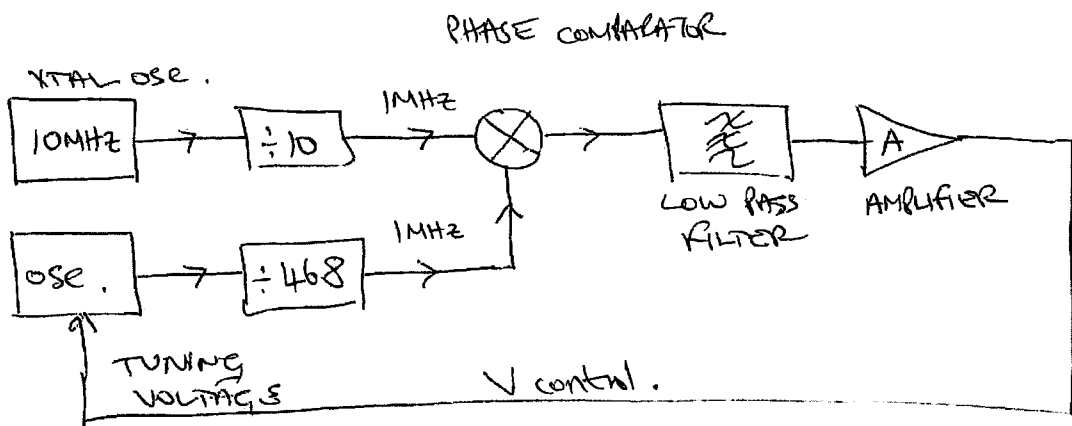

[40%]

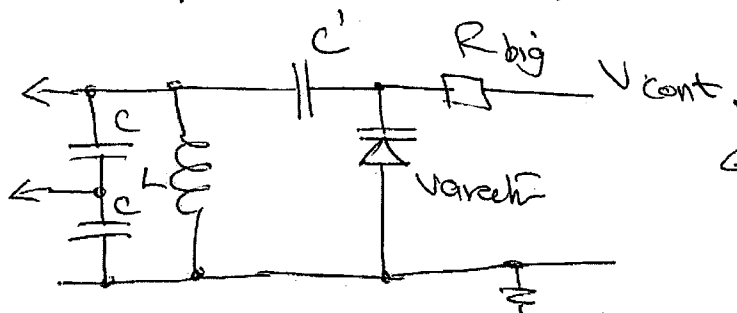Colpitts must be freq. tuneable by putting varactor across LC tank ckt. Varactor capacitance is tuned by low pass filtered output from phase comparator. Digital freq. counter/dividers bring each oscillator up to a common 1MHz freq. for phase comparison.



← parallel varactor with C d.c. blocking capacitor & Rbig bias resistor.

(d)

$$Q = \sqrt{\frac{300}{75} - 1} = \frac{X_s}{75} = \frac{300}{X_p}$$


$1.73 \quad \therefore |X_s| = 130 \Omega \quad |X_p| = 173 \Omega$

[20%]

3(d) cont.

$$\text{Let } X_s = \frac{1}{2\pi f C} = 130$$

capacitor

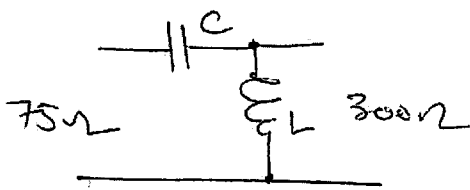

$$X_p = 2\pi f L = 173$$


inductor.

$$2\pi f = 2.94 \times 10^9 \text{ rad/s}$$

$$\therefore L = 59 \text{ nH}$$


$$\underline{C = 2.6 \text{ pF}}$$

or 1.97 pF X_p
44 nH X_s

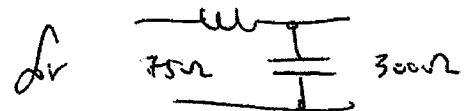

[15%]

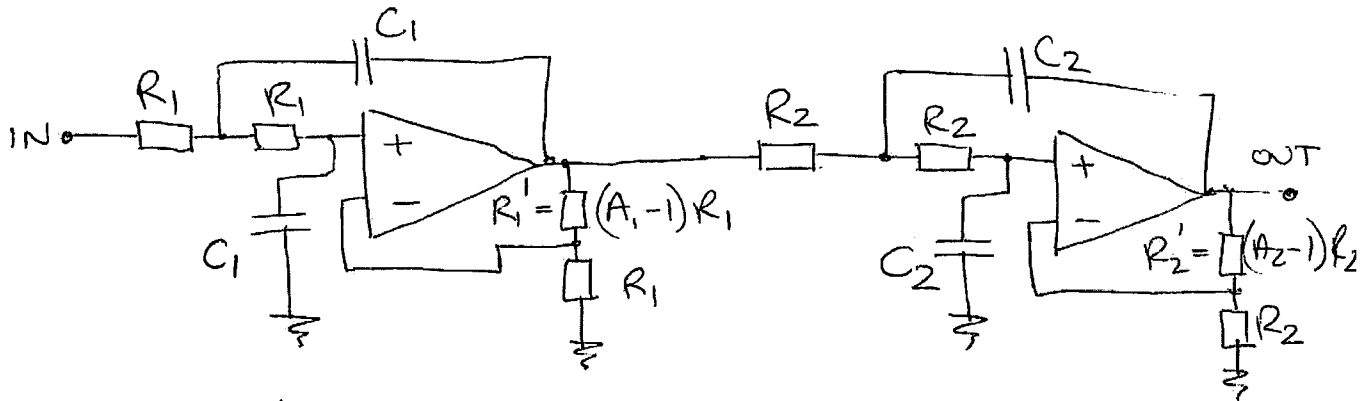4(a) Select Bessel filter, with 1kHz roll-off, as this retains waveform shape well in the time domain (at the expense of frequency cut-off steepness)



$$f_{3dB} = \frac{f_n}{2\pi RC f_n}$$

Set $R_1 = R_2 = 10k\Omega$ $\therefore R_1' = 840\Omega$: stage 1
 $R_2' = 7590\Omega$: stage 2

for stage 1: $10^3 = \frac{1}{2\pi \cdot 10^4 \cdot C_1 \cdot 1.432} \Rightarrow C_1 = 11 \text{ nF}$

stage 2: $10^3 = \frac{1}{2\pi \cdot 10^4 \cdot C_2 \cdot 1.606} \Rightarrow C_2 = 9.9 \text{ nF}$

(b) see Smith chart: [35%]


length of t/line = 0.446λ , series capacitor impedance = $-j0.95$
 (normalised to 75Ω)

$\therefore \lambda_g = \frac{3 \times 10^8}{468 \times 10^6 \cdot \sqrt{1.5}} = 0.523 \text{ m}$

\therefore length of t/line = $0.523 \times 0.446 = 0.233 \text{ m}$

[35%]

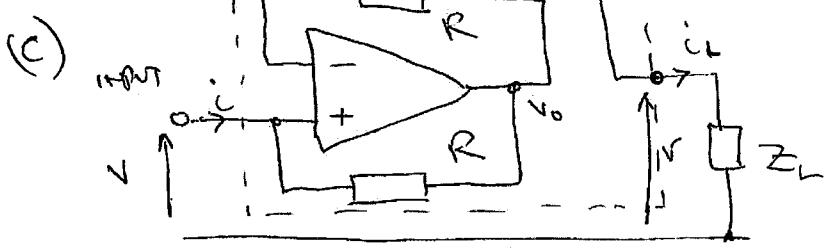$Z_{cap} = \frac{-j75 \times 0.95}{j2\pi f C} = -j71.3\Omega = \frac{1}{j2\pi f C} \therefore C = 4.8 \text{ pF}$




Use Negative Impedance Converter (NIC.)

- 4(b) • Measure of 0.44 on \odot Refl. coeff. scale and 32° \star on refl. coeff angle and plot point 'A'

Chart for question 4; to be detached and handed in with script.

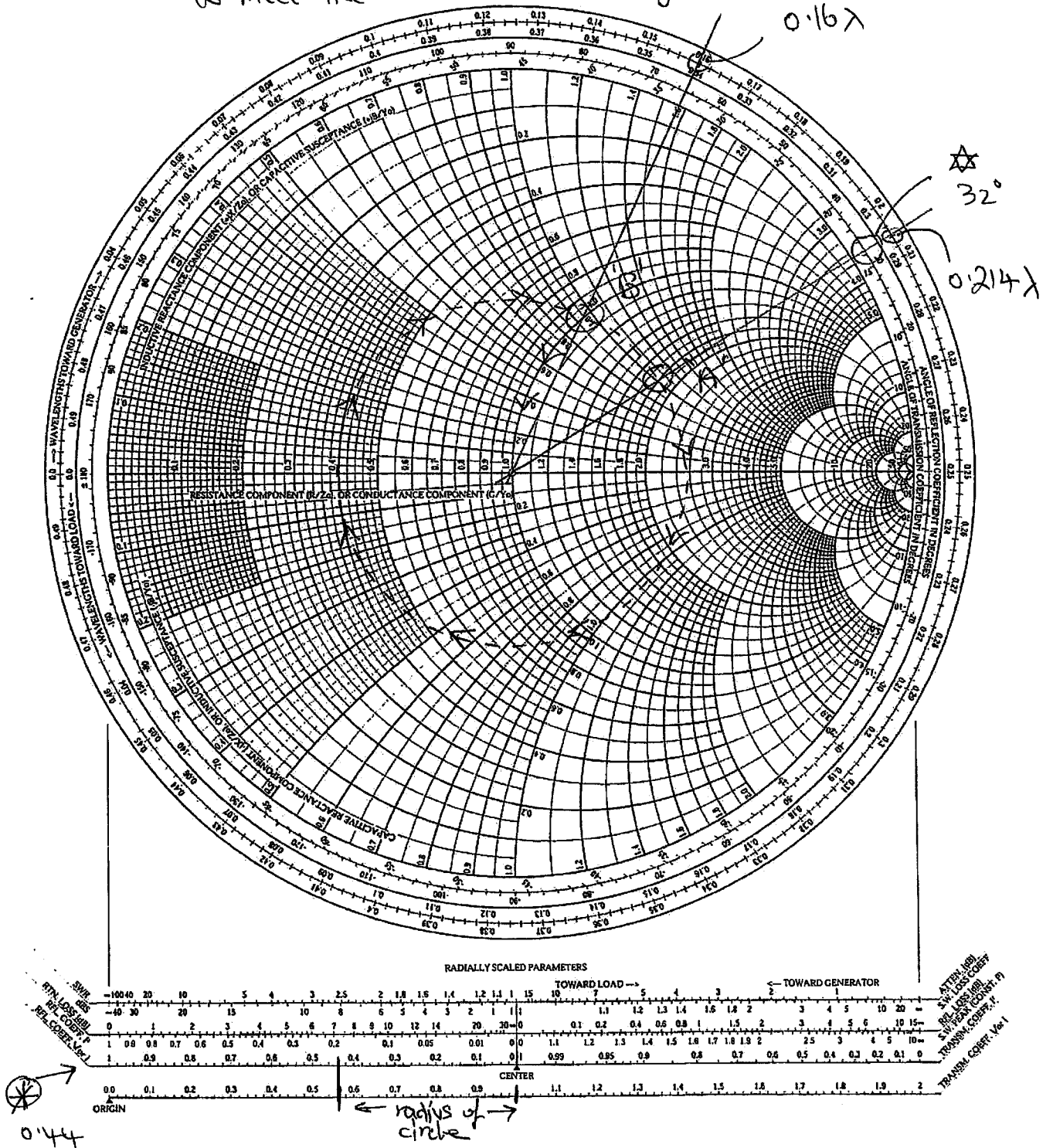- Track around transmission line clockwise from 'A' to 'B' to meet $Re=1$ circle: $B=1+j0.95$.



- Cancel $j0.95$ with series capacitor of $-j0.95$ impedance.
- Length of trans. line = $0.5\lambda - (0.214 - 0.16)\lambda = 0.446\lambda$

4(c) contd.


$$\dot{i} = \frac{V - V_0}{R} \quad \text{@ + node}$$

$$\dot{i}_L = \frac{V_0 - V}{R} \quad \text{@ - node}$$

and $V_+ = V_-$ in ideal opamp $\therefore \dot{i}_L = -\dot{i}$

So, at input Z_L appears as $-Z_L$

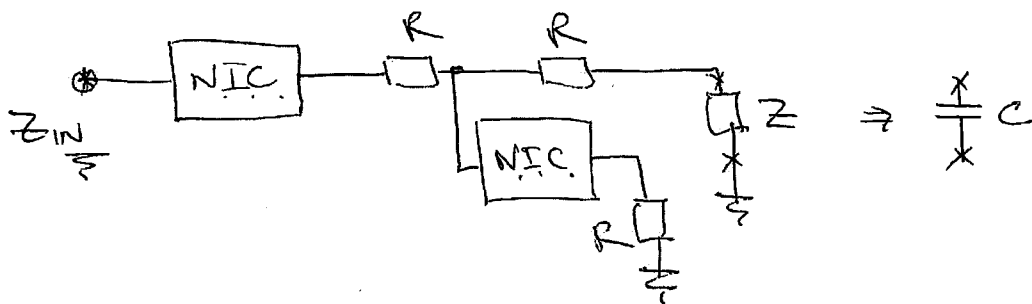To create an inductor, 2 of these must be used.



$$Z_{in} = - \left[R + \frac{-R(R+Z)}{Z} \right] = - \left[\frac{RZ - R^2 - RZ}{Z} \right]$$

$$= \frac{R^2}{Z}$$

So if $Z = \frac{1}{j2\pi f C}$ then $Z_{in} = j2\pi f \frac{R^2 C}{\omega} \equiv L$

So, for $L = 0.01 \text{ H}$ with $R = 10^4 \Omega$, $C = \frac{L}{R^2} = 100 \text{ pF}$

- Synthesised inductors can be large in value, but only over the freq. range where the op-amps ^{work well} and stray impedances do not impinge too much: this tends to mean low frequencies. A real inductor stores energy, synthesised inductors only appear to as regards the signals. Real inductors can also have large common-mode voltages, large signals and currents, but are sources of electromagnetic interference + coupling.

[30%]

3B1 Radio Frequency Electronics 2011 – Numerical Answers

1(b) $R_1 = 920 \Omega$, $R_2 = 120 \Omega$, $R_3 = 9 \Omega$, $R_4 = 75 \Omega$, $C = 10 \text{ nF}$

1(c) $R' = 43 \Omega$, $C' = 1.6 \text{ pF}$, $f_{-3\text{dB}} = 2.31 \text{ GHz / stage}$

2(b) $w = 0.72 \text{ mm}$

2(c) $\lambda/2 = 15.6 \text{ cm}$

2(d) $P_r = 3.9 \text{ nW}$, $V_r = 0.54 \text{ mV}_{\text{rms}}$

2(e) $\eta = 90 \%$

3(b) $C = 23.1 \text{ pF}$, $R_3 = 150 \Omega$, $R_2 = 18 \text{ k}\Omega$, $R_1 = 10 \text{ k}\Omega$, $R_d = 1 \text{ k}\Omega$, $\eta = 6 \%$

3(d) $X_s = 130 \Omega$, $X_p = 173 \Omega$ so, $L = 59 \text{ nH}$ & $C = 2.6 \text{ pF}$ OR $L = 44 \text{ nH}$, $C = 2 \text{ pF}$

4(a) Bessel, $C_1 = 11 \text{ nF}$, $R_1' = 840 \Omega$, $C_2 = 9.9 \text{ nF}$, $R_2' = 7590 \Omega$ with $R = 10 \text{ k}\Omega$

4(b) $T/\text{line length} = 0.233 \text{ m}$ ($= 0.446 \lambda$), $C = 4.8 \text{ pF}$

4(c) $L = CR^2$ hence for $R = 10 \text{ k}\Omega$, $C = 100 \text{ pF}$