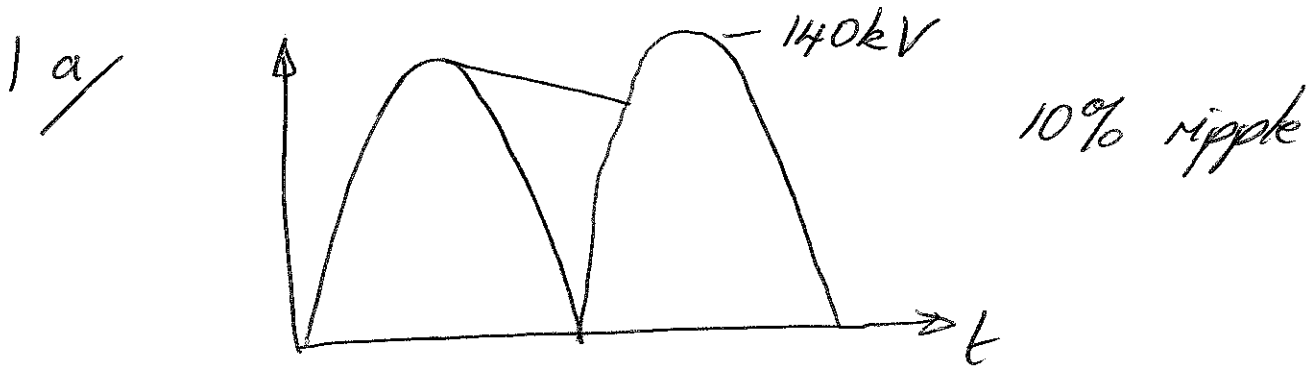


3B3 Crib 2011



$$V_0 = \hat{V}_0 - \frac{\Delta V}{2} = 140k - \frac{14k}{2} = 133kV$$

$$I = \frac{10000}{133k} = 75mA$$

Low ripple at 10% - assume constant current (linear decay)

- assume $\frac{1}{2}$ wave periods
(instant charging)

$$I = C \frac{dV}{dt} \therefore \Delta V = \frac{I}{2fC}$$



$$C = \frac{I}{2f\Delta V} = \frac{75m}{2 \times 10^4 \times 14k} = 268 pF$$

$50 pF m^{-1} \Rightarrow \approx 5m$
needed.

Less cable? Any two of: higher f ; different cable (diameter, materials); add an inductor (tricky at hv. but worth considering)

16/ 3 phase rectification into a battery ~
 peak voltage of $230\sqrt{3}\sqrt{2} = 563V$
 (quoting $\frac{3\sqrt{6}V}{\pi} = 538V$ works too!)

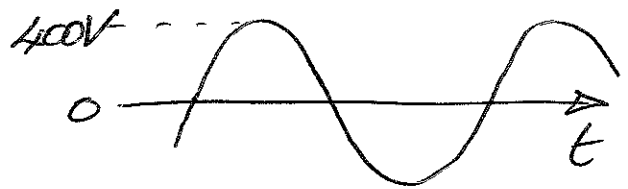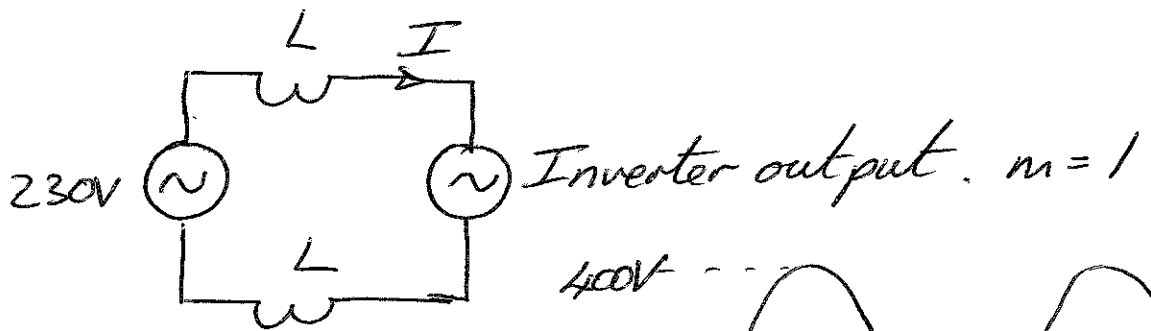
Sinusoidal Unity pf. \Rightarrow Inverter works using switching



assume no resistance
 & neglect on-state
 voltages.


$$V_{ac} = \frac{400}{\sqrt{2}}$$
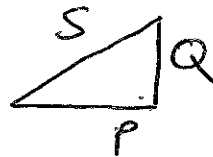
$$\left. \begin{aligned} P &= 230 \times 30 \\ Q_L &= 30^2 \cdot 2\omega L \end{aligned} \right\} \text{ matches } S_I = \frac{400 \cdot 30}{\sqrt{2}}$$



$$\omega L = 2\pi f L = \frac{1}{2 \times 30} \sqrt{\left(\frac{400 \times 30}{\sqrt{2}}\right)^2 - (230 \times 30)^2}$$
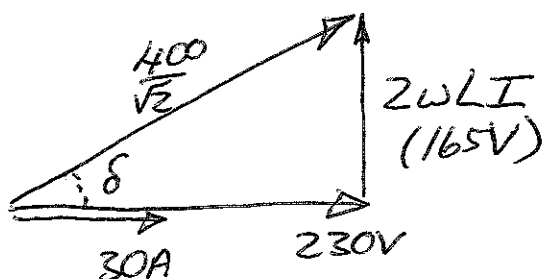
$$= 2.74 \text{ j}\Omega, \quad L = 8.7 \text{ mH.}$$



This must be controlled to happen: Change δ to set magnitude of $2\omega LI$ ie the current

20 kHz is out of audible range.



1 b cont.

check 20 kHz. $\hat{V} = L \frac{d\hat{i}}{dt}$

$$\therefore \hat{i} = \frac{1}{2L} \times 165\sqrt{2} \cdot \frac{1}{2f_s}$$

$$= 0.335 \text{ A. } (\ll 30\sqrt{2} \text{ A})$$

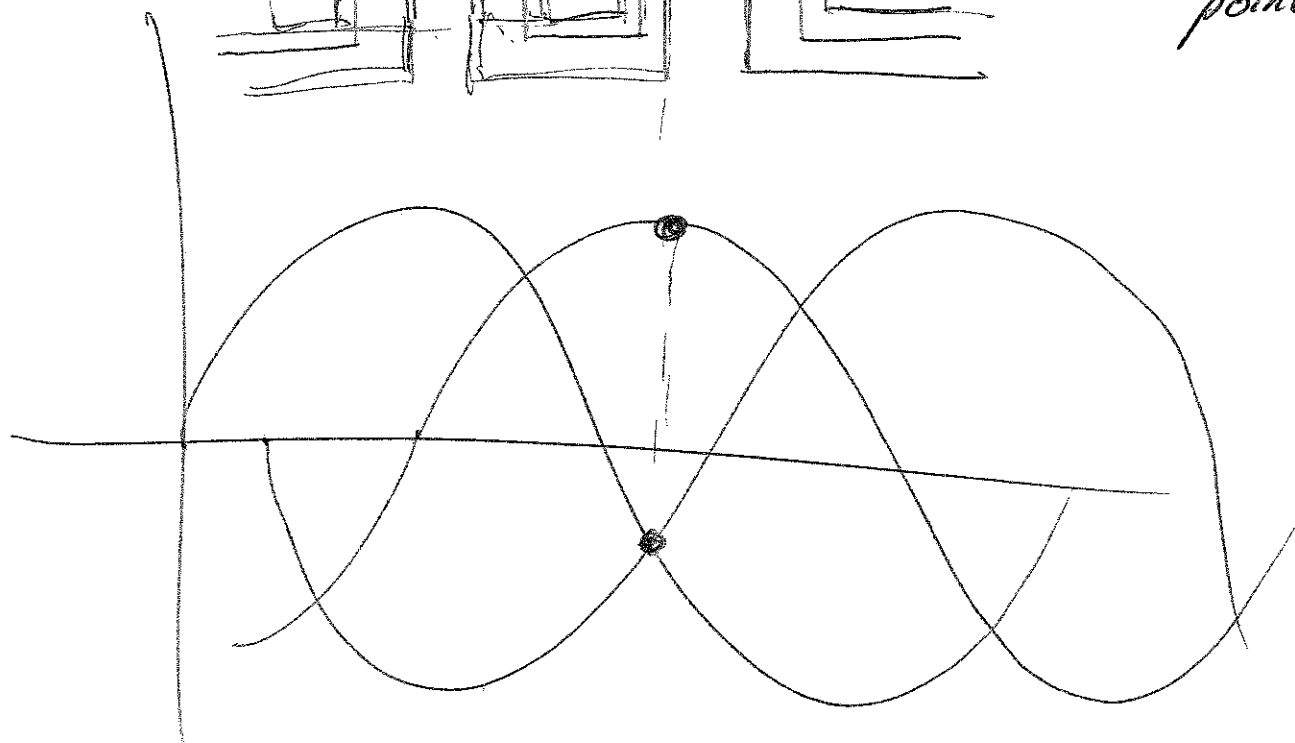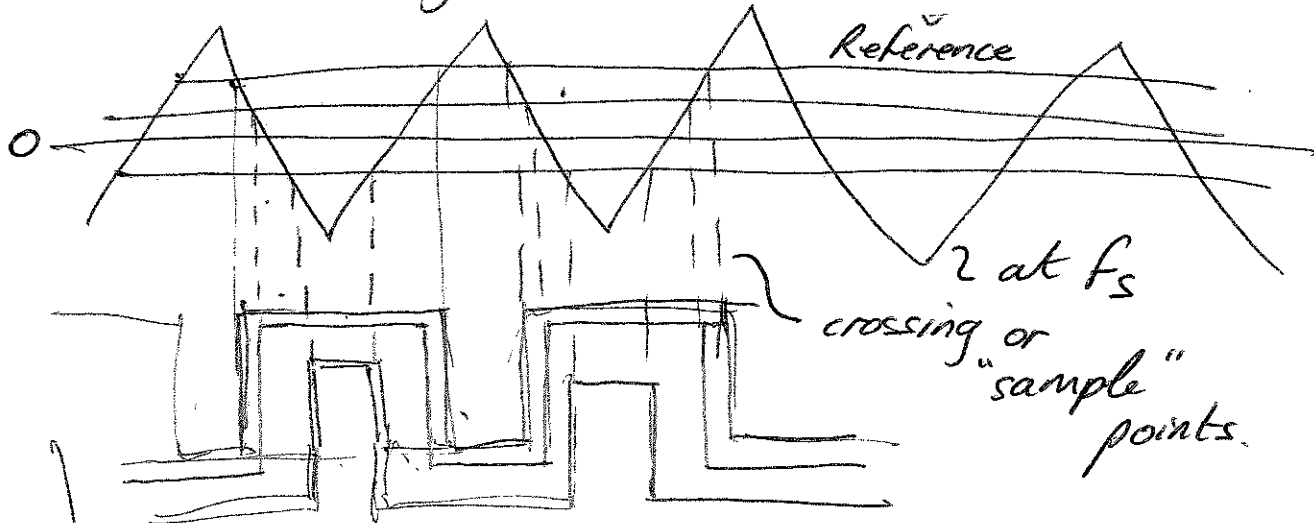2 a) *3 references are required.
+ triangular carrier




0	1	1	1	0
0	0	1	0	0
0	0	1	0	0


Three-phase references & outputs, so 3rd harmonics all cancel.*

(odd so $\frac{1}{2}$ series.)

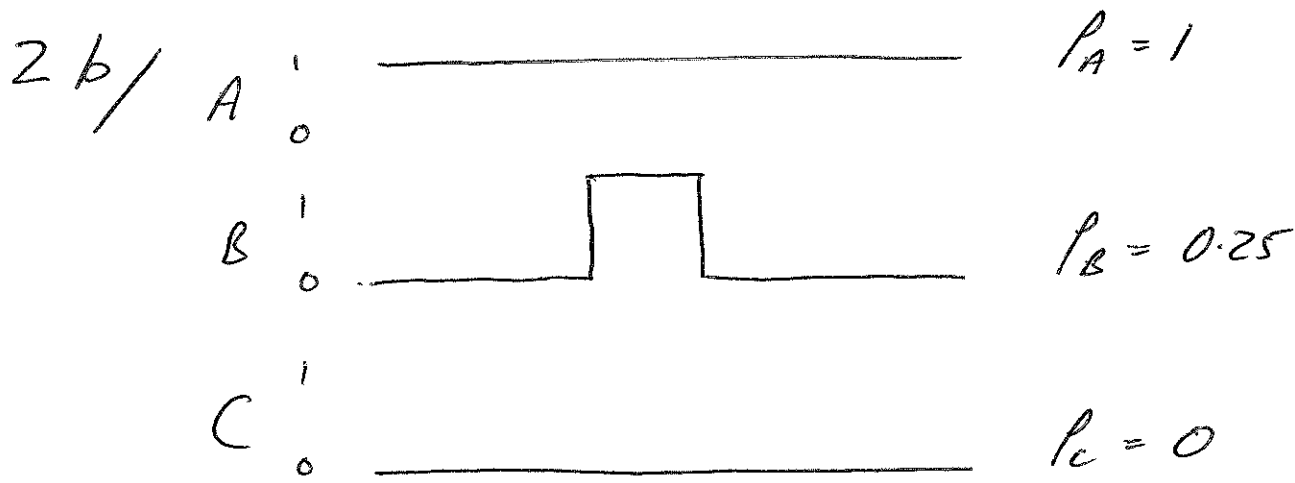Integer avoids subharmonics, but puts a 'gear' ratio in between f_s & f_1 . So use gear changing OR digital electronics, μP . repeat pulses.




$\therefore P_1 = 3/4, P_2 = 1/4$

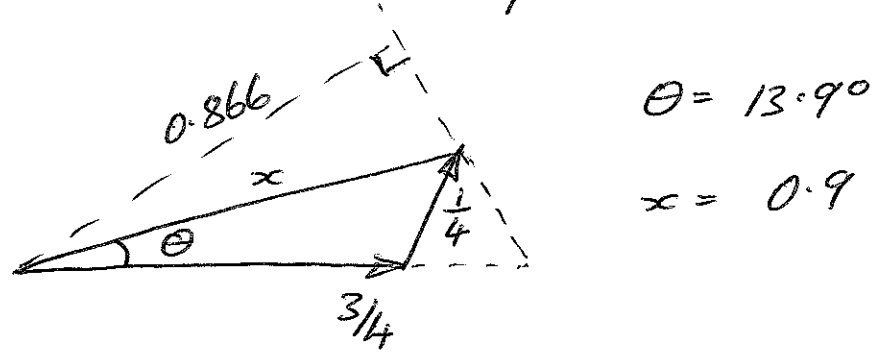

(Using P_A & P_B directly is quicker for the vector expert!)


"Relativity": $m = \frac{0.9}{0.866} = 1.041$ or $\frac{0.9 V_{oc}}{0.866}$

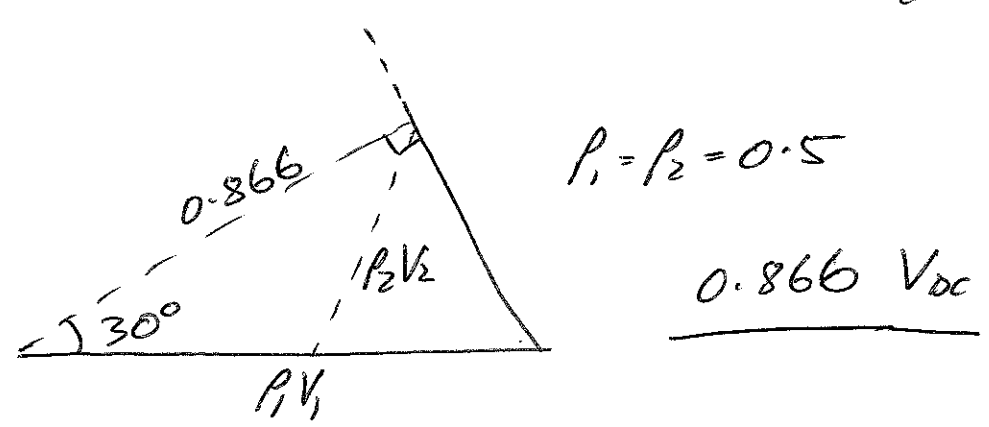The vector cannot go outside the hexagon envelope.



($P_A = 1, P_B = 0.5, P_C = 0$)

3/a

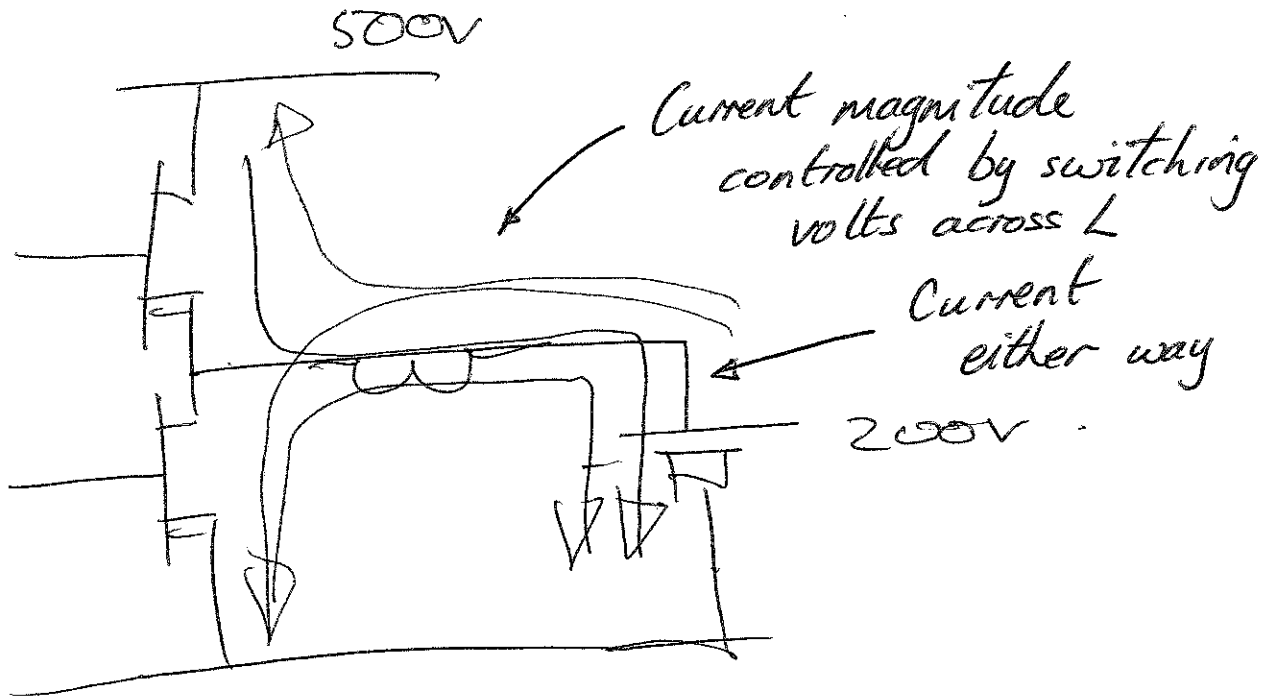

5 kHz, 30 kW, 200V.

$$\frac{30,000}{200} = 150A, 5 \text{ kHz}, 500V$$

Say $1 \mu s$ switching time


$$150 \times 500 \times 1 \mu \times 5 \text{ kHz} = 375W \text{ losses.}$$

- 1 No turn on losses,
- 2 No diode recovery current
- 3 Avoids Saturation of the inductor (or smaller L!)

Last part
of b

Current direction depends on which of T_1 and T_2 is switched in any cycle.

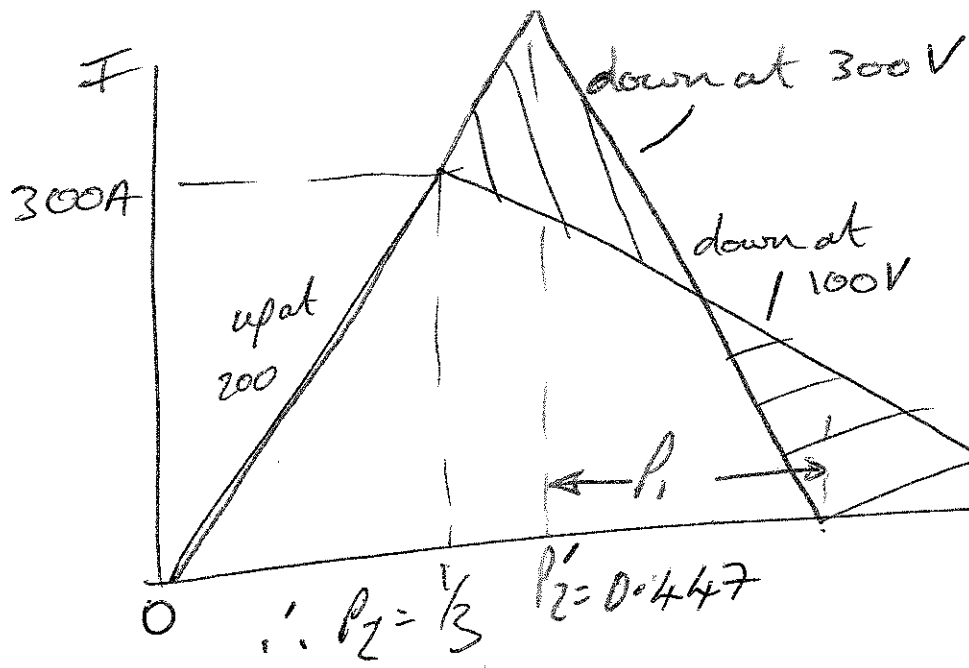3b "200V in 300 out" Current into inverter



150A average
from 200V
∴ area
must remain
the same.
∴ Discont.

200V, 30 kW \Rightarrow 150A average,
300 A peak

$$\hat{I} = \frac{1}{L} \int_0^{PT} V dt = \frac{1}{L} P T V$$

$$L = \frac{1}{300} \cdot \frac{1}{3} \cdot \frac{1}{5k} \cdot 2000 = 44.4 \mu H$$

At 500V on the inverter - fully discontinuous.

Find \hat{I} . $P_1 \cdot 500 \times \frac{1}{2} \hat{I} = 30 \text{ kW}$

$$\hat{I} = \frac{1}{L} P_1 T \times 300 = \frac{1}{L} P_2 T \cdot 200$$


$$P_1 \times 500 \times \frac{1}{2} \cdot \frac{1}{L} P_1 T \times 300 = 30k$$

$$P_1^2 = \frac{30k \times 2 \times 44.4 \mu \times 5k}{500 \times 300} = 0.0888$$

$$P_2' = P_1 \times \frac{300}{200} \quad P_2' = 0.447 \quad P_1 = 0.298 \quad \hat{I} = 402 \text{ A}$$


4 a) Inductor L needed as capacitive load. Put in series resonance / ^{high Q} so half bridge is simple & cheap.

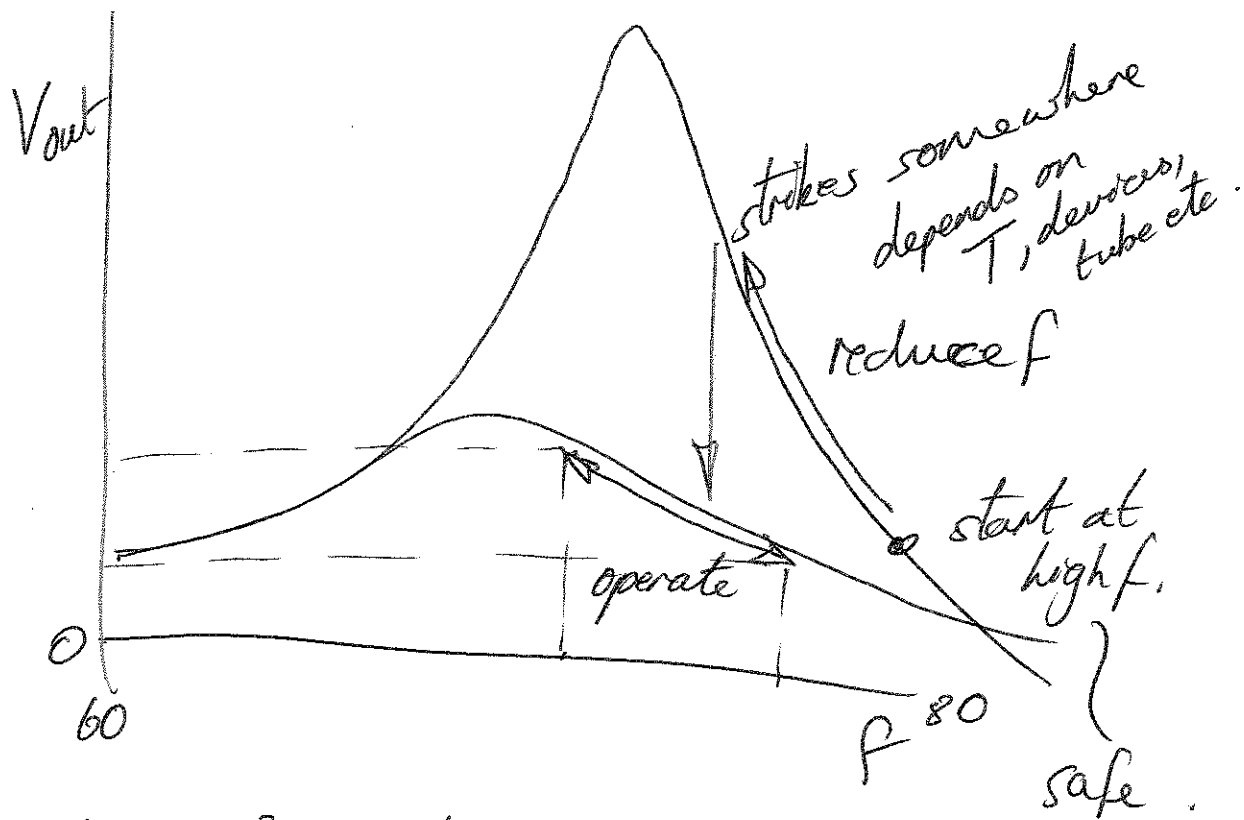But uses a Pch Mosfet (CMOS) which is lessy or expensive.



(light $\propto V^2$ so bigger adjustment than it first appears)



4a cont/

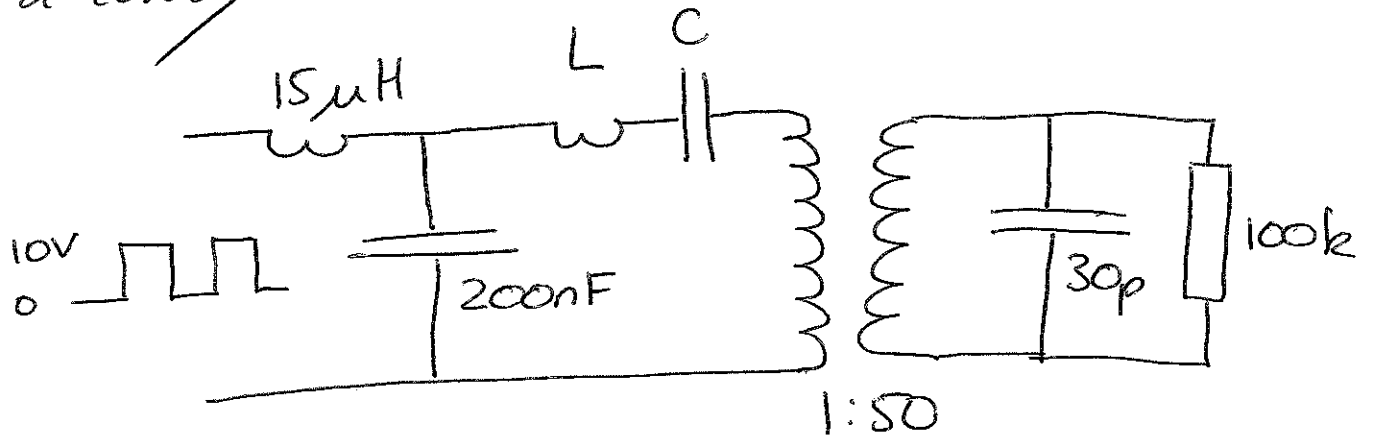

15µF/200nF act as filter, so we take the fundamental of the input.
 $\Rightarrow \frac{10}{2} \times \frac{4}{\pi}$ sinewave peak.

from 5(b)
 @ 69 kHz
 $N^2 = 2500$
 $30p \times 2500 = 75nF$
 $100k / 2500 = 40$

Peak resonance, so L & C disappear.

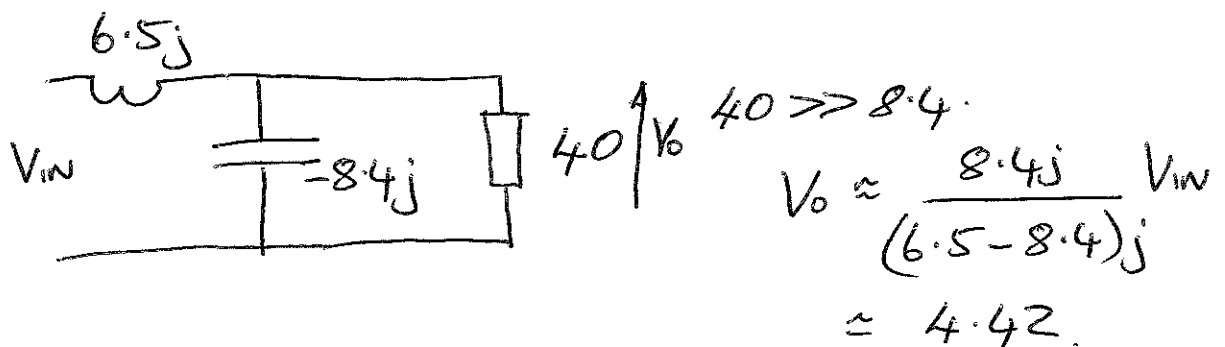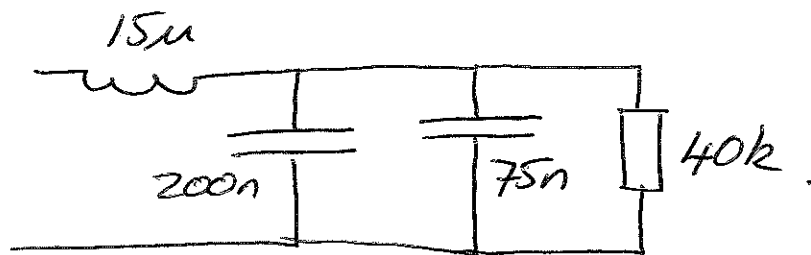


$$\frac{10}{2} \times \frac{4}{\pi} \times 4.42 \times 50 = 1407V$$

although the filter is working as a filter it does give a significant increase in voltage!

4 b. / Could replace pMOS with NMOS and a bootstrap driver IC. Lower losses but complicated.

Use full resonance ideas.

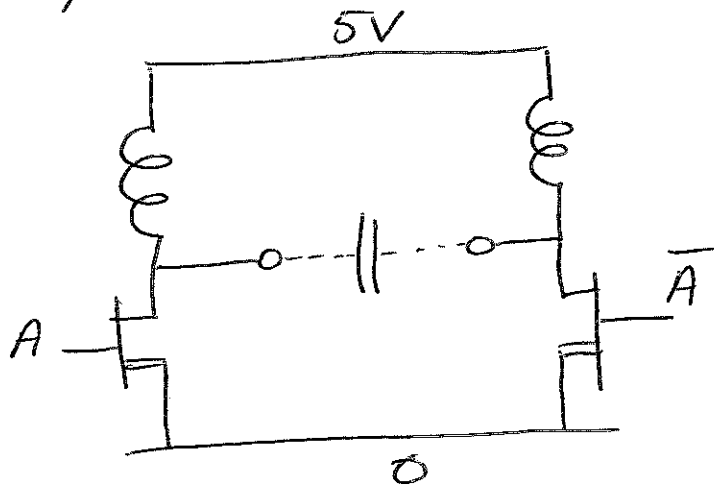

- i) Two lowside NMOS so easy gate drives.
- ii) Low losses with good NMOS
- (Lossless switching if operated carefully)
- (\pm Voltage swing ~ like full bridge)