

(a)

$$\text{Gain, } G = \frac{\text{Max. power radiated per unit area}}{\text{power per unit area from isotropic ant.}}$$

Effective Aperture, A_e (Area): power delivered to a matched load by an antenna = $A_e \times$ power density in incident radio wave

Radiation Resistance, R_r : power radiated = $\frac{1}{2} I^2 R_r$, where I is current feed to antenna

Polarisation describes the plane in which the electric field is aligned, orthogonal to the direction of wave propagation

Note: antenna eqn. $G = \frac{4\pi A_e}{\lambda^2}$ [20%]

(b) $v = f\lambda$ with $v = c = 3 \times 10^8 \text{ ms}^{-1}$ \therefore at 172 MHz
 $\lambda = \frac{3 \times 10^8}{172 \times 10^6} = 1.744 \text{ m}$ \therefore each element = 0.436 m $\frac{1}{2} \uparrow 0.436 \text{ m}$

Assuming gain of 1/4-wave dipole to be 1.5, power density 2km away = $\frac{30 \times 10^{-3} \cdot 1.5}{4\pi \cdot 2000^2} = 8.95 \times 10^{-10} \text{ Wm}^{-2}$ [20%]

(c) For receiving antenna, $A_e = G \lambda^2 / 4\pi$ with $G = 1.5$
 $\lambda = 1.744 \text{ m}$

$$\therefore A_e = 0.363 \text{ m}^2$$

$$\therefore \text{Power received} = 8.95 \times 10^{-10} \cdot 0.363 = 3.25 \times 10^{-10} \text{ W}$$

1(c) contd.

$$P_{\text{rec}} = V_r^2 / R \quad \text{where } R = 50 \Omega$$

$$\therefore V_r = \underline{1.27 \times 10^{-4} \text{ V}_{\text{rms}}} \quad [20\%]$$


(d) skin depth in stainless steel @ 172 MHz.

$$\delta = \sqrt{\frac{2\rho}{\omega\mu}}$$

$$\begin{aligned} \rho &= 7.2 \times 10^{-7} \Omega\text{m} \\ \omega &= 2\pi f = 1.08 \times 10^9 \text{ rad/s} \\ \mu &= 4\pi \times 10^{-7} \text{ H/m} \end{aligned}$$

$$\therefore \delta = 3.26 \times 10^{-5} \text{ m}$$

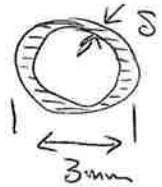\therefore resistance given by conducting cross-section over antenna length



$$R_{\text{ohmic}} = \frac{\rho l}{A} = \frac{7.2 \times 10^{-7} \cdot 1.744/2}{2\pi \cdot 1.5 \times 10^{-3} \cdot 3.26 \times 10^{-5}} = 2.05 \Omega$$

$$\text{Hence radiation efficiency} = \frac{R_r}{R_r + R_{\text{ohmic}}} = \frac{50}{52.05} = 0.96$$

or 96%

(taking R_r to be matched to 50Ω).

[25%]

(e) $P = \frac{1}{2} E^2 / \eta$ where $\eta = 120\pi$ (impedance of free space)


$$\therefore E = (120\pi \cdot 2 \cdot 8.95 \times 10^{-10})^{1/2} = 8.21 \times 10^{-4} \text{ Vm}^{-1}$$

$$\therefore V_{\text{sig}} = \frac{1.744}{2} \times 8.21 \times 10^{-4} = 7.16 \times 10^{-4} \text{ V} = \underline{5 \times 10^{-4} \text{ V}_{\text{rms}}}$$

This is higher than part (c) result as the antenna is unloaded (open ckt.) and potential distribution is rather optimistic for a simple dipole.

[15%]

2(a)

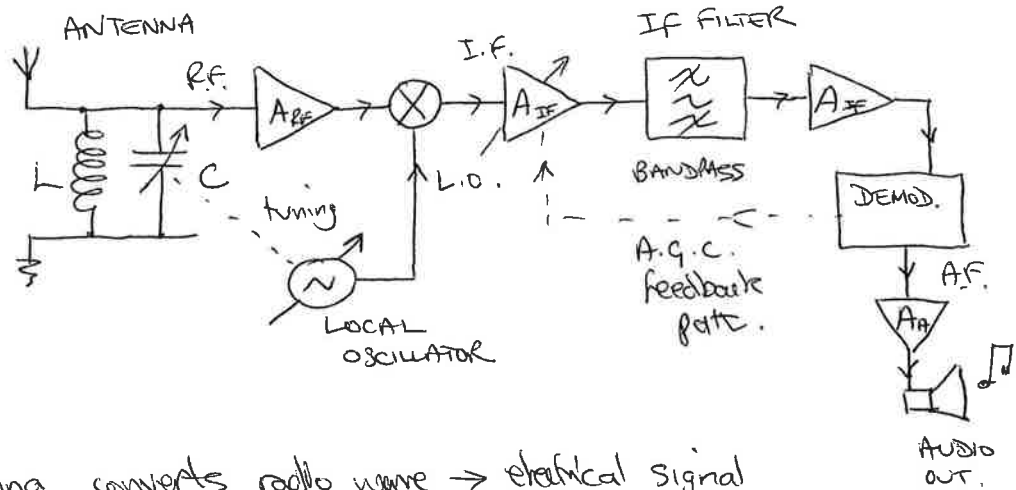


- Antenna converts radio wave \rightarrow electrical signal
- LC front end selects signal freq. and magnifies its amplitude by Q-factor
- A_{RF} boosts RF signal to feed into mixer
- Mixer multiplies RF signal by LO to give sum and difference frequencies (from $\cos \times \cos$ trig relation)
- A_{IF} amplifies the mixer output (and b/w can remove sum freq.)
- IF filter selects difference freq: $I.F. = (L.O. - R.F.)$
- A_{IF} amplifies IF signal before demodulation, which eg: with envelope detection for AM, recovers original signal, A.F.
- This is then amplified and output as audio.
- Tuning is effected by sweeping LO freq. and LC (RF) freq. together, maintaining the IF. fixed separation.
- A.G.C. can be achieved by using dc from demodulator to control IF. gain.

[20%] gain.

(b)

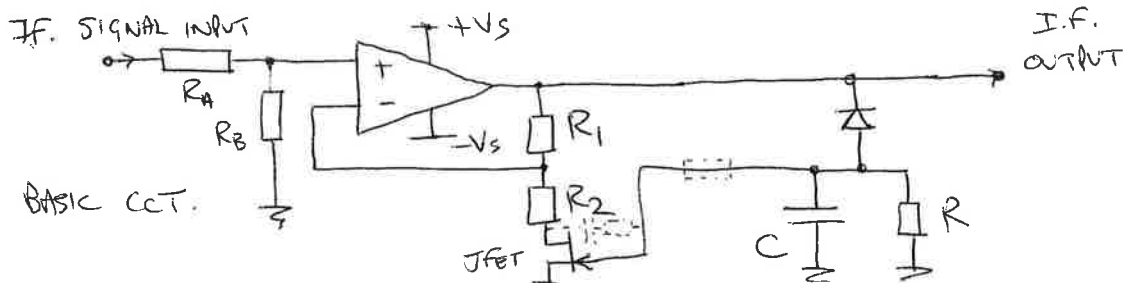Use JFET as variable resistance element in op-amp circuit:




2(b) control


to maximize JFET small sig. linearity, the dotted components can be added $R=1M\Omega, C=100nF$: adds $\frac{V_{gs}}{2} \approx V_{gs}$.

- 1stly R_A and R_B divide signal by 10 $R_A=9k\Omega, R_B=1k\Omega$
- this is because the op-amp at has gain ≥ 1 and we need $\times 0.1$
- select R_2 and R_1 to give max gain of 200 for op-amp
 $\therefore R_1=200k\Omega, R_2=1k\Omega$
- the conduction resistance of JFET (depletion mode) sets gain.
- the diode and RC circuit gives a smoothed -ve bias to the gate: choose $10 = \frac{1}{2\pi RC}$ for response time τ :
 $\therefore R=10k\Omega$
 $C=1.6\mu F$ [35%]

(c) we want bandpass filter

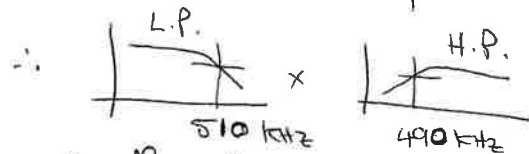

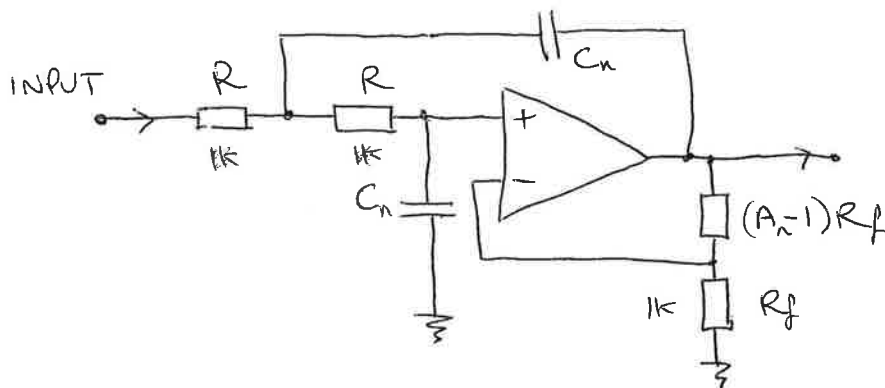choose chebyshev for sharpest cut-off (200kHz - 500kHz is quite sharp) - and ripple in gain doesn't matter much here.



Low Pass
SECTIONS
(x2)
followed by
HIGH PASS SECTIONS
(x2)

For high pass, swap R's and C's at input/feedback and cascade.

2(c) contd.

$$\text{For low pass } f_{-3dB} = 510 \times 10^3 = \frac{1}{2\pi f_n R C}$$

\therefore with $R = 1 \text{ k}\Omega$ throughout = $R_f 100$

$$\begin{array}{l} \text{stage 1:} \\ \text{LP1} \end{array} \quad \begin{array}{l} C_1 = 1 \text{ nF} \\ (A_1 - 1) R_f = 582 \Omega \end{array} \quad , \quad \begin{array}{l} R_1 = 523 \Omega \\ R_f = 1 \text{ k}\Omega \end{array}$$

$$\begin{array}{l} \text{stage 2:} \\ \text{LP2} \end{array} \quad \begin{array}{l} C_2 = 1 \text{ nF} \\ (A_2 - 1) R_f = 1.66 \text{ k}\Omega \end{array} \quad , \quad \begin{array}{l} R_2 = 303 \Omega \\ R_f = 1 \text{ k}\Omega \end{array}$$

$$\text{For high pass } f_{-3dB} = 490 \text{ kHz} = \frac{f_n}{2\pi R C}$$

$$\begin{array}{l} \text{stage 3:} \\ \text{HP3} \end{array} \quad \begin{array}{l} C_3 = 1 \text{ nF} \\ (A_3 - 1) R_f = 582 \Omega \end{array} \quad , \quad \begin{array}{l} R_3 = 194 \Omega \\ R_f = 1 \text{ k}\Omega \end{array}$$


$$\begin{array}{l} \text{stage 4:} \\ \text{HP4} \end{array} \quad \begin{array}{l} C_4 = 1 \text{ nF} \\ (A_4 - 1) R_f = 1.66 \text{ k}\Omega \end{array} \quad , \quad \begin{array}{l} R_4 = 335 \Omega \\ R_f = 1 \text{ k}\Omega \end{array}$$

[35%]

(d) 'Tracking' is the term which describes how well the RF resonant LC peak freq. moves with the LO. freq. to give a constant IF. . If they misalign, then the IF. signal freq. does not match the fixed I.F. filter - and the signal is attenuated. A low Q-factor gives a wider LC bandwidth, ~~so~~ so tracking is not so critical - but the signal magd. is lower.

[10%]

3(a)

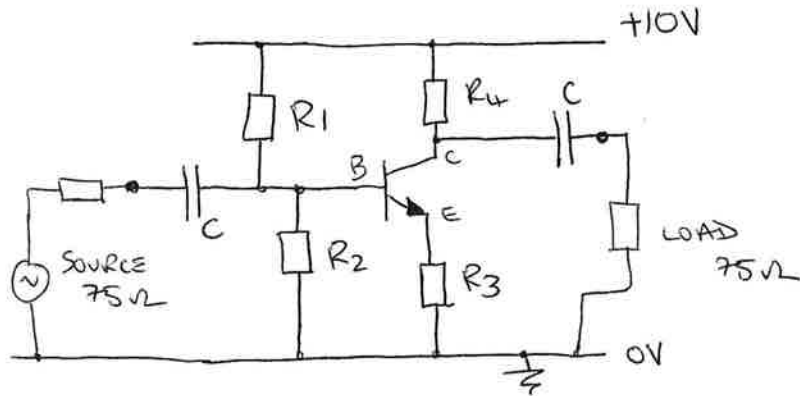

- Choose $R_4 = 75\Omega$ for match impedance
- 10 dB gain = $\times 3$ linear gain loaded = $\times 6$ unloaded at output
 $\therefore R_3 \approx \frac{75}{6} \therefore$ say 12Ω

- with collector biased to 5V dc., $I_c = \frac{5}{75} = 67\text{mA}$
 $\therefore r_e = \frac{0.025}{0.067} = 0.37\Omega$

$\therefore |gain| = 75/12.4 = 6.06$ and $V_E = 0.8V$


- choose R_1 and R_2 to give $V_B = V_E + 0.65V \approx 1.5V$ dc.
 \therefore with $R_2 = 100\Omega$, $R_1 = 560\Omega$
($\approx 1.5 \times 75$)

$R_{in} = \left(\frac{1}{100} + \frac{1}{560} + \frac{1}{12 \times 250} \right)^{-1} = 82\Omega \cdot \text{OK}$

- choose C to be large eg: 100nF . $\left(\frac{1}{2\pi f C} @ 172\text{MHz} = 0.01\Omega \right)$
[25%]

- (b) with $f_t = 18\text{GHz}$ and $r_e = 0.38\Omega$, $C_{ie} = 23\text{pF}$
 $f_t = \frac{1}{2\pi r_e C_{ie}}$

Input circuit in small sig. Model

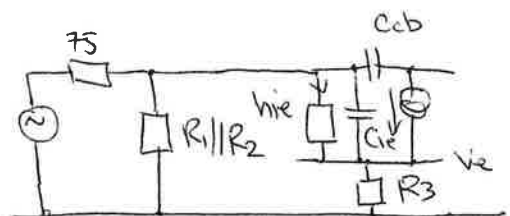

3(b) Control.


$$V_e = \frac{R_3}{R_3 + r_e}, V_i = 0.97$$

From Miller effect $C_{cb} \rightarrow C_{cb} \times (1+G)$

when loaded $G = 3 \therefore C_{cb}' \text{ referred to ground} = 0.80 \text{ pF}$

and C_{ie} referred to ground is $\div \left[\frac{1}{(1-0.97)} \right]$ due to -ve feedback from emitter node. $\therefore C_{ie}' = \frac{23}{33} = 0.70 \text{ pF}$.

So input s/sun. \approx

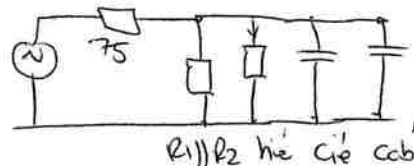

$$h_{ie}' = h_{ie} \times r_e \times 33 \approx 3 \text{ k}\Omega$$

$$\text{So, roll off at } \approx \frac{1}{2\pi R_{e'} C'} = f_{-3dB}$$


$$R' = 75 \parallel 82 = 39 \Omega$$

$$C' = C_{ie}' + C_{cb}' = 1.5 \text{ pF}$$

$$f_{-3dB} = 2.72 \text{ GHz}$$

[35%]

(c)

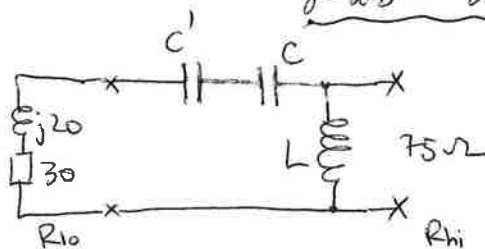

$$f = 172 \text{ MHz}$$

$$\text{First, cancel } j20 \text{ with } C' \text{ giving } -j20 \Rightarrow 20 = \frac{1}{2\pi f C'}$$

$$\therefore C' = 46.3 \text{ pF}$$

Then use filter design eqns:

$$Q = \frac{R_{hi}}{X_p} = \frac{X_s}{R_{lo}} = \sqrt{\frac{R_{hi}}{R_{lo}} - 1} = \sqrt{\frac{75}{30} - 1} = 1.22$$


$$\therefore X_p = 75 / 1.22 = 61.5 = 2\pi f L \therefore L = 57 \text{ nH}$$

$$X_s = 1.22 \times 30 = 36.7 = \frac{1}{2\pi f C} \therefore C = 25 \text{ pF}$$

So we can combine $C_{and} C'$ into 1 capacitor $\left(\frac{1}{25} + \frac{1}{46} \right)^{-1} \Rightarrow 16 \text{ pF}$

3(c) control


So, matching circuit is this :-

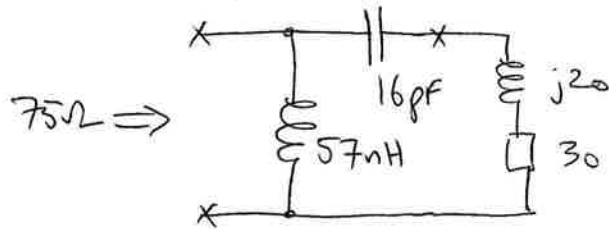

[30%]

(d) To act as a filter, we can transform the impedance to an intermediate value to get high Q values


eg:

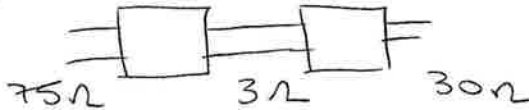

then, the match is quite sharp with f_{eq} . eg: $Q \approx 5$ to 10 .

or can cascade more stages with ever higher Q 's. [10%]

4 (a)

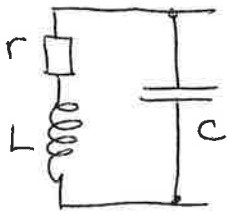

$$f_{res.} = \frac{1}{2\pi\sqrt{LC}}$$


$$Q = \frac{\omega L}{r} = \frac{2\pi f L}{r}$$

with $f = 172 \times 10^6$ Hz and $C = 18 \times 10^{-12}$ F $\Rightarrow L = 47.6$ nH

$$\therefore Q = 25.7$$

[20%]

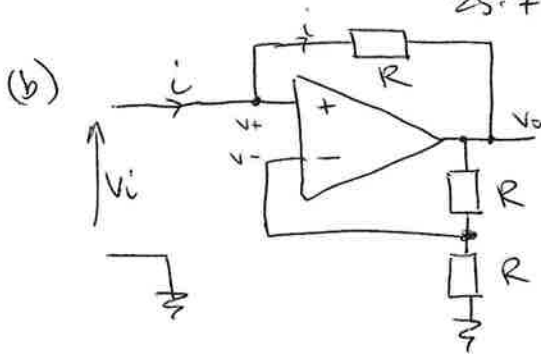So the bandwidth = $\frac{172}{25.7}$ MHz = 6.69 MHz.



$$v_+ = v_- = v_i$$

$$i = \frac{v_i - v_o}{R}$$

$$\text{and } v_- = \frac{v_o}{2} = v_i$$


$$\therefore i = \frac{v_i - 2v_i}{R} = -\frac{v_i}{R}$$

$$\therefore Z_{in} = \frac{v_i}{i} = -R$$

negative resistance.

This can be used to increase Q-factor (but not too far or it will oscillate).

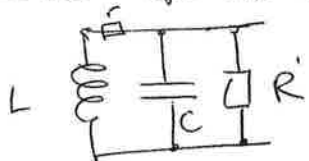we can refer the series resistance r to a parallel resistance R



$$Q = \frac{R}{\omega L} = \left(\frac{r}{\omega L}\right)^{-1} \therefore R = \frac{(\omega L)^2}{r}$$

and with $R' \parallel -R$ we can increase the effective value of R'

eg: $5k\Omega \parallel -10k\Omega \Rightarrow 10k\Omega$
 [15%] so doubles Q.

4(c) $33\Omega + 10nH$ @ $960MHz$

$$= 33 + j60 \Omega \div 50 \Rightarrow 0.66 + j1.2$$

normalized, point A'

length of stripline: $(0.176\lambda - 0.153\lambda) = 0.026\lambda$

series capacitor is cancel $j1.5 \Rightarrow -j75\Omega$ at $960MHz$

$$\text{So } 75 = \frac{1}{2\pi \cdot 960 \times 10^6 \cdot C} \quad \therefore C = \underline{2.21 pF}$$

If the freq. changes to $1060MHz$, then the length of stripline = $0.026\lambda \times \frac{1060}{960} = 0.029\lambda$

and C has a normalized impedance of $\frac{-j68}{50} = -j1.36$

Also, the input impedance will be $0.66 + j1.33$

'x' @ $0.159\lambda \rightarrow 0.159\lambda + 0.029\lambda = 0.188\lambda$

\therefore 'x' $\rightarrow 1.15 + j1.85 - j1.36$

$$= 1.15 + j0.49$$

$\therefore p = 0.22$ from radial scale

[40%]

(d) If $\epsilon_r = 3$ then $v_{line} = \frac{3 \times 10^8}{\sqrt{3}} = 1.73 \times 10^8 \text{ m/s}^{-1}$


$$\therefore \lambda @ 960MHz = 0.18 \text{ m}$$

$$\therefore 0.026\lambda = \underline{4.7 \text{ mm}}$$

For 50Ω trace: $v_{line} = \frac{1}{\sqrt{L \cdot C}}$ and $Z_0 = \frac{\sqrt{L}}{\sqrt{C}}$

$$\therefore Z_0 = \frac{1}{\sqrt{line} \cdot C} \quad \text{and} \quad C = \frac{2(w + 2t)}{t} \epsilon_0 \epsilon_r$$

includes fringing fields

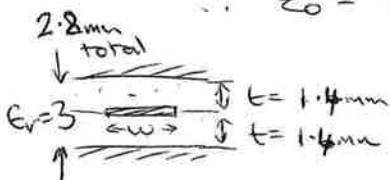

$$\therefore 50 = \frac{1.4}{1.73 \times 10^8 \cdot 2(w + 2 \cdot 2) \cdot 8.854 \times 10^{-12} \cdot 3}$$

$$\therefore w = \underline{0.24 \text{ mm}}$$

[25%]

3B1 2012 – Numerical answers

- 1 (b) $8.95 \times 10^{-10} \text{ W m}^{-2}$
(c) $1.27 \times 10^{-4} \text{ V rms}$
(d) 96 %
(e) $5 \times 10^{-4} \text{ V rms}$
- 2 (c) 510 kHz, high pass, $R_f = 1 \text{ k}\Omega$
 $R_1 = 523 \Omega$, $(A-1)R_f = 582 \Omega$
 $R_2 = 303 \Omega$, $(A-1)R_f = 1.66 \text{ k}\Omega$
- 490 kHz, low pass, $R_f = 1 \text{ k}\Omega$
 $R_3 = 194 \Omega$, $(A-1)R_f = 582 \Omega$
 $R_4 = 335 \Omega$, $(A-1)R_f = 1.66 \text{ k}\Omega$
- 3 (a) $R_1 = 100 \Omega$, $R_2 = 560 \Omega$, $R_3 = 12 \Omega$, $R_4 = 75 \Omega$
(b) 2.72 GHz
(c) 57 nH, 16 pF
- 4 (a) $Q = 25.7$, $B/w = 6.69 \text{ MHz}$
(c) 0.029λ , 2.21 pF, $\rho = 0.22$
(d) $w = 0.24 \text{ mm}$, $l = 4.7 \text{ mm}$