

3B1 CRIB 2013

1(a) Butterworth : compromise between freq. and time domain responses - approx. 10% overshoot for step response and medium sharp roll off in frequency domain.

Bessel : constant time delay filter across freq. band, hence good step response (no overshoot, fast response) but freq. roll off is very slow.

Chebyshev: best freq. domain sharp cut-off but time domain 'rings' on after step for several cycles.


for 1st order filters (low pass) @ twice cut-off freq. :-

Bessel = -10 dB, Butterworth = -30 dB, Chebyshev = -45 dB.

[20%]

1(b) for bandpass cascade low-pass and high-pass sections :-

(to 3kHz) (over 250Hz)

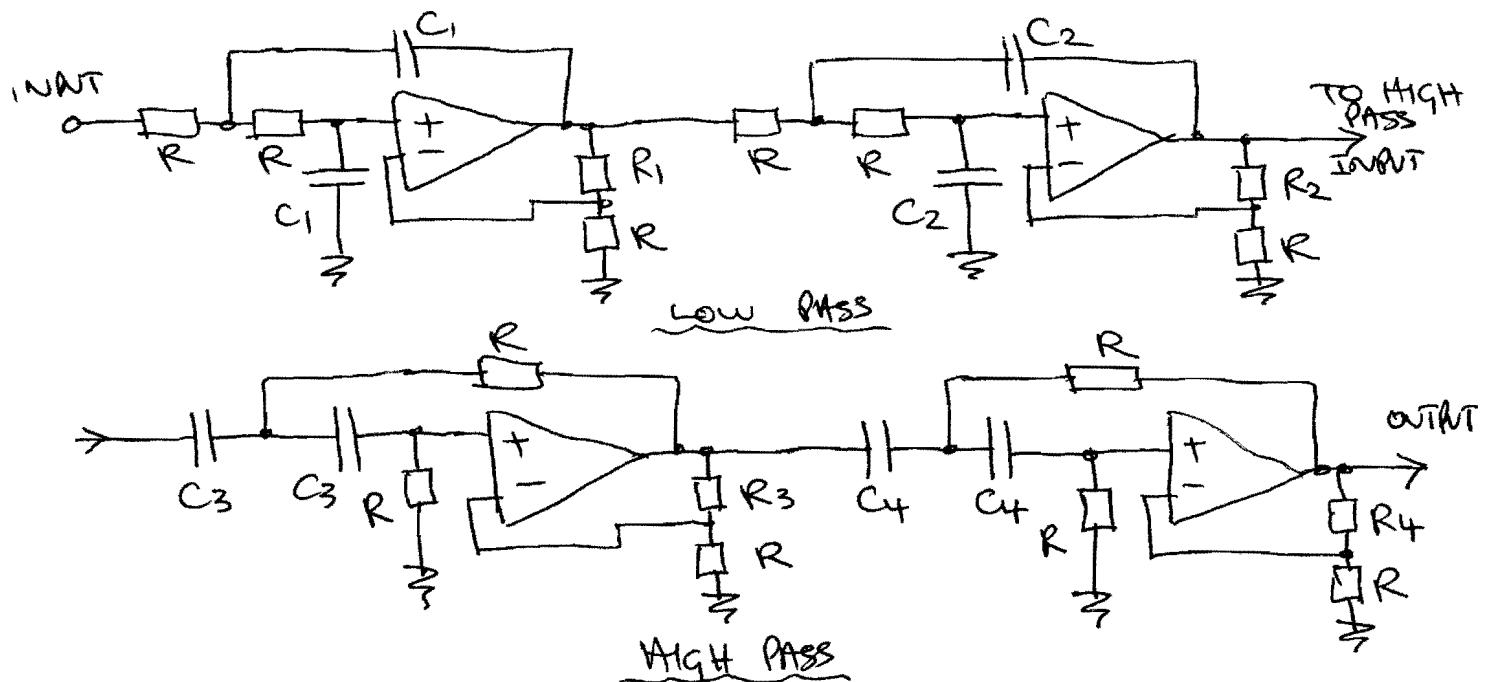

use Chebyshev filter for sharp cut-off.

(b) contd.

$\frac{f_r}{0.597}$	$\frac{A}{1.582}$	$R = 10\text{k}\Omega$ in all stages
1.031	2.660	

Stage 1 $G = 1.582 \quad \therefore R = (1.582 - 1) \times 10\text{k}\Omega = 5.8\text{k}\Omega$
 $f_c = 3000 = \frac{1}{2\pi R C_1 f_n} \Leftrightarrow 0.597$ (or $5.6\text{k}\Omega$ std)


Stage 2 $R_2 = 16.6\text{k}\Omega$ ($18\text{k}\Omega$) $\therefore G = 8.9\text{nF}$ (10nF std)

Stage 3 $C_2 = 5.1\text{nF}$ (4.7nF std)

Stage 4 $R_3 = R_4 = 16.6\text{k}\Omega$ ($8\text{k}\Omega$) $f_c = 250 = \frac{1}{2\pi R C_3 f_n} \Rightarrow C_3 = 38\text{nF}$ (39nF)

Stage 4 $C_4 = 66\text{nF}$ (68nF std.) [40%]

1(c)

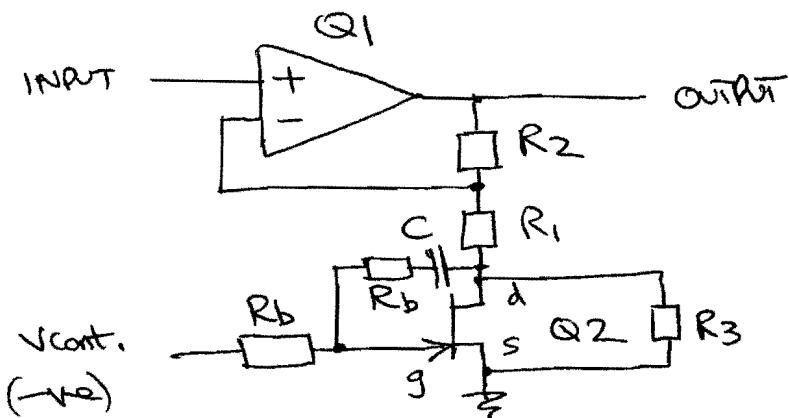

Q1: operational amplifier to provide gain

Q2: JFET used as voltage controlled resistor

R2: feedback resistor

R1: gain limit resistor, when Q2 fully on (low resistance) then

$$\text{Max. gain} = 1 + R_2/R_1$$

Rb: bias resistors for gate, to improve linearity of amplifier by cancelling non-linear term

C: d.c. block capacitor.

[20%]

R3: gain limit resistor for min. gain when Q2 is off $= 1 + \frac{R_2}{(R_1 + R_3)}$

1(d) Need to get amplitude control, so demodulate with diode to give -ve voltage, for amplifier:-

$$\therefore \text{choose } R_2 = 100\text{ k}\Omega \quad 10\text{ dB} \equiv \times 3.2 \quad \text{min.}$$

$$30\text{ dB} \equiv \times 32 \quad \text{max.}$$

$$\therefore R_1 = 3.2\text{ k}\Omega \quad (3.3\text{ k}\Omega \text{ std})$$


$$\therefore R_3 = 42.3\text{ k}\Omega \quad \text{taking } R_1 \text{ into account}$$

(43 k std)

$$R_b = 1\text{ M}\Omega \quad \left. \right\} \text{large; not much current flow to gate.}$$

$$C = 100\text{ nF}$$


To demodulate output: of-Amp.

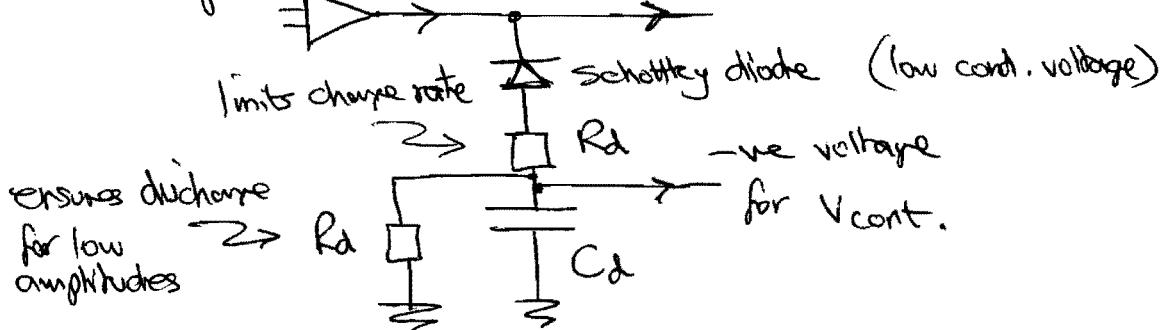

$$\text{choose } 0.1s = 2.2 C_d R_d \quad [t_{rise} \approx 2.2 CR]$$


$$\therefore \underline{C_d = 10\mu F} \quad \therefore \underline{R_d = 9.1\text{ k}\Omega \text{ or } 10\text{ k}\Omega} \quad [20^\circ]$$

2(a) (i)

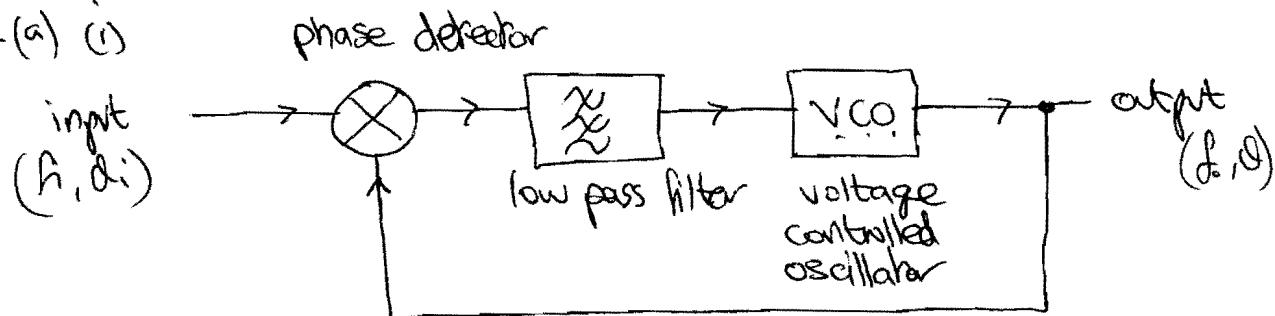

An oscillator in the PLL has its output compared in phase (and freq.) to an input signal by the phase detector (mixer). The output voltage from the phase detector is proportional to the phase diff. between the input and oscillator. The low pass filter passes the dc component of this to the VCO, which increases the output frequency (advances phase) until the phases match. The low pass filter gives the output freq. "inertia" i.e. it can free-wheel for a while if the input disappears. Putting digital freq dividers at the input and/or in the feedback path enables frequency multiplication & division to be achieved.

[20%]

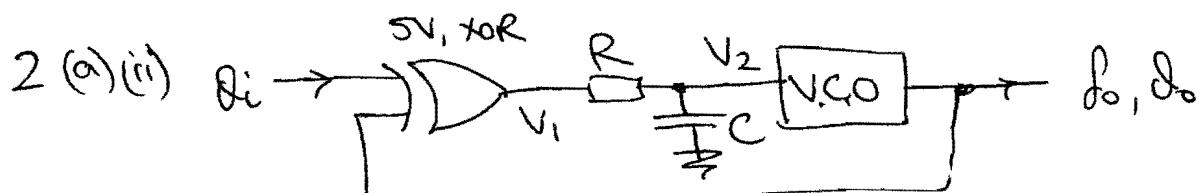

$$V_1 = k_p(\delta_o - \delta_i)$$

phase det.

$$2\pi f_o = \frac{d\delta_o}{dt} = j\omega \delta_o = k_o V_2$$

v.c.o.

$$\frac{V_2}{V_1} = \frac{1}{1 + j\omega CR}$$

RC low pass filter

$$\therefore j\omega \delta_o = \frac{V_1 k_o}{(1 + j\omega CR)} \Rightarrow j\omega \delta_o = \frac{k_o k_p (\delta_o - \delta_i)}{(1 + j\omega CR)}$$

$$j\omega \delta_o - \omega^2 CR \delta_o - k_o k_p \delta_o = -k_o k_p \delta_i$$

$$\Rightarrow \omega^2 \frac{CR}{k_o k_p} \delta_o - j\omega \frac{1}{k_o k_p} \delta_o + \delta_o = \delta_i$$

$$2(a)(ii) \text{ contd.} \quad \text{If } \omega_n^2 = -\frac{k_0 k_p}{CR} \text{ and } c = \frac{\omega_n}{-2k_0 k_p}$$

$$\text{Then. } -\frac{\omega^2}{\omega_n^2} \dot{\theta}_o + \frac{2c}{\omega_n} j\omega \dot{\theta}_o + \dot{\theta}_o = \ddot{\theta}_i$$

$$\text{Since } \dot{\theta}_o = e^{j(\omega t + \theta)} \quad \text{then } \omega^2 \dot{\theta}_o = \ddot{\theta}_o \\ j\omega \dot{\theta}_o = \dot{\theta}_o$$

$$\therefore \underbrace{\frac{\dot{\theta}_o}{\omega_n^2} + \frac{2c}{\omega_n} \dot{\theta}_o + \dot{\theta}_o}_{\ddot{\theta}_i} = \ddot{\theta}_i \quad \text{pgs. 8 & 9 of mechanics d/back}$$

For 10% overshoot, $c \approx 0.55$ from graph on pg 9

$$\text{with } k_0 = 1 \text{ MHz/V} = 2\pi \times 10^6 \text{ rad/s/V}$$


$$k_p = 5V \text{ for } \pm 180^\circ = \frac{5V}{\pi \text{ rad}} = \pm 1.59 \text{ V/rad.}$$

(-ve in
this case
for stability)

$$\therefore 0.55 = \frac{\omega_n}{2\pi \times 10^6 \cdot 1.59 \cdot 2} \quad \text{and } \omega_n = \sqrt{\frac{2\pi \times 10^6 \cdot 1.59}{CR}} = 11 \times 10^6 \text{ rad/s}$$

$$\therefore CR = 82.7 \text{ ns} \quad [55\%]$$

2(b)

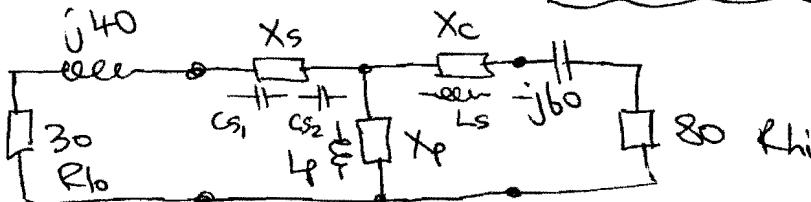

Need to cancel reactive components with series L or C, and combine those for minimum parts where possible.

$$\alpha = \frac{R_{hi}}{X_p} = \frac{X_s}{R_{hi}} = \sqrt{\frac{R_{hi}}{R_{hi}} - 1} = \sqrt{\frac{80}{30} - 1} = 1.291$$


$$\therefore X_p = j62 \Omega \quad \text{we know } \therefore \omega L = 2\pi f L_p = 62 \quad \therefore L_p = 11.4 \text{ nH}$$

$$X_c = j60 \Omega \quad = \text{inductor } L_s = 11.0 \text{ nH}$$

$$C_{S1} = -j40 \Omega \quad \therefore \frac{1}{2\pi f C_{S1}} = 40 \quad \therefore C_{S1} = 4.58 \text{ pF} [25\%]$$

$$C_{S2} = j30 \times 1.291 = j38.7 \Omega \Rightarrow C_{S2} = 4.73 \text{ pF}$$
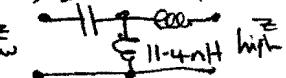
$$\therefore \text{in series} = 1 \text{ capacitor } C_S = 2.33 \text{ pF}$$



3(a) Gain, $G = \frac{\text{Max power radiated per unit area}}{\text{power per unit area from isotropic antenna}}$

Effective Aperture, A_e : power delivered to a matched load
(Area) by an antenna = $A_e \times \text{power density}$
in incident radio wave

Radiation Resistance, R_r : power radiated = $\frac{1}{2} I^2 R_r$, where
 I is current feed to antenna

[Radiation Efficiency] : proportion of power radiated by an antenna relative to power input
 $= \frac{R_r}{(R_r + R_{ohm})}$

Antenna eqn. $G = \frac{4\pi A_e}{\lambda^2}$ [15%]

3(b)  speed of light in PTFE, $\epsilon_r = 2$
 $v = \frac{C_0}{\sqrt{\epsilon_r}} = 2.12 \times 10^8 \text{ m/s}$

$$v = f\lambda = 2.12 \times 10^8 = 86.8 \times 10^6 \lambda \quad \therefore \lambda = 0.244 \text{ m}$$

$$\text{For efficient antenna patch, length} = \lambda_2 = \underline{\lambda} = 0.122 \text{ m}$$

For microstrip track, $C/\text{unit length} = \frac{(w+2d)\epsilon_0\epsilon_r}{d}$

$$v = \frac{1}{\sqrt{LC}} \quad \text{and} \quad Z_0 = \sqrt{\frac{L}{C}} \quad \Rightarrow \quad \sqrt{L} = \frac{1}{v\sqrt{C}} \quad \text{and} \quad Z_0 = \frac{1}{v\sqrt{C}}$$


$$\therefore Z_0 = \frac{\sqrt{2}}{C_0} \cdot \frac{d}{(w+2d)\epsilon_0\epsilon_r} = 73 = \frac{1.2}{(w+2.4)\epsilon_0\epsilon_r} \frac{\sqrt{2}}{3 \times 10^8}$$

$$8.884 \times 10^{-2}$$

$$\therefore w = 1.98 \text{ mm}$$

[30%]

3(c)

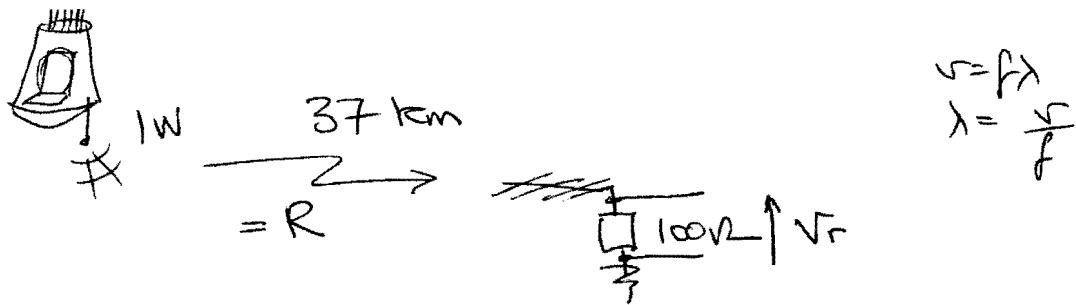

Power density at Rx antenna = $\frac{1 \text{ W}}{4\pi R^2}$ = 58.1 pW/m²
 (assuming isotropic G=1 @ Tx)
 or G=1.5 dipole, G=3 dipole w/ 12 spheres

Gain of antenna = 20dB = x100 = G = $\frac{4\pi A_e}{\lambda^2}$

$\lambda @ 868 \text{ MHz in air} = \frac{3 \times 10^8}{868 \times 10^6} = 0.346 \text{ m}$

$\therefore A_e = \frac{100 \cdot 0.346^2}{4\pi} = 0.95 \text{ m}^2$

$\therefore \text{Power from antenna} = 0.95 \times 58.1 \times 10^{-12} \text{ W} = \frac{v_r^2}{100}$

$\therefore \text{Signal, } v_r = 74.3 \mu\text{V} \text{ into matched } 100\Omega \text{ resistor}$
 (or 148.6 μV into open circuit) [25%]



3(d) Skin depth, $\delta = \sqrt{\frac{2}{\omega \mu_0 \sigma}} = \sqrt{\frac{2f}{2\pi f \mu_0}}$ @ 868 MHz in Cu
 $\delta = 2.96 \mu\text{m}$

$\therefore \text{dime resistance of patch } R_{\text{ohm}} = \frac{\rho L}{A} = \frac{3 \times 10^8 \cdot 0.122}{2.96 \times 10^6 \cdot 10 \times 10^{-3}} = 0.124 \Omega$

$\therefore \text{Radiation Effic.} = \frac{R_r}{R_r + R_{\text{ohm}}} = \frac{100}{100 + 124} = 99.88\%$ [20%]

3(e) With linear polarisation, the antennas can be orthogonal giving rise to poor coupling. A pair of antennas at 90° at the base station, with outputs coupled via a 90° phase shift (by posn or cable length) will create a circular polarisation reception (could also do for Tx) - so no orientation null is seen. Can also be achieved with twin fed or nulled patch. [10%]

4(a)

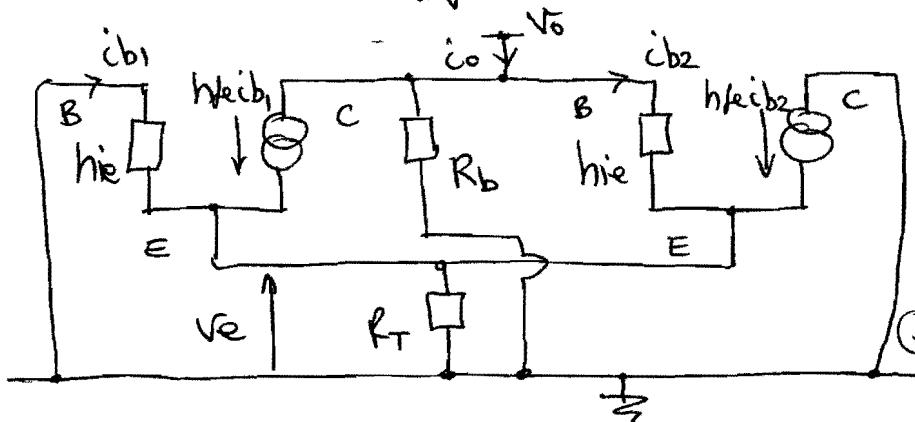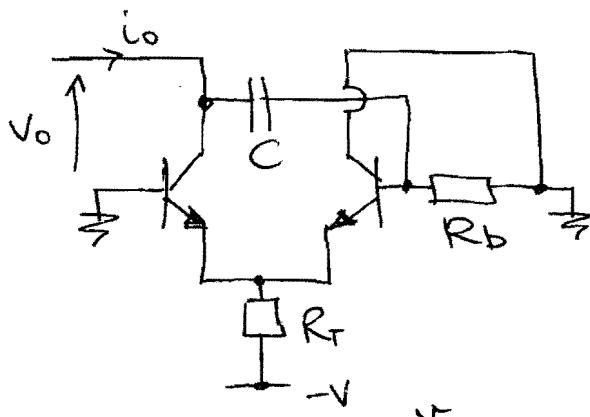

$$\textcircled{1} \quad i_b = \frac{-V_e}{h_{ie}}$$

$$\textcircled{2} \quad i_b = \frac{V_o - V_e}{h_{ie}}$$

$$\textcircled{3} \quad V_e \approx R_T \cdot h_{ie} (i_b + i_b)$$

$$\textcircled{4} \quad i_o = h_{fe}i_b + i_b + V_o / R_b \quad \text{substituting } \textcircled{1} \text{ and } \textcircled{2} \text{ into } \textcircled{3}: -$$

$$V_e = -\frac{R_T h_{fe} V_e}{h_{ie}} + R_T h_{fe} \frac{V_o}{h_{ie}} - R_T h_{fe} \frac{V_e}{h_{ie}}$$


$$\therefore V_e \left(1 + 2 \frac{R_T h_{fe}}{h_{ie}} \right) = R_T h_{fe} \frac{V_o}{h_{ie}} \quad \therefore V_e \approx \frac{V_o}{2} \quad \textcircled{5}$$

sub. \textcircled{1} and \textcircled{2} into \textcircled{4} and sub. for V_e using \textcircled{5}

$$\therefore i_o = -\frac{h_{fe} V_o}{2 h_{ie}} + \underbrace{\frac{V_o}{2 h_{ie}}}_{\text{small}} + \frac{V_o}{R_b} = V_o \left(\frac{1}{R_b} - \frac{h_{fe}}{2 h_{ie}} \right)$$

$$\text{with } r_e = h_{ie}/h_{fe} \Rightarrow Z_o = \frac{V_o}{i_o} = \underbrace{\left(\frac{1}{R_b} + \frac{1}{2r_e} \right)^{-1}}_{= R_b || 2r_e} \quad [40\%]$$

4(b)

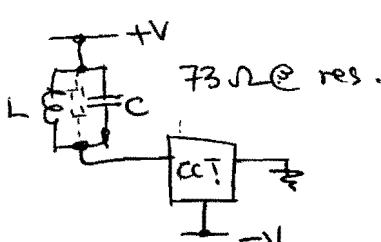

For 1W power across 73 ohm:

$$I = \frac{V^2}{R} \Rightarrow V = 8.5 \text{ V rms} \\ = 24 \text{ V p-p}$$

Hence supply must be 36V say

\therefore put +V at 24V and -V at -12V


4(b) contd. for 73Ω impedance, we need a -ve resistance of say -35Ω to be sure it is unstable $\therefore R_e = 18\Omega$ say
 $R_b = 1k\Omega$ choice arb. $C = 100\text{ nF}$ choice arb.

$$R_e = 18 = \frac{V_e}{I_e} \Leftrightarrow 0.025 \quad \therefore I_c = 1.4 \text{ mA}$$

\therefore current thro' $R_T \approx 2.8 \text{ mA}$ with p.d. $= (12 - 0.6)\text{V}$

$$\therefore R_T = 4.1 \text{ k}\Omega \quad (3.9 \text{ k}\Omega \text{ say}) \quad [20\%]$$

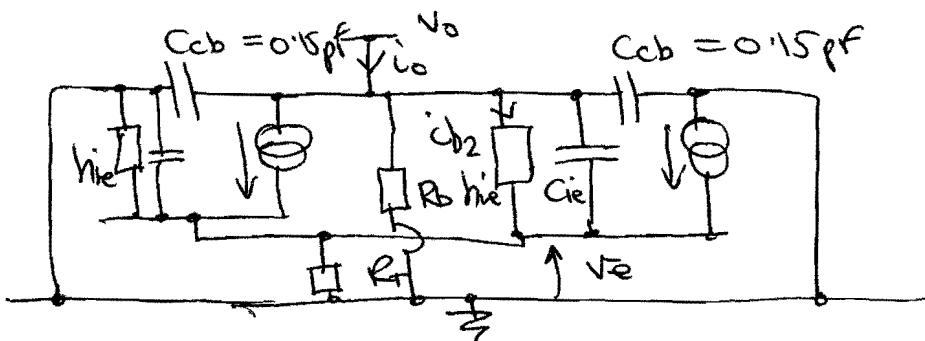4(c) Consider small sig. model @ i_o/v_o node:



$$R_e = 18 \Omega \quad f_t = 22 \times 10^9 = \frac{1}{2\pi R_e C_{ie}} \quad \therefore C_{ie} = 0.40 \text{ pF}$$

as $v_e = v_o/2$ then effective $C_{ie} = \frac{0.40}{2} = 0.20 \text{ pF}$ to gnd.

\therefore total capacitance @ input $= 0.15 + 0.15 + 0.20 = 0.50 \text{ pF}$

$R_b = 1k\Omega$, $h_{ie} = h_{fe} \times R_e = 4500 \Omega$ \therefore dominating low impedance $= 73\Omega$ from antenna

$$f_{-3\text{dB}} = \frac{1}{2\pi \sqrt{73 \cdot 0.5 \times 10^{-9}}} = 4.36 \text{ GHz} \quad [25\%]$$

4(d) Use a varactor with nominal $C_v = \frac{1}{(2\pi f)^2 L} \Leftrightarrow 10 \times 10^{-9} \text{ H}$
 $C_v = 3.36 \text{ pF}$ $\inf \text{ inf F (big)}$ $\frac{1}{(2\pi f)^2 L} \Leftrightarrow 868 \times 10^6 \text{ Hz}$

