 



2004  
4B7 Q1

Dr. 1.2.2004

 
a) Complementary MOS technology has the decisive advantage over NMOS that either the p channel or the n-channel transistor is off at any time and the current drawn is small (except at the switch transient)



In addition to Low Power the technology also has a wide margin of device operation. Hence VLSI can be successful.




 The fabrication technology is more complex than NMOS but now it is well established and dominant.



three input NAND  $E = \overline{A \cdot B \cdot C}$   
 upper right p-type for PMOS  
 lower right n-type for NMOS  
 upper left n-type for ohmic to substrate  
 lower left p-type for ohmic to p-well

 All three n channel gates have to be high to connect VSS to out.



In self aligned technology the polysilicon gate is in place when the n+ source and drain implants are performed with a result that the undoped channel is only the region under the gate i.e. self aligned. The lithographic step for the gate therefore defines the distance xy which determines the switching speed from the carrier transit time



2004 4B7 Q1 (continued)

The electrical width is determined by the active area. Dfm 1.2.2004

In this case  $\frac{\text{width p-channel}}{\text{width n-channel}} = \frac{2}{3}$

Worst case rise time is with 1 p-channel device conducting.

" " full time is the series connection of 3 n-channel devices.

But  $\frac{\text{electron mobility}}{\text{hole mobility}} = 2$


Hence  $\frac{\text{rise time}}{\text{fall time}} = \frac{3}{2} \times \frac{1}{3} \times 2 = 1$  Equal

d) Truth table

	A	0	1
B	0	1	0
	1	0	1


confirm that output is only low when both inputs are different

 confirm that no input combination gives a conduction path right through



The layout can be simple two active regions. (shown as outline H)

The polysilicon gates are shown dotted.

 

Worst case output rise time is through 2 p devices in series.

Worst case fall time is through 2 n devices in series.

i.e. equalize the worst case times by choosing transistor widths in inverse proportion to the electron and hole carrier mobilities.

2004 4B7 Q2 (continued)

Dfm 1.2.2004\*

An inverting device is required in the ring and the 11 member example has a period corresponding to  $2 \times 11 \times \tau = 22\tau$  where  $\tau$  is the single gate delay. As seen with the 0.1.010 sequence an odd numbered ring is unstable giving oscillations which are observed through a buffer device. Practical devices are slower than unloaded ring oscillators.


c) The power/stage goes from  $30 \mu\text{W}$  at  $2\text{V}$  to  $0.2 \mu\text{W}$  at  $0.4\text{V}$ .

As the power supply is reduced towards threshold the ring frequency goes linearly down.

$V_{dd}$	1V	0.7	0.5	0.4
Delay (ps)	34ps	55	100	200
$\sqrt{\text{Delay}}$ (1000ps)	29	18	10	5

Extrapolated threshold  $\boxed{0.25\text{V}}$

(1000ps)  
delay

 

- d) Let  $C$  be input capacitance of  $n+p$  gates  
 $n$  number of gates in the ring  
 $V$  power supply  $V_{DD}$   
 $P$  the power per gate in the ring

The energy dissipated when a gate is either charged or discharged is  $\sim CV^2$

the frequency at which the voltage is either switched up or down is  $\frac{1}{n\tau}$

Hence  $P = \frac{CV^2}{n\tau}$  modelling as a simple capacitor

$$\therefore C = \frac{PA\tau}{V^2} = \frac{1 \times 10^{-6} \times 101 \times 55 \times 10^{-12}}{0.7 \times 0.7} = 11 \times 10^{-15} \text{ F}$$

But total area of  $p+n$  channel transistor gates is  $(3 \times 10^{-6} + 4 \times 10^{-6}) \times 100 \times 10^{-9} = 7 \times 10^{-13} \text{ m}^2$


Simple capacitor  $C = \frac{A\epsilon_0\epsilon_r}{d}$  take  $\epsilon_r = 4$  for  $\text{SiO}_2$   
 $\epsilon_0 = 8.9 \times 10^{-12}$

$$\therefore \text{oxide thickness } d = \frac{A\epsilon_0\epsilon_r}{C} = \frac{7 \times 10^{-13} \times 8.9 \times 10^{-12} \times 4}{11 \times 10^{-15}} = 2.3 \times 10^{-9}$$

Assuming no stray capacitance or ignoring the interconnect line capacitance the gate oxide thickness is  $\boxed{2.3 \text{ nm}}$  which is physically reasonable.

 a) Scaling CMOS devices involves reducing all the device dimensions the most important of which is the source drain distance.

This brings the benefits of reduced device switching speed and increased circuit density allowing more devices on a chip and fewer interconnections.



The figure of power supply voltage vs. FET channel length shows how  $V_{DD}$  is of order 1 volt for  $0.05 \mu\text{m}$  devices. There has to be a corresponding scaling down of the threshold voltage to ensure successful device operation.

(i) Gate oxide thickness is reduced to maintain device operating currents.


In memory devices the leakage current per device is important for determining system power in the off state. Here the most aggressively small gate-drain distance is not necessarily used.

(ii) For high performance devices in microprocessors short switching speed is more important than low leakage current, and the shortest feasible source-drain distances are used.

One physical limit is tunnelling through the gate insulator which can lead to an unacceptable mixing of the controlling fluid (electrons) with the controller fluid (channel charge). Using higher dielectric materials than  $\text{SiO}_2$  can alleviate this problem to enable high specific capacitance and low tunnel currents at the same time.

In the 5 year time scale CMOS technology is going to be governed by the cost and practicality of deep UV photolithography rather than physical device limits and line width will be reduced towards 50 nm.

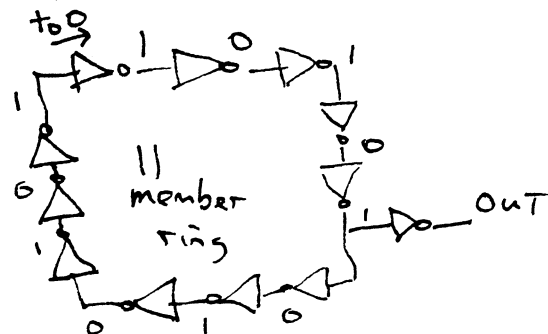b) Ring oscillator circuits have a lower frequency output than single gates and measurement via a low frequency output pad to a frequency counter is possible.



2004 4B7 Qn3 (i) (Rather more detailed than expected from candidates)

The gain stage in a typical OA is a differential amplifier with high voltage gain but low power capability. An output stage is required to provide:-

- high current gain (limited voltage gain acceptable)
- distortion-free amplification
- efficiency
- protection from loading effects including short circuit

In CMOS there are various ways to accomplish this, eg.

- source follower (unity voltage gain)
- class A amplifier (various forms including class B "push-pull")

In this (class A, single-ended) design, power consumption is to be minimised by sizing the devices to deliver the smallest standing currents necessary to deliver the required slew rate.

Slew rate is determined from available op current:

$$i = C_L \frac{dV_{out}}{dt}$$

The current needed to charge/discharge  $C_L$  at the given rate:-

$$i_s = \pm 40 \times 10^{-12} \times 20 \times 10^6 \text{ A} = 0.8 \text{ mA}$$

M2 is provided with fixed gate bias  $V_{gs} = 0\text{V}$ . Hence  $V_{es2}$  is  $-3\text{V}$ . We assume all the current available from M2,  $i_{d2}$  can be available to charge  $C_L$ , i.e. that M1 draws negligible current while this happens. WDS also assume that  $V_{out} = 0$  (the middle of the required range,  $\pm 1\text{V}$ ). Hence  $V_{DS} = -3\text{V}$ .

M2 is always in saturation mode. Rearranging the S-H eqn: provided  $V_{out} < +1\text{V}$

2004 4B7 Qn 3 (2)

$$W_2 = L_2 \cdot \frac{i_{D2}}{\frac{1}{2} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \mu E / \text{tox}}$$

$$\frac{W_2}{L_2} = \frac{0.8 \times 10^{-3}}{\frac{1}{2} (-3 + 1)^2 (1 + 0.02 \times (-3)) \times 10^{-5}} = \frac{160}{4 \times 0.94} = 42.5$$

Under quiescent conditions,  $M_1$  draws the same current; however, since  $M_2$  delivers  $0.8 \mu A$  over the whole of the range while in saturation,  $M_1$  must be sized for  $1.6 \mu A$  to allow  $C_L$  to be discharged at the required rate.

When  $V_{out} = 0$ ,  $V_{DS1} = 3V$ .  $M_1$  will stay in saturation provided  $V_{GS1} < V_{DS1} + V_T$ , or  $+4V$ . Considering the other key points:

not required in answer

$V_{out} (V)$	$V_{DS1} (V)$	Limit $V_{GS1}$ for Sat (V)	$V_{in} (V)$
+1	4	5	+2
0	3	4	+1
-1	2	3	+0

In the worst case, if  $V_{GS1} = 3V$  while  $V_{out}$  is  $0V$ , the size for  $M_1$  should be chosen as:-

$$\frac{W_1}{L_1} = \frac{1.6 \times 10^{-3}}{\frac{1}{2} (3-1)^2 (1 + (0.01) \times 3) \times 1.8 \times 10^{-5}} = \frac{320}{4 \times 1.03 \times 1.8} = 172.6$$


not eq. n NBS

Other assumptions, eg.  $V_{GS1} = 4, 5$  can be justified. Note that if  $V_{GS}$  is  $+5V$ ,  $i_{d1} = (5-1)^2 / (3-1)^2 = 4 \times$  as great

NB DC output voltage is highly dependent on precise control of  $V_{GS1}$ . The biasing arrangements of  $M_1$  are not shown but are critical.


A real ckt needs a self-bias arrangement to define quiescent values for  $V_{in}$  and  $V_{out}$ . Current negative feedback can achieve this.

## 2004 Qn 3(3)

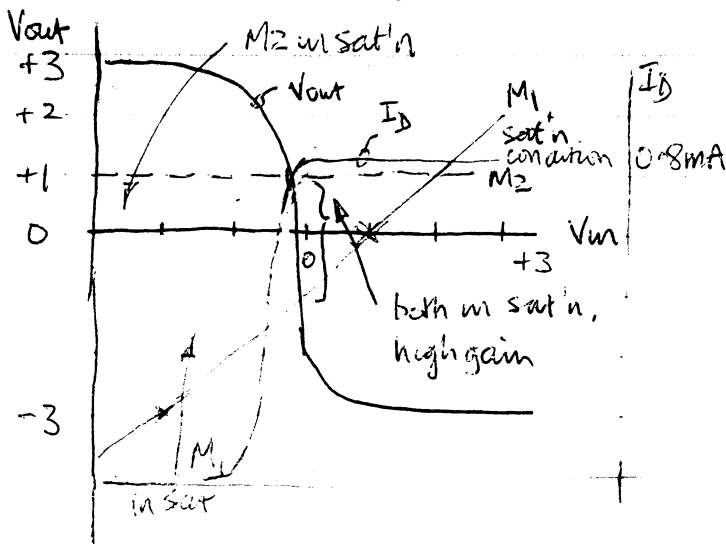

Note that the req. range of outputs  $\pm 1V$  can be accommodated while both devices stay in saturation - just!

 To calculate  $s_f$  gain, note the ssec for the o/p



$$g_{ds} = I_D \lambda$$


$$g_m = \sqrt{2 \frac{\mu C}{t_{ox}} \frac{W}{L} I_D}$$

We will assume  $I_D = 0.8mA$  quiescent

$$\begin{aligned} \text{SS gain} &= - \frac{g_{m1}}{g_{ds1} + g_{ds2}} = - \frac{\sqrt{2 \times 10^{-5} \times 172.6 \times 0.8 \times 10^{-3}} \times \frac{1}{0.01 + 0.02}}{\sqrt{2 \times 172.6 \times 0.8} \times \frac{1}{0.03}} = -55.4 \end{aligned}$$

$$\begin{aligned} r_{out} &= r_{ds1} \parallel r_{ds2} = \frac{1}{0.8 \times 10^{-3}} \times \frac{1}{0.01 + 0.02} \\ &= 41.67 k\Omega \end{aligned}$$

 Considering the Thevenin eqvt of the output




For  $-3dB$  pt,  $\text{Re}al = \text{Im}ag$

$$\begin{aligned} \omega_3 CR &= 1 \\ \omega_3 &= 1 / (40 \times 10^{-12} \times 41.7 \times 10^3) \rightarrow 95 \text{ kHz} \end{aligned}$$

This can be improved by reducing  $r_{out}$  - can be achieved by application of  $-ve$  current feedback, which requires a resistor between output & input. This also has benefit of stabilising the bias point, but the voltage gain is reduced.


2004 4B7 Qn4 (1) (More detailed than expected from candidates)

 A transmission gate in CMOS comprises a pair of complementary transistors with source & drain regions strapped together



The gates are driven with complementary signals  $C, \bar{C}$ . When  $C=1, \bar{C}=0$ , both the p & n device conduct. In the opposite state both are non-conductive. NB the device is bilateral when seen from I or O - it can conduct in either direction.

 To understand the performance issue, consider a single n-channel pass-transistor used as a switch. The n-type device conducts when



C is high, non-conductive when C is low. To allow a channel to form  $V_{GS}$  must be greater than  $V_t$ .

If C is set to logic 1 =  $V_{DD}$ , then if I is also driven to  $V_{DD}$ , O cannot rise above  $V_{DD} - V_t$ , typically a drop of  $\sim 1$  volt. Thus O would be a 'weak' version of the high at I. Note that a logic low is transferred reliably to O without offset. As a result of the logic 'drop' it is unpracticable to cascade single transistor switches. A similar state of affairs is found for the p-type device, which can transfer a logic 1 without offset, but a logic 0 is transferred only weakly, with 'rise' of  $|V_t|$ .

By combining the two devices in parallel a switch can be made which has neither problem.

TT for T/gate

I	C	O
0	0	Z
1	0	Z
0	1	0
1	1	1


Z means high impedance

Hence a near-perfect digital switch can be achieved with only two devices

In digital cts a t-gate may be used to realise a multiplexer. They are commonly used to control feedback paths & signal paths in sequential gates e.g. dynamic S-type FF



2004 - 4B7 Qn 4 (2)

 

Advantages:

- low device count for MUX / FF etc
- bilateral characteristic
- high performance, no losses
- can be cascaded

Disadvantages:


- A passive device - does not regenerate logic levels
- requires complementary control signals (extra logic)
- May be sensitive to clock dispersion or skew, charge sharing

In analogue ccts t-gates may be used in switches, multiplexers for linear signals, sample holds, DA converters.

Advantages:

- Efficient switch with low  $\sigma$ /set voltage
- good frequency response
- Good ratio  $R_{off}/R_{on}$
- Compact structure

Disadvantages

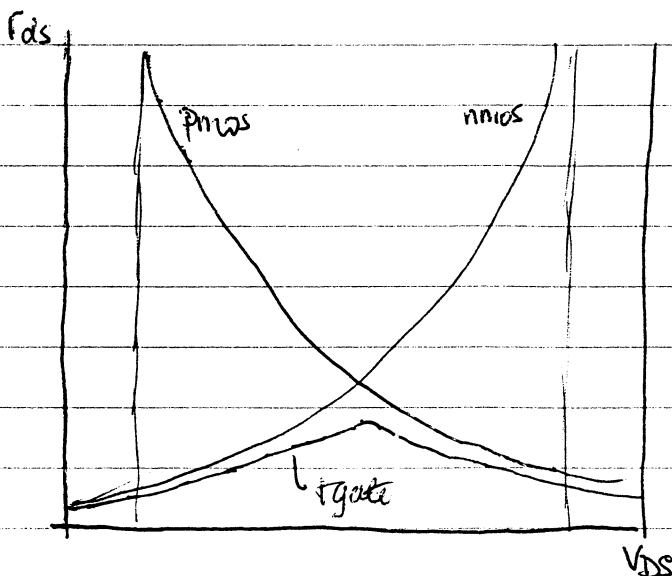

Notwithstanding above comments, the effective resistance of the paralleled devices in a tgate is significant and varies with applied voltage. In sensitive linear applications this can cause distortion


Effective channel resistance of p,n devices and t-gate

Input pad structures are required to protect MOSFET inputs from:

- over & undervoltages
- consequential latchup conditions
- electrostatic discharge

Gate oxide thicknesses in modern processes are  $\sim 30\text{nm}$  thick with breakdown voltages around  $10\text{V}$ . Input resistances may exceed  $10^{12}\ \Omega$ . Since the gate electrode typically has capacitance of a fraction of a pF, only a small packet of charge is required to generate voltages far in excess of  $V_{\text{breakdown}}$ . The human being is often modelled (for evaluation of static 'risk') as a capacitance  $\sim 100\text{pF}$  charged to  $\sim 1.5\text{kV}$  in series with a resistance of a few k $\Omega$ . The energy available is sufficient to vaporise a considerable volume of Si.

 
Protection can be achieved with the ckt below:



R may be implemented as a strip of poly Si 20-100 sq. long

Diodes become fwd biased as

 $V_{\text{pad}}$  exceeds  $V_{\text{DD}} + 0.7$ ,  $V_{\text{SS}} - 0.7$  sinking excess current to the rails



Diodes are provided with guard rings & generous well/substrate taps to minimise carrier injection

C is parasitic capacitance due to D & E

Selection of values is necessarily a compromise. Excessive RC will give good protection, but will delay legitimate digital edges and cause slower rise/fall

Often punch-through devices are used in place of the diodes (very short, closely spaced S<sub>d</sub>D, no gate, which avalanche at  $\sim 10\text{V}$ )

2004 4B7 Qn 5 (i) (More detailed answer than exp. from candidates)

The threshold voltage  $V_T$  of a MOSFET is that potential which must be applied between gate and source in order to bring about strong inversion within the channel. There are three main components to this potential:

- $\Phi_{sc}$ , the difference in work functions between the gate material and the Si substrate on the channel side
- a negative potential arising from the existence of undesired positive charge within the gate oxide and at the oxide/substrate interface. - referred to as  $Q_{ox}$ , and assumed to reside entirely at the interface
- a voltage  $-2\Phi_F - Q_B/C_{ox}$  needed
  - (a) to bring the surface potential to the strong inversion condition
  - (b) to offset the induced depletion layer charge,  $Q_B$  i.e., to 'unbend' the energy bands that result when the MOS system is first brought together, and to bring the surface potential  $\phi_s$  to be equal to  $\phi_F$

In essence, the originally p-type s/c becomes n-type with this gate potential applied. Further increases in  $V_{gs}$  produce only slight change in surface potential  $\phi_s$


Hence the main factors determining  $V_T$  are:

- Materials used for the gate electrode (Al or polysi), determining its work function
- properties of the dielectric used for the gate insulator, fixing the capacitance  $C_{ox}$ ; its thickness  $t_{ox}$
- channel dopant density
- impurities, defects, dangling bonds etc at Si-SiO<sub>2</sub> interface
- potential between source and substrate - which acts as a second, or "back"-gate
- temperature

2004 487 Qn 5 (2)

The 'flash' memory has a very simple structure, akin to that of the one-transistor DRAM cell, except that no storage capacitance is required. This leads to a compact layout. The design stores data through use of an unusual MOS structure which allows the threshold voltage of the FET to be modified electrically, in a non-volatile manner.

 In the transistor structure an extra floating gate is interposed between the gate & channel.




The dielectric that separates the upper (control) gate from the floating gate is typically an oxide-nitride-oxide sandwich. I.e. the floating gate is electrically isolated, but is capacitively coupled to the control gate and to the substrate.

Writing data involves 'programming' the floating gate and hence adjusting the FET to have two or more different threshold voltages  $V_T$  relative to the control gate. If the floating gate contains a large electronic charge, the device has a higher  $V_T$ . This is regarded as the '1' state.

If the charge is removed from the floating gate, the MOSFET has a lower  $V_T$  - the device is in the '0' state.

## 2004 4B7 Qn 5(3)

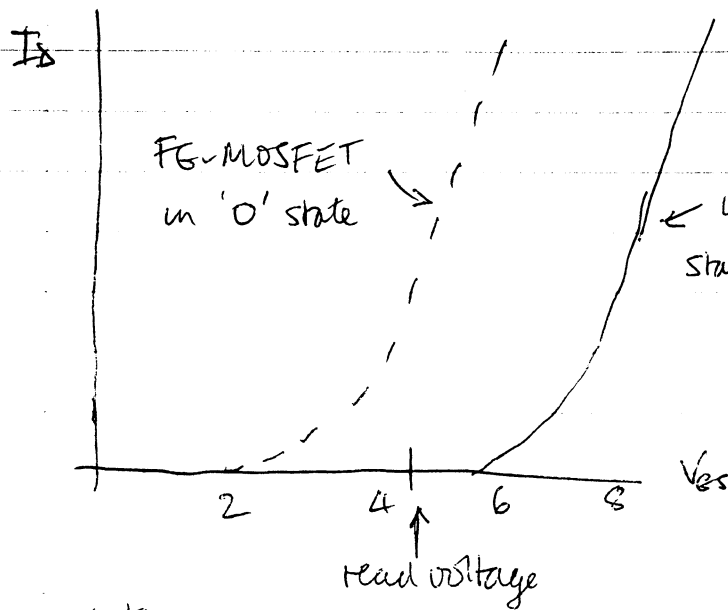

### Advantages:-

- Compact, high density
- Non-volatile
- No capacitor needed
- Less sensitive to charge sharing and noise

### Disadvantages

- More complex process,
- Slower write operation
- Need for higher voltages

### Writing

Transferring charge into the FG by 'hot carrier' effects. A high field is applied to the drain and gate so the device is in saturation. The carriers in the pinch-off region are then 'hot' - highly energetic - and a proportion of them are scattered into the floating gate. This action can be enhanced by thinning the gate oxide in the vicinity of the drain. Once in the floating gate, electrons are trapped in a potential well and remain so indefinitely, or until the cell is erased.

Erase involves removing charge. This is achieved by inducing Fowler-Nordheim tunnelling between FG & source. The gate is grounded and the source taken to a high voltage. This allows electrons to tunnel through the oxide barrier from the FG to the source.

### Reading

This is done by observing the channel current with a suitably chosen gate voltage (read voltage) to discriminate the state. For the device above a suitable value would be c. 4.5V.

A moderate voltage, say 3V, is applied to the gate.

- If the device is in the '1' state, negligible current flows
- If " " " '0' state,  $V_{GS}$  exceeds  $V_t$  and current flows

This concept can be extended to give devices with e.g. 4 or even 8 different  $V_t$ s, allowing 2 or 3 bits to be stored in one cell.