

ENGINEERING TRIPOS PART IIB

Monday 19 April 2010 9 to 10.30

Module 4B2

POWER MICROELECTRONICS

*Answer not more than **three** questions.*

All questions carry the same number of marks.

*The **approximate** percentage of marks allocated to each part of a question is indicated in the right margin.*

There are no attachments.

STATIONERY REQUIREMENTS

Single-sided script paper

SPECIAL REQUIREMENTS

Engineering Data Book

CUED approved calculator allowed

You may not start to read the questions printed on the subsequent pages of this question paper until instructed that you may do so by the Invigilator

1 Fig. 1 shows a simplified inductive switching circuit for a high voltage system such as a Switch Mode Power Supply (SMPS),

(a) Assuming that the switch is ideal, draw the current and voltage waveforms of the PIN diode, D_f , during reverse recovery operation. [30%]

(b) Assume now that the switch is a Power MOSFET and its waveforms are as shown in Fig. 2. The switch operates at a switching frequency of 10 kHz with a duty cycle $D = 50\%$. The other parameters are: $V_{dc} = 300$ V, the off-state leakage current I_{OFF} can be neglected ($I_{OFF} = 0$), the on-state current $I_{ON} = 1$ A, the on-state voltage $V_{ON} = 5$ V, the turn-on current rise time $t_r = 0.1$ μ s, the turn-on voltage fall time $t_d = 0.1$ μ s, the turn-off delay time $t_s = 0.1$ μ s, the turn-off voltage growth time $t_g = 0.2$ μ s, the turn-off current fall time $t_f = 0.1$ μ s.

(i) Estimate the static, switching and total power losses in the switch [40%]

(ii) Comment on the switching versus on-state losses. What would be the effect of increasing the switching frequency on the overall losses? [10%]

(iii) Give one system advantage and three disadvantages of increasing the switching frequency in the SMPS. [20%]

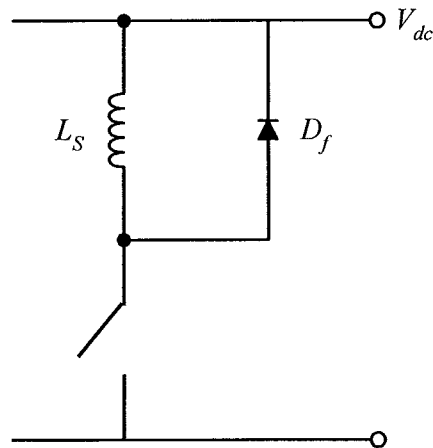


Fig. 1

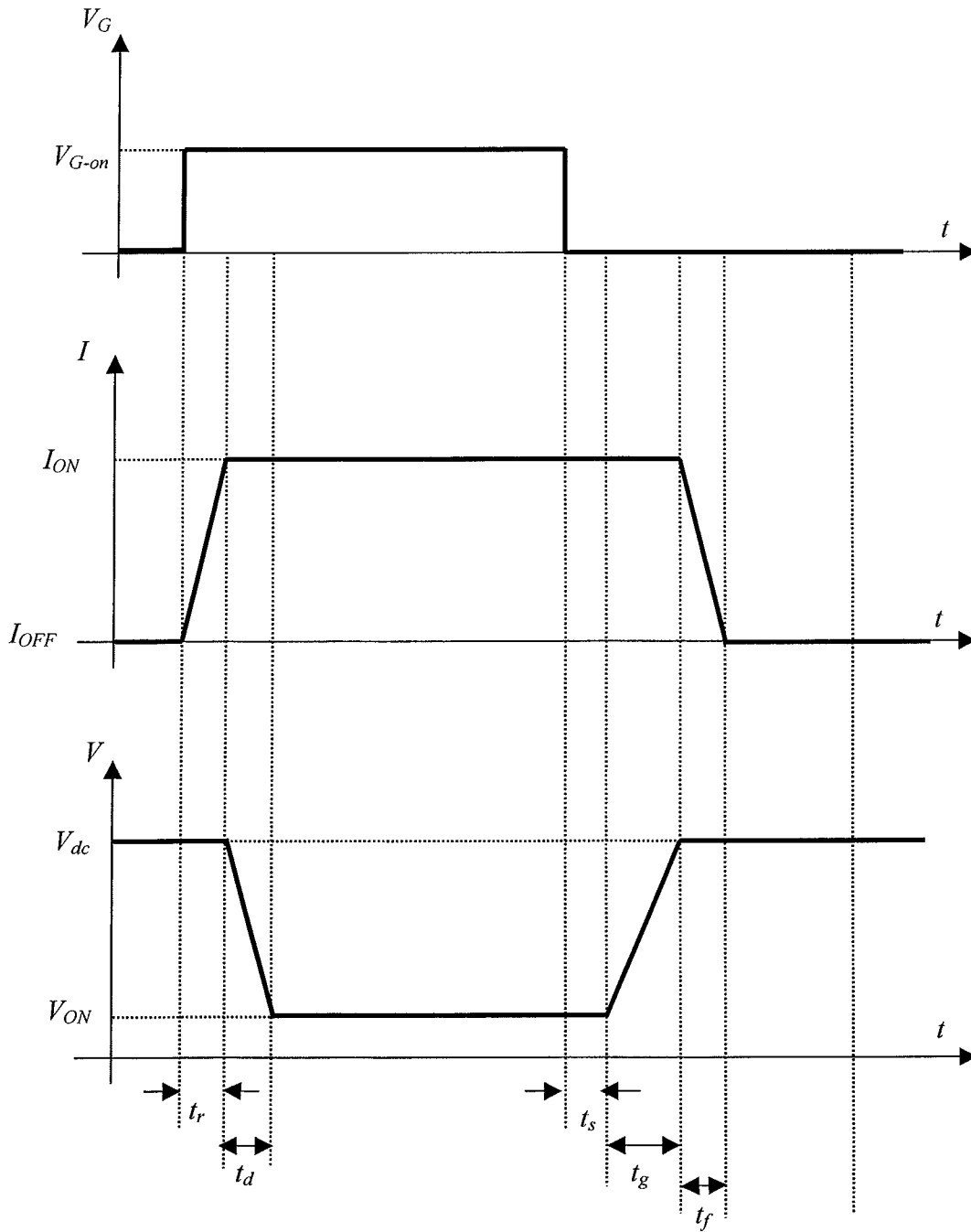


Fig. 2

2 (a) Explain the dV/dt effect in thyristors. Give two solutions to improve the dV/dt ratings and discuss their advantages and disadvantages. [40%]

(b) Table 1 shows some material parameters for a Silicon Power MOSFET and a Diamond Power MOSFET. Both designs are optimised to have a specific drift on-state resistance of $10 \text{ m}\Omega\text{cm}^2$.

Calculate the relative increase in the breakdown voltage of the Diamond MOSFET with respect to that of the Silicon MOSFET. State any assumptions made. [40%]

Given the result obtained, give four reasons why diamond MOSFETs are not commercially available. [20%]

	Silicon	Diamond
Critical Electric field, E_{cr} [V/cm]	$3 \cdot 10^5$	$2 \cdot 10^6$
Relative permittivity, ϵ_r	12	9
Electron mobility, μ_n [$\text{cm}^2/(\text{Vs})$]	1200	800

Table 1

You may assume the following equations in the calculations of breakdown and specific on-state resistance:

$$w = \left[\frac{2\epsilon_r\epsilon_0V}{q} \frac{1}{N_D} \right]^{\frac{1}{2}}$$

$$R_{\text{specific-drift}} = \frac{w_{\text{drift}}}{q\mu_n N_D}$$

where w is the depletion region width, N_D is the doping concentration of the drift region, w_{drift} is the width of the drift region, μ_n is the electron mobility in the drift region, V is the reverse voltage and the other symbols have their usual meaning.

3 The structure in Fig. 3 is a vertical MOS controllable power device with a trench gate.

(a) Explain briefly its operation during on-state, off-state, turn-on and turn-off. [40%]

(b) Draw an equivalent circuit for the device. [25%]

(c) Give one advantage and one disadvantage of this device compared to a conventional Trench Insulated Gate Bipolar Transistor (IGBT). [10%]

(d) The device in Fig. 3 is based on vertical trench gate technology. Draw an equivalent device using a lateral technology with a planar gate. Give two advantages and two disadvantages of the vertical structure compared to the lateral structure. [25%]

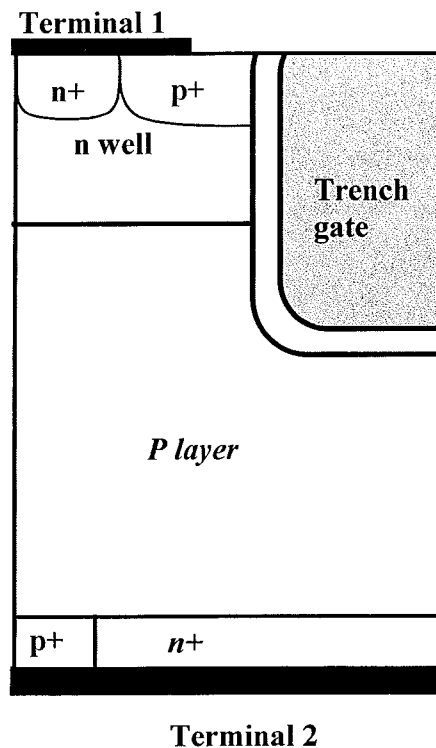


Fig. 3

4. (a) Draw schematically two AC to DC converters, first using linear electronics (LE) and second using switch mode power electronics (SMPS). Describe their operation and discuss their relative advantages and disadvantages. [40%]
- (b) Using a simplified equivalent circuit find the output voltage as a function of the rectified input voltage, the duty cycle and the turn ratio of the transformer for the AC to DC SMPS converter. State any assumptions made. [30%]
- (c) Explain the role of the feedback circuit in a flyback AC to DC SMPS controller. [10%]
- (d) Explain briefly the performance of an IGBT compared to that of a Power MOSFET in an AC to DC power supply as a function of frequency, temperature, and power. [20%]

END OF PAPER

List of Numerical answers**Question 1**

b)

$$P_{\text{on}} = 2.49 \text{ W}$$

$$P_{\text{turn-on}} = 0.30 \text{ W}$$

$$P_{\text{turn-off}} = 0.46 \text{ W}$$

$$P_{\text{total}} = 3.25 \text{ W}$$

Question 2

$$\text{b) } V_{\text{BRdiamond}} / V_{\text{BRsilicon}} = 12.17$$