

EGT2
ENGINEERING TRIPOS PART IIA

Tuesday 19 April 2016 2 to 3.30

Module 3B1

RADIO FREQUENCY ELECTRONICS

Answer not more than three questions.

All questions carry the same number of marks.

The approximate percentage of marks allocated to each part of a question is indicated in the right margin.

Write your candidate number not your name on the cover sheet.

STATIONERY REQUIREMENTS

Single-sided script paper

SPECIAL REQUIREMENTS TO BE SUPPLIED FOR THIS EXAM

CUED approved calculator allowed

Engineering Data Book

Smith Chart for question 4

10 minutes reading time is allowed for this paper.

You may not start to read the questions printed on the subsequent pages of this question paper until instructed to do so.

1 The International Space Station orbits the Earth every 93 minutes at a height of 375 km above the surface. A telecoms engineer wonders if it would be possible to make calls with a standard mobile phone onboard the space station if a suitable dish antenna has been set up on Earth, linked to a base-station. The dish would not be steerable, but would point directly upwards in a location which is periodically underneath the orbit path.

(a) Explain the terms *Gain* and *Effective Aperture* and give the formula showing how they are inter-related. What is the approximate gain of a small dipole antenna, such as that used on a mobile phone ? [15%]

(b) If the transmitted RF power from an astronaut's mobile phone is 4 W, at a carrier frequency of 2 GHz:

(i) What power density and electric field strength would be seen at the Earth's surface, ignoring any atmospheric attenuation of the signal ? [15%]

(ii) What is the required *Gain* of the dish antenna if the base-station requires a received signal strength of at least -100 dBm in order to operate ? [20%]

(iii) If the antenna drives a matched load of 75Ω , what voltage signal amplitude does this correspond to ? [10%]

(c) Given the required *Gain* above, estimate the beam angle of the dish antenna and hence, how long a telephone call could last during each overhead orbit. [20%]

(d) If the base-station is actually intended to work with a 150Ω rather than 75Ω antenna, design an impedance matching circuit using passive components to match the two together, and describe the effects of not having this circuit in place. [20%]

2 An RF amplifier is required to boost the signal from an antenna receiving mobile phone signals, so that it can feed a distributed antenna array inside a road traffic tunnel, to prevent mobile calls from dropping out during transit. The RF carrier frequencies are around 2 GHz.

(a) Draw the circuit diagram for a single-stage RF transistor amplifier and briefly describe the function of each of the circuit components. [20%]

(b) Design an RF amplifier to provide a net gain of 20 dB in power, with an input impedance of 75Ω and an output impedance of 50Ω . The circuit should operate from a 15 Vdc supply and be able to provide up to 100 mW of output power. You may assume that a suitable transistor with $h_{fe} = 250$ is available. [30%]

(c) In order to narrow the response of the amplifier to a peak around 2 GHz, a parallel LC resonant circuit is connected between the input and ground. If this circuit uses an inductor of 0.47 nH with a series resistance of 0.1Ω , what value of capacitor should be employed, and what is the expected resonant bandwidth of this arrangement when it is connected into the circuit? [20%]

(d) A cheaper, new RF transistor with the following properties is to be considered for this application: $h_{fe} = 300$, $f_t = 12 \text{ GHz}$, $c_{cb} = 0.15 \text{ pF}$, $c_{oe} = 0.12 \text{ pF}$. Calculate the expected bandwidth of this transistor in the circuit and hence comment on its suitability for this application. [30%]

3 (a) Draw the circuit for a 2-pole, low-pass *Voltage Controlled Voltage Source (VCVS)* filter and show how this circuit can be configured to produce a Butterworth filter response of the form:

$$\left| \frac{V_o}{V_i} \right| = A \left[1 + \left(\frac{f}{f_c} \right)^4 \right]^{-\frac{1}{2}}$$

where the input and output voltage signals are V_i and V_o respectively and f_c is the cut-off frequency. How should the circuit be modified to obtain a high-pass response instead? [40%]

(b) A serial digital data link operates at 16 Mbit/s, where the received data signal needs to be filtered in order to remove high frequency carrier components from the waveform. Design a suitable low-pass, 4-pole VCVS filter circuit with a reasonably sharp cut-off, in order to clean up the signal without introducing significant overshoot. [20%]

(c) Sketch the functional block diagram of a *Phase Locked Loop (PLL)* and briefly describe how such a circuit can be employed to recover the clock signal from serial data bits, in order to produce synchronised data and clock bit streams. [25%]

(d) The 16 Mbit/s serial data signals are routed around a passenger aircraft to provide entertainment and communication services. In order to save weight, the data cables comprise round polymer cores coated with a thin layer of copper, rather than solid copper cores. What thickness of copper is required to minimise weight without significantly increasing the effective resistance of the cables in operation? [15%]

VCVS filter design table

n	Bessel		Butterworth		Chebyshev (0.5 dB)	
	fn	A	fn	A	fn	A
2	1.274	1.268	1.000	1.586	1.231	1.842
4	1.432	1.084	1.000	1.152	0.597	1.582
	1.606	1.759	1.000	2.235	1.031	2.660

- 4 (a) A 1.5 GHz oscillator comprises a negative impedance transistor circuit connected to an LC resonant tank circuit, using an inductance of 3 nH. Show how a pair of transistors can be connected to realise a negative impedance, and select suitable circuit values for the oscillator if the inductor has a Q-factor of 30 and the circuit is to operate from ± 5 Vdc supply rails. [35%]
- (b) An RF amplifier module has a quoted input S-parameter value, $S_{11} = 0.35 \angle 40^\circ$ at a frequency of 2 GHz, when operated in a 50 Ω circuit.
- (i) Plot this point on the Smith Chart and determine the input impedance of the module, expressing the result in the form $X \pm jY \Omega$. [20%]
- (ii) Design an impedance matching circuit, using a length of transmission line with a dielectric *relative permittivity* of 2, and a series capacitor, to match the amplifier input impedance to 50 Ω . [20%]
- (iii) Express the equivalent unmatched input impedance as two passive components connected in series, and hence determine the expected S_{11} value for the input at 1 GHz assuming the passive component values are constant. [15%]
- (iv) What voltage reflection coefficient, at the input to the 2 GHz impedance matching circuit, would be expected when operating the circuit at 1 GHz? [10%]


END OF PAPER

THIS PAGE IS BLANK

ENCLOSURE

Candidate No.

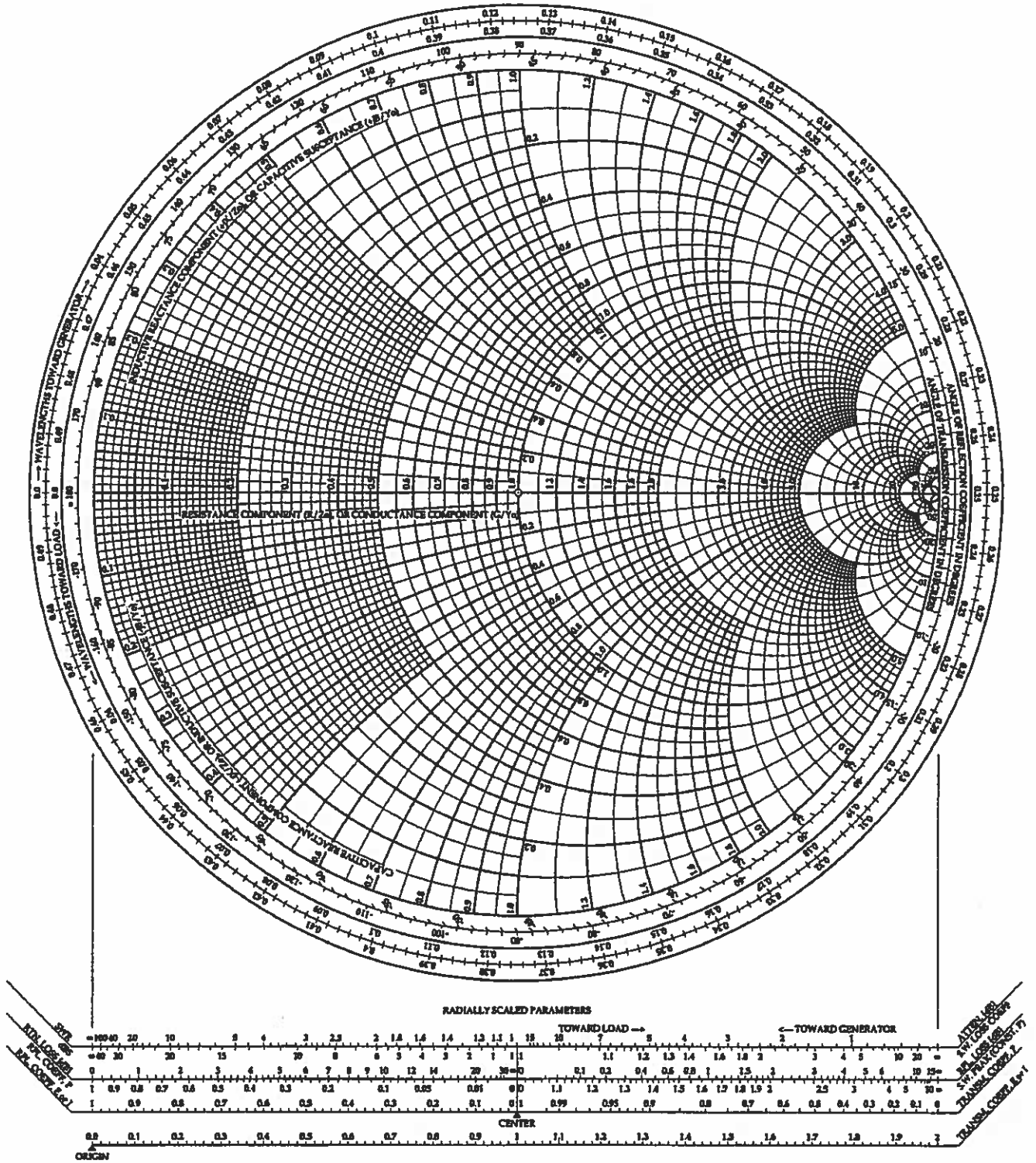Smith Chart for Question 4 – to be detached and handed in with script.



3B1 2016 – Numerical answers

- 1 (b)(i) 3.4 pW/m^2 , $50.6 \text{ } \mu\text{V/m}$
(b)(ii) $G = 16.4$ (12.2 dB)
(b)(iii) $2.74 \text{ } \mu\text{V rms}$
(c) 28° $\frac{1}{2}$ angle, ~ 14 mins.
(d) $C = 0.53 \text{ pF}$, $L = 5.97 \text{ nH}$ or 1.06 pF , 11.9 nH
- 2 (b) $R_1 = 1500 \text{ } \Omega$, $R_2 = 110 \text{ } \Omega$, $R_3 = 2.2 \text{ } \Omega$, $R_4 = 50 \text{ } \Omega$, Gain $\times 16.4$ ($\times 20$) unloaded gain, coupling caps. 10 nF
(c) 13.5 pF , $Q \text{ total} = 6.1$, $\Delta f = 328 \text{ MHz}$
(d) 538 MHz (not fast enough)
- 3 (b) Butterworth, $R = 100 \text{ } \Omega$, $C = 133 \text{ pF}$, $f_c = 12 \text{ MHz}$
(d) skin depth $\delta = 16 \text{ } \mu\text{m}$, therefore use $50 \text{ } \mu\text{m}$ to have minimal resistive losses
- 4 (b)(i) $75 + j40$
(ii) 48.6 mm , $C = 2.1 \text{ pF}$
(iii) $75 \text{ } \Omega$ in series with $3.18 \text{ nH} = 1.5 + j40$ normalised @ 1 GHz , $\rho = 0.25$
(iv) $\rho = 0.74$

