

EGT3
ENGINEERING TRIPOS PART IIB

Friday, 29th April 2016 09:30-11:00

Module 4B21

ANALOGUE INTEGRATED CIRCUITS

*Answer not more than **three** questions.*

All questions carry the same number of marks.

*The **approximate** percentage of marks allocated to each part of a question is indicated in the right margin.*

*Write your candidate number **not** your name on the cover sheet.*

STATIONERY REQUIREMENTS

Single-sided script paper

SPECIAL REQUIREMENTS TO BE SUPPLIED FOR THIS EXAM

CUED approved calculator allowed

Attachment: 4B21 Analogue Integrated Circuits Data Sheet (2 pages).

Engineering Data Book

10 minutes reading time is allowed for this paper.

You may not start to read the questions printed on the subsequent pages of this question paper until instructed to do so.

- 1 (a) With the aid of one or more circuit schematics, describe the operating principle of a current mirror and how one would scale the output current. [20%]
- (b) The circuit shown in Fig. 1 is to be designed using a 0.18 μm CMOS process. The transistors have the following parameters: $\mu_n \cdot C_{ox} = 387 \mu\text{A} \cdot \text{V}^{-2}$, $\mu_p \cdot C_{ox} = 86 \mu\text{A} \cdot \text{V}^{-2}$, $V_{tn} = -V_{tp} = 0.5 \text{ V}$, $V_{DD} = 1.8 \text{ V}$, $V'_{An} = 5 \text{ V}/\mu\text{m}$, and $V'_{Ap} = -6 \text{ V}/\mu\text{m}$. The output voltage is to swing between 0.2 V to 1.6 V and the voltage gain must be at least 10 V/V.
- (i) Using the same channel length of transistors, design the circuit for a bias current of 50 μA . [20%]
- (ii) If the channel length is to be an integer multiple of 0.18 μm , what is its value? [15%]
- (iii) What is the new value of channel length if the gain is to be increased by a factor of 2? [20%]
- (iv) What is the resulting increase in total gate area? [15%]
- (c) State one application of the current mirror in a multi-stage amplifier. [10%]

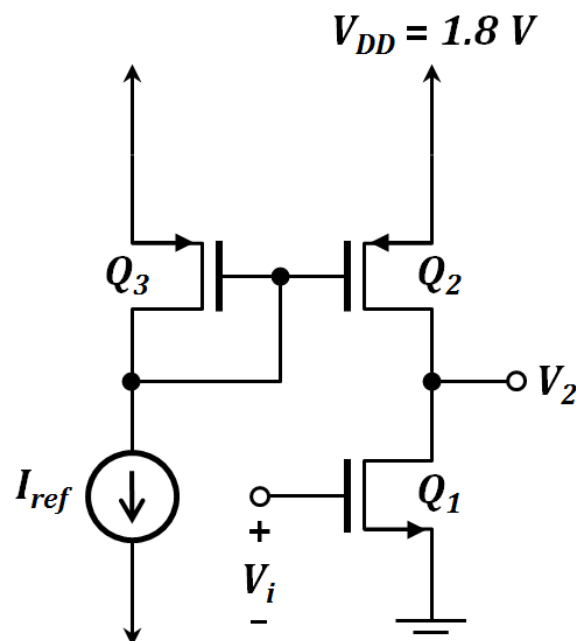


Fig. 1

2 (a) Explain what is meant by an ideal voltage source and an ideal current source. [25%]

(b) Shown in Fig. 2 are two common-base amplifiers, driven by an ideal voltage source Fig. 2 (a) and an ideal current source Fig. 2 (b), respectively.

(i) Assuming that each circuit has been properly biased, and that the biasing networks, which are not indicated in Fig. 2, do not affect the small-signal analysis, calculate the output resistance, r_{out} for circuits (a) and (b), using the following data: $r_{\pi} = 1\text{ k}\Omega$, $r_o = 100\text{ k}\Omega$, and $\beta = 100$. [50%]

(ii) Comment on the physical implications of the results for r_{out} for each of the two configurations. [25%]

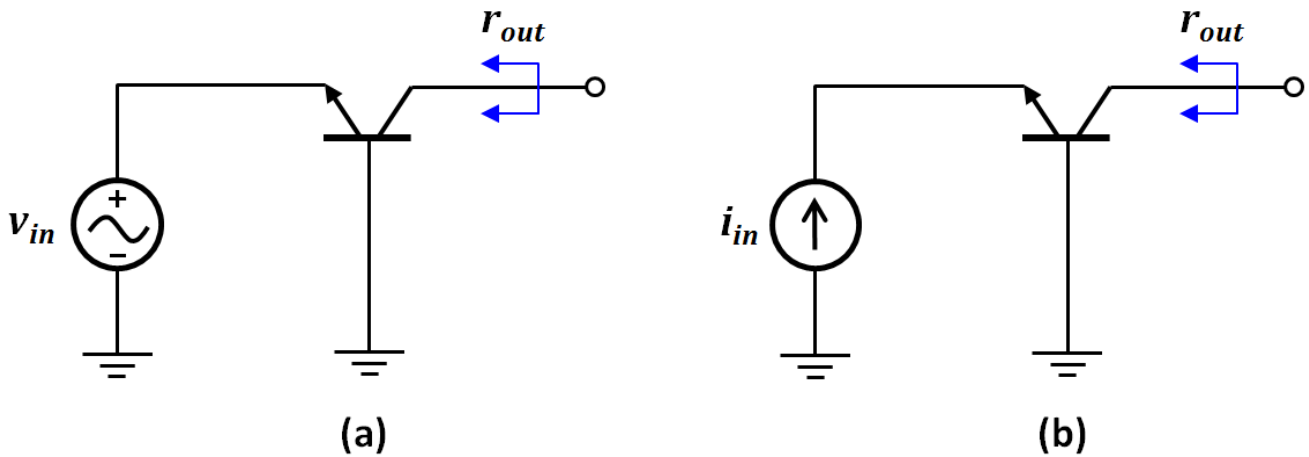


Fig. 2

- 3 (a) With the aid of circuit block illustrations, define negative feedback, as applied to electronic circuits, describing its effect on circuit characteristics such as gain, linearity, input and output impedances, and bandwidth. [25%]
- (b) What are the four negative feedback circuit topologies? State clearly whether the nature of the sampled and mixing signals is a voltage or current as applied to the different amplifier topologies. [25%]
- (c) A feedback trans-resistance amplifier circuit is shown in Fig. 3. Assuming $R_F \gg R_C$ and $r_o \gg R_C$ and that the feedback causes the signal voltage at the input node to be nearly zero:
- (i) Derive expressions for $A \equiv V_o/I_i$, $\beta \equiv I_f/V_o$ and $A_f \equiv V_o/I_s$. [30%]
- (ii) Find the value of A_f for the case of $R_C = 10 \text{ k}\Omega$, $R_F = 100 \text{ k}\Omega$ and the transistor current gain $\beta = 100$. [20%]

 


Fig. 3

4 (a) Consider a MOSFET fabricated in 0.18 μm CMOS technology. With the aid of a device schematic, describe the main sources of capacitances (along with typical values) that influence high frequency circuit performance. [25%]

(b) With the aid of a simplified equivalent circuit, show that the MOSFET's unity gain frequency ω_T can be approximated as $\omega_T = g_m / (C_{gs} + C_{gd})$, where g_m is the transconductance, and C_{gs} , C_{gd} the gate-source and gate-drain capacitances, respectively. [15%]

(c) The components in the circuit shown in Fig. 4 have the following parameters: $\mu_n C_{ox} (W/L) = 2 \text{ mAV}^{-2}$, $V_t = 0.5 \text{ V}$, $C_{gs} = C_{gd} = 10 \text{ fF}$, $R_1 = 100 \text{ k}\Omega$, $R_{G1} = 600 \text{ k}\Omega$, $R_{G2} = 1.4 \text{ M}\Omega$, $R_D = 2 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $R_S = 1 \text{ k}\Omega$ and $C_{C1} = C_{C2} = C_S = \infty$. The supply voltage $V_{DD} = 1.8 \text{ V}$ and Early voltage $V_A = -26 \text{ V}$.

(i) Construct the small signal equivalent circuit. [15%]

(ii) Find the mid band voltage gain v_o/v_i [15%]

(iii) What is the approximate upper -3dB frequency f_H ? [20%]

(iv) Briefly comment, using intuitive-based reasoning, on the circuit's high frequency behaviour in relation to the common-source amplifier. [10%]

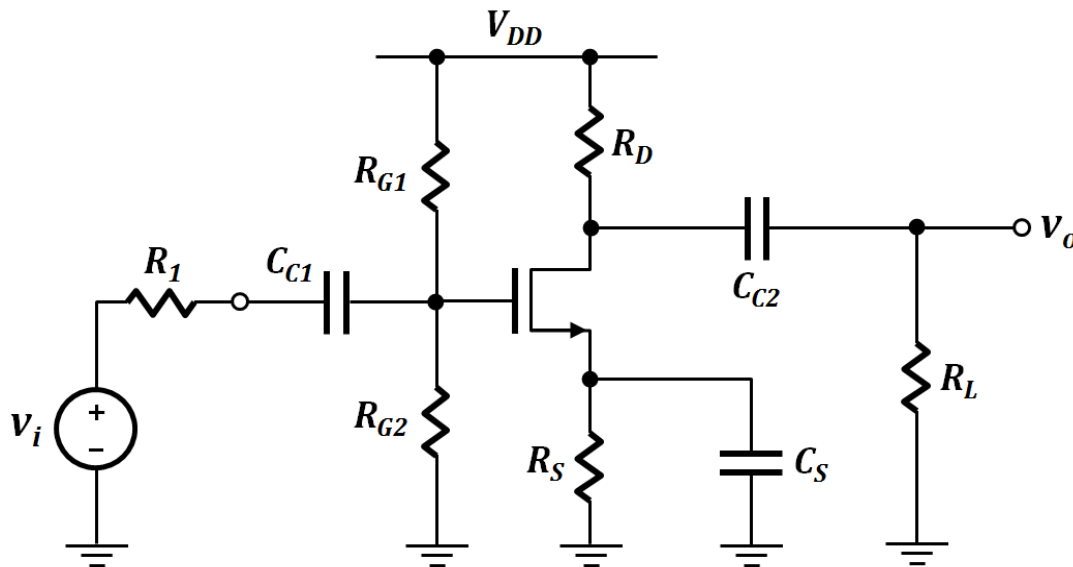


Fig. 4

5 (a) Give a short account of the applications in which integrated *phase-lock loop architectures* are commonly used. [20%]

In a frequency synthesiser design for a computer motherboard, a current-starved Voltage-Controlled Oscillator (VCO) comprising seven identical stages is to be designed, based on the circuit in Fig. 5. The figure shows a single stage of the circuit (comprising transistors *M1*, *M2*, *M3* and *M4*), enclosed in dashed lines, and the current control circuit (*M5* and *M6*).

(b) Complete the schematic circuit for the VCO, and explain its mode of operation, giving details of what determines the frequency of operation. [20%]

(c) The total capacitance being driven at the output node of each stage is 2 fF. Assume that the minimum value of the control voltage V_{inVCO} is equivalent to the threshold voltage for *M5*. The threshold voltage for all devices has magnitude 1 V. The supply voltage V_{DD} is 5 V, and the maximum drain current in each stage is to be 100 μ A. Stating any other assumptions made,

(i) estimate the maximum frequency that can be generated. [10%]

(ii) develop an equation for the VCO gain, K_V , and estimate its value. Comment on the linearity that can be achieved. [20%]

(d) With the help of a block diagram, explain how the VCO developed in parts (b) and (c) could be used in combination with other suitably chosen circuit elements to achieve a frequency synthesiser whose output frequency is to be exactly 4 times the frequency of a stable reference. [30%]

 


Fig. 5

END OF PAPER

4B21 ANALOGUE INTEGRATED CIRCUITS DATA SHEET

Bipolar Junction Transistors:

$$i_C = \alpha i_E \quad i_C = \beta i_B \quad i_B = (1-\alpha)i_E \quad i_E = (\beta+1)i_B$$

$$\beta = \frac{\alpha}{1-\alpha} \quad \alpha = \frac{\beta}{\beta+1} \quad V_T = \frac{kT}{q} = 25 \text{ mV at } 300\text{K}$$

$$g_m = \frac{I_C}{V_T} \quad r_\pi = \frac{V_T}{I_B} \quad r_e = \frac{V_T}{I_E} \quad r_o = \frac{V_A}{I_C}$$

MOSFETs:

$$i_D = K[2(v_{GS} - V_t)v_{DS} - v_{DS}^2] \quad K = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L} \right)$$

$$i_D = K(v_{GS} - V_t)^2 = \frac{k'}{2} \left(\frac{W}{L} \right) (v_{GS} - V_t)^2 \quad k' = \mu C_{ox}$$

$$g_m = 2K(v_{GS} - V_t) \quad r_o = \frac{|V_A|}{I_D}$$

Differential Amplifiers:

$$v_o = A_d v_d + A_{cm} v_{cm}$$

$$CMRR = 20 \log |A_d / A_{cm}| \quad A_{cm} = \frac{v_o}{v_{cm}} \quad A_d = \frac{v_o}{v_d} = g_m R_D$$

OR

OR

$$A_{cm} = \frac{\Delta R_D}{2R}$$

$$A_d = \frac{\Sigma R_C}{\Sigma R_E}$$

BJT small signal operation:

$$i_{C1} \approx \frac{\alpha I}{2} + \frac{\alpha I}{2V_T} \frac{v_d}{2} \quad i_{C2} \approx \frac{\alpha I}{2} - \frac{\alpha I}{2V_T} \frac{v_d}{2}$$

$$R_{id} = 2(\beta+1)(r_e + R_E) \quad R_E = \text{emitter resistance}$$

FET small signal operation:

$$i_{D1} \approx \frac{I}{2} + \left(\frac{I}{V_{GS} - V_t} \right) \frac{v_{id}}{2} \quad i_{D2} \approx \frac{I}{2} - \left(\frac{I}{V_{GS} - V_t} \right) \frac{v_{id}}{2}$$

Millers Theorem:

$$C_{eq} = C_{bridge}(1-K) \quad K \equiv \frac{V_2}{V_1}$$

Thermal Noise:

$$\langle v_n^2 \rangle = 4kTBR \quad k = 1.38 \times 10^{-23} \text{ J / K}$$

Feedback Architectures and Properties:

| | Series-Shunt | Series-Series | Shunt-Series | Shunt-Shunt |
|---------------------------------------|-------------------------|----------------------------|----------------------------|-------------------------|
| Feedback signal X_f | Voltage | Voltage | Current | Current |
| Sampled signal X_o | Voltage | Current | Current | Voltage |
| To find input loop, set ¹ | $V_o=0$ | $I_o=0$ | $I_o=0$ | $V_o=0$ |
| To find output loop, set ¹ | $I_i=0$ | $I_i=0$ | $V_i=0$ | $V_i=0$ |
| Signal Source | Thevenin | Thevenin | Norton | Norton |
| $\beta = X_f / X_o$ | V_f / V_o | V_f / I_o | I_f / I_o | I_f / V_o |
| $A = X_o / X_i$ | $A_v = V_o / V_i$ | $G_M = I_o / V_i$ | $A_I = I_o / I_i$ | $R_M = V_o / I_i$ |
| $D = 1 + \beta A$ | $1 + \beta A_v$ | $1 + \beta G_M$ | $1 + \beta A_I$ | $1 + \beta R_M$ |
| A_f | A_v / D | G_M / D | A_I / D | R_M / D |
| R_{if} | $R_i D$ | $R_i D$ | R_i / D | R_i / D |
| R_{of} | $R_o / (1 + \beta A_v)$ | $R_o (1 + \beta G_M)$ | $R_o (1 + \beta A_I)$ | $R_o / (1 + \beta R_M)$ |
| $R'_{of} = R_{of} \parallel R_L$ | R'_o / D | $R'_o (1 + \beta G_M) / D$ | $R'_o (1 + \beta A_I) / D$ | R'_o / D |

¹This procedure gives the basic amplifier circuit without feedback but taking the loading of β , R_L , and R_S into account.