


1B PAPER 5 2015

CRIB - DR. P. R. PALMER

- 1/ (a)(i) Finite bandwidth
Common-mode gain.
Finite output voltage
Finite input voltages.
Input bias currents
Input offset voltage.

(ii) There is no path for the dc bias current and nothing to set the dc voltage on the + input.

See 1A IEP:

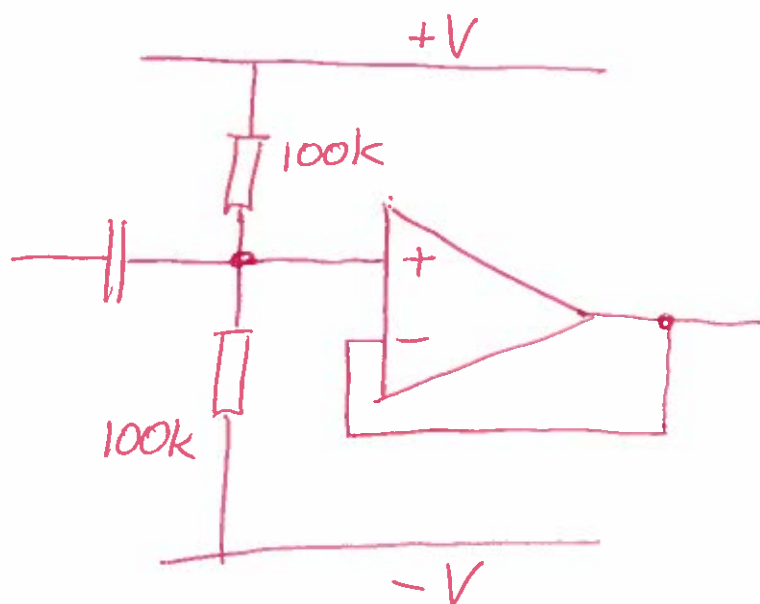

1/ (b)(i) Gain is $1 + \frac{50k}{R_G}$ (symmetry)

For 20 $R_G = \underline{\underline{2.63k}}$

For 1000 $R_G = \underline{\underline{50.05k}}$

(ii) Leave R_G open.

(iii) Instrumentation where common-mode noise is a problem, also high source impedance. eg. pH measurement in a chemical processing plant.

(c) Op-amp gain with frequency $\frac{A_1}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}}$

With f.b. $\omega_{3dB} > \omega_c$

Gain-BW: $\frac{A_1}{\sqrt{1 + (\frac{\omega_{3dB}}{\omega_c})^2}}$, $\omega_{3dB} \approx A_1 \omega_c$

The gain is set by the first stage (A_1, A_2)

$G \times BW$ $7 \times 1000 = 7000$, $70 \times 100 = 7000$

But $500 \times 10 = 5000$ so 2nd stage has cut in.

At $G=10$ BW should be 700 kHz .

At 500 kHz first stage gives a gain of 14, $10/14$
 A_2 is in unity gain so 500 kHz is 3dB of 2nd


2 (a) CLASS A as Q_1 and Q_2 should not be cut off. (with Q_2 base to ground the input voltage should be close to ground)

(b) DC bias on the base-emitter of Q_1 in the on state :- $0.6 - 0.8V$

Current in $R_3 = 2mA$.

Voltage $-0.7 - (-2.5) \Rightarrow \underline{\underline{R_3 = 0.9k}}$


$V_{CE} = 2V$.

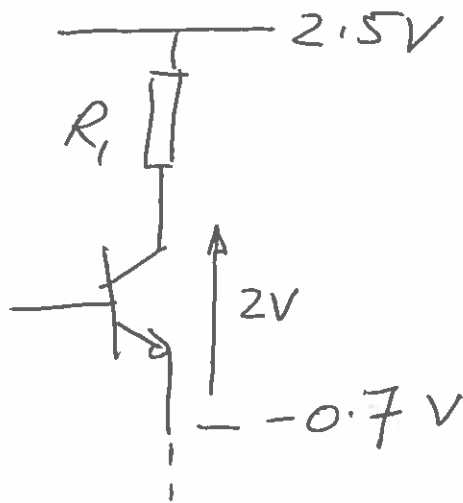

$R_1 = R_2 = 1.2k$

2 (c) Can do it in one go, or Differential Mode & Common Mode.

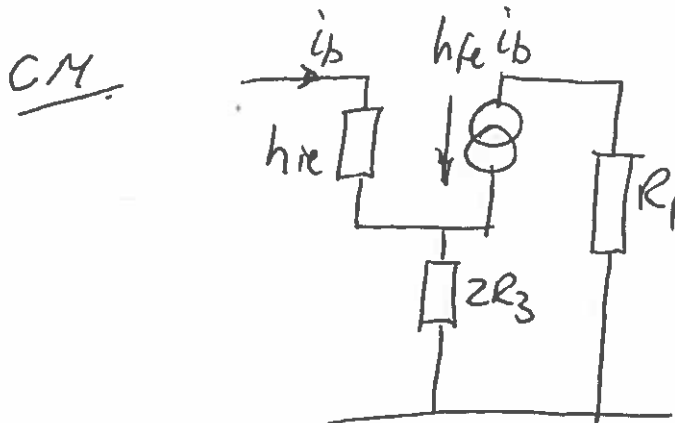
The second requires DM of $\frac{V_{in}}{2}$ & CM of the same.



$$i_b = \frac{V_i - i_b(h_{fe} + 1)2R_3}{h_{ie}}, \quad V_o = -i_b h_{fe} R_1$$

$$i_b h_{ie} = V_i - (h_{fe} + 1)i_b \cdot 2R_3$$
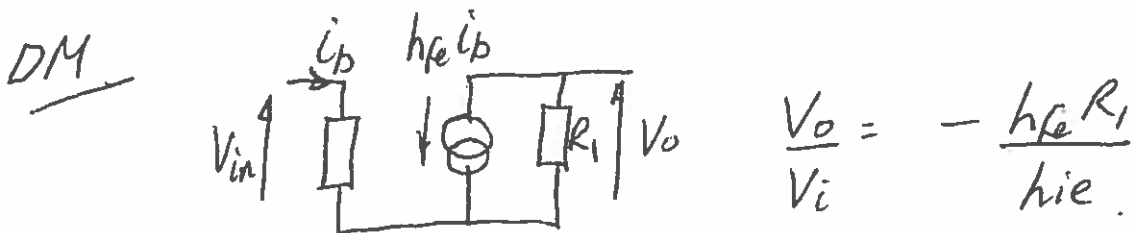
$$i_b = \frac{V_i}{h_{ie} + (h_{fe} + 1)2R_3} \quad \therefore \quad \frac{V_o}{V_i} = -\frac{h_{fe} R_1}{h_{ie} + (h_{fe} + 1)2R_3}$$



$$\frac{V_o}{V_i} = -\frac{h_{fe} R_1}{h_{ie}}$$

Overall

$$\frac{V_o}{V_i} = -\frac{h_{fe} R_1}{2} \left[\frac{1}{h_{ie}} + \frac{1}{h_{ie}(h_{fe} + 1)2R_3} \right]$$

(d) DM $R_{in} = h_{ie} = 1k$.

CM. $i_b = \frac{V_i - i_b(h_{fe}+1)2R_3}{h_{ie}}$


$$i_b (h_{ie} + (h_{fe}+1)2R_3) = V_i.$$

$$R_{in} = h_{ie} + (h_{fe}+1)2R_3 = 1k + 201k \times 2 \\ = 403k. \quad (R_3 \approx 1k)$$

So, as configured the input current is mostly DM \approx so $\frac{V_{in}}{2} \cdot \frac{1}{h_{ie}}$ so $R_{in} = \underline{\underline{2h_{ie}}}$.

If drawn as a whole there are two h_{ie} 's to consider in series!

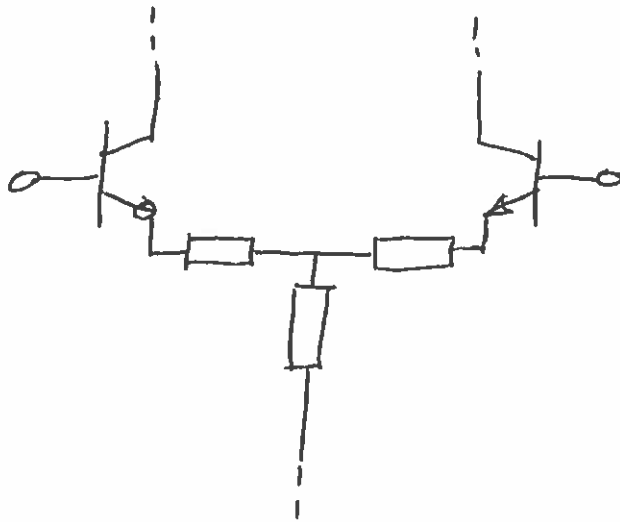(e) The effect of R_3 is excellent $(h_{fe}+1)R_3$ so a small resistor in the emitters of Q_1 & Q_2



3 a) Δ Loads expect balanced voltages

2) The currents sum to zero at the neutral ~ often no neutral used.

3) No fluxes in machines/generators.

(b) The power factor deals with power ($\int \text{energy } dt$) and reactive power ($\int \text{energy } dt$)

which are not phase quantities in time.

Therefore the load is a "black box".

$$P = \sqrt{3} V_L I_L \cos \phi$$

Really there are 3 Δ loads, but either branch

$$V_L = \sqrt{3} V_p \quad \underline{\text{OR}} \quad I_L = \sqrt{3} I_p.$$

$$\text{eg } P = \sqrt{3} V_L \sqrt{3} I_{ph} \cos \phi$$

$$= 3 V_L I_{ph} \cos \phi$$

The 3 branch loads are there still!

c) (i) 33kV 12.000 MW. 0.8pf

$$Q = \frac{12}{0.8} \sin \cos^{-1} 0.8 = 9 \text{ MVAR.}$$

$$\frac{Q_T}{3} = 3 \text{ MVAR} = \left(\frac{33k}{\sqrt{3}} \right)^2 \cdot \omega C \quad \underline{\underline{C = 26 \mu F}}$$

$$(ii) I_L = \frac{12 \text{ M}k}{\sqrt{3} \cdot 33k} = 210 \text{ A.}$$

$$I^2 R = 0.132 \text{ MW.}$$

$$I^2 \omega L = 210^2 \cdot 314 \times 36m = 0.499 \text{ MVAR.}$$

$$P_{TOT} = 12 + 3 \times 0.132 \text{ MW}$$

$$Q_{TOT} = 0.499 \times 3 \text{ MVAR, } S_{TOT} = \sqrt{P_{TOT}^2 + Q_{TOT}^2}$$

$$= 12.486$$

$$V_{Lg} = \frac{12.486 \text{ M}}{210 \sqrt{3}} = \underline{\underline{34.3 \text{ kV}}}$$

d/(i) Extra $5 \mu\text{F}$ at the load in Delta.

$$Q_c = 3 \times (33\text{k})^2 \times 314 \times 5\mu = 5.13 \text{ MVAR}$$

$$S_T = \sqrt{12^2 + 5.13^2} = 13$$

$$I = \frac{13}{\sqrt{3} \times 33\text{k}} = 227 \text{ A}$$

$$S_{TOT} = \sqrt{(12 + 3 \times 227^2 \times 3)^2 + 5^2} = 13.43$$


$$V_{Lg} = \frac{13.43}{227\sqrt{3}} = 34.2 \text{ kV.}$$

(ii) 50 km. \Rightarrow $25 \mu\text{F}$ at the load.
Could remove the $26 \mu\text{F}$ but
maybe distributed.

Also $25 \mu\text{F}$ at the generator so
high currents at that end.


4 (a) Load chart uses $\frac{3V_{ph}^2}{X_s}$ on x axis.
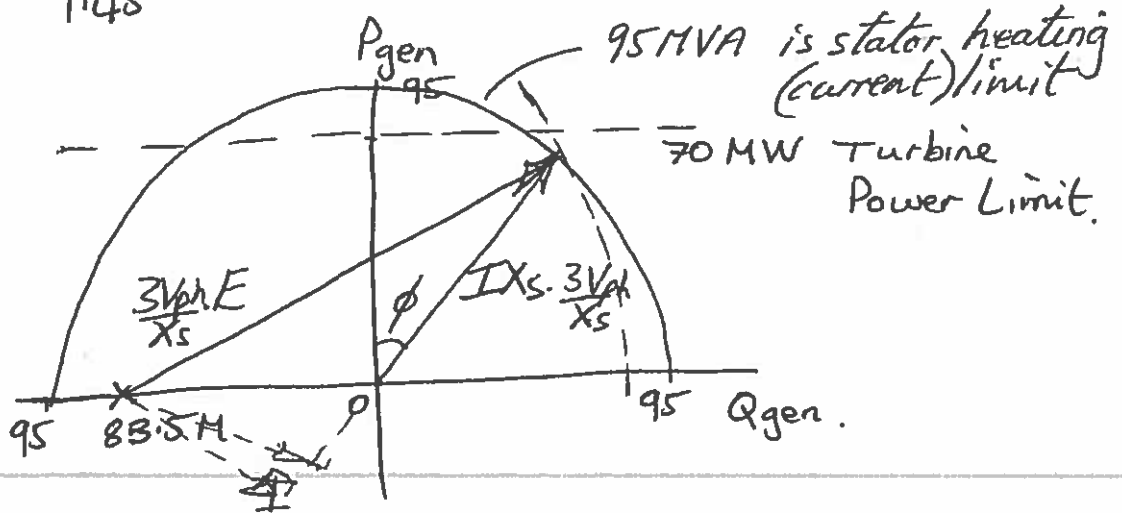
$$\frac{3 \times (11\text{kV}/\sqrt{3})^2}{1.45} = 83.5 \text{ MVAR.}$$



0.85 p.f. $\cos^{-1} 0.85 = 32^\circ = \phi$ Sets max E (rotor heating)
 ie. 95 MVA at a p.f. of 0.85

b/


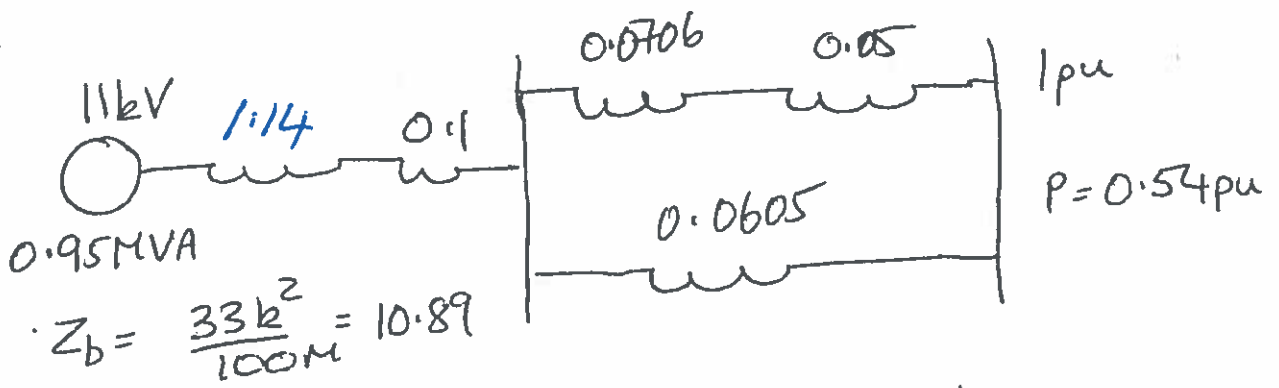


Line 1 $0.7686j\Omega \rightarrow 0.0706$

Line 2 $0.6588j\Omega \rightarrow 0.0605$

c/ Lines 1 & 2 in parallel now.
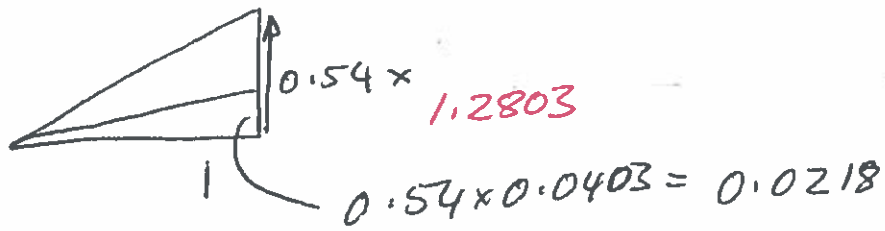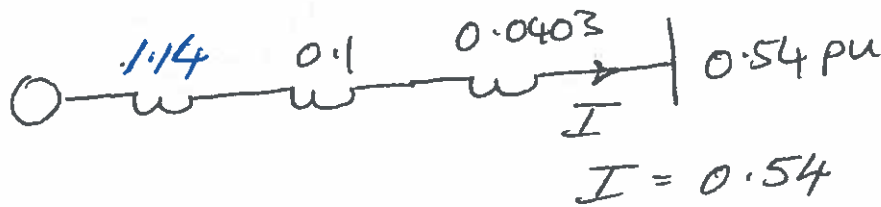
$$\frac{0.0605 \times 0.1206}{0.1811} = 0.0403$$



$$I_{\text{line 2}} = \frac{0.0218}{0.0605} = 0.3597$$

$$I_b = \frac{100M}{\sqrt{3} \cdot 33k} = 1,749.6 \text{ A} \quad I_{\text{line 2}} = 629.3 \text{ A}$$


$$\therefore I_{\text{line 1}} = \underline{\underline{315.7 \text{ A}}}$$

Note dropped 'j's as
all reactive

d/ (i) Need to Add 0.0601 pu ie $0.654 \text{ j} \Omega$

(ii) 2 lines with $0.1206 \text{ pu} \Rightarrow 0.0603 \text{ pu}$
 \therefore current in each line is 0.3597 pu .
 $\Rightarrow 0.7194 \text{ pu. total} \Rightarrow 72 \text{ MW}$


(iii)

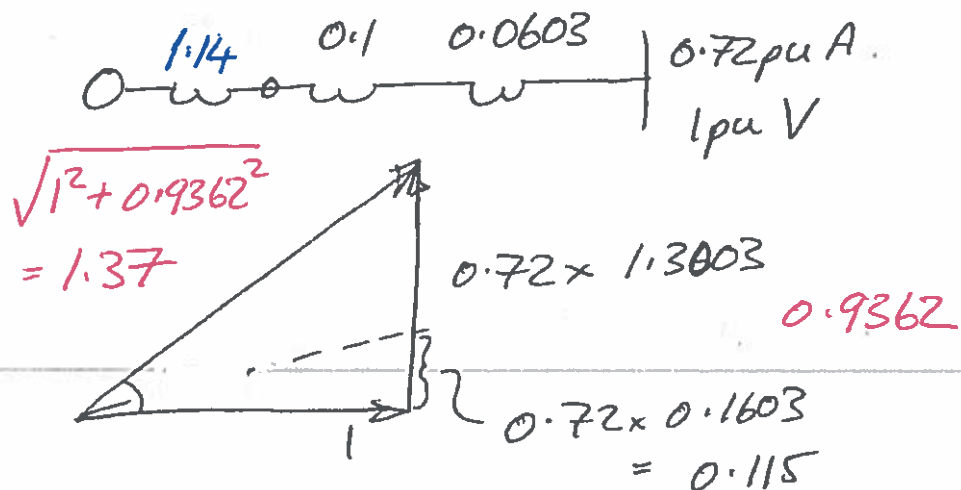


$$\tan^{-1} 0.9362 - \tan^{-1} 0.115 = \underline{\underline{36.5^\circ}}$$

...

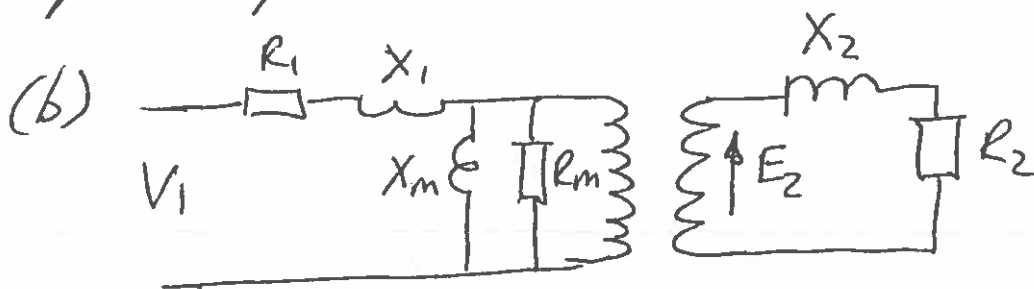5(a) Slip is the fractional difference in speed between the rotor and the magnetic field in the airgap set by the stator. Slip is necessary to provide a voltage to the rotor circuit, whereby a current flows and torque is produced.



as a transformer. When rotating sE_2

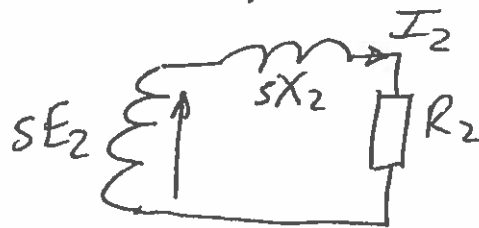

$$I_2 = \frac{sE_2}{R_2 + jX_2 \cdot s}$$

$$= \frac{E_2}{\frac{R_2}{s} + jX_2}$$


Next use power

$$P_{\text{gap}} = E_2 I_2 \cos \phi = E_2 \cdot \frac{E_2}{\sqrt{\left(\frac{R_2}{s}\right)^2 + X_2^2}} \cdot \frac{R_2/s}{\sqrt{\left(\frac{R_2}{s}\right)^2 + X_2^2}}$$

$$T_{\text{ws}} = \frac{E_2^2 R_2/s}{\left(\frac{R_2}{s}\right)^2 + X_2^2}$$

$\frac{R_2}{s}$ is mechanical power + losses.

(C) (i)

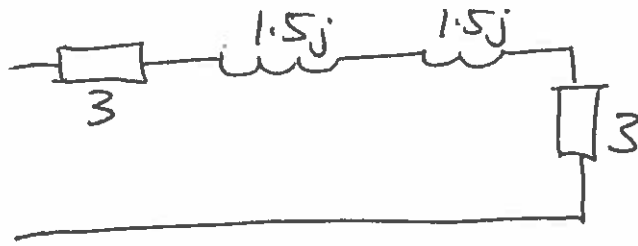

$$I_2' = \frac{415/\sqrt{3}}{6 + 3j} \quad I_2' = 35.7A$$


$$T = \frac{3 I_2'^2 R_2}{\omega_s s} = \frac{3 \times 35.7^2 \times 3}{50\pi} = \underline{\underline{73 \text{ Nm}}}$$

(ii) $s = \frac{1500 - 1425}{1500} = 0.05$

$$I_2' = \frac{415/\sqrt{3}}{3 + \frac{3}{0.05} + 3j} = 3.81A$$

$$T = \frac{3 \times 3.81^2 \cdot 3}{157 \cdot 0.05} = \underline{\underline{16.6 \text{ Nm}}}$$

(iii)

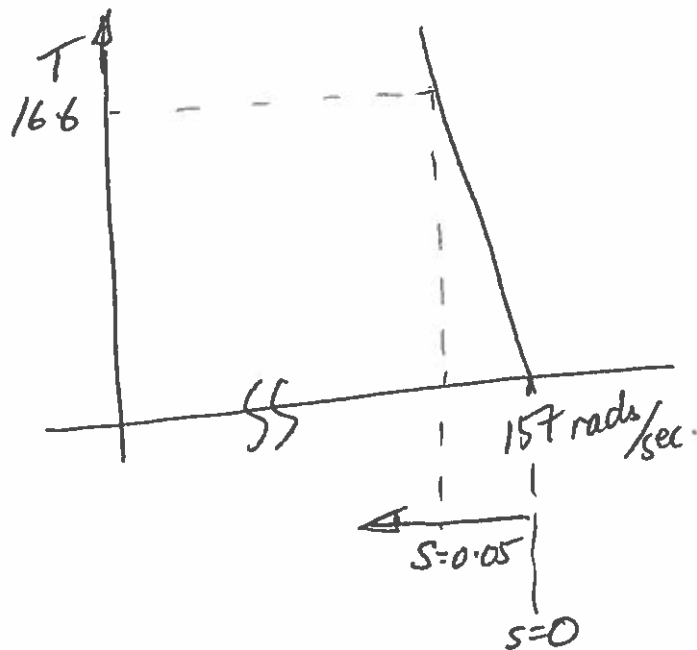

(d) Using the graph as a straight line

$$s = 0.05 \times 0.80 = 0.04.$$

$$T = 16.6 \times 0.80$$

$$s = 0.04 \Rightarrow 1500 \text{ rpm} - 60 \text{ rpm} = \underline{\underline{1440 \text{ rpm}}}$$

(The value of $R_z/s = 3/0.05 = 60 \Omega$.

$$60 \Omega \Rightarrow (3 + 3j)$$

and R_z/s gets bigger as $s \rightarrow 0$!

6 (a) Databook. (Free space)

$$\left. \begin{aligned} E_x &= E_0 e^{j(\omega t - \beta z)} \\ H_y &= H_0 e^{j(\omega t - \beta z)} \end{aligned} \right\} \begin{array}{l} \text{travelling waves} \\ \text{in } z \text{ direction.} \end{array}$$

$$\text{Maxwell } \nabla \times \mathbf{H} = \dot{\mathbf{D}} = \epsilon_0 \dot{\mathbf{E}} = \epsilon_0 \frac{d\mathbf{E}}{dt}$$

$$\text{OR } \left(\nabla \times \mathbf{E} = -\dot{\mathbf{B}} = -\frac{dB}{dt} \right)$$

$$\frac{dH_y}{dz} = \epsilon \frac{dE_x}{dt}$$

$$H_0 \cdot \cancel{-\beta} e^{j(\omega t - \beta z)} = \epsilon E_0 \omega \cancel{e^{j(\omega t - \beta z)}} \quad \text{--- ①}$$

$$\frac{H_0}{E_0} = -\frac{\epsilon \omega}{\beta} \quad \beta = \omega \sqrt{\mu \epsilon}$$

$$= -\frac{\epsilon}{\sqrt{\mu \epsilon}} = -\sqrt{\frac{\epsilon}{\mu}} = -\frac{1}{Z_0}$$

Looking at ① H_0 & E_0 are maximum at the same z & t , and travelling at $v=c$. Both represent ~~densities~~ stresses, so energy flows in the direction of z .

b (i) Need the travel time around trip.
Shortest time at 100 km.

$$t = \frac{200 \times 10^3}{3 \times 10^8} = \frac{2}{3} \text{ ms} = \underline{\underline{0.667 \mu\text{s}}}$$

(ii) Databook $\frac{\eta_2 - \eta_1}{\eta_2 + \eta_1} = \frac{\sqrt{\frac{\mu_0}{1.5\epsilon_0}} - \sqrt{\frac{\mu_0}{\epsilon_0}}}{\sqrt{\frac{\mu_0}{1.5\epsilon_0}} + \sqrt{\frac{\mu_0}{\epsilon_0}}} = \frac{\frac{1}{\sqrt{1.5}} - 1}{\frac{1}{\sqrt{1.5}} + 1}$

$$= \frac{0.816}{1.816}$$

$$= -0.10$$

Isotropic radiation $\times G$, distance r

$$P_t = \frac{850 \times 10^3}{4\pi r^2} \times G \quad P_t \times 0.1^2 \text{ reflected at cloud.}$$

i.e. for 1 W m^{-2} , $P_t = 100 \text{ W m}^{-2}$

$$G = \frac{4\pi \times 25 \times 10^{10}}{850 \times 10^3} \times 100 = \frac{77 \times 10^{10}}{85}$$

$$= 0.37 \times 10^9$$

This is huge, but 100 W/m^2 at 500 km is huge!

(c) For 1m^2 of cloud....

$G = 500$, 1W , 4m^2 antenna

$$P_r = \frac{1 \times 500 \times 4}{4\pi \times 25 \times 10^{10}}$$
$$= \frac{20 \times 10^{-10}}{\pi} \text{ W} = \frac{1}{2} \hat{I}^2 Z_0$$

$$\hat{I}^2 = \frac{40 \times 10^{-10}}{75\pi}$$

$$\hat{I} = \underline{\underline{4.12 \times 10^{-6} \text{ A}}}$$

(d) at 90GHz $\lambda = \frac{3 \times 10^8}{90 \times 10^9} = \frac{1}{300} \text{ m.}$

This is a nice size for raindrops so they will act like cats eyes

(Also little atmospheric loss)

$$7(a)(i) \quad v = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\epsilon_0 \epsilon_r \mu_0 \mu_r}}$$

In a free space system $v = \frac{1}{\sqrt{\mu_0 \epsilon_0}}$, so the same eq'n but no materials.

The waves travel $A(t, x) = A_0 \cos(kx - \omega t)$

$$\text{eg. } V(x, t) = V_F e^{j(\omega t - \beta x)} \quad (\text{infinite line})$$

As a point of constant phase which moves: ie $\omega t = \beta x$ $\frac{x}{t} = \frac{\omega}{\beta} = v$

v is materials based so constant so $\beta \propto \omega$.

$$(ii) \quad Z_0 = \sqrt{\frac{L}{C}} \quad Z_0 = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \ln\left(\frac{r_2}{r_1}\right) \quad \eta = \sqrt{\frac{\mu}{\epsilon}}$$

The coax constrains the fields, whereas the y & x directions are unlimited in free space.

$$(iii) \quad v = \frac{1}{\sqrt{\epsilon_0 \epsilon_r \mu_0 \mu_r}} \sim \text{light in space } \frac{1}{\sqrt{\epsilon_0 \mu_0}}$$

so $\frac{1}{\mu_r \epsilon_r}$ is different by $(0.66)^2$. The insulators usually have $\mu_r = \mu_0$ so ϵ_r is 2.3.

(a) (iii) cont.

$$\text{from (ii)} \quad Z_0 = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \ln\left(\frac{r_2}{r_1}\right) = 50$$

$$\frac{1}{2\pi} \sqrt{\frac{1.257 \times 10^{-6}}{2.3 \times 8.85 \times 10^{-12}}} \cdot \ln\left(\frac{r_2}{r_1}\right) = 50$$

$$\ln\left(\frac{r_2}{r_1}\right) = \frac{100\pi}{0.25 \times 10^3} = \frac{\pi}{2.5}$$

eg. if $r_1 = 1 \text{ mm} \Rightarrow r_2 = 3.5 \text{ mm}$.

$$(b)(i) \quad P_L = \frac{50-50}{100} = 0 \Rightarrow \text{no reflections.}$$

The 50Ω cable has a "characteristic" impedance, but the 50Ω source & 50Ω load have real impedances, so form a potential divider. $\Rightarrow \underline{\underline{E=2V}}$

(ii) Matched at source so no repeated reflections.

$$P_L = 1 \quad \text{Delay} \frac{1 \text{ m}}{0.66 \times 3 \times 10^8} = 5 \text{ ns}$$

1V at source \Rightarrow 1V out.

(0.5V into the line, 100% reflection: 1V out)

$$\underline{\underline{1V}}$$


(b)(ii) Fully matched 2V at DC.
 (2V at pulse as T.L. "disappears")

$$P = \frac{2^2}{100} = 40 \text{ mW}$$

$$\text{Unmatched } P = \frac{1^2}{1 \times 10^6} = \underline{1 \mu\text{W}}$$

(c) 50 MHz $\frac{1}{50 \times 10^6} = 20 \text{ ns period}$

5ns delay so 1m is $\frac{\lambda}{4}$

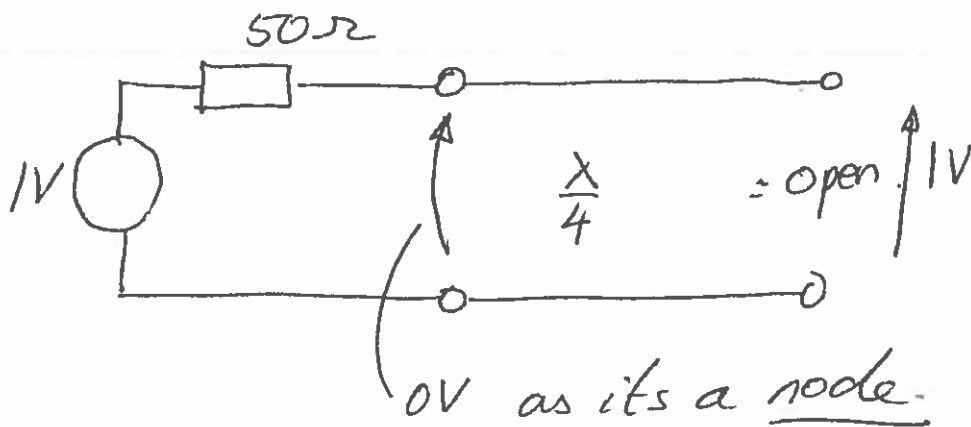

$$\left(\text{Power} = \frac{1^2}{50} = 20 \text{ mW} \right)$$